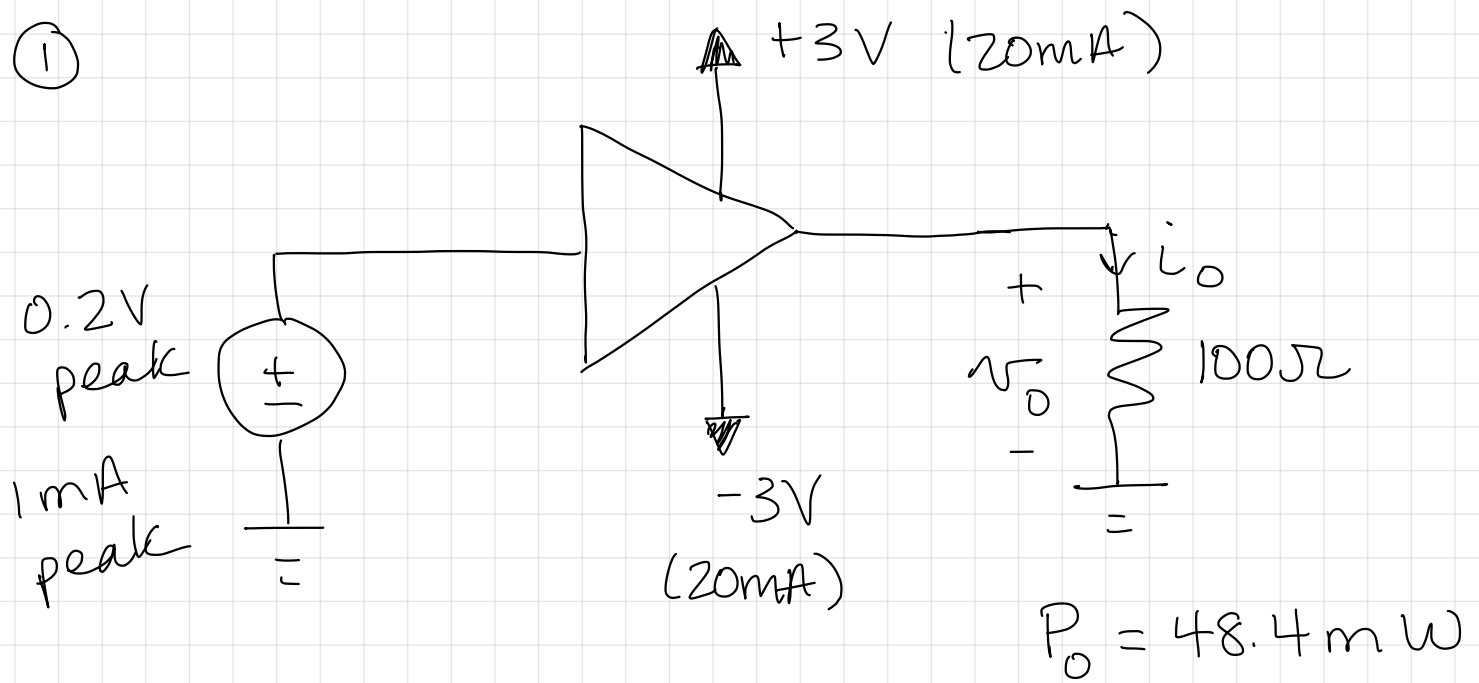


EE 315 HW #1 Solutions

①



$$P_o = \frac{v_o^2}{100}$$

$$v_o^2 = 100(48.4 \times 10^{-3})$$

$$v_o = 2.2 \text{ V}$$

$$i_o = \frac{v_o}{100} = 22.0 \text{ mA}$$

$$a) A_v = \frac{v_o}{v_i} = \frac{2.2}{0.2} = 11 \frac{\text{V}}{\text{V}} \text{ or } 20.83 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{22 \times 10^{-3}}{1 \times 10^{-3}} = 22 \frac{\text{A}}{\text{A}}$$

$$\text{or } 26.85 \text{ dB}$$

$$A_p = \frac{P_o}{P_i} = \frac{v_o i_o}{v_i i_i} = \frac{(2.2)(22 \times 10^{-3})}{(1.2)(1 \times 10^{-3})}$$

$$A_p = 242 \frac{\text{W}}{\text{W}} \text{ or } 23.84 \text{ dB}$$

b) & now we have to deal w/ rms units or remember that average power is $\frac{1}{2} VI$.

$$P_{dc} + P_i = P_L + P_{diss}$$

$$P_{dc} = 3(20 \times 10^{-3})(2)$$

↑
same
as P_o

there
are
2
supplies
↯

↑
assume
average
values
=

$$P_{dc} = 120 \text{ mW}$$

$$P_o = \frac{1}{2} \left(\frac{v_o^2}{100} \right) = 24.2 \text{ mW}$$

$$P_i = \frac{P_o}{A_p} = \frac{24.2}{242} = 0.1 \text{ mW}$$

$$\eta = \frac{P_o}{P_{dc}} \times 100 = \frac{24.2}{120} \times 100$$

$$\eta = 20.17\%$$

$$c) P_{diss} = P_{dc} + P_i - P_o$$

$$P_{diss} = 95.9 \text{ mW}$$

②

DC supplies	input at clipping	output at clipping
$\pm 2V$	$\pm 8.5 \text{ mV}$	$v_o = \pm 200(8.5 \times 10^{-3})$ $v_o = \pm 1.7 \text{ V}$
$\pm 5V$	$\pm 21.5 \text{ mV}$	$v_o = \pm 200(21.5 \times 10^{-3})$ $v_o = \pm 4.3 \text{ V}$
$\pm 10V$	$\pm 42.5 \text{ mV}$	$v_o = \pm 200(42.5 \times 10^{-3})$ $v_o = \pm 8.5 \text{ V}$

$$v_o = A v_i$$

$$A = 200 \text{ V/V}$$

so: for $\pm 2V$, $-1.7 \text{ V} \leq v_o \leq 1.7 \text{ V}$


$\pm 5V$, $-4.3 \text{ V} \leq v_o \leq 4.3 \text{ V}$

$\pm 10V$, $-8.5 \text{ V} \leq v_o \leq 8.5 \text{ V}$

Clipping occurs at : $\sim 85\%$ of DC Supply

$$\frac{1.7}{2} = 0.85 \quad ; \quad \frac{4.3}{5} = 0.86$$

$$\frac{8.5}{10} = 0.85$$

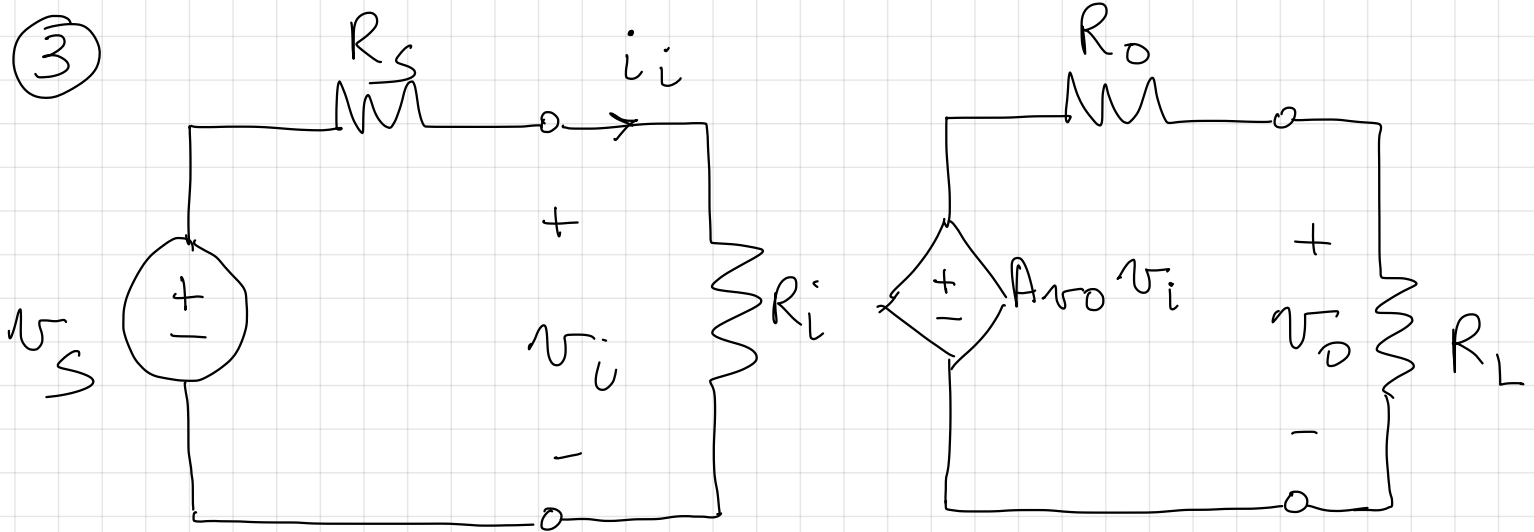

$$R_s = 200 \text{ k}\Omega \quad R_i = 1 \text{ M}\Omega \quad R_L = 150 \Omega$$

$$v_s = 2 \text{ V peak} \quad R_o = 40 \Omega \quad A_{vo} = 1 \text{ V/V}$$

$$v_o = \frac{R_L}{R_L + R_o} (A_{vo} v_i)$$

$$v_i = \frac{R_i}{R_i + R_s} v_s$$

$$v_o = \left(\frac{R_L}{R_L + R_o} \right) (A_{v_o}) \left(\frac{R_i}{R_i + R_s} \right) v_s$$

$$\frac{v_o}{v_s} = \left(\frac{150}{150 + 40} \right) (1) \left(\frac{1 \times 10^6}{1 \times 10^6 + 200 \times 10^3} \right)$$

$$\frac{v_o}{v_s} = (0.789)(1)(0.833)$$

$$A_v = \frac{v_o}{v_s} = 0.6575 \text{ V/V or } -3.64 \text{ dB}$$

means attenuation

$$v_o = 0.6575 \cdot (2) = 1.315$$

$$i_o = \frac{v_o}{R_L} = \frac{1.315}{150} = 8.77 \text{ mA}$$

$$i_i = \frac{v_s}{R_i + R_s} = \frac{2}{1.2 \times 10^6} = 1.67 \mu\text{A}$$

$$A_i = \frac{i_o}{i_i} = 5.25 \times 10^3 \text{ A/A or } 74.4 \text{ dB}$$

$$A_p = \frac{P_o}{P_s} = \frac{v_o i_o}{v_s i_s} = \frac{(1.315)(8.77 \times 10^{-3})}{(2)(1.67 \times 10^{-6})}$$

$$A_p = 3.45 \times 10^3 \frac{W}{W}$$

$$\text{or } 35.38 \text{ dB}$$


I would also expect:

$$A_p = \frac{P_o}{P_i} = \frac{v_o i_o}{i_o^2 (R_i)} = \frac{(1.315)(8.77 \times 10^{-3})}{(1.67 \times 10^{-6})^2 (1 \times 10^6)}$$

$$A_p = 4.14 \times 10^3 \frac{W}{W} \text{ or } 36.16 \text{ dB}$$

↑
does not take into account
the source resistance - it
is pretty minimal.

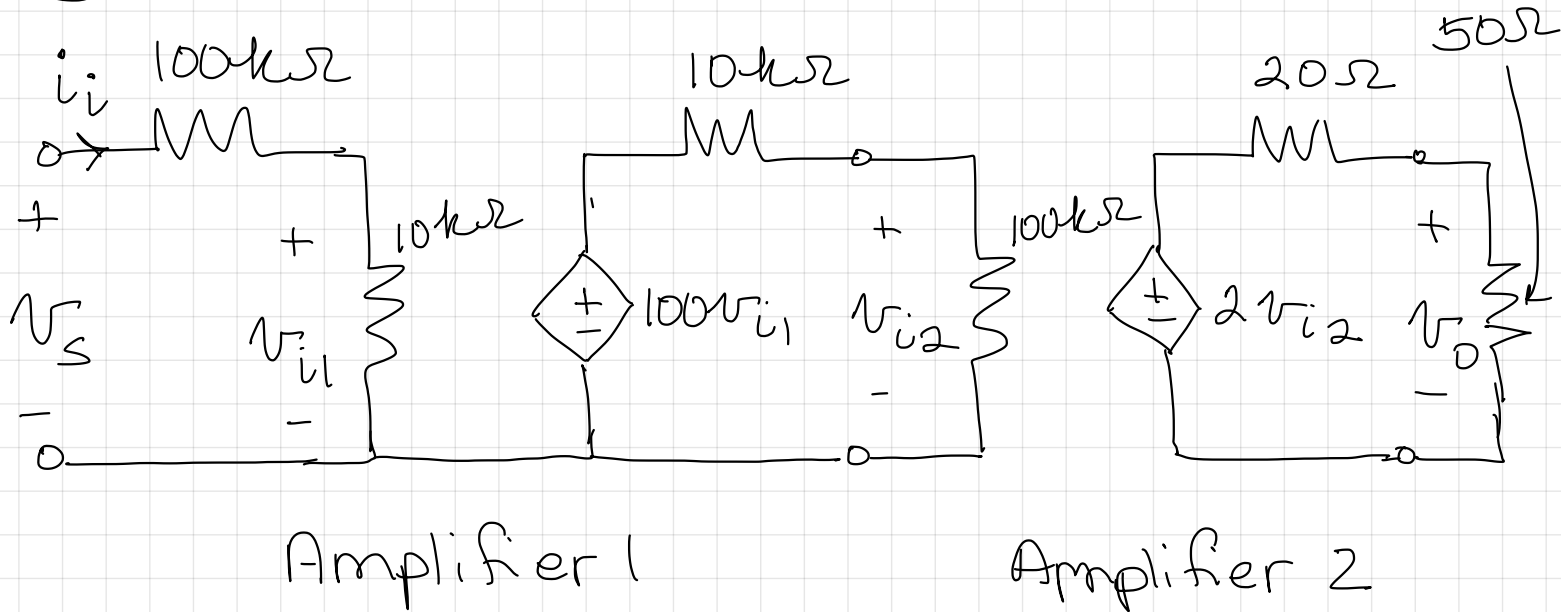④ $v_s = 10 \text{ mV}$ $40 \text{ dB} = 100 \text{ V/V}$ $60 \text{ dB} = 2 \text{ V/V}$



Solve for A_v , A_i , A_p

$$\frac{v_o}{v_s} = \left(\frac{50}{50+20} \right) (2) \left(\frac{100 \times 10^3}{110 \times 10^3} \right) (100) \left(\frac{10 \times 10^3}{110 \times 10^3} \right)$$

$$= (0.714)(2)(0.909)(100)(0.0909)$$

$$\frac{v_o}{v_s} = 23.14 \frac{\text{V}}{\text{V}}$$

A_v

$$v_o = 23.14 (10 \times 10^{-3})$$

$$= 231.47 \text{ mV}$$

$$i_o = \frac{v_o}{50} = 4.63 \text{ mA}$$

$$i_i = \frac{v_s}{110 \times 10^3} = \frac{10 \times 10^{-3}}{110 \times 10^3}$$


$$i_i = 9.09 \times 10^{-8} \text{ A}$$

$$A_i = \frac{i_o}{i_i} = \frac{4.63 \times 10^{-3}}{9.09 \times 10^{-8}}$$

$$= 5.09 \times 10^4 \text{ A/A}$$

$$A_p = \frac{P_o}{P_s} = \frac{v_o i_o}{v_s i_i} = 1.18 \times 10^6 \frac{\text{W}}{\text{W}}$$

Now, let's switch the order:

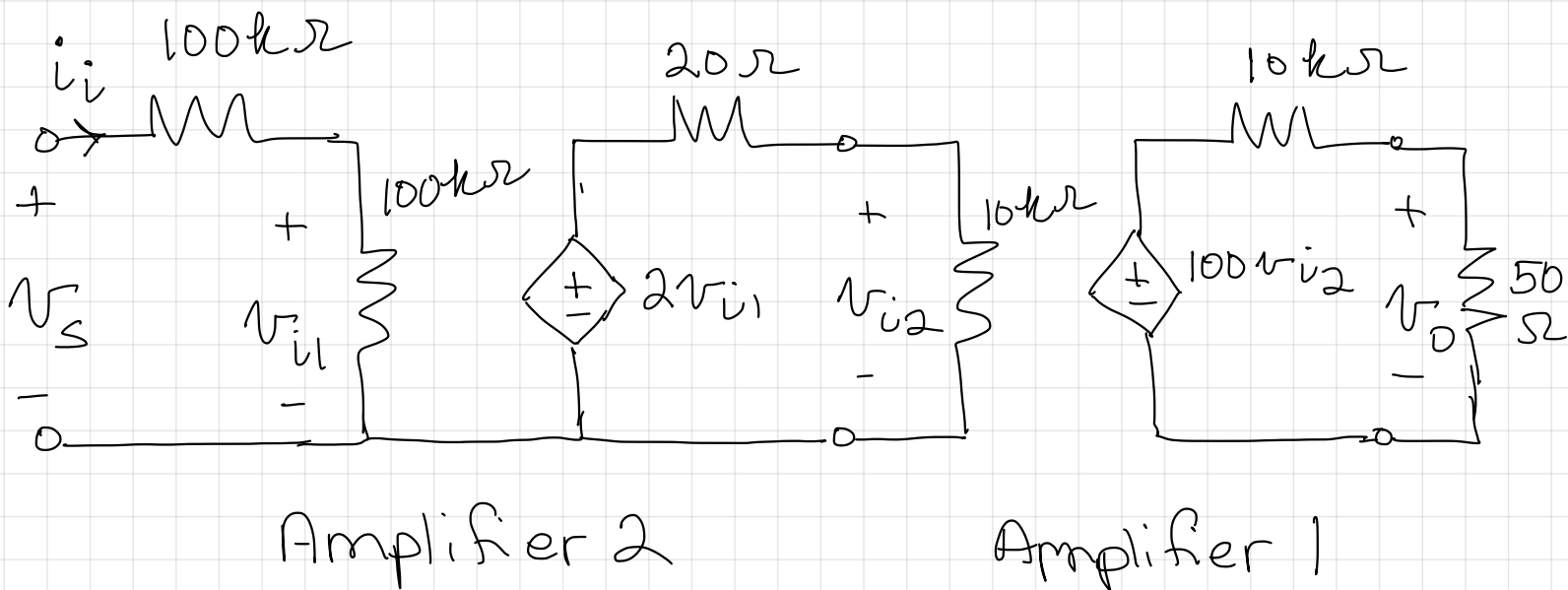

$$\frac{v_o}{v_s} = \left(\frac{50}{50 + 10 \times 10^3} \right) (100) \left(\frac{10 \times 10^3}{10 \times 10^3 + 20} \right) (2) \left(\frac{100 \times 10^3}{200 \times 10^3} \right)$$

$$= (0.005)(100)(0.998)(2)(0.5)$$

$$\frac{v_o}{v_s} = 0.5 \frac{V}{V}$$

$$v_o = 0.5 (10 \times 10^{-3})$$

$$v_o = 5 \text{ mV}$$

$$i_i = \frac{v_s}{200 \times 10^3} = 5 \times 10^{-8} \text{ A}$$

$$i_o = \frac{v_o}{50} = 0.1 \text{ mA}$$

$$A_i = \frac{i_o}{i_i} = 2,000 \text{ A/A}$$

$$A_p = \frac{v_o i_o}{v_s i_i} = 1,000 \text{ W/W}$$

Compare order	A_v	A_i	A_p
Amp1, Amp2	23.14 V/V	5.09×10^4 A/A	1.18×10^6 W/W
Amp2, Amp1	0.5 V/V	2000 A/A	1000 $\frac{W}{W}$

which is better?

It depends, I could make an argument for both.

Amp1, Amp2 : good A_v but very high A_i & A_p - can the load handle it?

Amp2, Amp1 : A_v is small - maybe too small depending on the application but A_i & A_p are pretty good.

My point here is that there is no "right" answer - it depends on the application and what is needed at the load.

And - don't simply pick a stage based on one factor. Based on lectures, you might have been tempted to just go w/ the high R_i as Amp stage 1 and low R_o as Amp stage 2,

that design plan is never
a good one!

→ Get used to this!

We are not in EE 213 land
anymore!

gme