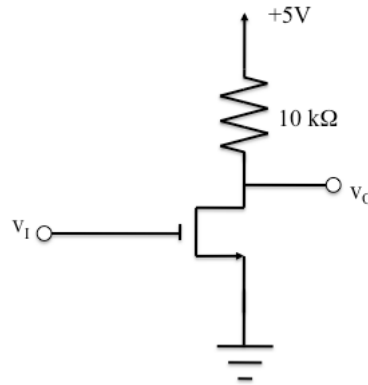


## Module 6: Homework

EE 315

1. Consider the following common source amplifier, where  $V_t = 1.5\text{V}$ ,  $k'_n W/L = .2 \text{ mA/V}^2$ .



- Sketch the voltage transfer characteristic, clearly labeling the transition points, A, B and C.
  - The device is biased for a  $0.15 \text{ mA}$  drain current. Find the Q-point.
  - Find the voltage gain at this bias point.
2. A common source amplifier uses an NMOS transistor with  $k'_n = 0.4 \text{ mA/V}^2$ ,  $W/L = 10$ ,  $V_t = 0.4 \text{V}$ ,  $V_{DD} = 2.5 \text{V}$  and  $V_A = 10 \text{V}$ . The amplifier Q-point is at  $I_{DQ} = 0.2 \text{ mA}$  and uses a drain resistor of  $6.2 \text{ k}\Omega$ .
- Find  $V_{GSQ}$  and  $V_{DSQ}$ .
  - Draw the small signal model and find  $g_m$ ,  $R_{in}$ ,  $A_{vo}$ , and  $R_o$ .
  - If a load resistor is connected to the drain where  $R_L = 15 \text{ k}\Omega$ , what is the gain,  $A_v$ . Update your small signal model.
  - If a source signal,  $v_{sig}$  in series with a resistance of  $R_{sig} = 300 \text{ k}\Omega$  is connected to the gate, what is the gain,  $G_v$ .
3. A common gate amplifier uses an NMOS transistor with  $g_m = 4 \text{ mA/V}$  and a drain resistor of  $5 \text{ k}\Omega$  and a load resistor of  $7.5 \text{ k}\Omega$ . The amplifier is driven by a source,  $v_{sig}$ , that has  $R_{sig} = 500 \text{ ohms}$ .
- Find the input resistance ( $R_{in}$ ) and the overall voltage gain,  $G_v$ . Draw the small signal model.
  - Suppose we want the input resistance to equal the signal resistance at the Q-point,  $I_{DQ}$ . What would the drain current Q-point need to change to for this to happen?

4. A common drain amplifier has the following characteristics:  $k'_n=0.1\text{mA/V}^2$  and  $V_t = 0.6\text{V}$ . The operating point is  $V_{GSQ}=0.85\text{ V}$ .
- What is the  $W/L$  ratio for an output resistance of 300 ohms?
  - What is the drain current at the operating point?
  - This amplifier is connected to a 10kohm potentiometer as the load. What is the range of possible overall voltage gain?