

Find I_B & V_B
Using Nodal Analysis

Know: $V_1 = 8V$

$$V_B = -V_2$$

$$I_B = \frac{V_3 - V_2}{5}$$

Node 1: don't need it

$$\text{Node 2: } \frac{V_2 - V_3}{5} + \frac{V_2}{4} + \frac{V_2 + 0.5I_B - V_1}{1} = 0$$

$$\text{Node 3: } 2V_B + (-2) + \frac{V_3 - V_2}{5} = 0$$

$$V_\alpha - V_2 = 0.5I_B$$

$$V_\alpha = 0.5I_B + V_2$$

$$\frac{V_\alpha - V_1}{1} = \frac{V_2 + 0.5I_B - V_2}{1}$$

$$N2: V_2(1.35) + V_3(-0.1) = 8$$

$$N3: V_2(-2.2) + V_3(0.2) = 2$$

$$V_2 = 36V$$

$$V_3 = 406V$$

\Rightarrow

$$V_B = -36V$$

$$I_B = 74A$$

Mesh Analysis

Streamlined version of KVL
write KVL eqns in terms of
mesh current variables.

- mesh is a loop that contains no other loops



Mesh Analysis Steps

① Identify the ckt meshes and give each mesh a mesh current variable and a loop direction.

② Write KVL equations for each mesh \rightarrow mesh eqns



Hierarchy for writing down voltages

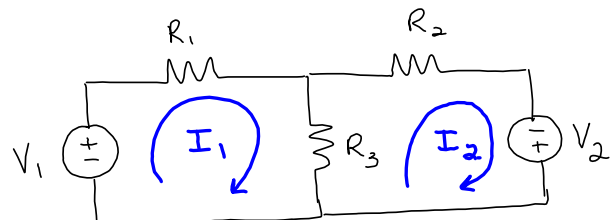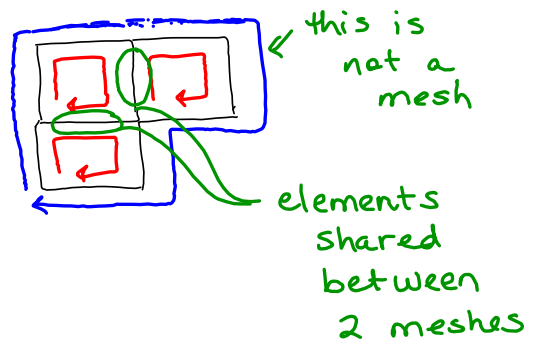- ① Voltage source?
 - ② Resistor $\Rightarrow V = IR$
 - ③ Label a variable/polarity
- ③ Solve the equations




The Rule :

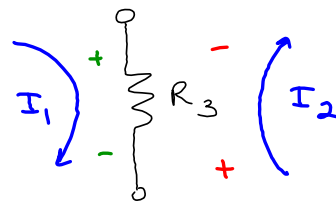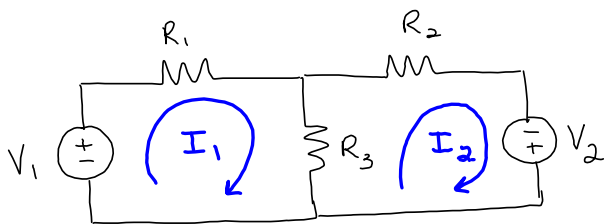whichever mesh is being analyzed, that mesh current flows from (+) to (-) for the resistors in that mesh.



$$m1: V_1 - I_1 R_1 - (I_1 - I_2) R_3 = 0$$
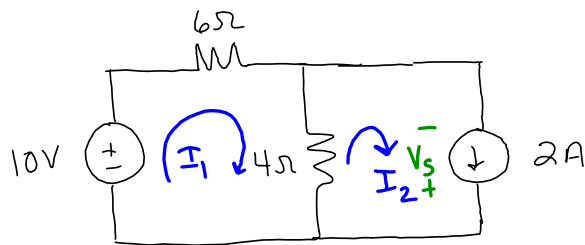
$$m2: -I_2 R_2 + V_2 - (I_2 - I_1) R_3 = 0$$



Know: $I_2 = 2A$

$$m1: 10 - 6I_1 - 4(I_1 - \overset{2A}{I_2}) = 0$$


$$-10I_1 = -18$$

$$I_1 = 1.8A$$

m2: Don't need

$$m2: -4(I_2 - I_1) + V_S = 0$$

$$V_S = 4(I_2 - I_1) = 0.8V$$

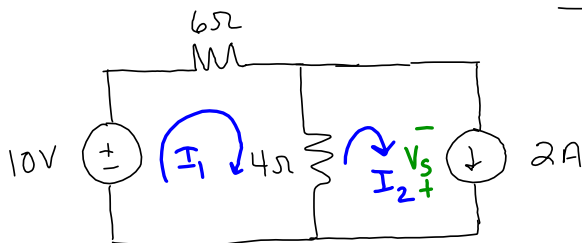

$$I_1 = 1.8A$$

$$I_2 = 2A$$

$$V_S = 0.8V$$

Sources: $P = VI$

$$10V: P = (10)(I_1) = 18W, \text{ Del}$$

$$2A: P = V_S(2) = 1.6W, \text{ Del}$$


$$\sum P_{del} = 19.6W$$

$$\sum P_{abs} = 19.6W$$

Resistors $P = I^2R$

$$6\Omega: P = I_1^2(6) = 19.44W, \text{ Abs}$$
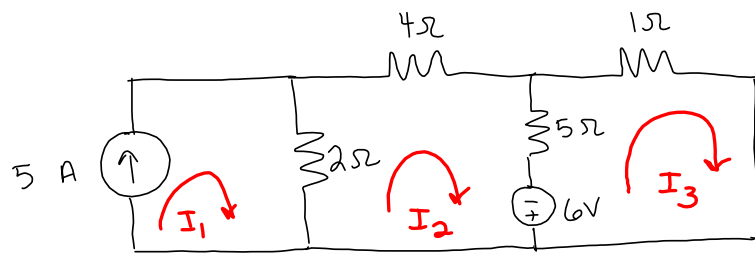
$$4\Omega: P = (I_2 - I_1)^2(4) = 0.16W, \text{ Abs}$$



Find mesh
currents and
 V_S .

Know: $*I_1 = 5A$

$$V_S = 2(I_1 - I_2)$$

$$m2: -2(I_2 - \overset{5A}{I_1}) - 4I_2 - 5(I_2 - I_3) + 6 = 0$$

$$m3: -6 - 5(I_3 - I_2) - 1I_3 = 0$$

$$m2: -11I_2 + 5I_3 = -16$$

$$m3: 5I_2 - 6I_3 = 6$$

$$I_2 = 1.61 A$$

$$I_3 = 0.341 A$$

$$V_S = 6.78 V$$