
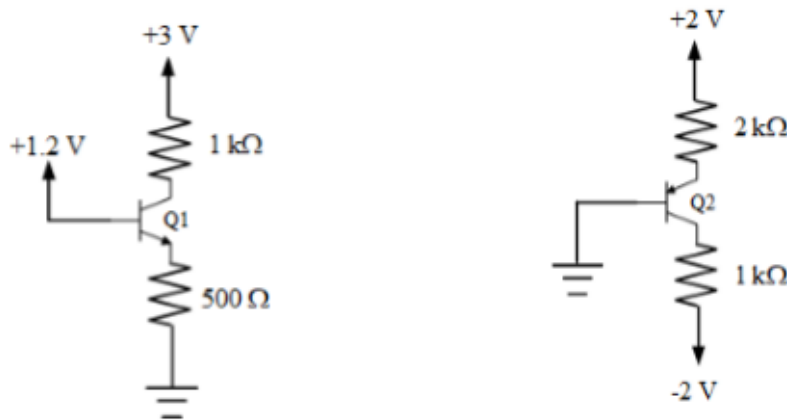


Practice Problems Module 5

1. For an npn BJT, the voltage $v_{BE}=0.74\text{ V}$ for $i_C=9.5\text{mA}$. What i_C for $v_{BE}=0.714\text{ V}$?
2. For a given BJT, $i_B=0.010\text{mA}$ and $i_C=0.6\text{mA}$. What are I_S , β , α , and i_E ?
3. A BJT has $I_S=5\times 10^{-15}\text{ A}$ and β fall in the range of 50 to 500. If the BJT operates in the active mode with $v_{BE} = 0.64\text{V}$, find the expected range of the collector, base, and emitter currents.
4. For Q_1 and Q_2 below, find the collector, base, and emitter currents for $\beta=50$ and $|V_{BE}|=0.8\text{V}$. What is the mode of operation for each circuit?

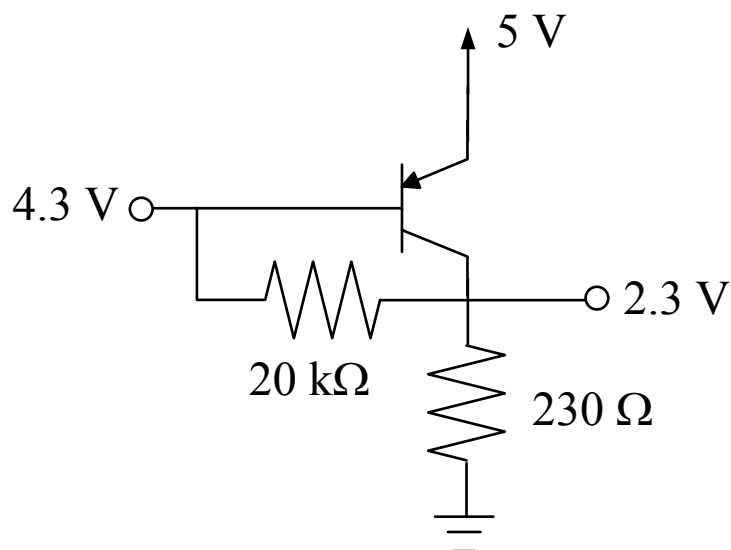

5. For the pnp transistor circuit below, find I_C and β .



6. For the following transistor, find the collector, base, and emitter currents and the collector and emitter voltages for the case where $\beta=100$ and β being very large. Assume $V_{BE}=0.7$ V. Do this for each of the following base voltages: $V_B=0$ V, $V_B=1$ V, and $V_B=2$ V.


$$V_{BE} = 0.7 \text{ V} \quad \alpha = \frac{100}{101} = .99$$

$$V_E = -0.7 \text{ V} = 0.3 \text{ V} = 1.3 \text{ V}$$

$$I_E = -.28 \text{ mA} = .12 \text{ mA} = .52 \text{ mA}$$

$$I_C = -.27 \text{ mA} \\ = 0.12 \text{ mA} \\ = .515 \text{ mA}$$
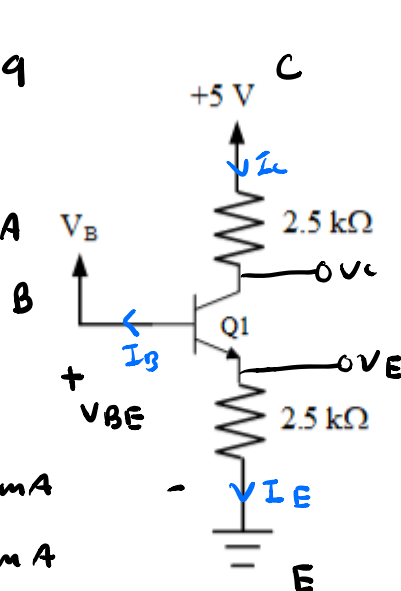
$$I_B = -2.7 \text{ mA} \quad I_E = -.28 \text{ mA} \\ = 1.2 \text{ mA} \quad = .12 \text{ mA} \\ = 5.1 \text{ mA} \quad = .52 \text{ mA}$$



$$\left. \begin{array}{l} I_C \\ I_B \\ I_E \\ V_C \\ V_E \end{array} \right\} ? \quad I_C = \frac{5 - V_C}{2.5}$$

$$V_B = 0 = 1 = 2$$

$$V_E = 0 - .7 = -0.7 \text{ V}$$

$$V_E = 1 - .7 = 0.3 \text{ V}$$

$$V_E = 2 - 0.7 = 1.3 \text{ V}$$

$$I_E = \frac{-0.7 - 0}{2.5 \text{ k}\Omega}$$

$$I_E = \frac{0.3 - 0}{2.5 \text{ k}\Omega}$$

$$I_E = \frac{1.3 - 0}{2.5 \text{ k}\Omega}$$

$$I_C = \alpha I_E = (.99)(-.28) = (.99)(.12) = (.99)(.52)$$

$$I_B = \frac{-.27 \text{ mA}}{100}$$

$$I_B = \frac{.12}{100}$$

$$I_B = \frac{.515}{100}$$

$$I_C = \frac{5 - V_C}{2.5 \text{ k}\Omega}$$

$$(2.5 \text{ E} 3)($$

1. For an npn BJT, the voltage $v_{BE}=0.74$ V for $i_C=9.5$ mA. What i_C for $v_{BE}=0.714$ V?

$$\begin{array}{ll} v_{BE} = 0.74 \text{ V} & v_{BE} = 0.714 \text{ V} \\ i_C = 9.5 \text{ mA} & i_C = ? \end{array}$$

$$v_{BE2} - v_{BE1} = V_T \ln \left(\frac{i_{C2}}{i_{C1}} \right)$$

$$\begin{aligned} 0.714 - 0.74 &= -0.025 \ln \left(\frac{i_{C2}}{9.5} \right) \\ -1.04 &= \ln \left(\frac{i_{C2}}{9.5} \right) \end{aligned}$$

$$x = \frac{9.5}{e^{1.04}} ; x = 3.36 \text{ mA}$$

Metric Prefix	Symbol	Multiplier (Traditional Notation)	Exponential	Description
Yotta	Y	1,000,000,000,000,000,000,000,000	10^{24}	Septillion
Zetta	Z	1,000,000,000,000,000,000,000,000	10^{21}	Sextillion
Exa	E	1,000,000,000,000,000,000,000	10^{18}	Quintillion
Peta	P	1,000,000,000,000,000,000	10^{15}	Quadrillion
Tera	T	1,000,000,000,000,000	10^{12}	Trillion
Giga	G	1,000,000,000	10^9	Billion
Mega	M	1,000,000	10^6	Million
kilo	k	1,000	10^3	Thousand
hecto	h	100	10^2	Hundred
deca	da	10	10^1	Ten
base	b	1	10^0	One
deci	d	1/10	10^{-1}	Tenth
centi	c	1/100	10^{-2}	Hundredth
milli	m	1/1,000	10^{-3}	Thousandth
micro	μ	1/1,000,000	10^{-6}	Millionth
nano	n	1/1,000,000,000	10^{-9}	Billionth
pico	p	1/1,000,000,000,000	10^{-12}	Trillionth
femto	f	1/1,000,000,000,000,000	10^{-15}	Quadrillionth
atto	a	1/1,000,000,000,000,000,000	10^{-18}	Quintillionth
zepto	z	1/1,000,000,000,000,000,000,000	10^{-21}	Sextillionth
yocto	y	1/1,000,000,000,000,000,000,000,000	10^{-24}	Septillionth

2. For a given BJT, $i_B=0.010$ mA and $i_C=0.6$ mA. What are I_S , β , α , and i_E ?

$$\begin{array}{ll} i_B = 0.010 \text{ mA} & \beta = 60 \\ i_C = 0.6 \text{ mA} & \alpha = .984 \end{array}$$

$$\begin{aligned} i_B &= \frac{i_C}{\beta} & \beta &= \frac{\alpha}{\alpha-1} & \alpha &= \frac{\beta}{\beta+1} \\ i_E &= i_B + i_C \\ i_E &= i_B + i_C \end{aligned}$$

$$i_E = .010 + .6 = 0.61 \text{ mA} \quad i_E = 0.61 \text{ mA}$$

$$\beta = \frac{0.6}{.010} = 60$$

$$\alpha = \frac{60}{61} = .984$$

3. A BJT has $I_S = 5 \times 10^{-15}$ A and β fall in the range of 50 to 500. If the BJT operates in the active mode with $V_{BE} = 0.64$ V, find the expected range of the collector, base, and emitter currents.

$$I_S = 5 \times 10^{-15}$$

$$50 \leq \beta \leq 500$$

$$\text{Active mode ; } V_{BE} = 0.64 \text{ V}$$

$$\left. \begin{matrix} i_C \\ i_B \\ i_E \end{matrix} \right\} \text{ ranges?}$$

$$I_C = I_S \exp(V_{BE}/V_T)$$

$$i_B = \frac{i_C}{\beta} \quad \beta = \frac{\alpha}{\alpha - 1} \quad \alpha = \frac{\beta}{\beta + 1}$$

$$i_E = i_B + i_C$$

$$I_C = 5 \times 10^{-15} \exp\left(\frac{0.64}{0.025}\right) = \underline{0.000656} \quad 0.656 \text{ mA}$$

$$i_B = \frac{i_C}{\beta} \Rightarrow \frac{.656 \times 10^{-4}}{50} \quad \text{or} \quad \frac{.656 \times 10^{-4}}{500}$$

$$i_B = 13.1 \text{ nA} \quad \text{to} \quad 1.31 \text{ nA}$$

$$i_E = i_C + i_B$$

$$i_E = 13.1 \text{ nA} + .656 \text{ mA}$$



$$i_E = 13.1 \times 10^{-6} + .656 \times 10^{-3}$$

$$i_E = 1.31 \text{ nA} + .656 \text{ mA}$$

$$i_E = 1.31 \times 10^{-6} + .656 \times 10^{-3}$$

$$i_E = .669 \text{ mA} \quad \text{to} \quad .657 \text{ mA}$$

4. For Q₁ and Q₂ below, find the collector, base, and emitter currents for $\beta=50$ and $|V_{BE}|=0.8V$. What is the mode of operation for each circuit?

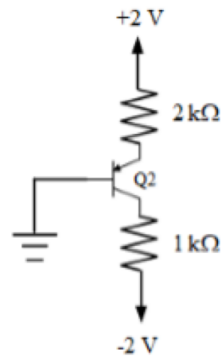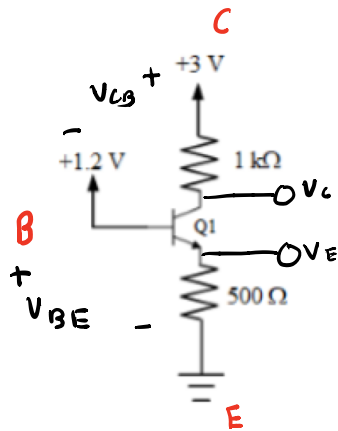

$$V = IR$$

$$V_B = 1.2V$$

$$V_E = 1.2 - 0.8 = 0.4V$$

$$\alpha = \frac{50}{51} = .98$$

$$V_{BE} > 0$$

$$V_{CB} = ?$$

$$I_E = \frac{0.4}{500} = 0.8mA$$

$$I_C = \alpha I_E$$

$$I_C = .98 \times .8mA = .784mA$$

$$I_B = I_E - I_C$$

$$I_B = .8 - .784$$

$$I_B = .02mA$$

$$I_C = \frac{3 - V_C}{1k\Omega}$$

$$.784 = 3 - V_C$$

$$I_E = .8mA$$

$$I_C = .784mA$$

$$I_B = .02mA$$


$$\left| \begin{array}{l} \beta = 50 \\ \alpha = .98 \\ V_B = 1.2V \end{array} \right|$$

$$V_E = 0.4V$$

$$V_C = 2.22V$$

$$V_C > V_B > V_E \Rightarrow \text{Active}$$

4. For Q_1 and Q_2 below, find the collector, base, and emitter currents for $\beta=50$ and $|V_{BE}|=0.8V$. What is the mode of operation for each circuit?

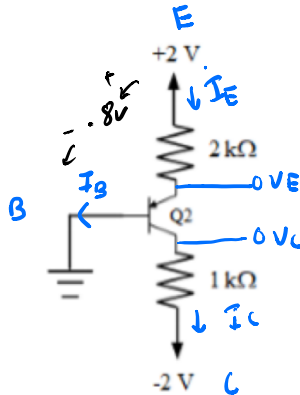

Answers

$$\begin{aligned} \beta &= 50 & V_B &= 0 & I_E &= .6 \text{ mA} \\ |V_{BE}| &= .8 \text{ V} & V_E &= .8 \text{ V} & i_C &= .58 \text{ mA} \\ \alpha &= .98 & V_C &= -1.42 \text{ V} & i_B &= .02 \text{ mA} \\ V_C &< V_B < V_E & \rightarrow & \text{Active} \end{aligned}$$

Work

$$V_E - V_B = .8 \text{ V}$$

$$I_E = \frac{2 - .8 \text{ V}}{2 \text{ k}\Omega} = .6 \text{ mA}$$

$$\alpha = \frac{50}{51} = .98$$

$$i_C = .98 (.6 \text{ E-}3)$$


$$i_B = i_E - i_C$$

$$i_B = .6 - .58$$

$$I_C = \frac{V_C + 2}{1000} \Rightarrow V_C + 2 = .58$$

$$V_C = -1.42 \text{ V}$$

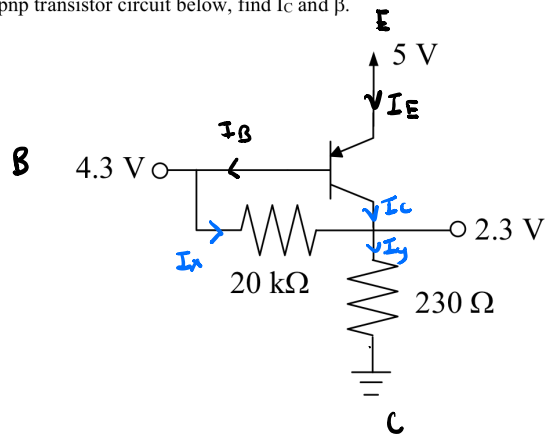5. For the pnp transistor circuit below, find I_C and β .



$$I_Y = \frac{2.3 - 0}{230} = 10 \text{ mA}$$

$$I_X = \frac{4.3 - 2.3}{20000} = 0.1 \text{ mA}$$

$$I_C = I_Y - I_X \quad I_B = 0.1 \text{ mA}$$

$$I_C = 10 - 0.1$$

$$I_C = 9.9 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} \Rightarrow \frac{9.9}{0.1} = 99$$

$$\beta = 99$$