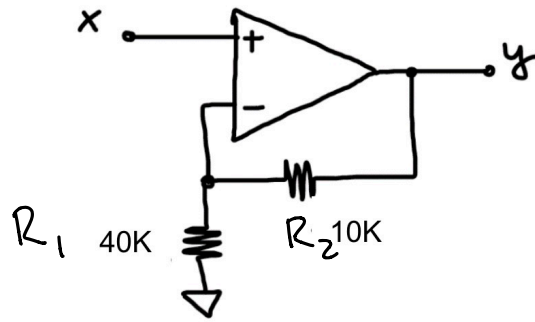


1. (10 points) What is the transfer function of the following circuit:



$$y(t) \cdot \frac{R_1}{R_1 + R_2} = x(t)$$

$$y(t) = \frac{R_1 + R_2}{R_1} \cdot x(t)$$

$$H(s) = \frac{Y(s)}{X(s)} = \frac{\mathcal{L}[y(t)]}{\mathcal{L}[x(t)]}$$

$$y(t) = \frac{40k + 10k}{40k} \cdot x(t)$$

$$y(t) = \frac{5}{4} x(t)$$


$$\mathcal{L}[y(t)] = \frac{5}{4} \mathcal{L}[x(t)]$$

$$H(s) = \frac{\mathcal{L}[y(t)]}{\mathcal{L}[x(t)]} = \boxed{\frac{5}{4}}$$

3. (10 points)

Find impulse response of capacitor and its unit step response. How step response depends on the capacitance of the capacitor?

Impulse Response of a Capacitor

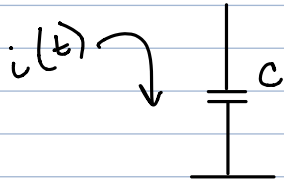

$$v_C(t) = \frac{1}{C} \int_0^t i(t) dt$$

$$h(t) = \frac{1}{C} \int_0^t \delta(z) dz$$

↑ impulse

$$h(t) = \frac{1}{C} u(t)$$

impulse

Unit step:

$$v(t) = \int_{-\infty}^{\infty} x(z) h(t-z) dz$$

$$v(t) = \int_0^t 1 \cdot \frac{1}{C} dz = \frac{1}{C} \int_0^t dz$$


$$v(t) = \frac{1}{C} t = \boxed{\frac{t}{C}} \text{ Unit step response}$$

$$v_C(t) = \int_{-\infty}^{\infty} h(t-z) i(t-z) dz$$

$$= \int_{-\infty}^{\infty} \frac{1}{C} u(t-z) u(t) dz$$

$$= \frac{1}{C} \int_0^t dz = \boxed{\frac{1}{C} v(t)}$$

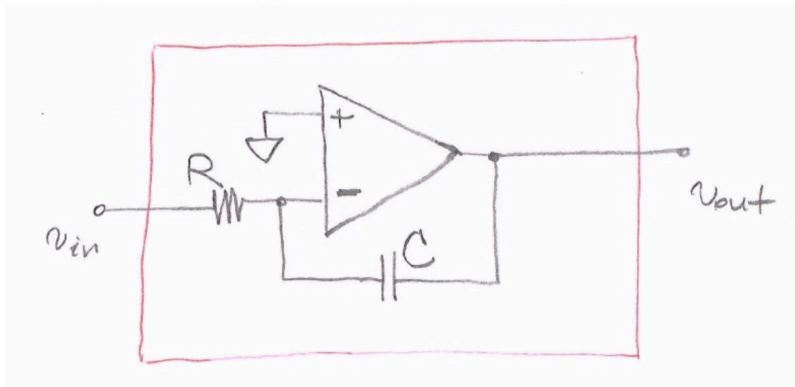4. (15 points) Find transfer function of the following circuit. What is the output voltage at $t=0.4s$ if the input is step function $u(t)$, $R=10K\Omega$, and $C=10\mu F$?



$$v_c(t) = \frac{1}{C} \int_0^t i(t) dz$$

$$v_{out} = -v_{in}$$

$$V = IR \rightarrow I = \frac{V}{R}$$

$$\Rightarrow v_{out}(t) = -\frac{1}{C} \int_0^t \frac{v_i(t)}{R} dz$$

$$v_{out}(t) = -\frac{1}{RC} \int_0^t v_i(t) dz$$

$$v_{out}(t) = -\frac{1}{RC} [v_i t]_0^t = -\frac{v_i}{RC} [t]_0^t$$

$$\frac{v_o(t)}{v_i(t)} = -\frac{1}{RC} [t]_0^t$$

$$\frac{v_o(t)}{v_i(t)} = -\frac{1}{RC} [t - 0] = -\frac{t}{RC}$$

$$H(s) = \frac{\mathcal{L}[v_o(t)]}{\mathcal{L}[v_i(t)]} = \mathcal{L}\left[-\frac{t}{RC}\right] = -\frac{1}{RC} \mathcal{L}[t] \quad \mathcal{L}[t] = \frac{1}{s}$$

Transfer function: w/ $R = 10 k\Omega$ and $C = 10 \mu F$

$$H(s) = \frac{-1}{RCs} \quad \text{or} \quad h(t) = \frac{-t}{RC}$$

$$h(0.4) = \frac{v_o(0.4)}{v_i(0.4)} = \frac{-(0.4)}{(10k)(10\mu)}$$

$$v_o(t) = \frac{-(0.4)}{(10k)(10\mu)} \cdot v_i(t) = \boxed{-4 V} \quad \text{or} \quad -4v_i$$

given no v_i

6. (10 points)

Describe the basic properties of the one sided Laplace transform.

1. It is linear, so $\mathcal{L}[af(t) + bg(t)] = aF(s) + bF(s)$

2. It can be shifted by time or freq. so:

$$\mathcal{L}[f(t-a)u(t-a)] = e^{-as}F(s)$$

$$\mathcal{L}[e^{at}f(t)] = F(s-a)$$

3. For multiplication by t :

$$\mathcal{L}[t f(t)] = -\frac{dF(s)}{ds}$$

4. For the derivative + second derivative:

$$\mathcal{L}\left[\frac{df(t)}{dt}\right] = sF(s) - f(0-)$$

$$\mathcal{L}\left[\frac{d^2f(t)}{dt^2}\right] = s^2F(s) - sf(0-) - f'$$

5. For integrals:

$$\mathcal{L}\left[\int_0^t f(t') dt'\right] = \frac{F(s)}{s}$$

6. For expansion / contraction:

$$\mathcal{L}[f(at)] = \frac{1}{|a|} F\left(\frac{s}{a}\right) \quad \text{where } a \neq 0$$

7. For initial value:

$$\mathcal{L}[f(0-)] = \lim_{s \rightarrow \infty} sF(s)$$

7. (15 points)

Find and use the Laplace transform of $e^{j(\Omega_0 t + \theta)} u(t)$ to obtain the Laplace transform of $x(t) = \cos(\Omega_0 t + \theta) \cdot u(t)$

Consider the special cases for $\theta = 0$, $\theta = -\pi/2$, and $\theta = \pi/4$.

$$\begin{aligned}\mathcal{L}[e^{j(\Omega_0 t + \theta)} u(t)] &= \int_0^{\infty} e^{j(\Omega_0 t + \theta)} e^{-st} dt \\&= e^{j\theta} \int_0^{\infty} e^{-(s - j\Omega_0)t} dt = \frac{-e^{j\theta}}{s - j\Omega_0} e^{-st - j(\Omega_0 - \Omega_0)t} \Big|_0^{\infty} \\&= \frac{e^{j\theta}}{s - j\Omega_0} \rightarrow \text{complex causal side}\end{aligned}$$

By Euler's Identity:

$$\cos(\Omega_0 t + \theta) = \frac{e^{j(\Omega_0 t + \theta)} + e^{-j(\Omega_0 t + \theta)}}{2}$$

Knowing \uparrow and linearity of the integral:

$$\begin{aligned}X(s) &= \mathcal{L}[\cos(\Omega_0 t + \theta) u(t)] \\&= 0.5 \mathcal{L}[e^{j(\Omega_0 t + \theta)} u(t)] + 0.5 \mathcal{L}[e^{-j(\Omega_0 t + \theta)} u(t)]\end{aligned}$$

solved for in first step

$$= 0.5 \left[\frac{e^{j\theta} (s + j\Omega_0) + e^{-j\theta} (s - j\Omega_0)}{s^2 + \Omega_0^2} \right]$$

$$= \boxed{0.5 \left[\frac{s \cos(\theta) - \Omega_0 \sin(\theta)}{s^2 + \Omega_0^2} \right]}$$

Case $\theta = 0$

$$\mathcal{L}[\cos(\Omega_0 t) u(t)] = \boxed{\frac{s}{s^2 + \Omega_0^2}}$$

Case $\theta = -\frac{\pi}{2}$

$$\cos(\omega_0 t - \pi/2) = \sin(\omega_0 t) \quad \text{so:}$$

$$\mathcal{L}[\sin(\omega_0 t)] = \boxed{\frac{\omega_0}{s^2 + \omega_0^2}}$$

Case $\theta = \frac{\pi}{4}$

$$\cos\left(\frac{\pi}{4}\right) = \sin\left(\frac{\pi}{4}\right) = \frac{\sqrt{2}}{2}$$

$$\mathcal{L}\left[\cos\left(\omega_0 t + \frac{\pi}{4}\right)\right] = \boxed{\frac{\frac{\sqrt{2}}{2}(s + \omega_0)}{s^2 + \omega_0^2}}$$