




Thur.

Solutions on  
Canvas



Hint :  $I_S = 1.889 \text{ A}$

## Voltage Division

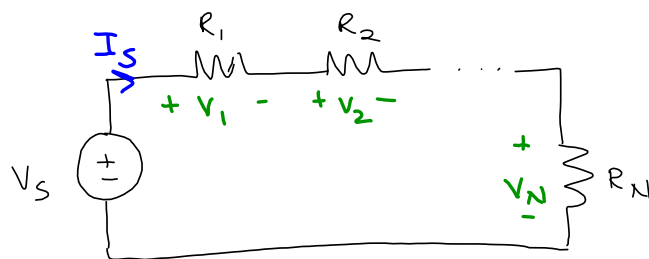

$$I_s = \frac{V_s}{R_1 + R_2 + \dots + R_N}$$

$$V_1 = I_s R_1$$

$$V_2 = I_s R_2$$

$$\vdots$$

$$V_N = I_s R_N$$

$$V_1 = \left( \frac{V_s}{R_1 + R_2 + \dots + R_N} \right) R_1$$


Let  $R_{eq} = R_1 + R_2 + \dots + R_N$

$$V_1 = V_s \left( \frac{R_1}{R_{eq}} \right)$$


$$V_2 = V_s \left( \frac{R_2}{R_{eq}} \right)$$

$$V_i = V_s \left( \frac{R_i}{\sum R} \right)$$


voltage divider

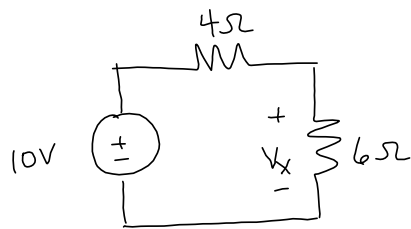
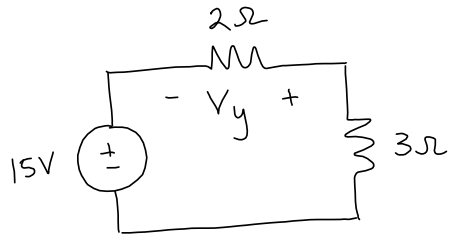
$$V_x = 10 \left( \frac{6}{4+6} \right) = 6V$$



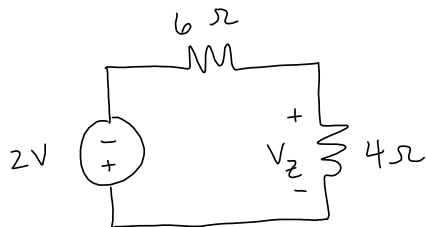
$$V_y = -(15) \left( \frac{2}{3+2} \right) = -6V$$



$$V_z = -(2) \left( \frac{4}{10} \right) = -0.8V$$

## Current Division

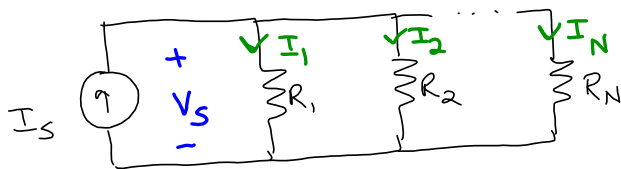

$$V_s = I_s \left( \frac{1}{\underbrace{\left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)}_{R_1 \parallel R_2 \parallel \dots \parallel R_N}} \right)$$

by Ohm's Law

$$\rightarrow V_s = I_s (R_1 \parallel R_2 \parallel \dots \parallel R_N)$$

$$I_1 = \frac{V_s}{R_1}$$

$$I_1 = \frac{I_s (R_1 \parallel R_2 \parallel \dots \parallel R_N)}{R_1} \quad \text{let } R_{eq} = (R_1 \parallel R_2 \parallel \dots \parallel R_N)$$


$$I_2 = \frac{V_s}{R_2}$$

$$I_1 = I_s \left( \frac{R_{eq}}{R_1} \right)$$


$$I_N = \frac{V_s}{R_N}$$

$$I_2 = I_s \left( \frac{R_{eq}}{R_2} \right)$$
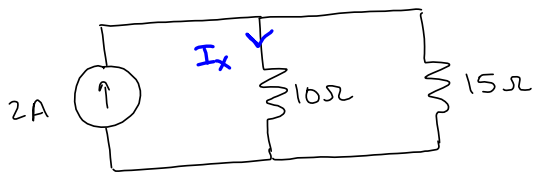
$$I_i = I_s \left( \frac{R_{eq}}{R_i} \right) \Rightarrow \text{current division}$$


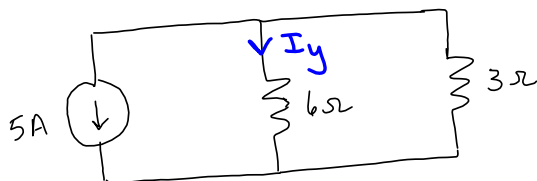
$$I_x = 2 \left( \frac{10 \parallel 15}{10} \right) = 1.2 \text{ A}$$



$$I_y = -5 \left( \frac{6 \parallel 3}{6} \right) = -1.67 \text{ A}$$


## Nodal Analysis

- streamlined version of KCL
- write KCL in terms of node voltage variables

## Steps

① Identify nodes w/  
3 or more connections.

② Ground one of those nodes.

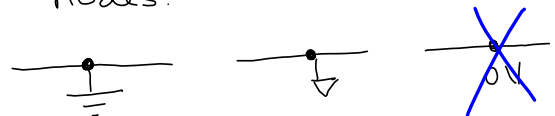

Call this node  $\equiv$  reference node

③ Assign a node voltage variable to the remaining nodes from ①

$$V_1, V_2 \dots$$

$$V_A, V_B \dots$$


## Hierarchy of writing currents

- ① Current source
- ② Resistor  $\frac{V}{R}$
- ③ Label a current variable | reference

④ Write KCL at each node from ③

$\Sigma$  currents leaving node.

⑤ Solve

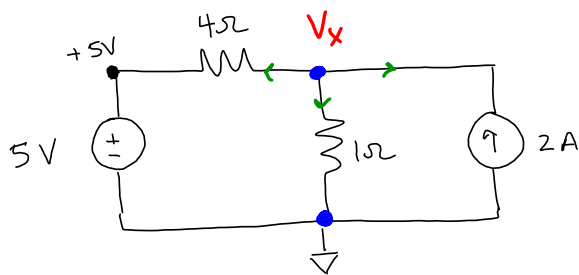

→ KCL = Nodal equations

$$-(2) + \frac{V_x - 0}{1} + \frac{V_x - 5}{4} = 0$$

$$V_x \left( \frac{1}{1} + \frac{1}{4} \right) = 2 + \frac{5}{4}$$

$$V_x (1.25) = 3.25$$

$$V_x = 2.6 \text{ V}$$

Sources:  $P = VI$

$$2A: P = V_x (2) = 5.2 \text{ W, Del}$$

$$5V: P = 5 \left( \frac{V_x - 5}{4} \right) = -3 \text{ W, Abs}$$

$$P_1 = +3 \text{ W, Del}$$

Resistors  $V^2/R$

1Ω:

$$P = \frac{V_x^2}{1} = 6.76 \text{ W, Abs}$$

$$4\Omega: P = \frac{(V_x - 5)^2}{4} = 1.44 \text{ W Abs}$$

$$\sum P_{del} = 8.2 \text{ W} \quad \sum P_{abs} = 8.2 \text{ W}$$

