

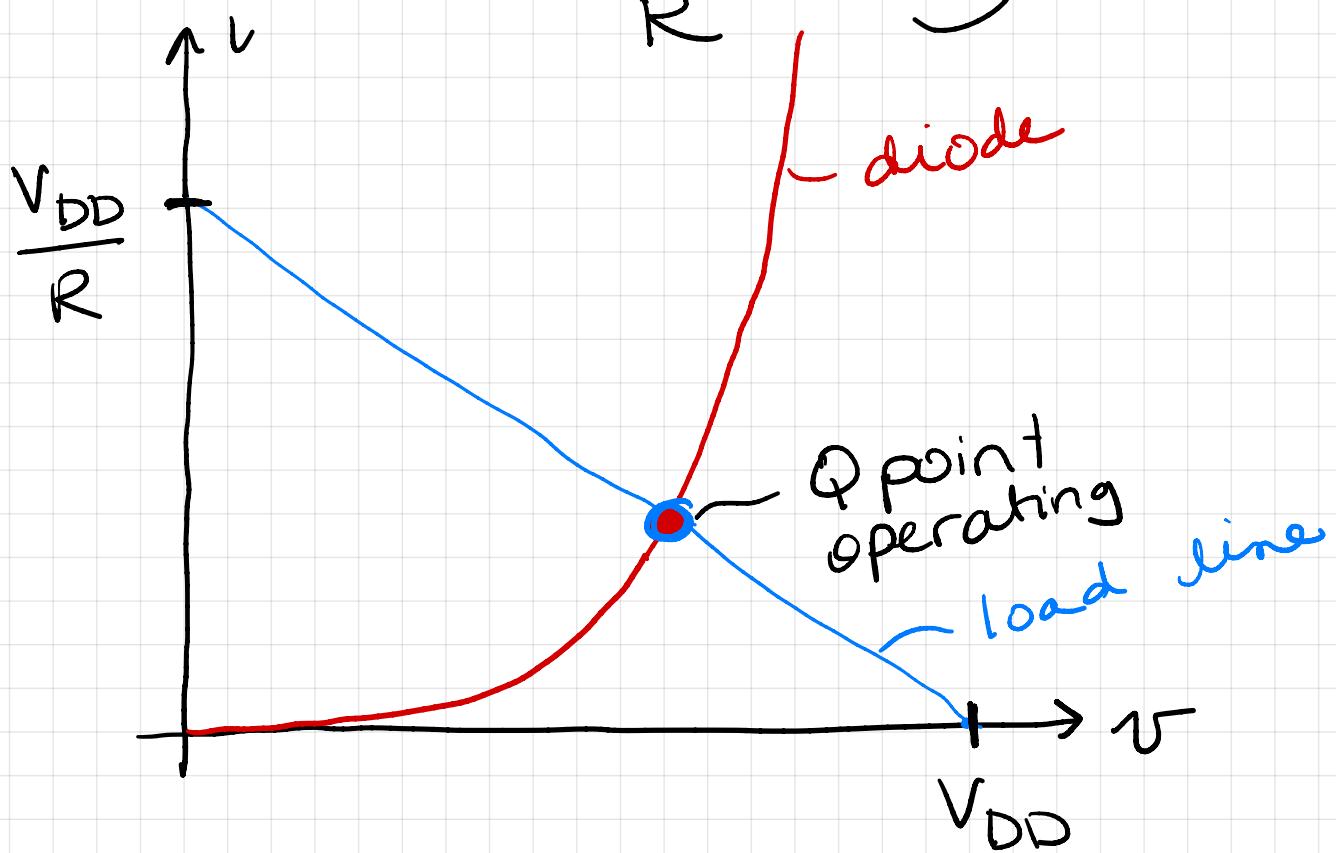


$$- I_D = I_S \exp\left(\frac{V_D}{V_T}\right)$$

most accurate model

$$- I_D = \frac{V_{DD} - V_D}{R}$$

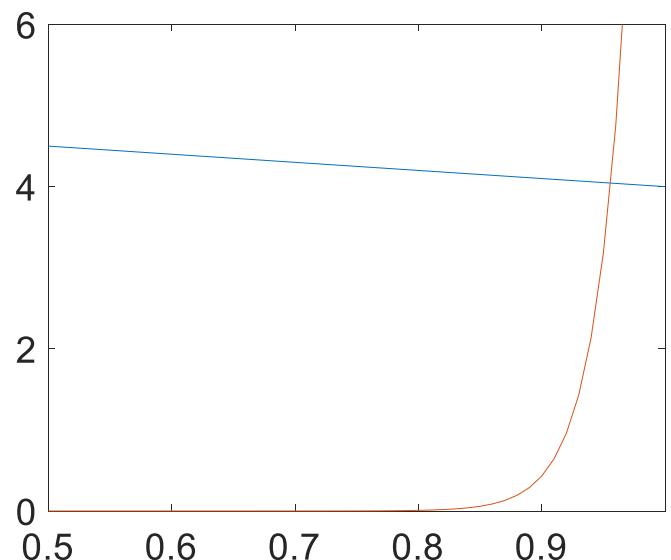

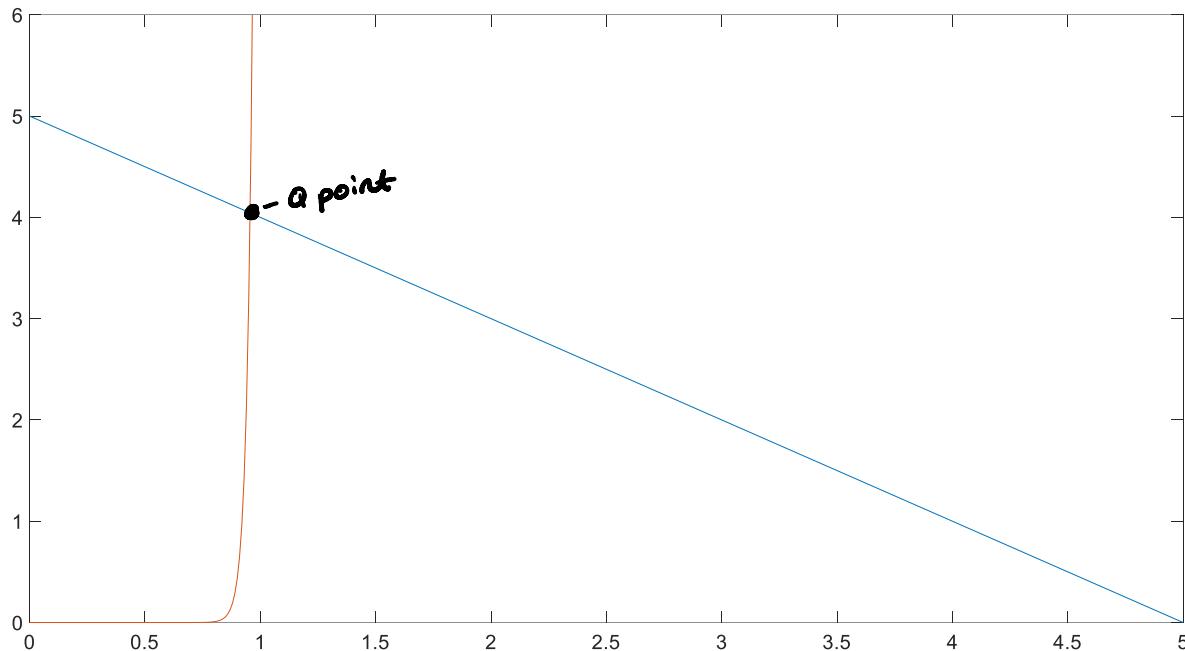


```
%Diode Model
close all
clc

Vdd=5;
R=1; %Resistor is in kohms
Is=1e-16;

Vd1=[0:.1:5];
Vd2=[0:.01:1];
ID1=(Vdd-Vd1)/R; %currents are in mA
ID2=Is*exp(Vd2/0.025);

plot(Vd1, ID1)
hold on
plot(Vd2, ID2)
```

Or, we can iterate

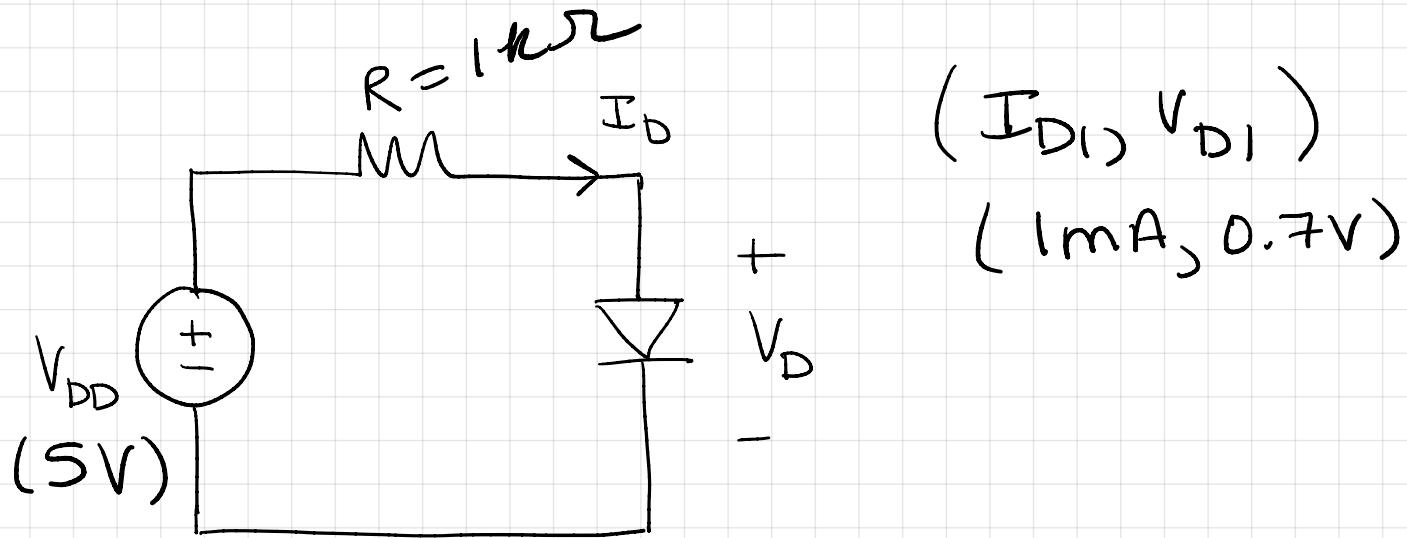

$$I_{D2} = \frac{V_{DD} - V_{D1}}{1} = 4.3 \text{ mA}$$

(I_{D1}, V_{D1})

$(1 \text{ mA}, 0.7 \text{ V})$

$$I_{D2} = 4.3 \text{ mA}$$

$$V_{D2} = ? \text{ } 0.736 \text{ V}$$

$$V_{D2} - V_{D1} = V_T \ln \left(\frac{I_{D2}}{I_{D1}} \right)$$

$$V_{D2} = V_{D1} + V_T \ln \left(\frac{I_{D2}}{I_{D1}} \right)$$

$$V_{D2} = 0.7 + (.025) \ln \left(\frac{4.3}{1} \right)$$

$$V_{D2} = 0.736 \text{ V}$$

$$I_{D3} = \frac{5 - V_{D2}}{1} = 4.264 \text{ mA}$$

$$(I_{D2}, V_{D2}) \Rightarrow I_{D3} = 4.264 \text{ mA}$$

4.3mA, .736V

$$V_{D3} =$$

$$V_{D3} - V_{D2} = V_T \ln \left(\frac{I_{D3}}{I_{D2}} \right)$$

$$V_{D3} = 0.736 \text{ V}$$

Q point

$$(I_{D3}, V_{D3}) = (4.264 \text{ mA}, 0.736 \text{ V})$$

this is not fun


this is time consuming
tedious

We need a model that is more accurate than the ideal model but less tedious than the exponential/iterative model.


Constant Drop Model

assume that the diode is a battery with a fixed voltage. $V = 0.7V$

$$\frac{V}{I} = \frac{1}{I} 0.7V$$

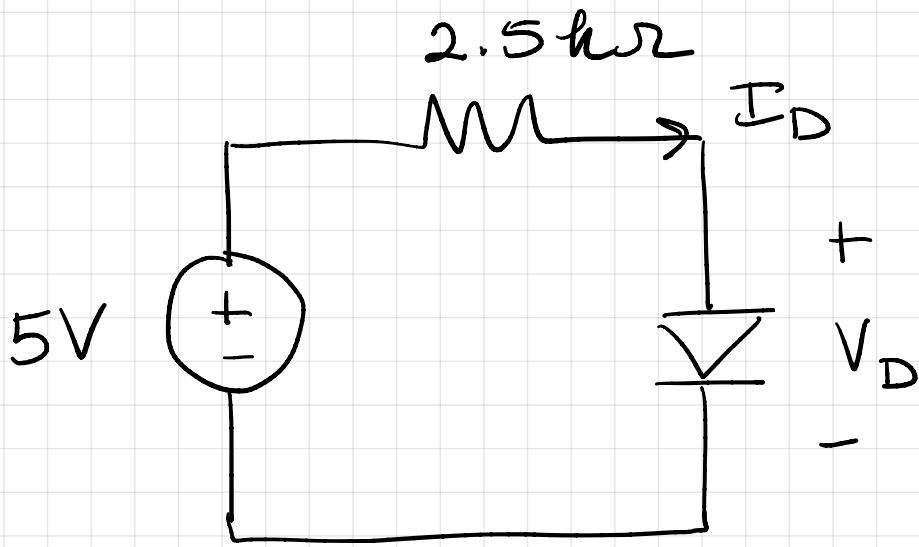


constant drop

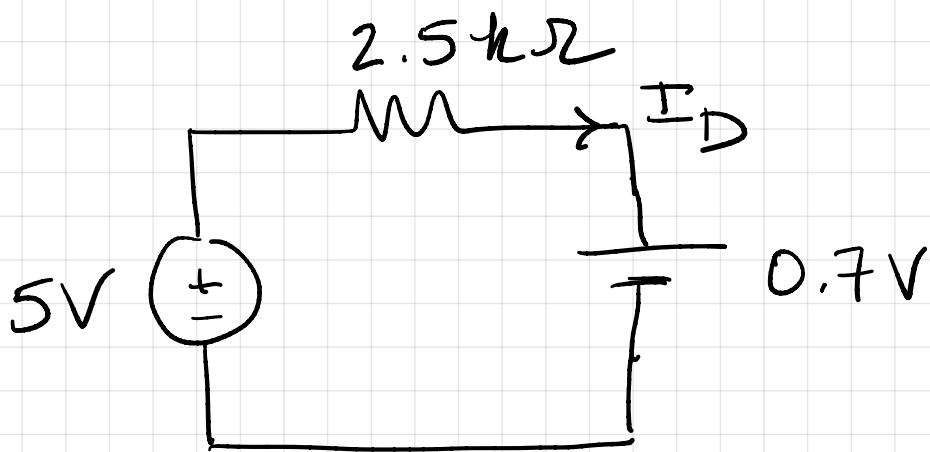

$$V_D = 0.7\text{ V} \quad I_D = \frac{5 - 0.7}{2.5\text{ k}\Omega} = 1.72\text{ mA}$$

ideal model

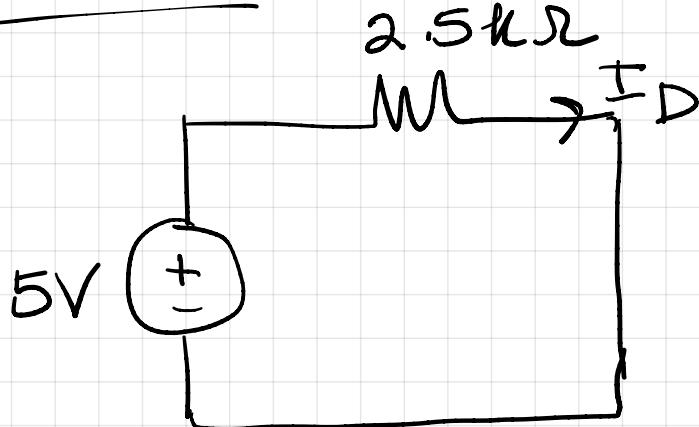

$$V_D = 0$$

$$I_D = \frac{5}{2.5\text{ k}\Omega} = 2\text{ mA}$$

iterative model

$$I_{D1}, V_{D1} = 1mA, 0.7V$$

$$I_{D2} = \frac{5 - 0.7}{2.5 \times 10^3} = 1.72 \text{ mA}$$

$$V_{D2} = V_{D1} + V_T \ln\left(\frac{I_{D2}}{I_{D1}}\right)$$

$$V_{D2} = 0.7136 \text{ V}$$

$$I_{D3} = \frac{5 - V_{D2}}{2.5 k\Omega} = 1.715 \text{ mA}$$

$$V_{D3} = V_{D2} + V_T \ln\left(\frac{I_{D3}}{I_{D2}}\right)$$

$$V_{D3} = 0.713 \text{ V}$$

$$I_{D4} = \frac{5 - V_{D3}}{2.5 \times 10^3} = 1.714 \text{ mA}$$

$$V_{D4} = V_{D3} + V_T \ln\left(\frac{I_{D4}}{I_{D3}}\right)$$

$$\boxed{V_{D4} = 0.713 \text{ V}}$$

EXP model V_{D4} , $I_{D4} = (0.713V, 1.714 \text{ mA})$

ideal model $V_D, I_D = (0, 2 \text{ mA})$

constant drop $V_D, I_D = (0.7V, 1.72 \text{ mA})$

$\% \text{ error}$	V_D	I_D
ideal relative to exp	100%	16.7%
constant drop to exp	1.82%	0.35%

