
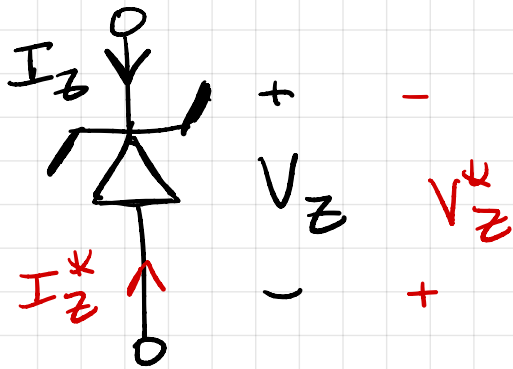


Zener Diodes

operate in breakdown or reverse-biased.

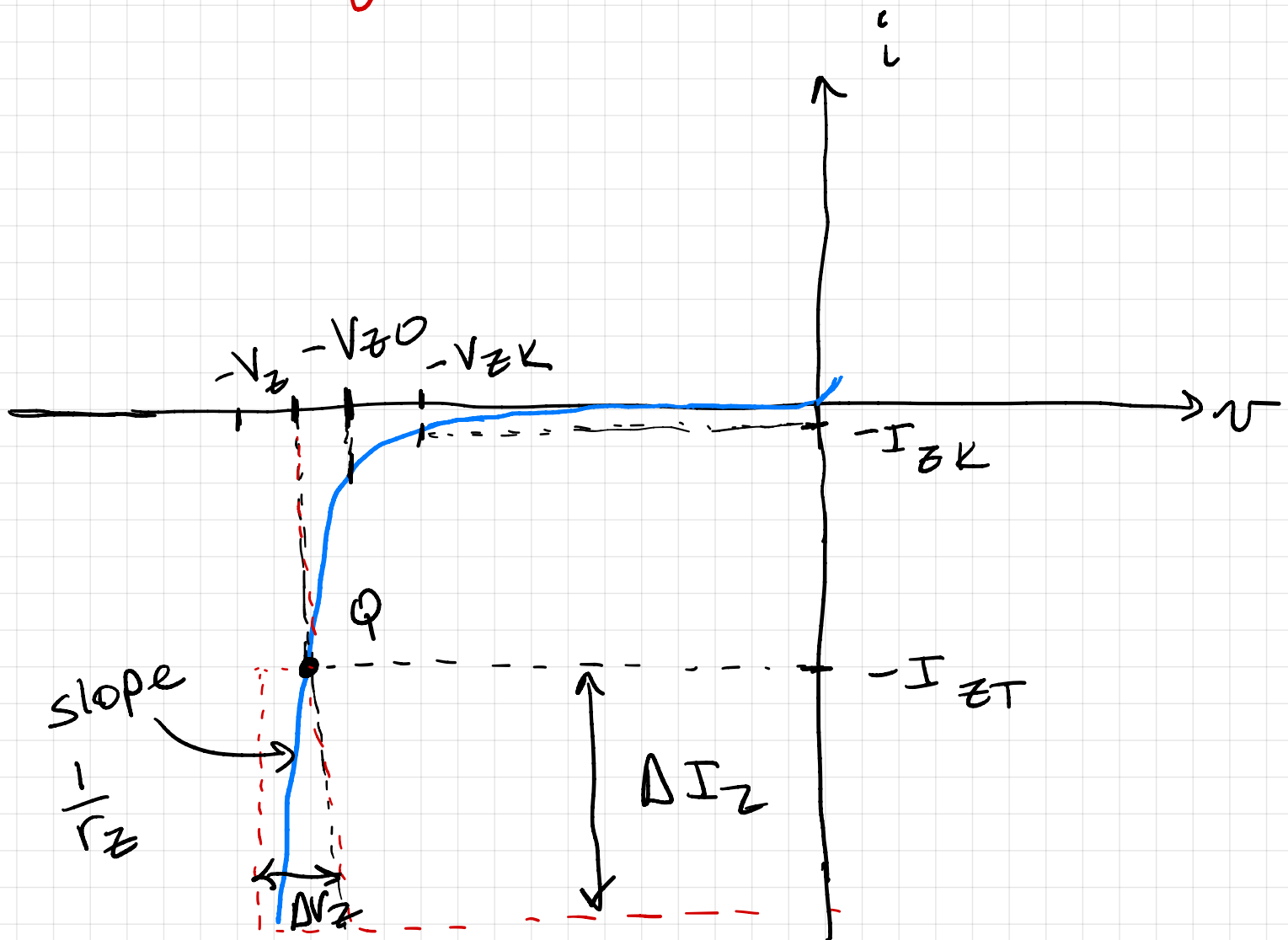

I_Z^* is negative
 V_Z^* is negative



V_{zk} : Knee voltage

I_{zk} : Knee current

I_{zt} : Zener current for
a zener voltage, V_z

(V_z, I_{zt})

r_z : incremental zener
resistance.

1 - 50 Ω


2.4 V zeners

3.3 V

5.6 V

6.8 V


9.1 V

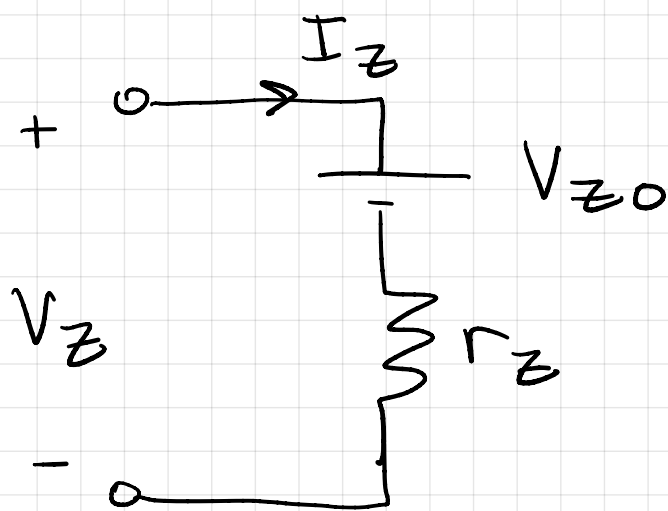

$V_z \approx V_{z0}$ as
 r_z decreases

Ex $r_z = 15\Omega$

$(V_z, I_{zT}) = (6.8V, 10mA)$

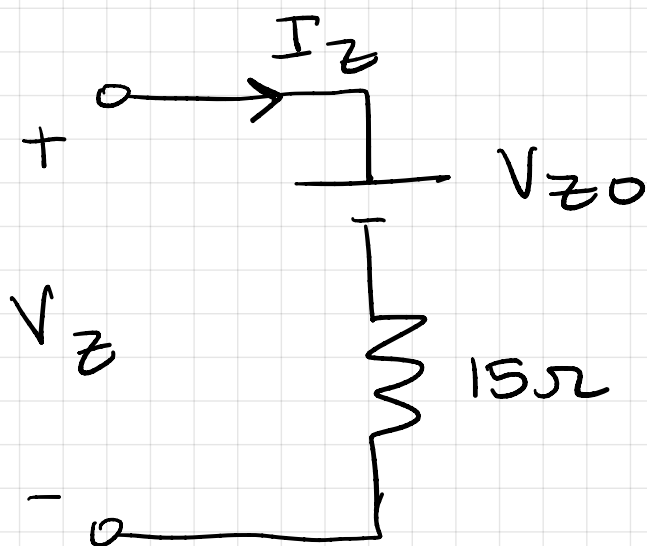

$$V_z = V_{z0} + I_z r_z$$

$$\rightarrow V_{z0} = V_z - I_z r_z$$

$$V_{z0} = 6.8 - (10 \times 10^{-3})(20)$$

$$V_{z0} = 6.65V$$


what is V_z for $I_z = 5mA$

$$\begin{aligned} V_z &= V_{z0} + I_z r_z \\ &= 6.65 + (5 \times 10^{-3})(15) \end{aligned}$$

$$V_z = 6.725V$$

EX $(V_Z, I_Z) \Rightarrow 10V, 10mA$
 $r_Z = 50\Omega$

what is V_Z if I_Z is doubled?

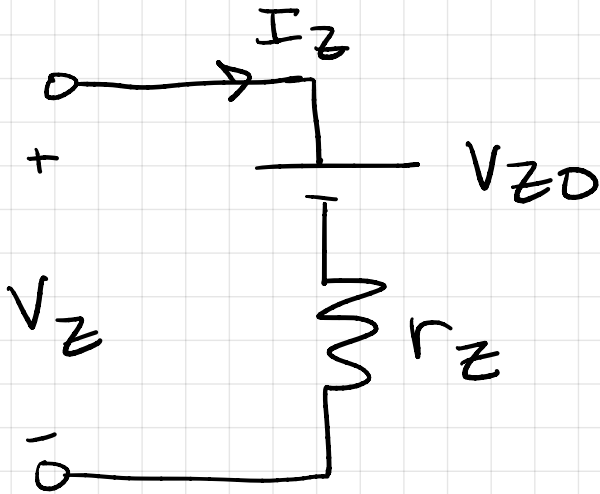


$$V_{Z0} = V_Z - I_Z r_Z \\ = 9.5V$$

$$I_Z = 20mA \\ V_Z ?$$

$$V_Z = V_{Z0} + I_Z r_Z \\ = 9.5 + (20 \times 10^{-3})(50)$$

$$V_Z = 10.5V$$

EX

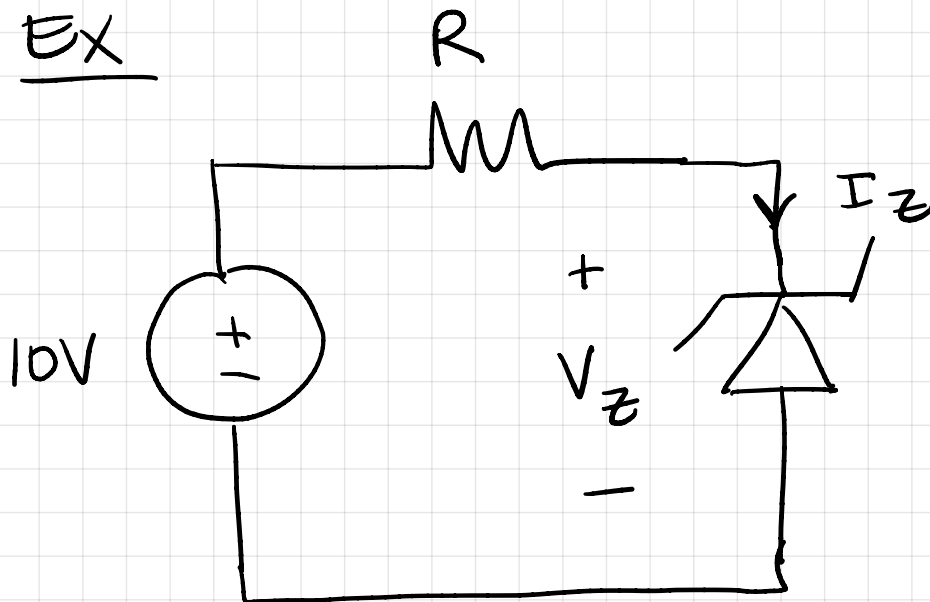


$$V_Z = 6.8V$$

$$I_Z = 10mA$$

$$r_Z = 10\Omega$$

Find R such that $I_Z = 8mA$

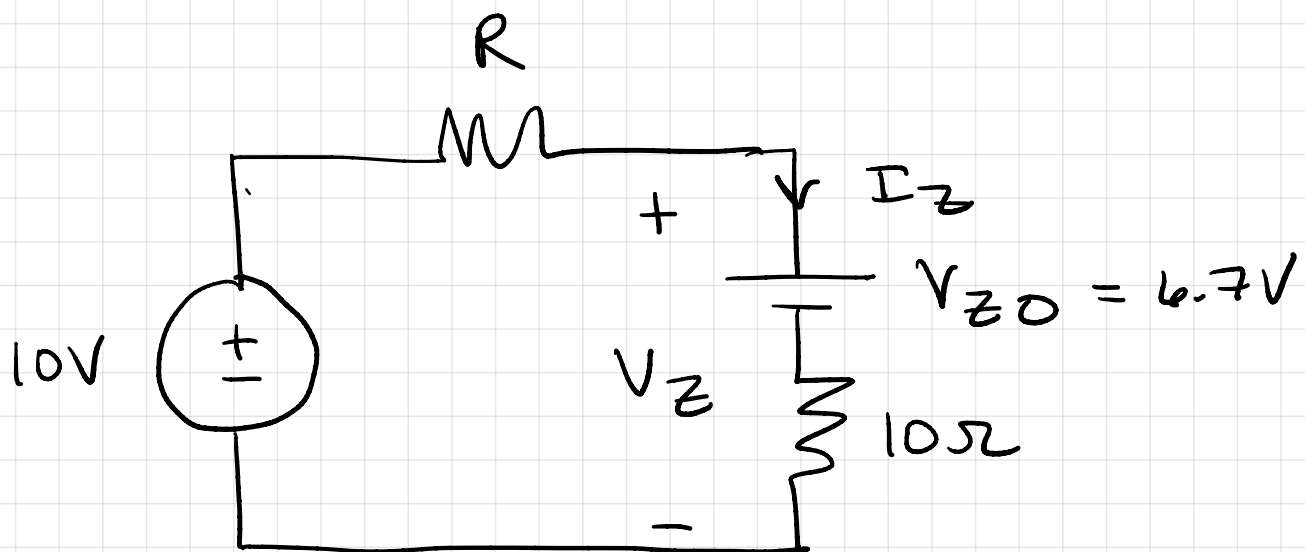

$$\begin{aligned} V_{Z0} &= V_Z - I_Z r_Z \\ &= 6.8 - (10 \times 10^{-3})(10) \end{aligned}$$

$$V_{Z0} = 6.7V$$

$$\begin{aligned}V_Z &= V_{Z0} + I_Z r_Z \\&= 6.7 + (8 \times 10^{-3})(10)\end{aligned}$$

$$V_Z = 6.78 \text{ V}$$

$$R = \frac{10 - V_Z}{I_Z}$$

$$R = \frac{10 - 6.78}{8 \times 10^{-3}}$$

$$R = 0.4025 \text{ k}\Omega$$

$$\boxed{R = 402.5 \Omega}$$