

$i_c \downarrow$


$+ v_{BE} -$   
 $+ v_{CE} -$

Voltage gain will be  $\frac{d v_{CE}}{d v_{BE}} \Rightarrow$

$\rightarrow$   
 $\checkmark$   
 $\rightarrow$   
 $\downarrow$

$\rightarrow$  non linear

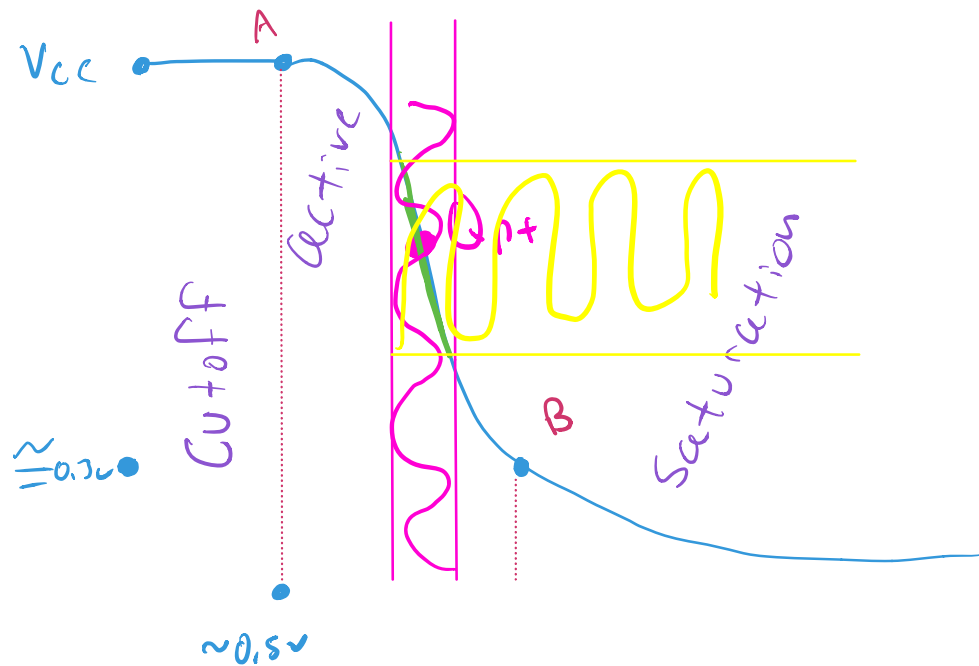Will need to linearize the BJT amplifier at a DC Q-point



$$A_v = \frac{dV_{CE}}{dV_{BE}} \bigg|_{V_{BE}=V_{BE} \rightarrow Q_{pt}}$$

} 180° phase shift  
 $A_v \sim R_c, I_{CQ}$

DC Analysis




→ only swing on .3,  
less than.

Collector  
Current  
↑

$\equiv$  transconductance

← Q point related

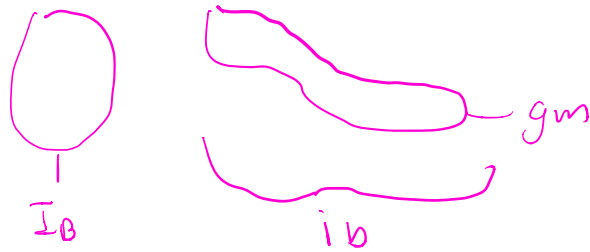

Small signal input resistance

$$\uparrow \\ I_E$$

$$\uparrow \\ i_e$$

$$i_c = I_c \quad \frac{V_{be}}{V_T}$$

$r_e \equiv$  Resistance between base and emitter looking into the emitter.

hybrid pi

Early effect

↙ Qpoint

