
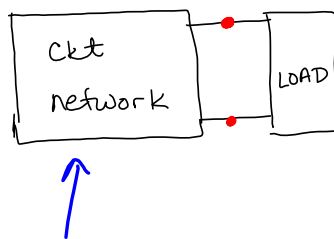


Equivalent Ckts

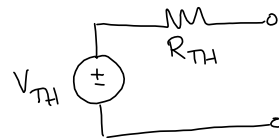


create equivalent ckt = 2 elements

Thevenin Eq. Ckt




Norton Eq. Ckt

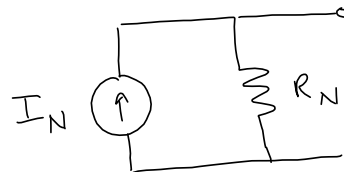


Thevenin Eq. Ckt Steps


① Identify ckt network | load.

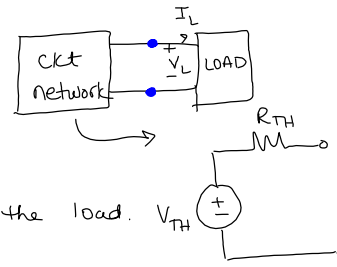

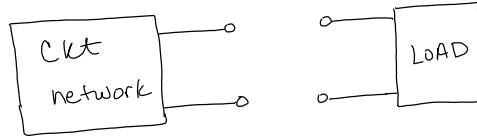② Separate the ckt network from the load. V_{TH}



③ a) Find the $V_{TH} = V_{oc}$

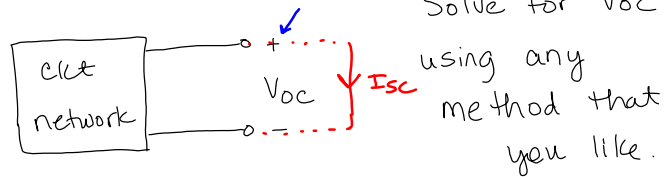

$$V_{TH} = V_{oc}$$


b) Find R_{TH}

1. Quick method. May be used iff the ckt network contains zero dependent sources.

- turn off all sources (à la superposition)
- left with a network of resistors which may be simplified to a single resistor. (R_{eq})
- $R_{TH} = R_{eq}$


2. Long method: may be used for any ckt network.


$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

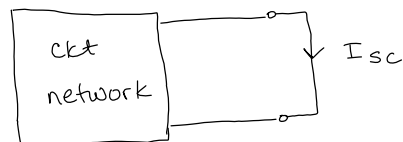



Solve for I_{sc} using any method you like

④ Build our eq. ckt.

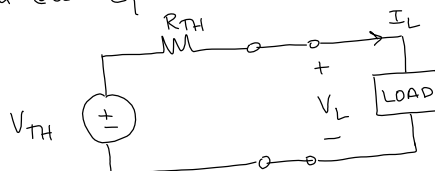


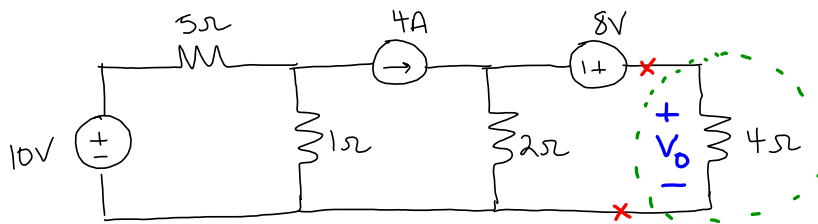

Find V_0 using
a Thev. Eq. Ckt.

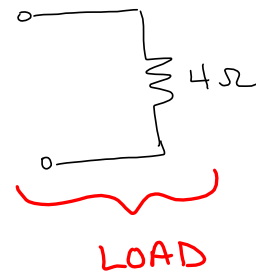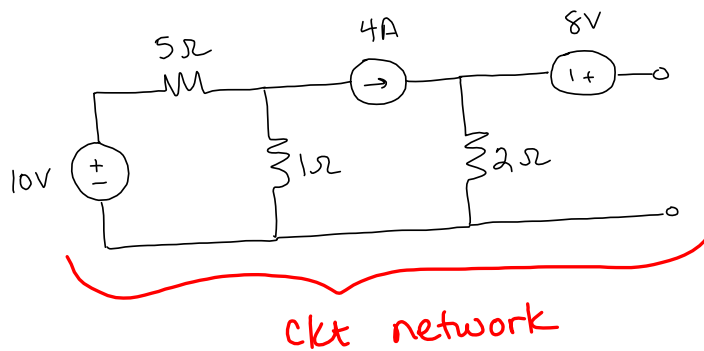

Find V_{TH}

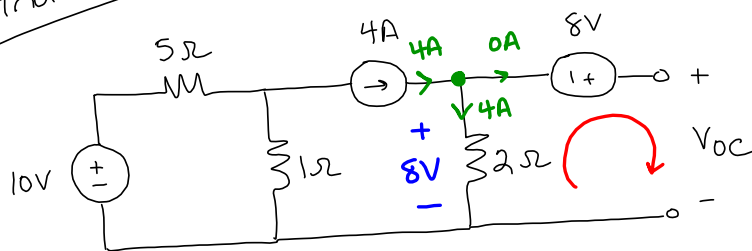


by KVL

$$8 + 8 - V_{OC} = 0$$

$$V_{OC} = 16V$$


$$V_{TH} = 16V$$

Find R_{TH}

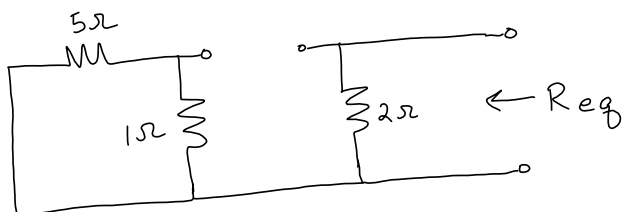


$$R_{eq} = 2\Omega$$

$$R_{TH} = 2\Omega$$


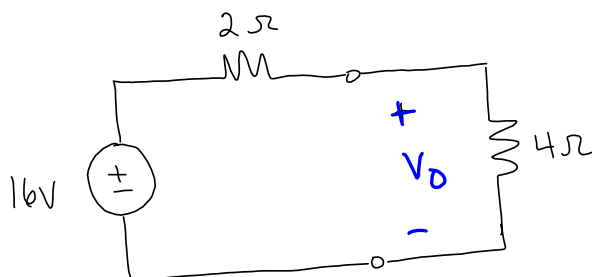


$$V_0 = 16 \left(\frac{4}{6} \right)$$

$$V_0 = 10.67V$$

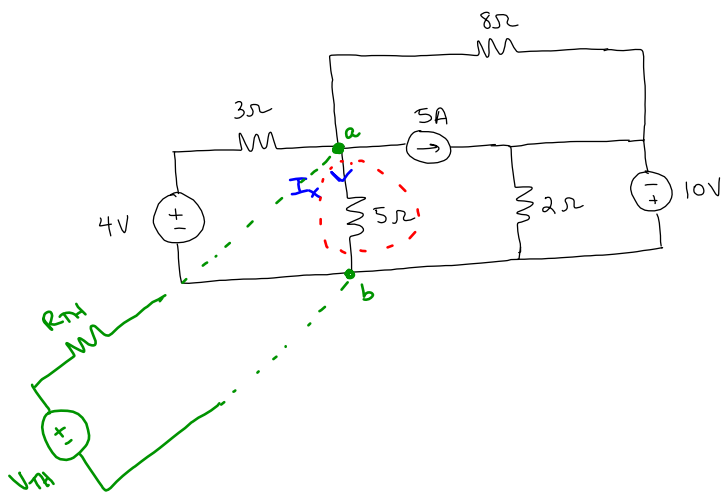

Find I_x
using thev.
Eq.
ckt.

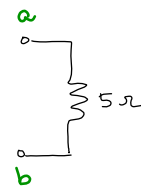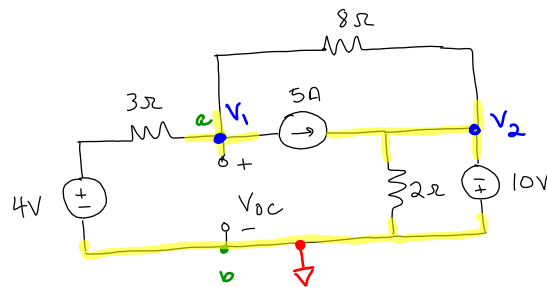

nodal

$$\frac{V_1 - 4}{3} + \frac{V_1 - V_2}{8} + 5 = 0$$

Know



$$V_2 = -10V$$

$$V_1 = V_{oc}$$



$$V_1 = -10.72V$$

$$V_{oc} = -10.72V$$

Find R_{th}

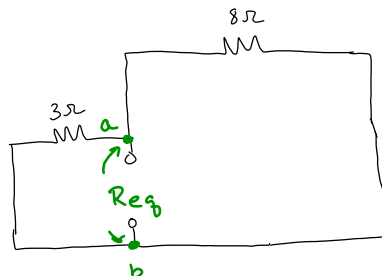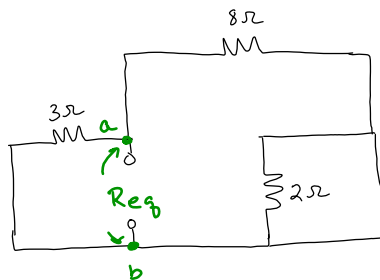


$$R_{eq} = 3 \parallel 8 = 2.18\Omega$$

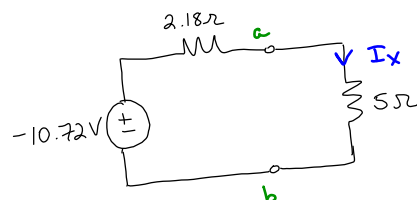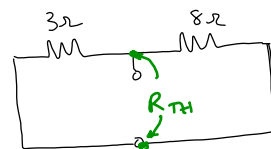

$$I_x = \frac{-10.72}{2.18 + 5}$$

$$I_x = -1.44A$$

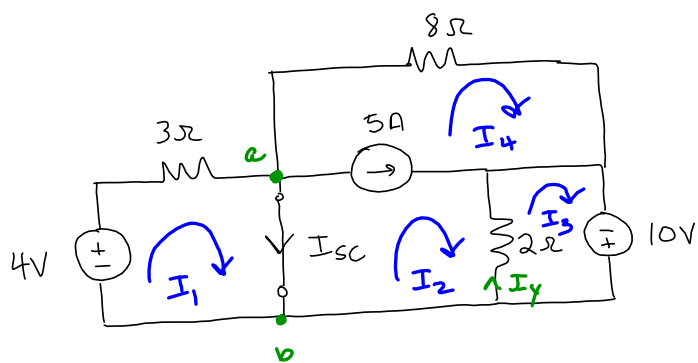

Know

$$I_{sc} = I_1 - I_2$$

$$I_2 - I_4 = 5A$$

$$I_1 = \frac{4}{3} = 1.33A$$

$$I_y = \frac{10}{2} = 5A$$

$$I_3 - I_2 = 5$$