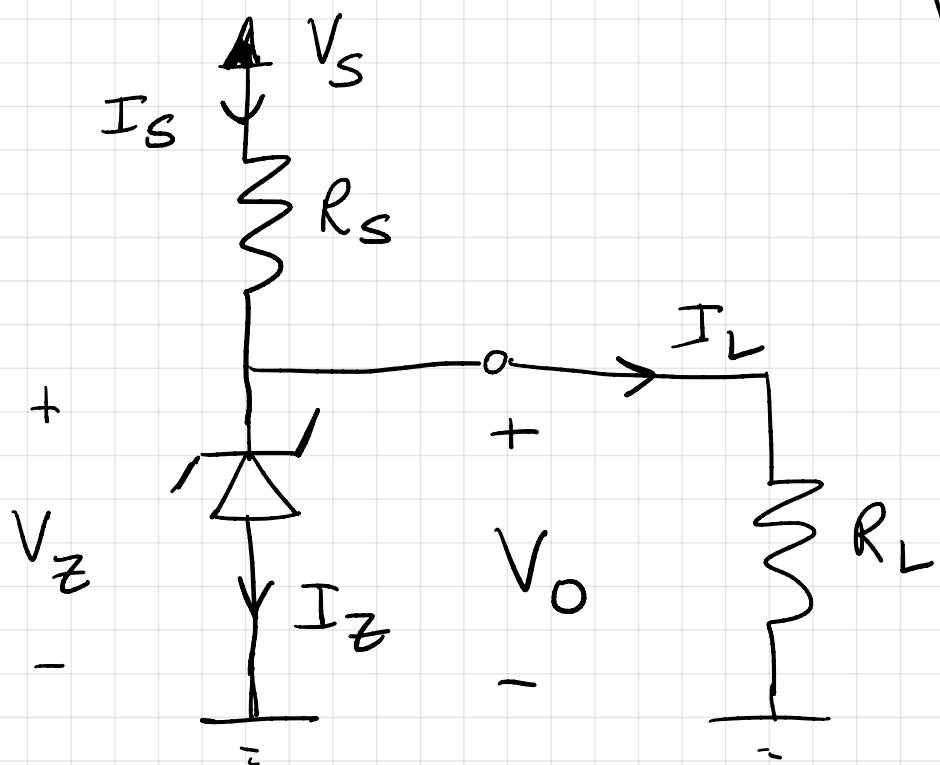


6.8 V Zener diode
Voltage Regulator



$$V_S = 10 \pm 1 \text{ V}$$


$$R_S = 500 \Omega$$

$$V_Z = 6.8 \text{ V}$$

$$I_Z = 5 \text{ mA}$$

$$r_Z = 20 \Omega$$

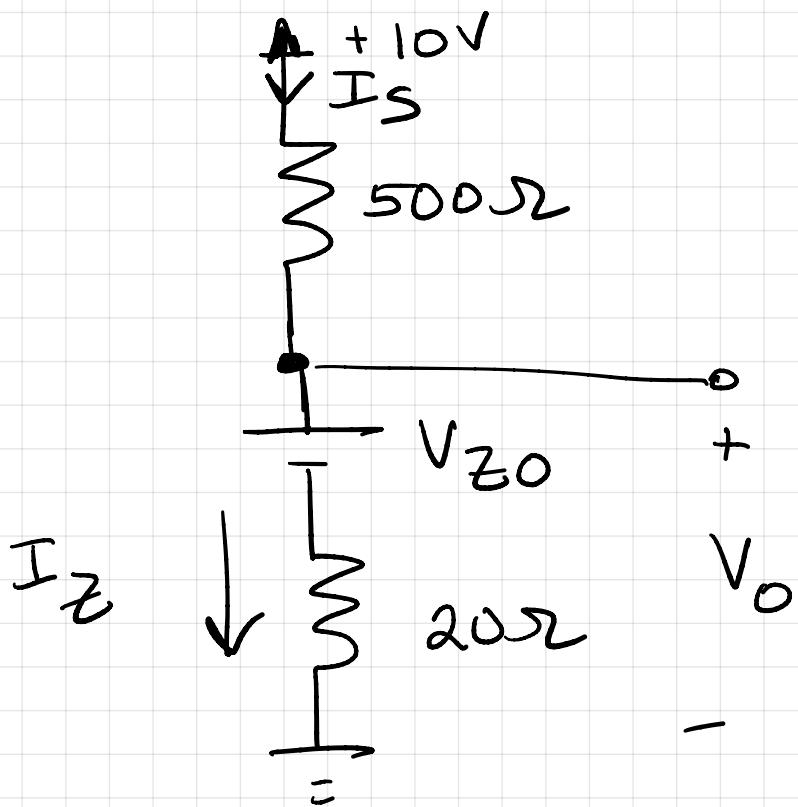- a) Find V_O assume no load $R_L \rightarrow \infty$
and V_S is nominal 10V



$$V_Z = 6.8 \text{ V}$$

$$I_Z = 5 \text{ mA}$$

$$\begin{aligned} V_{Z0} &= V_Z - I_Z r_Z \\ &= 6.8 - (5 \times 10^{-3})(20) \end{aligned}$$

$$\begin{aligned} V_{Z0} &= 6.7 \text{ V} \\ I_Z &= \frac{10 - V_{Z0}}{500 + 20} \end{aligned}$$

$$I_Z = \frac{10 - 6.7}{520} = 6.35 \text{ mA}$$

$$\begin{aligned} V_O &= V_{Z0} + 20 I_Z \\ &= 6.7 + 20(6.35 \times 10^{-3}) \end{aligned}$$

$V_O = 6.83 \text{ V}$

b) ΔV_O w/ respect to V_S

$\pm 1 \text{ V}$ change in $V_S \Rightarrow \Delta V_O$

$$\frac{\Delta V_O}{\Delta V_S} = \text{(line regulation)} \frac{mV}{V}$$

$$I_Z = \frac{V_S - V_{Z0}}{R_S + r_Z}$$

$$V_O = V_{Z0} + I_Z r_Z$$

$$V_O = V_{Z0} + (V_S - V_{Z0}) \left(\frac{r_Z}{R + r_Z} \right)$$

ΔV_o as function of ΔV_s

$$\boxed{\Delta V_o = \frac{r_z}{R+r_z} (\Delta V_s)}$$

$$\frac{\Delta V_o}{\Delta V_s} = \frac{r_z}{R+r_z} = \frac{20}{520} = 38.5 \times 10^{-3}$$

$$= 38.5 \frac{mV}{V} \rightarrow \text{line regulation}$$

$$\Delta V_o = \left(38.5 \frac{mV}{V} \right) (\pm 1)$$

$$\underline{\Delta V_o = 38.5 mV} \rightarrow \text{output voltage change for a given } \pm 1V$$

c) Find ΔV_o if we connect a load resistor that draws 1mA away from the zener diode

$$I_L = 1mA$$

$$\frac{\Delta V_o}{\Delta I_L} = \text{load regulation}$$

$$\frac{\Delta V_o}{\Delta I_L} \Rightarrow \frac{mV}{mA}$$

$$V_o = V_{Zo} + I_Z r_Z$$

$$\Delta V_o = \Delta I_Z (r_Z)$$

$$\frac{\Delta V_o}{\Delta I_Z} = r_Z = 20 \frac{mV}{mA}$$

$$\Delta I_Z = -1mA$$

$$\frac{\Delta V_o}{\Delta I_L} = -20 \frac{mV}{mA}$$

$$I_L = 1mA$$

$$\Delta V_o = -20mV$$

d) ΔV_o for $R_L = 2k\Omega$

$$I_L \approx \frac{6.8}{2000} = 3.4mA$$


$$\Delta V_o = r_Z \Delta I_Z = -(20)(3.4 \times 10^{-3})$$

$$\Delta V_0 = -68 \text{ mV}$$

e) $R_L = 500 \Omega$

$$I_L \approx \frac{6.8}{500} = 13.6 \text{ mA}$$


Zener diode is no longer
in breakdown

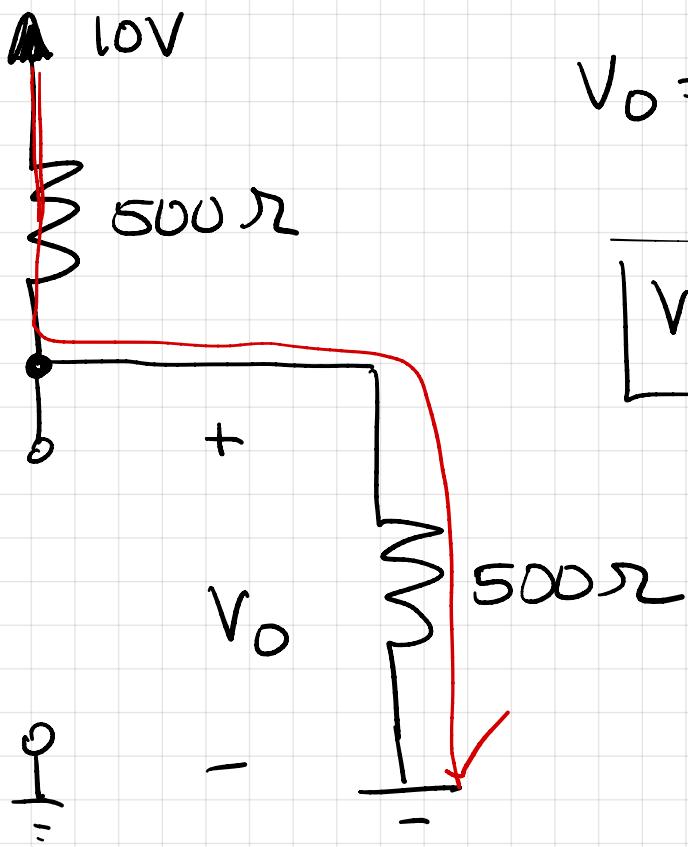

$$V_o = 10 \left(\frac{500}{1000} \right)$$

$$V_o = 5 \text{ V}$$

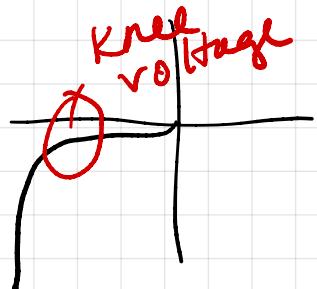f) What is the minimum R_L value such that we are on the edge of breakdown.




$$I_{ZK} = 0.2 \text{ mA}$$

$$I_Z \approx I_{ZK} = 0.2 \text{ mA}$$

$$V_Z \approx V_{Z0} = 6.7 \text{ V}$$
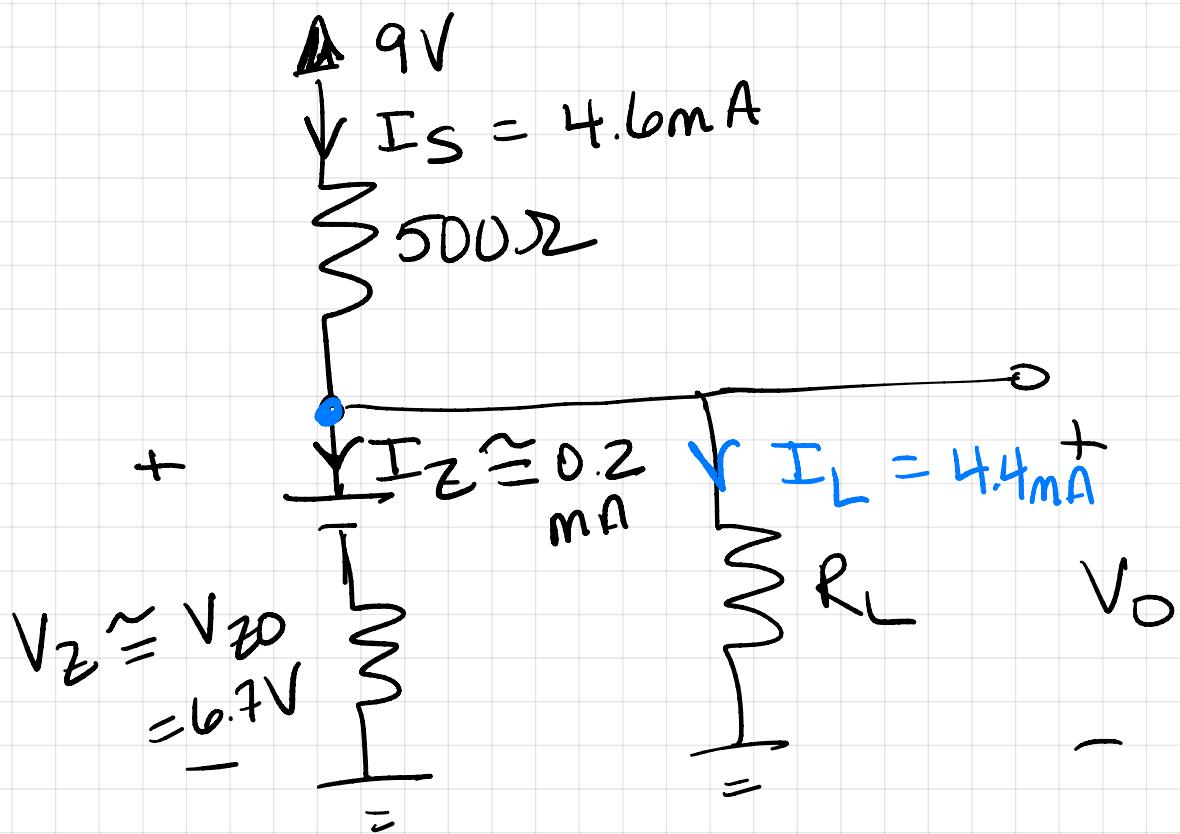
$$I_S = \frac{9 - 6.7}{500} = 4.6 \text{ mA}$$



$$R_L = \frac{V_Z}{I_L} = \frac{6.7}{4.4 \times 10^{-3}}$$

$$R_L \approx 1.5 \text{ k}\Omega$$