
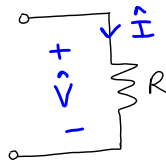


$$\hat{V} = Z \hat{I}$$

$Z \equiv \text{impedance } [\Omega]$

$\uparrow$  freq domain quantity


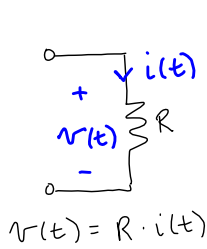


$$\hat{V} = Z_R \hat{I}$$

$$Z_R = R + j0 \Omega$$

$$= R \angle 0^\circ \Omega$$

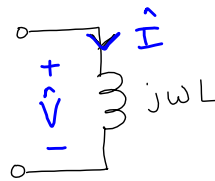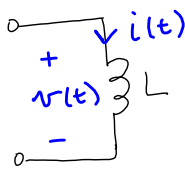$Z_R$  is purely real  
voltage and current are  
"in phase"





$$\hat{V} = Z_L \hat{I}$$

$$Z_L = 0 + j\omega L \Omega$$

$$= \omega L \angle 90^\circ \Omega$$

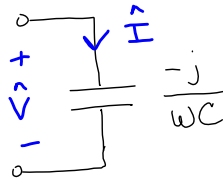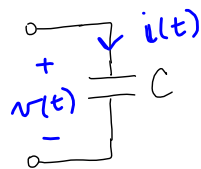$Z_L$  is purely imaginary  
voltage and current are  
 $90^\circ$  out of phase



$$\hat{V} = Z_C \hat{I}$$

$$Z_C = 0 - \frac{j}{\omega C} \Omega$$

$$= \frac{1}{\omega C} \angle -90^\circ \Omega$$

$Z_C$  is purely imaginary  
voltage and current are  
 $-90^\circ$  out of phase

my convention

phasors	magnitudes of phasors
$\hat{V}$	$ \hat{V} $
$\hat{I}$	$ \hat{I} $

$$\angle \hat{V}$$

$$\angle \hat{I}$$

phasors (book)
$V$
$I$

$$\angle V$$

$$\angle I$$

mag. of phasors (book)
$V$
$I$


impedances  $Z = R \pm jX$


$R$  is the real part  $\equiv$  resistance  $[\Omega]$

$X$  is the imag. part  $\equiv$  reactance  $[\Omega]$


if  $X$  is positive  $\Rightarrow Z$  is inductive

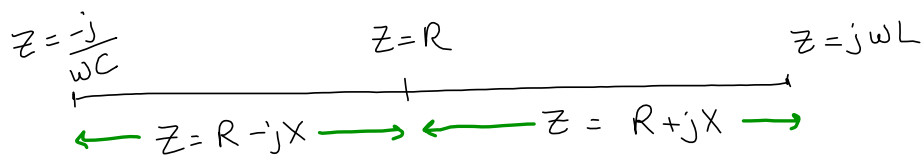if  $X$  is negative  $\Rightarrow Z$  is capacitive



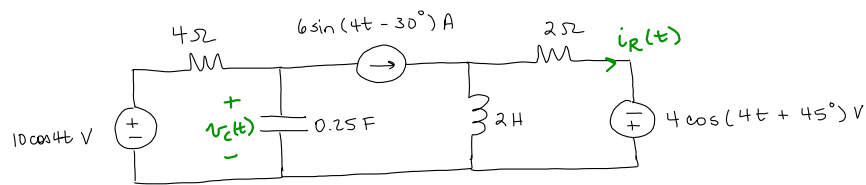

Sources	Impedances
$10 \cos 4t \rightarrow 10 \angle 0^\circ \text{ V}$	$4 \Omega \rightarrow 4 \Omega$
$4 \cos(4t + 45^\circ) \rightarrow 4 \angle 45^\circ \text{ V}$	$2 \Omega \rightarrow 2 \Omega$
$6 \sin(4t - 30^\circ)$	$2 \text{ H} \rightarrow j\omega L = j(4)(2) = j8 \Omega$
$6 \cos(4t - 30^\circ - 90^\circ)$	$0.25 \text{ F} \rightarrow \frac{-j}{\omega C} = \frac{-j}{(4)(.25)} = -j1 \Omega$
$6 \cos(4t - 120^\circ) \rightarrow 6 \angle -120^\circ \text{ A}$	

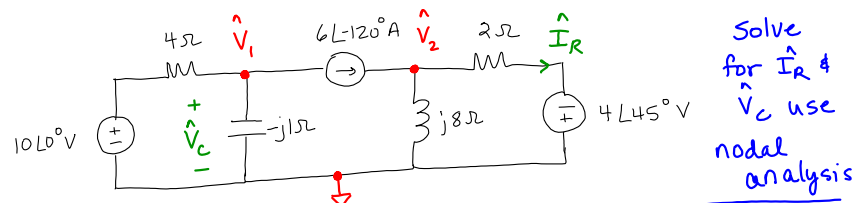

Solve for  $\hat{I}_R$  &  $\hat{V}_c$  use nodal analysis

$$N1: \frac{\hat{V}_1 - 10 \angle 0^\circ}{4} + \frac{\hat{V}_1}{-j1} + 6 \angle -120^\circ = 0$$

$$N2: \frac{\hat{V}_2 + 4 \angle 45^\circ}{2} + \frac{\hat{V}_2}{j8} + (-6 \angle -120^\circ) = 0$$

$$\hat{I}_R = \frac{\hat{V}_2 + 4 \angle 45^\circ}{2}$$

$$\hat{V}_c = \hat{V}_1$$

$$N1: \hat{V}_1 \left( \frac{1}{4} + \frac{1}{-j1} \right) = \frac{10 \angle 0}{4} - 6 \angle -120^\circ$$

$$N2: \hat{V}_2 \left( \frac{1}{2} + \frac{1}{j8} \right) = 6 \angle -120^\circ - \frac{4 \angle 45^\circ}{2}$$

$$\hat{V}_1 (0.25 + j1) = \frac{2.5 \angle 0}{2.5 + j0} - (-3 - j5.2)$$

$$\hat{V}_1 (0.25 + j1) = 5.5 + j5.2$$

$$\hat{V}_1 (1.03 \angle 75.96^\circ) = 7.57 \angle 43.39^\circ$$

$$\hat{V}_1 = \frac{7.57 \angle 43.39}{1.03 \angle 75.96} = 7.34 \angle -32.57^\circ \text{ V}$$

$$\hat{V}_2 = 15.42 \angle -109.70^\circ \text{ V}$$

$$\hat{V}_c = 7.34 \angle -32.57^\circ \text{ V}$$

$$\hat{I}_R = 5.96 \angle -101.46^\circ \text{ A}$$

$$= \frac{15.42 \angle -109.70 + 4 \angle 45}{2}$$

$$v_c(t) = 7.34 \cos(4t - 32.57^\circ) \text{ V}$$

$$i_R(t) = 5.96 \cos(4t - 101.46^\circ) \text{ A}$$