

Module 1 Amplifier Fundamentals

Amplifier types

- o Voltage amps: $V_o = A_v \cdot V_I$ $A_v \equiv$ Voltage gain $A_v = \frac{V_o}{V_I} \quad (V/V)$
- o Current amps: $i_o = A_i \cdot i_I$ $A_i \equiv$ Current gain $A_i = \frac{i_o}{i_I} \quad (A/A)$
- o Power amps: $P_o = A_p \cdot P_I$ $A_p \equiv$ Power gain $A_p = \frac{P_o}{P_I} \quad (W/W) = \frac{V_o \cdot i_o}{V_I \cdot i_I} \quad (V^2/W)$


Log Scale

↳ express gain in dB.

$$o A_v = 20 \log |A_v|$$

$$o A_i = 20 \log |A_i|$$

$$o A_p = 10 \log |A_p|$$

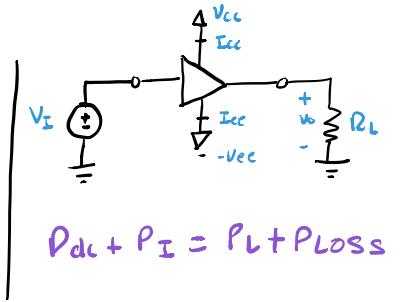

Amplifier efficiency

$$\eta = \frac{P_L}{P_{dc}} \times 100 \% \text{ efficiency.}$$

$$P = \frac{V^2}{R}$$

Standard Amp

$$\frac{V_o}{V_i} = A_{vo} \left(\frac{R_L}{R_s + R_o} \right) \left(\frac{R_i}{R_s + R_i} \right)$$

Module 2A Operational Amplifiers

Ideal op-amps

- ① Draws zero input current: $i_+ = i_- = 0A$
- ② V_o is not a function of i_o : $R_o = 0$
- ③ Open loop gain is ∞ : $V_t = V_o$
- ④ Inf common mode rejection: $V_o = 0$
- ⑤ Inf bandwidth: A is not a func of freq

Inverting Op-amps

$$\frac{V_o}{V_I} = \frac{-R_2}{R_1} \rightarrow G_v = -\frac{R_2}{R_1}$$

closed loop gain

$$R_i = \frac{V_I}{i_+} = R_1 ; R_o = 0$$

$$i_+ = \frac{V_I}{R_1}$$

$$i_2 = \frac{0 - V_o}{R_2}$$

Non-Ideal Op-Amps (Finite A)

inverting : $\frac{V_o}{V_I} = \frac{-R_2/R_1}{1 + 1/A(1 + R_2/R_1)}$


non-inverting : $\frac{V_o}{V_I} = \frac{(1 + R_2/R_1)}{1 + 1/A(1 + R_2/R_1)}$

Non-inverting Op-amp

$$R_i = \frac{V_I}{i_+} = \infty \quad R_o = 0$$

$$G_v = 1 + \frac{R_2}{R_1}$$

Non-inverting amp

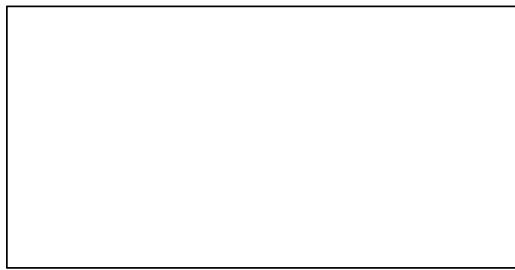

Weighted Summer

$$V_o = V_{o1} + V_{o2} + V_{o3} =$$

$$V_o = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 + \frac{R_F}{R_3} v_3 \dots$$

$$i_F = \frac{V_{omax}}{R_F}$$

Voltage Follower

$$R_1 = \infty$$

$$R_2 = 0$$

$$V_o = V_I$$

Module 2B Difference Amplifiers

Difference Amplifier


$$\circ V_{I1} = V_{ICM} - \frac{1}{2} V_{ID}$$

$$\circ V_{I2} = V_{ICM} + \frac{1}{2} V_{ID}$$

$$\circ V_{O1} = \left(-\frac{R_2}{R_1} \right) V_{I1}$$

$$\circ V_{O2} = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_{I2}$$

$$\circ V_O = V_{O1} + V_{O2}$$

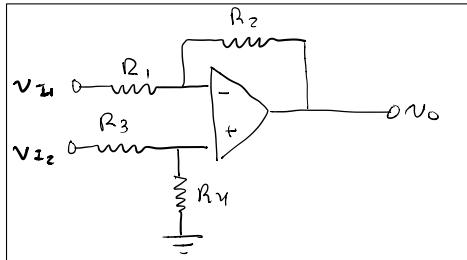

$$\circ A_{CM} = -\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right)$$

$$\circ A_d = \frac{1}{2} \left(\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) \right)$$

$$\circ CMRR = 20 \log \left| \frac{A_d}{A_{CM}} \right| \text{ (dB)} \quad * \text{ IF } A_{CM} = 0 \text{ (ideal) then } CMRR = \infty$$

When $A_{CM}=0$...

$$\circ A_d = \frac{R_2}{R_1} ; \circ R_{id} = 2R_1 ; \circ R_1 = R_3 ; \circ R_2 = R_4$$

Instrumentation Amplifier


$$\circ V_o = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1} \right) V_{ID}$$

\hookrightarrow w/ R_2 mismatch:

$$\circ V_{ID} = V_{I2} - V_{I1}$$

$$\circ V_o = \frac{R_4}{R_3} \left(1 + \frac{R_{21} + R_{22}}{R_1} \right) V_{ID}$$
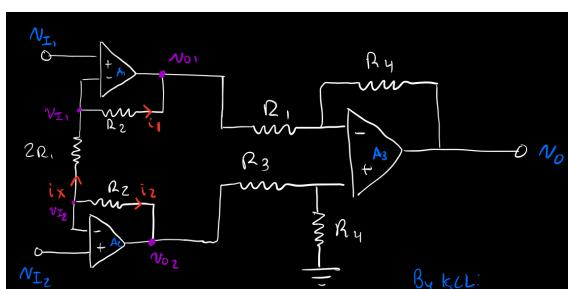
$$i_1 = \frac{V_{I1} - V_{O1}}{R_1} \quad i_2 = \frac{V_{I2} - V_{O2}}{R_2} \quad i_x = \frac{V_{ID}}{2R_1}$$



Ideal Diodes

- OFF: Reverse Bias region: $V < V_{OJ} := 0$
 ↳ Looks like an open circuit
- ON: Forward bias region: $V > V_{OJ}, i > 0$
 ↳ Looks like a short circuit

Assume Diode state and
 Solve to check

Forward bias Diodes

$$V_T = 25 \text{ mV}$$

$$k = 8.62 \times 10^{-5} \text{ eV/K}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

- $\frac{I_2}{I_1} = \exp\left(\frac{V_2 - V_1}{V_T}\right)$
- $i \cong I_S \exp\left(\frac{V}{nV_T}\right)$

- $V_T = \frac{kT}{q}$
- $V_2 - V_1 = V_T \ln\left(\frac{I_2}{I_1}\right)$

Modeling Diodes

Iterate: $I_D = \frac{V_{DD} - V_D}{R}$

Const Drop: Use ↑ w/ $V_D = 0.7$ unless told otherwise.

Ideal: Solve w/ $V_D = 0$


Zener Diodes

- $V_Z = V_{Z0} + I_Z r_Z$ or $V_{Z0} = V_Z - I_Z r_Z$

- $\Delta V_D = \frac{r_Z}{R + r_Z} (\Delta V_S)$

Module 4 MOSFET Fundamentals

NMOS

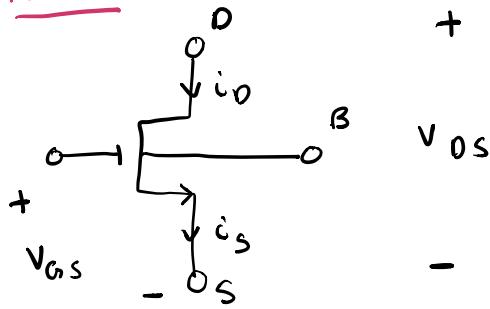

Symmetric Device:

$$i_D = i_S; i_G = 0 \\ n n \text{ Cox}; V_{tN} = V_t$$

Triode


- ① $V_{GS} > V_t$, V_{DS} is very small
 - $i_D = k'n \left(\frac{w}{l}\right) (V_{GS} - V_t) V_{DS}$
 - $r_{ds} = \frac{1}{k'n \left(\frac{w}{l}\right) (V_{GS} - V_t)}$

- ② $V_{GS} > V_t$, V_{DS} is small
 - $V_{DS} \ll (V_{GS} - V_t)$
 - $i_D = k'n \left(\frac{w}{l}\right) [(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2]$

Saturation region

- $V_{GS} > V_t$ Edge of Saturation:
- $V_{DS} > V_{GS} - V_t \rightarrow V_{DS} = V_{GS} - V_t$
- $i_D = \frac{1}{2} k'n \left(\frac{w}{l}\right) (V_{GS} - V_t)^2$

PMOS

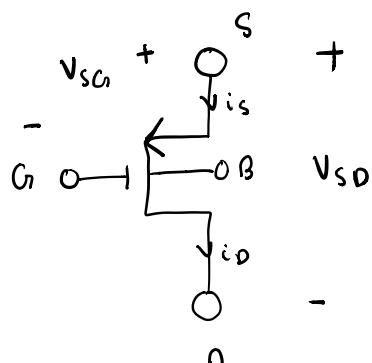

Symmetric Device:

$$i_D = i_S; i_G = 0 \\ n n \text{ Cox}; V_{tP} < 0 \text{ so } |V_{tP}|$$

Triode

- ① $V_{GS} > |V_{tP}|$, V_{DS} very small
 - $i_D = k'p \left(\frac{w}{l}\right) (V_{GS} - |V_{tP}|) V_{DS}$
 - $r_{ds} = \frac{1}{k'p \left(\frac{w}{l}\right) (V_{GS} - |V_{tP}|)}$

- ② $V_{GS} > V_t$, V_{DS} is small
 - $V_{DS} \ll V_{GS} - |V_{tP}|$
 - $i_D = k'p \left(\frac{w}{l}\right) [(V_{GS} - |V_{tP}|) V_{DS} - \frac{1}{2}V_{DS}^2]$

Saturation region


- $V_{GS} > V_t$ Edge of Saturation:
- $V_{DS} > V_{GS} - V_t \rightarrow V_{DS} = V_{GS} - V_t$
- $i_D = \frac{1}{2} k'p \left(\frac{w}{l}\right) (V_{GS} - V_t)^2$

$m_p \text{ Cox}$
 \uparrow
 mobility of holes in
 silicon.
 $V_{tP} < 0; |V_{tP}|$

Module 5: BJTs Fundamentals

BJT operation and DC biasing

nPN

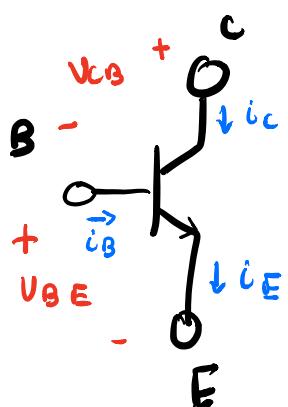


$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$i_B = \frac{i_C}{\beta} \quad \beta = \frac{\alpha}{\alpha - 1} \quad \alpha = \frac{\beta}{\beta + 1}$$

$$i_E = i_B + i_C$$

active: $V_{BE} > 0$ $V_{CB} > -0.4 \text{ V}$

pNp

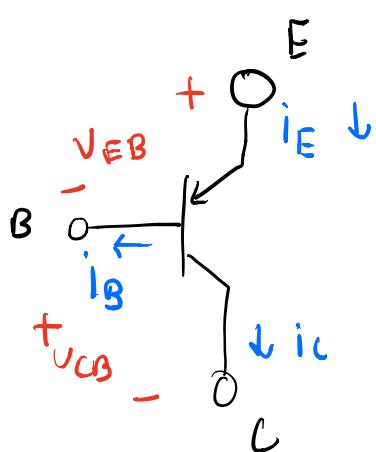

- $I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right)$

- $i_B = \frac{i_C}{\beta}$
- $\beta = \frac{\alpha}{\alpha - 1}$
- $\alpha = \frac{\beta}{\beta + 1}$

- $i_E = i_C + i_B$
- $i_C = \alpha i_E$

active mode $V_{EB} > 0$ $V_{BC} > -0.4 \text{ V}$

Forward Bias equation

↳ used in the diode and BJT forward bias lectures
 * know how and when to use them.

General Forms

$$\circ \frac{I_2}{I_1} = e^{\frac{V_2 - V_1}{V_T}} \quad \circ V_2 - V_1 = V_T \ln \left(\frac{I_2}{I_1} \right)$$

Example for BJT to find V_{BE2}

$$V_{BE2} - V_{BE1} = V_T \ln \left(\frac{I_{C2}}{I_{C1}} \right)$$

Transition Equations

$$A: V_{DS} = V_t \quad V_{DS} = V_{DD}$$

$$B: V_{DS} = V_t + \frac{\sqrt{1 + 2R_D k' n(\omega_L) V_{DD}} - 1}{R_D k' n(\omega_L)}$$


$$V_{DS} = V_{DS} - V_t$$

$$C: V_{DS} = V_{DD} \quad V_{DS} = \frac{V_{DD}}{(1 + R_D k' n(\omega_L)(V_{DD} - V_t))}$$

Module 6: MOSFET amplifiers and Amplifier Configurations

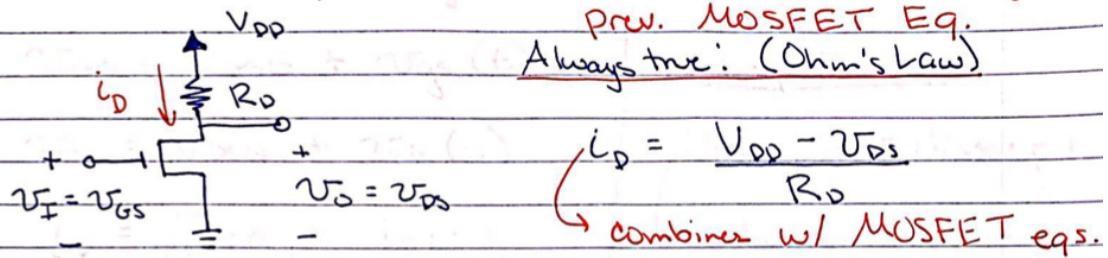(5)

- MOSFETs + Amplifiers ★ Know how we are using prev. MOSFET Eq.



- Cutoff: $V_{GS} < V_t$ $i_D = 0$ $\rightarrow 0 = V_{DD} - V_{DS}$
 $V_{DS} = V_{DD}$ $\Rightarrow V_{DS} = V_{DD}$

- Saturation: $(V_{DS} \geq V_{GS} - V_t)$

$$V_{DS} = V_{DD} - \frac{1}{2} R_D k' n \left(\frac{w}{l} \right) (V_{GS} - V_t)^2$$

$R_D i_D$

- Triode: $(V_{DS} < V_{GS} - V_t)$

$$V_{DS} = \frac{V_{GS}}{1 + R_D k' n \left(\frac{w}{l} \right) (V_{GS} - V_t)}$$

max V_{GS} = V_{DD}

$$V_{DS} = \frac{V_{DD}}{1 + R_D k' n \left(\frac{w}{l} \right) (V_{DD} - V_t)}$$

- Edge of Saturation:

$$V_{GS} = V_t + \sqrt{1 + 2(R_D k' n \left(\frac{w}{l} \right) V_{DD})} - 1$$

$R_D k' n \left(\frac{w}{l} \right)$

(6)

- MOS Amplifier Voltage Gain + the Q-Point:

$$V_{GS} = V_{GSQ} + v_{gs}(t)$$

$$V_{DS} = V_{DSQ} + v_{ds}(t)$$

$$i_D = \underbrace{I_{DQ}}_{\substack{\text{DC-bias} \\ \text{point} \\ (\text{Q-point})}} + \underbrace{i_d(t)}_{\substack{\text{Small} \\ \text{Signal}}}$$

$$v_{ds} = A_v v_{gs}$$

\nwarrow small signal volt. gain

$$A_v = -R_D k' n \left(\frac{w}{l}\right) (V_{GSQ} - V_t)$$

* can pick resistors, transistors, and Q-Point to get desired gain when designing.

- Small Signal Eq.:

$$i_d = k' n \left(\frac{w}{l}\right) [v_{gs} (V_{GSQ} - V_t)]$$

$$g_m = \frac{i_d}{v_{gs}} = k' n \left(\frac{w}{l}\right) (V_{GSQ} - V_t) \quad \begin{matrix} \text{units} \\ \left[\frac{A}{V}\right] \end{matrix}$$

$$A_v = -g_m R_D \quad \begin{matrix} \text{reminder:} \\ r_o = \frac{V_A}{I_{DQ}} \end{matrix}$$

* coupling capacitors act as open circuits for DC and as short circuits for AC.

Finding Max v_i :

$$V_{GSQ} - |A_v| v_i = V_{GSQ} + v_i - V_t$$

\hookrightarrow solve for v_i

comes from:

$$V_{DS, \min} = V_{GS, \max} - V_t$$

(6)

- MOS Amplifier Voltage Gain + the Q-Point:

$$V_{GS} = V_{GSQ} + v_{gs}(t)$$

$$V_{DS} = V_{DSQ} + v_{ds}(t)$$

$$i_D = \underbrace{I_{DQ}}_{\substack{\text{DC-bias} \\ \text{point} \\ (\text{Q-point})}} + \underbrace{i_d(t)}_{\substack{\text{Small} \\ \text{Signal}}}$$

Finding Max v_i :

$$V_{GSQ} - |Av|v_i = V_{GSQ} + v_i - V_t$$

→ solve for v_i

comes from:

$$V_{DS, \min} = V_{GS, \max} - V_t$$

$$v_{ds} = Av v_{gs}$$

small signal volt. gain

$$Av = -R_D k'n \left(\frac{w}{l}\right) (V_{GSQ} - V_t)$$

* can pick resistors, transistors, and Q-Point
to get desired gain when designing.

- Small Signal Eq.:

$$i_d = k'n \left(\frac{w}{l}\right) [v_{gs} (V_{GSQ} - V_t)]$$

$$g_m = \frac{i_d}{v_{gs}} = k'n \left(\frac{w}{l}\right) (V_{GSQ} - V_t) \quad \begin{matrix} \text{units} \\ [\frac{A}{V}] \end{matrix}$$

$$Av = -g_m R_D$$

$$\text{reminder: } r_o = \frac{V_A}{2I_{DQ}} = \frac{V_A}{I_{DQ}}$$

* coupling capacitors act as open circuits for DC
and as short circuits for AC.

U



- MOS Amps: * Combined w/ the Small sig. eqs.

$$R_{in} = \frac{V_i}{I_i} \quad V_i = \frac{R_{in}}{R_{in} + R_{sig}} \cdot V_{sig}$$

$$A_{v0} = \frac{V_0}{V_i} \Big|_{R_L \rightarrow \infty} \quad A_v = \frac{V_0}{V_i}$$


$$G_v = \frac{V_0}{V_{sig}}$$

- Common Source Amp: ("Source Grounded")

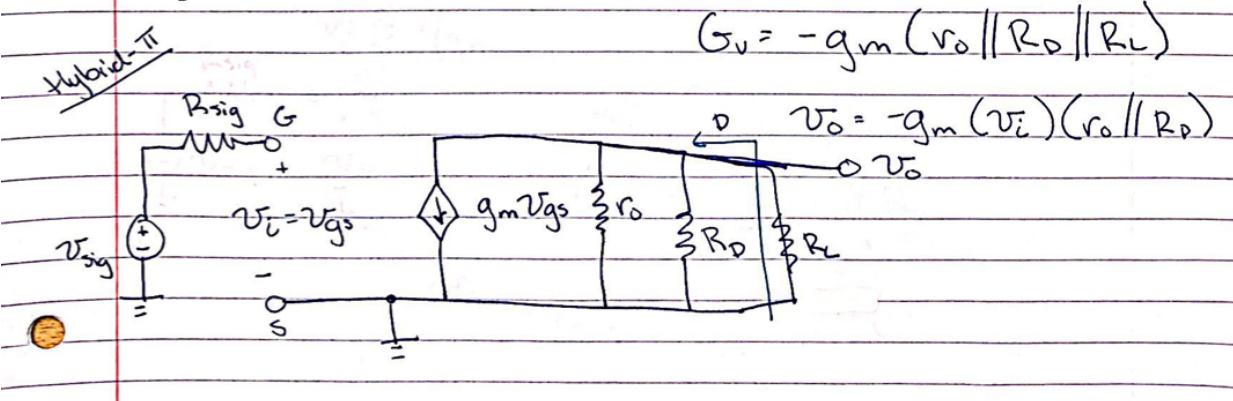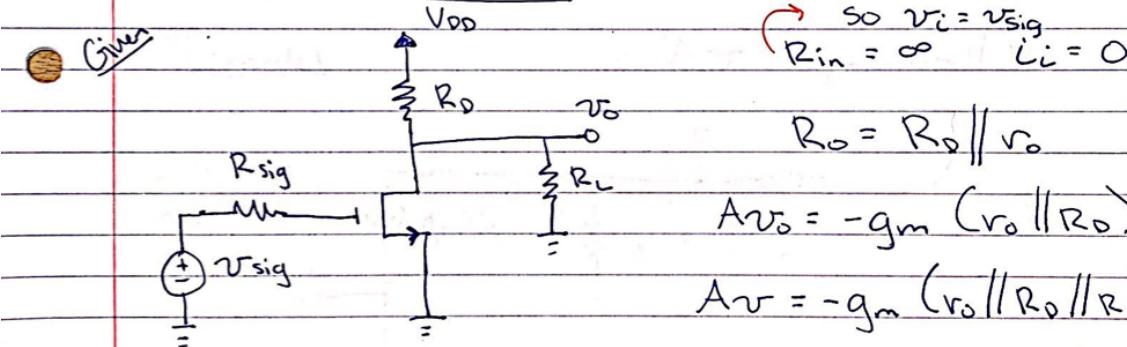

- Common Gate Amp: (gate grounded, v_i is @ source)

Given

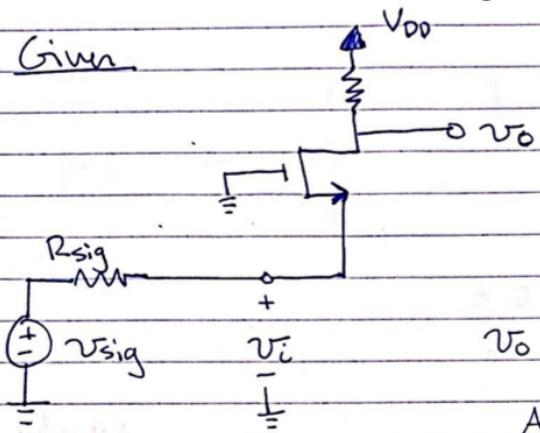

$$R_{in} = 1/g_m$$

$$R_o = R_o$$

$$v_{gs} = -v_i$$

$$V_0 = -g_m(R_0)(-v_i) = g_m R_0 v_i$$

$$Av_o = g_m R_o$$


T-model

$$Av = g_m(R_D \parallel R_L)$$

note: -
-

~50%

2505

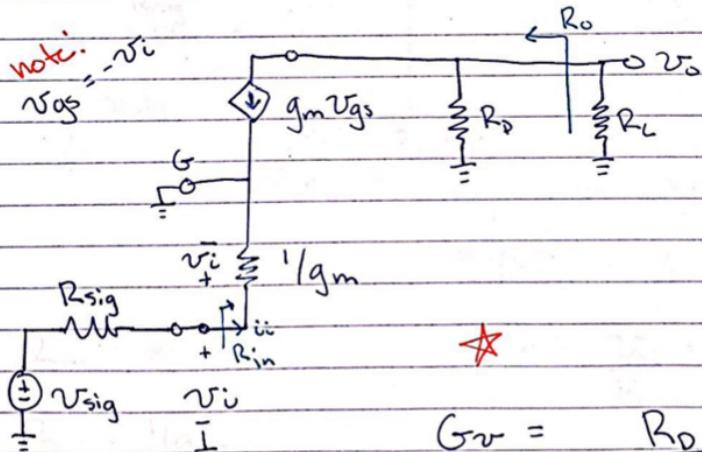


$$G_{\text{var}} = \frac{R_D // R_L}{R_{\text{sig}} + 1/g_m}$$

or


$$G_{\text{av}} = \frac{R_D // R_L}{R_{\text{sig}} + R_{\text{in}}}$$

Common Drain Amp: (voltage follower, v_i at gate)

Given

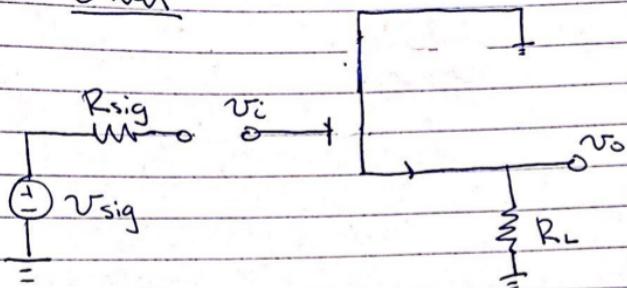

Model

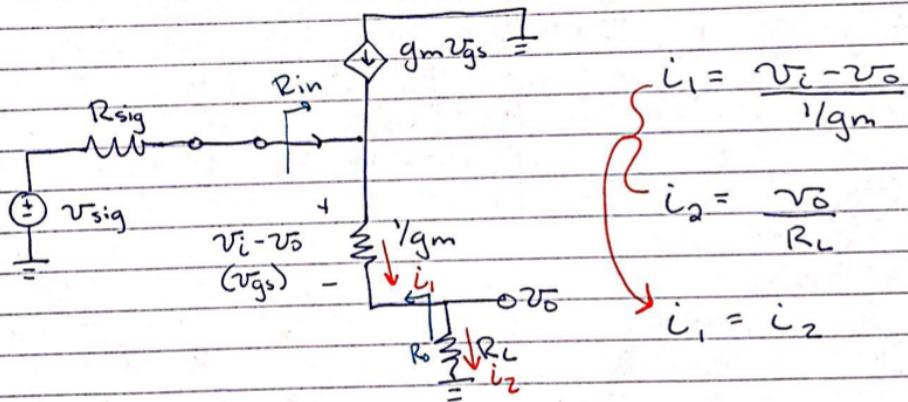

$$R_{in} = \infty$$

$$Av = \frac{v_o}{v_i} = \frac{R_L}{R_L + 1/g_m}$$

$$R_o = 1/g_m$$

$$G_v = \frac{v_o}{v_{sig}} = \frac{R_L}{R_L + 1/g_m}$$

$$Av_o = \left. \frac{v_o}{v_i} \right|_{R_L \rightarrow \infty} = 1$$

if R_L is $\gg 1/g_m$ then $G_v \approx 1$