

Cover Page

CPE 324-02: Digital Hardware Design Fundamentals

Lab 5

Simulation of Finite State Machine Designs

Submitted by: Nolan Anderson

Date of Experiment: 28 March 2021

Report Deadline: 28 March 2021

1. Introduction:

1.1 - What is to be studied, what is the purpose, and how is this purpose accomplished?

This lab is split into 3 separate parts, all implemented in the Modelsim program. We are to implement a (2.1) behavioral simulation of a Mealy FSM, a (2.2) Structural Implementation of a Mealy FSM, and (2.3) a Behavioral simulation of a Moore FSM. We are to implement these 3 different models for a two's complement serial adder. We do this by feeding the implementations with a testbench file that has predefined values passed into the FSM. I will first cover the theory behind these three implementations in section 2 and share my implementation in section 3. Section 4 will cover what I learned running the experiment, and section 5 will provide an overview of the outputs for each of the simulations.

2. Experiment Description

Theory, analysis, and purpose:

2.1 Two's complement adder

A two's complement adder uses a DFF in its design and two bit-wide inputs to produce a result S. This output S will be the result of the circuit. One thing to note, is that the output depends on the value the DFF produces. So there are technically 3 inputs to the Full Adder. Figure 2.1 shows a functional overview.


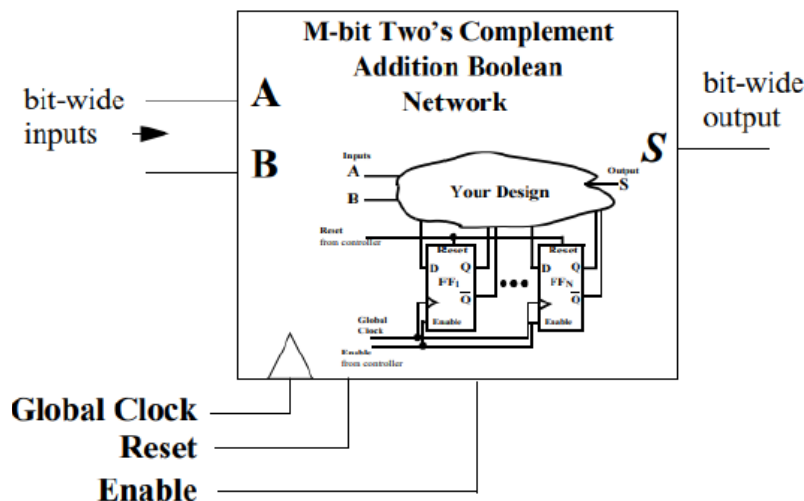


Figure 1: Two's complement adder network

 
2.2 Mealy FSM Behavioral Simulation

The image below shows a state graph for the Mealy FSM that is implemented in Appendix 1. It is a Mealy Machine because its outputs depends on the current inputs.



 
2.3 Mealy FSM Structural Simulation

Like section 2.2, this will have the same state graph. The only different here for the code is how it is implemented. The output produced will be identical and can be seen in section 5. The next figure shows the design for this circuit.



 2.4 Moore FSM Behavioral Simulation

The image below shows a state graph for the Moore FSM that is implemented in Appendix 3. We can see that it is a Moore machine as its outputs only depends on the current state.



2.4 Structural vs Behavioral

As shown in the appendix, the main difference between the behavioral and structural implementations of Verilog code is structural uses module instances and gates / flip flops. Behavioral refers to using always @ blocks. This is important to note as we are implementing part 1 in two different ways, just one is with structural and the other is behavioral.

3. Demonstration

3.1 Implementation method:

3.1.1 Mealy Behavioral:

See appendix 1.

3.1.2 Mealy Structural:

See appendix 2.

3.1.3 Moore Behavioral:

See appendix 3.

3.2 Video Link:

Video uploaded to shared drive.

4. Experimental Results

4.1 Observations:


When observing the outputs from the different waveforms (see section 5) from part one and part 2, we can see that the outputs are the same. Even though the implementation method is completely different, the output is the same. This is the power of structural vs behavioral models. They do the same thing but are fundamentally different. Lastly, looking at the Moore model, we can see the results are as expected.

5. Conclusions


5.1 - Results and lessons learned:

Sections 5.2-5.4 will show the outputs produced from the implementation methods. Overall, the results found in modelsim line very closely with the results expected. In this lab I learned how to use modelsim and all its features, along with a better understanding of Verilog code.


5.2 – Mealy Behavioral Output

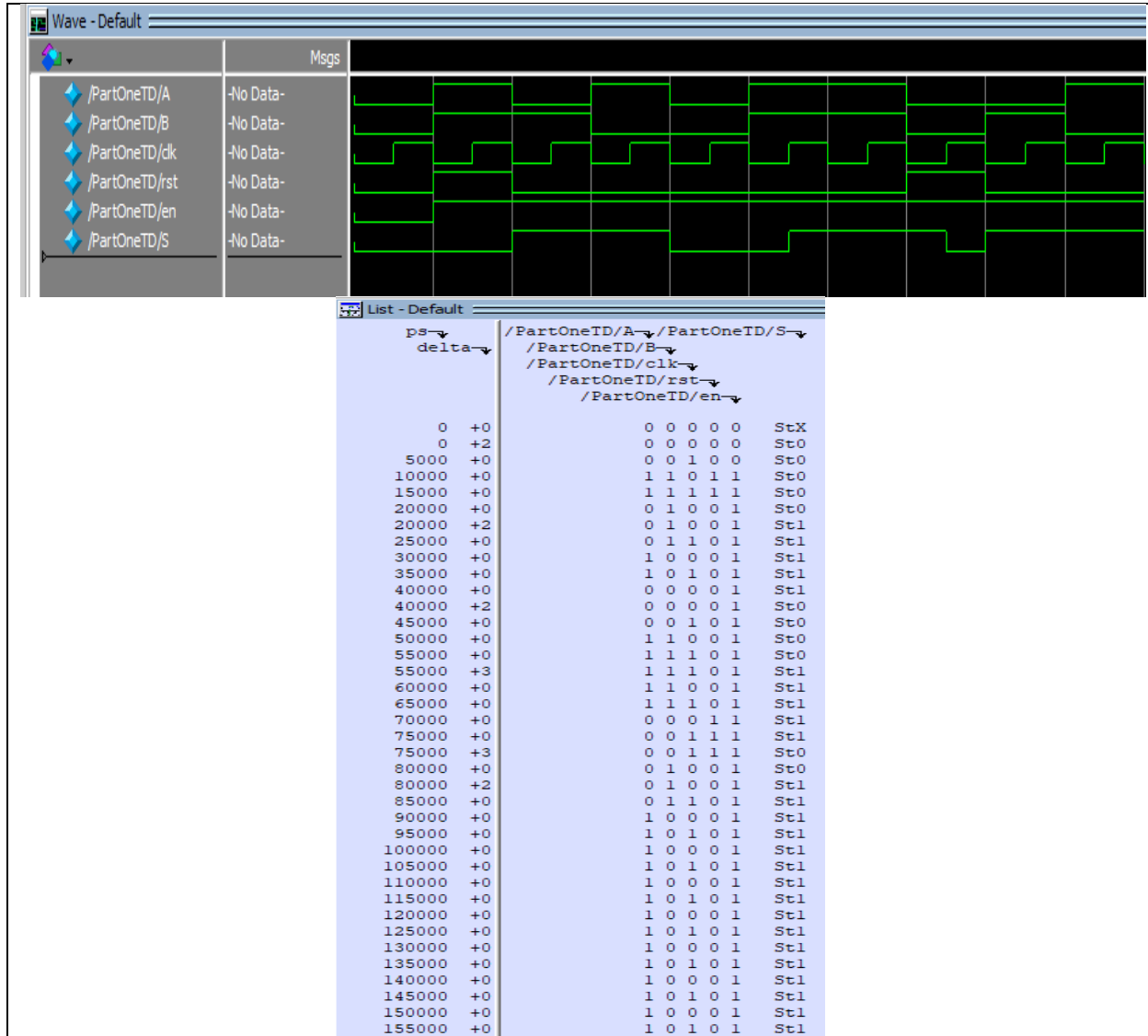

5.3 – Mealy Structural Output

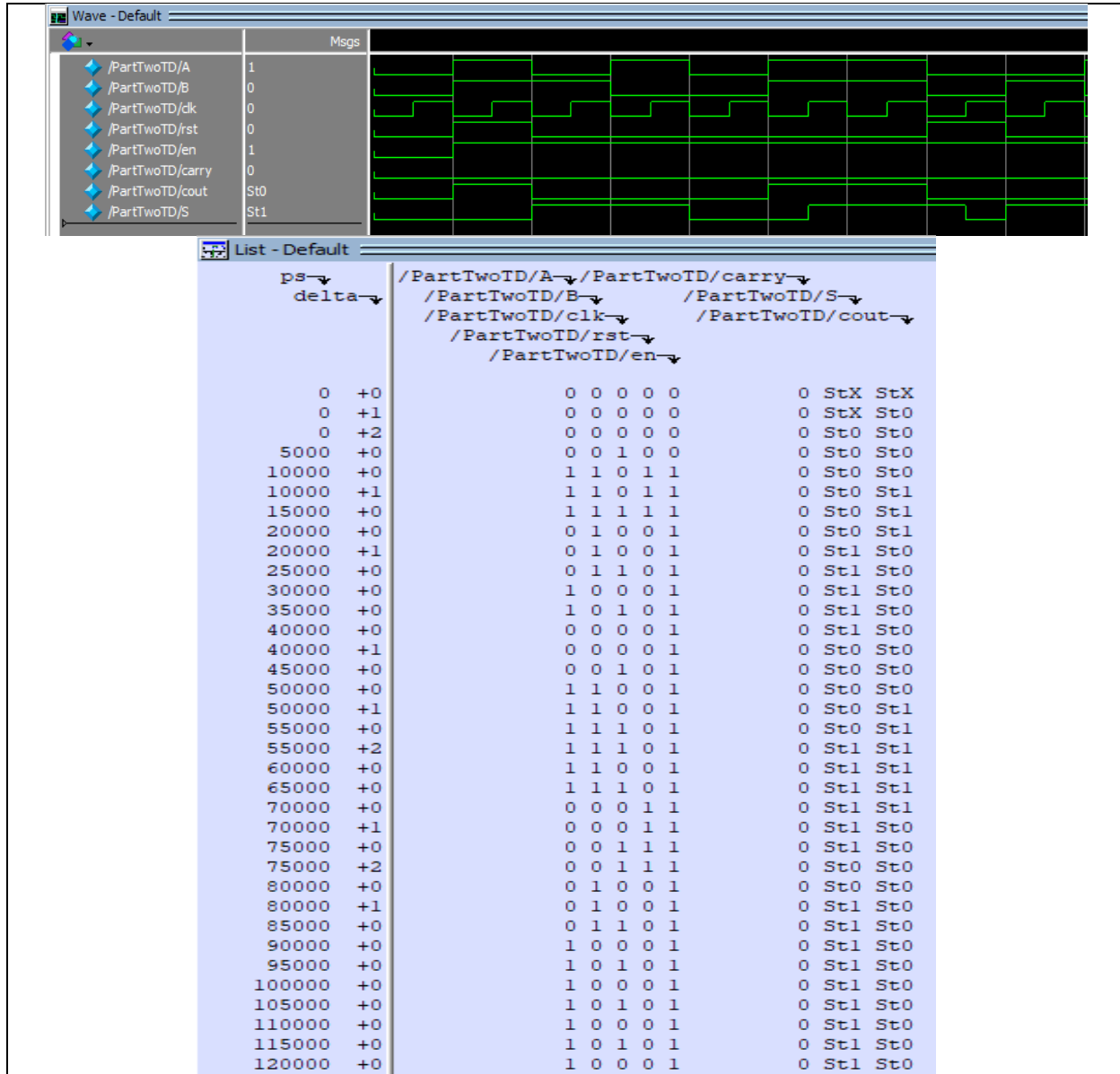

5.4 – Moore Behavioral Output

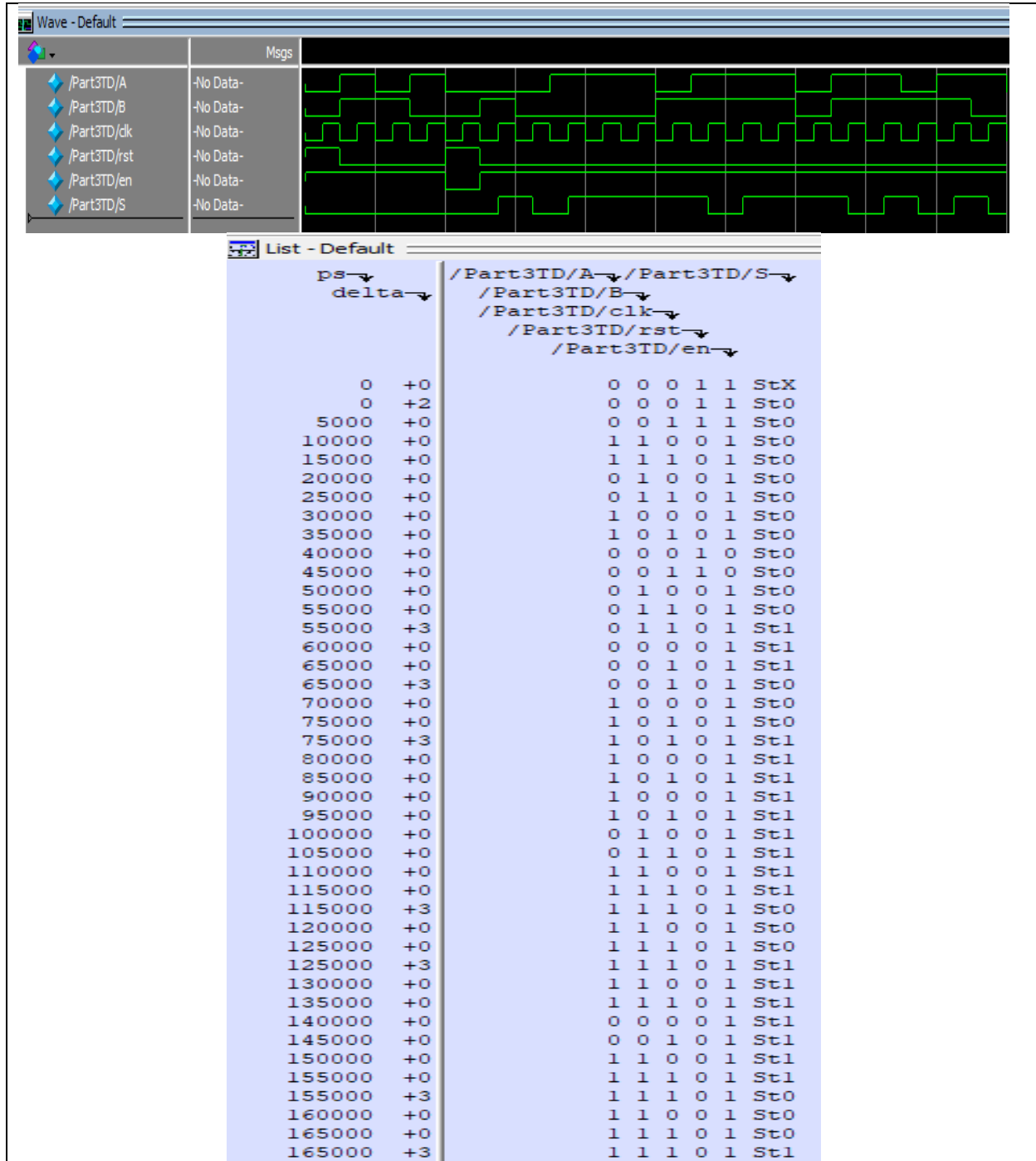

6. Appendix

Appendix 1: Mealy Behavioral Implementation and Test Bench

```
module PartOne(input A, B, clk, rst, en, output reg S);

    reg state = 0;
    reg next = 0;

    always @( A,B,state)begin
        case(state)
            0 : if (A == 0 && B == 0) begin next = 0; S= 0; end
                else if (A ==1 && B == 1) begin next = 1; S = 0; end
                else begin next = 0; S = 1; end
            1 : if (A == 0 && B == 0) begin next = 0; S= 1; end
                else if (A ==1 && B == 1) begin next = 1; S = 1; end
                else begin next = 1; S = 0; end
        endcase
    end

    always @(posedge clk)begin

        if (rst)begin
            state = 0;
        end
        else begin
            if (en) begin state = next; end
        end
    end
endmodule
```

```
`timescale 1ns/100 ps
module PartOneTD;
    reg A = 0, B = 0, clk = 0, rst = 0, en = 0;
    wire S;

    initial
        begin

            #10    // 0ns
            rst = 1; A = 1; B = 1; en = 1;

            #10    // 10ns
            rst = 0; A = 0; B = 1; en = 1;
```

```

#10 // 20ns
rst = 0; A = 1; B = 0; en = 1;

#10 // 30ns
rst = 0; A = 0; B = 0; en = 1;

#10 // 40ns
rst = 0; A = 1; B = 1; en = 1;

#10 // 50ns
rst = 0; A = 1; B = 1; en = 1;

#10 // 60ns
rst = 1; A = 0; B = 0; en = 1;

#10 // 70 ns
rst = 0; A = 0; B = 1; en = 1;

#10 // 80 ns
rst = 0; A = 1; B = 0; en = 1;
end

always
begin
clk = #5 ~clk;
end

PartOne uut (.A(A),.B(B),.clk(clk),.en(en),.rst(rst),.S(S));

endmodule

```

Appendix 2: Mealy Structural Implementation and Test Bench

```

module Mealy(input A, B, carry, en, rst, clk, output S, cout);
  wire cin, x1, x2, x3;
  wire w0, w1, w2, w3, w4, w5, w6;

  // Cin value
  DFF A0(carry, clk, rst, en, cin);

  // XOR A and B
  and(w0, A, B);
  or (w1, A, B);
  not(w2, w0);
  and(w3, w2, w1);

```

```

        // XOR A, B, and CIN
        and(w4, w3, cin);
        or (w5, w3, cin);
        not(w6, w4);
        and(S, w6, w5);
        // Perform operation on inputs
        and A2(x1, A, B);
        and A3(x2, A, cin);
        and A4(x3, B, cin);
        or A5(cout, x1, x2, x3);
    endmodule

module DFF(input D, clk, rst, en, output reg Q);
    initial
    begin
        Q <= 0;
    end
    always @(posedge clk) begin
        if(rst) Q <= 0;
        else if(en) Q <= D;
    end
endmodule

```

```

`timescale 1ns/100 ps

module PartTwoTD;
    reg A = 0, B = 0, carry = 0, clk = 0, rst = 0, en = 0;
    wire S, cout;

    initial
    begin

        //0ns
        rst = 1; A = 1; B = 1; en = 1;

        #10    //10ns
        rst = 0; A = 0; B = 1; en = 1;

        #10    //20ns
        rst = 0; A = 1; B = 0; en = 1;

        #10    //30ns
        rst = 0; A = 0; B = 0; en = 1;

        #10    //40ns
        rst = 0; A = 1; B = 1; en = 1;
    end
endmodule

```

```

#10    //50ns
rst = 0; A = 1; B = 1; en = 1;

#10 //60ns
rst = 1; A = 0; B = 0; en = 1;

#10    //70ns
rst = 0; A = 0; B = 1; en = 1;

#10    //80ns
rst = 0; A = 1; B = 0; en = 1;
end

always
begin
clk = #5 ~clk;
end

Mealy uut (.A(A),.B(B),.carry(cout),.en(en),.rst(rst),.clk(clk),.S(S),.cout(cout));

endmodule

```

Appendix 3: Moore Behavioral Implementation and Test Bench

```

module Part3(input A,B,clk,rst,en, output reg S);

reg [1:0] state = 0;
reg [1:0] next = 0;

always @(A, B, state)begin
    case(state)
        0 : begin    S = 0;
                    if (A == 0 && B == 0) begin next = 0; end
                    else if (A ==1 && B == 1) begin next = 2; end
                    else begin next = 1; end
                end
        1 : begin S = 1;
                    if (A == 0 && B == 0) begin next = 0; end
                    else if (A ==1 && B == 1) begin next = 2; end
                    else begin next = 1; end
                end
        2 : begin S = 0;
                    if (A == 0 && B == 0) begin next = 1; end

```

```

        else if (A == 1 && B == 1) begin next = 3; end
        else begin next = 2; end
    end
    3 : begin S = 1;
        if (A == 0 && B == 0) begin next = 1; end
        else if (A == 1 && B == 1) begin next = 3; end
        else begin next = 2; end
    end
endcase
end

always @(posedge clk)begin

    if (rst)begin
        state = 0;
    end
    else begin
        if (en) begin state = next; end
    end
end

```

endmodule

```
`timescale 1ns/100 ps
```

```

module Part3TD;
    reg A = 0, B = 0, clk = 0, rst = 0, en = 0;
    wire S;

    initial
        begin

            // 0ns
            rst = 1; A = 0; B = 0; en = 1;

            #10 // 10ns
            rst = 0; A = 1; B = 1; en = 1;

            #10 // 20ns
            rst = 0; A = 0; B = 1; en = 1;

            #10 // 30ns
            rst = 0; A = 1; B = 0; en = 1;

            #10 // 40ns
            rst = 1; A = 0; B = 0; en = 0;
        end
    endmodule

```

```
#10 // 50ns  
rst = 0; A = 0; B = 1; en = 1;
```

```
#10 // 60ns  
rst = 0; A = 0; B = 0; en = 1;
```

```
#10 // 70ns  
rst = 0; A = 1; B = 0; en = 1;
```

```
#10 // 80ns  
rst = 0; A = 1; B = 0; en = 1;
```

```
#10 // 90 ns  
rst = 0; A = 1; B = 0; en = 1;
```

```
#10 //100ns  
rst = 0; A = 0; B = 1; en = 1;
```

```
#10 //110ns  
rst = 0; A = 1; B = 1; en = 1;
```

```
#10 // 120ns  
rst = 0; A = 1; B = 1; en = 1;
```

```
#10 // 130ns  
rst = 0; A = 1; B = 1; en = 1;
```

```
#10 // 140ns  
rst = 0; A = 0; B = 0; en = 1;
```

```
#10 // 150ns  
rst = 0; A = 1; B = 1; en = 1;
```

```
#10 // 160ns  
rst = 0; A = 1; B = 1; en = 1;
```

```
#10 // 170ns  
rst = 0; A = 0; B = 1; en = 1;
```

```
#10 // 180ns  
rst = 0; A = 1; B = 1; en = 1;
```

```
#10 // 190ns  
rst = 0; A = 1; B = 0; en = 1;
```

```
#10 // 200ns
```

```
    rst = 0; A = 0; B = 0; en = 1;  
end
```

```
always  
begin  
    clk = #5 ~clk;  
end
```

```
    Part3 uut (.A(A),.B(B),.clk(clk),.rst(rst),.en(en),.S(S));
```

```
endmodule
```