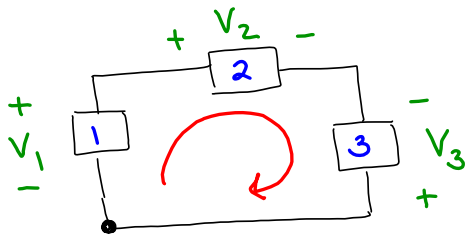


KVL : sum the voltages around a loop
sum must equal = 0



$$\text{PSC: } -V_1 + V_2 - V_3 = 0$$

$$\text{ASC: } +V_1 - V_2 + V_3 = 0$$

KVL process


- ① Pick a loop direction
CW or CCW
- ② Sign Convention
relative to the polarities

Active sign convention

Passive sign convention.


Passive Sign Convention : whatever sign (from the polarity) is encountered is the arithmetic operation performed for that voltage.

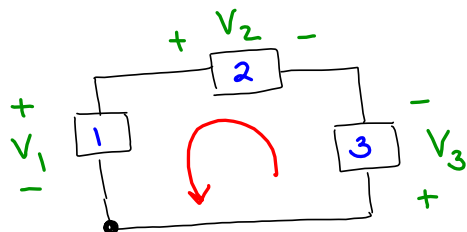Active Sign Convention : moving from (-) to (+) \Rightarrow ADD
moving from (+) to (-) \Rightarrow Subtract



$$\text{PSC: } +V_3 - V_2 + V_1 = 0$$

$$\text{ASC: } -V_3 + V_2 - V_1 = 0$$

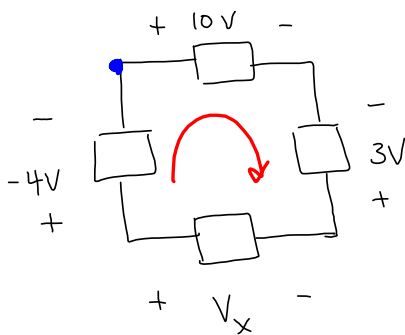

$$\text{PSC: } +10 - 3 - V_x + (-4) = 0$$

$$V_x = 3V$$

$$\text{ASC: } -10 + 3 + V_x - (-4) = 0$$

$$V_x = 3V$$

Ohm's Law : the current that flows through a conducting medium is proportional to the voltage across that medium.



proportionality constant \equiv resistance

$R \equiv$ resistance

$$R = \frac{V}{I} \text{ or } \frac{v(t)}{i(t)} = \frac{V}{A} \Rightarrow \text{ohm } [\Omega]$$


ohm's law \Rightarrow $V = IR$ \Rightarrow passive elements
resistor *
capacitor
inductor

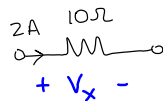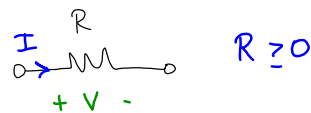for a resistor, if V and I have the same sign \Rightarrow current flows from (+) to (-) for the voltage.



$$V_x = IR = 2(10) = 20V$$
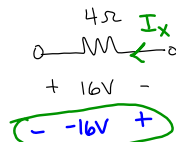
$$\begin{aligned} P &= VI \\ P &= (20)(2) \\ &= 40W, \text{ Abs} \end{aligned}$$




$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I_x = \frac{-16}{4} \quad \text{or} \quad -I_x = \frac{16}{4}$$


$$I_x = -4A$$
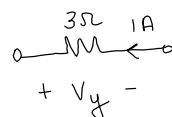
$$\begin{aligned} P &= VI \\ P &= (16)(-4) \\ &= -64W, \text{ Del} \\ &+ 64W, \text{ Abs} \end{aligned}$$




$$V_y = 3(-1) = -3V$$
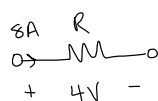
$$\begin{aligned} P &= (V_y)(1) = -3(1) = -3W, \text{ Del} \\ &\text{or } +3W, \text{ Abs} \end{aligned}$$


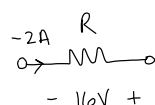
$$R = \frac{V}{I} = \frac{4}{8} = 0.5 \Omega$$



$$R = \frac{V}{I} = \frac{16}{-(-2)} = 8 \Omega$$

$$V = IR$$

$$P = VI$$

$$P = (IR)I$$

$$= I^2 R$$

$$I = \frac{V}{R}$$

$$P = VI$$


$$P = V\left(\frac{V}{R}\right) = \frac{V^2}{R}$$



$$P = I^2(R)$$

$$= (-1)^2(3)$$

$$= 3W, \text{ Abs}$$

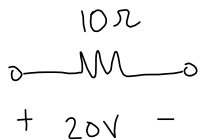



$$P = \frac{V^2}{R} = \frac{(20)^2}{10} = 40W, \text{ Abs}$$

Special Cases:

$$R = 0$$

$$V = IR$$


$$V = 0 \text{ if } R = 0$$

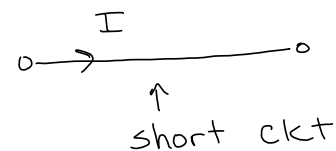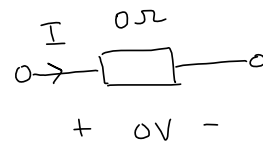

$$R \rightarrow \infty$$


$$I = \frac{V}{R}$$

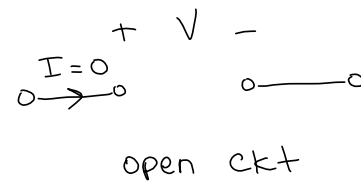
$$I = 0 \text{ if } R \rightarrow \infty$$



$$\text{Conductance} \equiv G = \frac{1}{R} = \frac{I}{V} \quad \text{mhos } \mathcal{U}$$

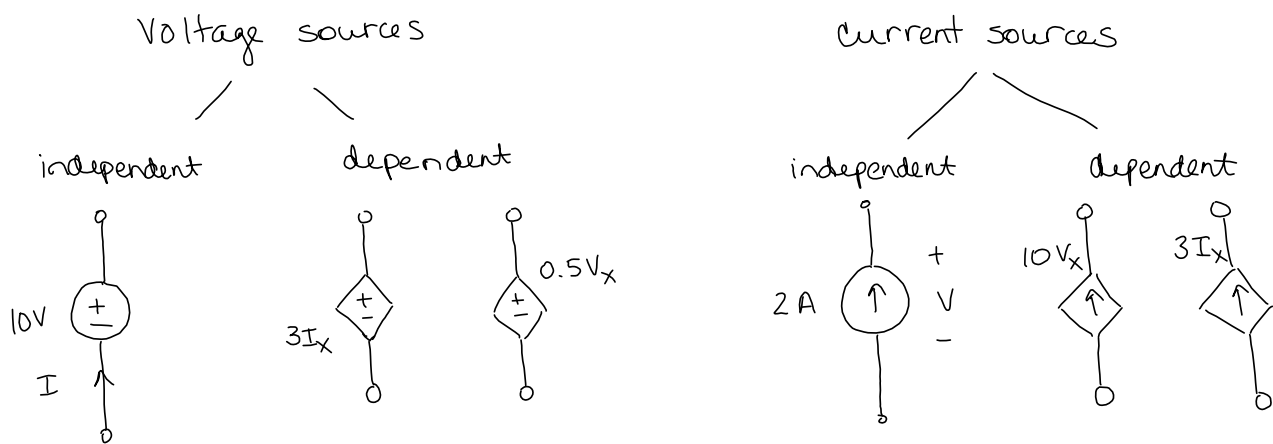Active Elements \Rightarrow Deliver or Absorb power



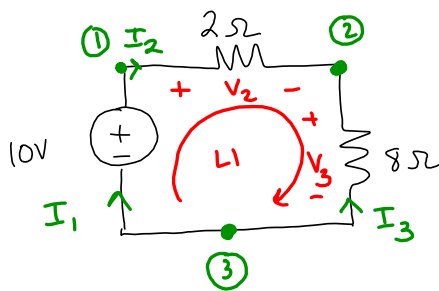

KCL

- ① $I_1 = I_2$
- ② $I_2 + I_3 = 0$
- ③ $0 = I_1 + I_3$

Brute Force

- ① Identify all nodes and loops in a ckt.
- ② Label all voltages and currents as appropriate.
- ③ Write KCL, KVL, & Ohm's law equations
- ④ Solve