

Op, Reference Amp:

* Use Super position

$$CMRR = 20 \log \left| \frac{A_d}{A_{CM}} \right|$$

→ If A_{CM} is zero, (ideal) → $CMRR = \infty$

Want $A_{CM} = 0$

$$\left. \begin{array}{l} R_4 = R_2 \\ R_1 = R_3 \end{array} \right\} \begin{array}{l} \text{Zero common} \\ \text{mode gain} \end{array}$$

A_d

$$A_d = R_2 / R_1$$

$$\boxed{V_o = A_{CM} V_{ICM} + A_d V_{ID} \rightarrow V_o = A_d V_{ID}}$$

\uparrow
ideally 0

$$V_o = \frac{R_2}{R_1} V_{ID}$$

*issue! $R_4 = R_2$ & $R_3 = R_1$, rather restrictive.

Example:

↑
large

much larger
← than R_1

