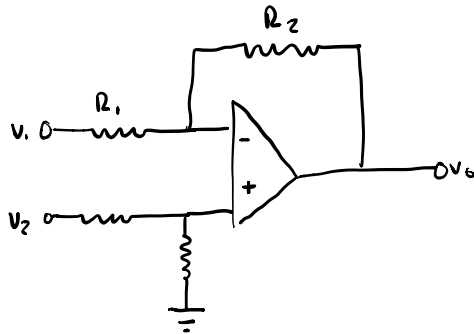


Nolan Anderson

a)



$$G = 25\%$$

$$R_{id} = 2R_1 = 100k\Omega$$

$$R_1 = 50k\Omega$$

$$A_d = 25 = \frac{R_2}{R_1} \Rightarrow R_2 = 50 \times 25 = 1.25m\Omega$$

$$\text{For } A_{cm} = 0 \dots R_4 = R_2 = 1.25m\Omega$$

$$R_1 = R_3 = 50k\Omega$$

$$A_{cm} = -\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) \quad \boxed{A_{cm} = 0}$$

$$\frac{1.25E6}{50E3} + \left(1 + \frac{1.25E6}{50E3}\right) \left(\frac{1.25}{50 + 1.25}\right)$$

b

$$R_4 = 1.375m\Omega \quad R_2 = 1.125m\Omega$$

$$R_3 = 50k\Omega \quad R_1 = 50k\Omega$$

$$A_d = \frac{1}{2} \left(\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) \right)$$

$$\frac{1}{2} \left(\frac{1.125 \text{E}6}{50 \text{E}3} + \left(1 + \frac{1.125 \text{E}6}{50 \text{E}3} \right) \left(\frac{1.375 \text{E}6}{50 \text{E}3 + 1.375 \text{E}6} \right) \right)$$


$$A_d = 22.587 \text{ V/V}$$

$$A_{cm} = -\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) \quad \boxed{A_{cm} = 0}$$


$$\frac{-1.125 \text{E}6}{50 \text{E}3} + \left(1 + \frac{1.125 \text{E}6}{50 \text{E}3} \right) \left(\frac{1.375 \text{E}6}{50 \text{E}3 + 1.375 \text{E}6} \right)$$

$$A_{cm} = .175 \text{ V/V}$$

Z

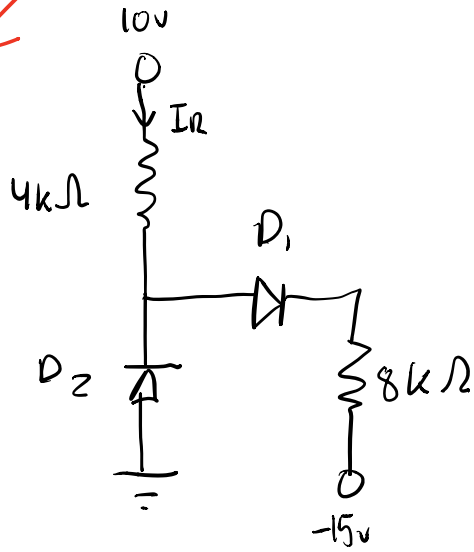

Both on:

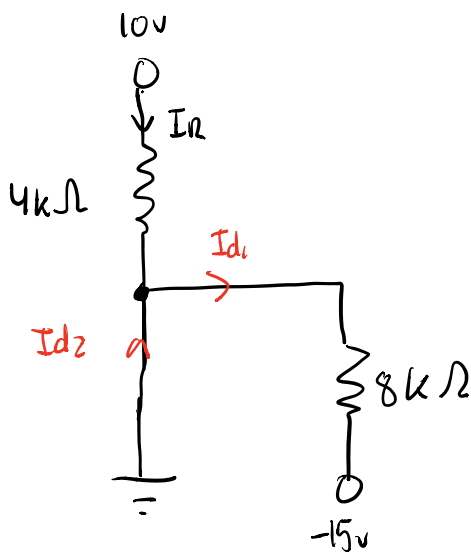


$$I_{D1} ; I_{D2} > 0$$

$$I_{D1} = \frac{0 - (-15V)}{8} = \frac{15}{8} = 1.875$$

$$I_{D2} = \frac{0 - 10V}{4} = -.4$$

$I_{D2 \text{ off}} / I_{D1 \text{ on}}$

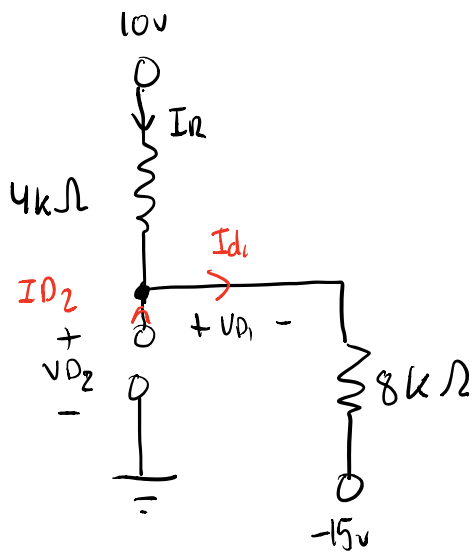

$$I_{D2} = 0$$

$$I_{D1} = 1.875 \text{ A}$$


$$V_{D1} = I_{D1} (8) \Rightarrow V_{D1} = 15 \text{ V}$$

$$V_{D1} = 15 \text{ V}$$

$$V_{D2} = 0 (4 \text{ k}\Omega) = 0 \text{ V}$$

$$I_R = \frac{-10 + 15}{4 + 8} \Rightarrow I_R = 0.416 \text{ A}$$

3)

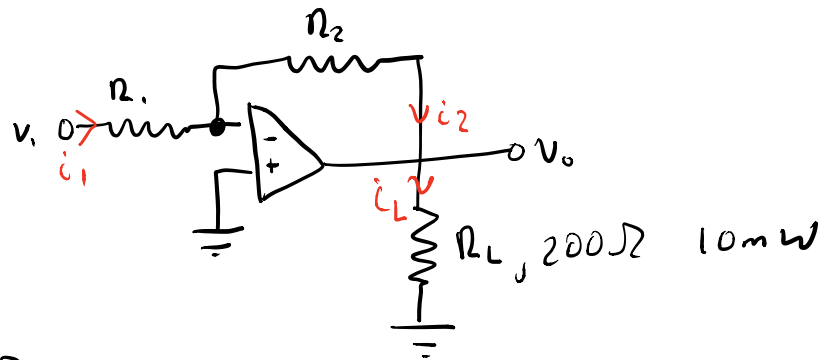

$$G = 18 \text{ dB}$$

$$I_R = 400 \mu\text{A}$$

$$\frac{V_o^2}{200\Omega} = 10 \text{ mW} \quad V_o^2 = 2$$

$$V_o = 1.41 \text{ V}$$

$$G = 18 = 7.94 \text{ V/V} = \frac{V_o}{V_s} = 7.94 = \frac{1.41}{V_s}$$

$$V_s = 0.1776 \text{ V}$$


$$i_L = \frac{V_o}{R_L} = \frac{1.41}{200} = 0.00705 \text{ A}$$

$$i_2 = \frac{0 - V_o}{R_2} = R_2 = \frac{1.41}{0.00705} \quad R_2 = 200\Omega$$

$$G = \frac{V_o}{V_s} = \frac{V_o}{V_i} = -\frac{R_2}{R_1} = 7.94 \quad -\frac{200}{R_1} = 7.94$$


$$7.94 R_1 = 200 \Rightarrow R_1 = 25.19 \Omega$$

4

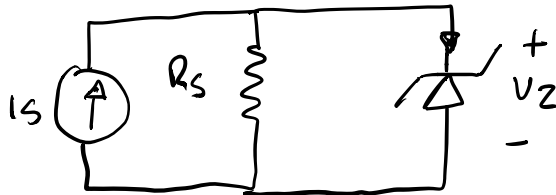

$$V_Z = 5.6 \text{ V}$$

$$I_Z = 3.25 \text{ mA}$$

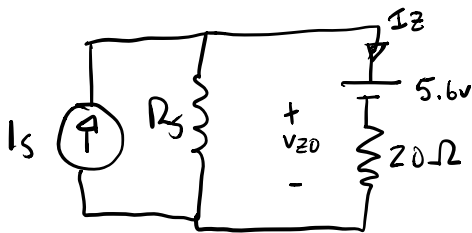

$$V_{Z0} = V_Z - I_Z R_Z$$

$$V_{Z0} = 5.6 - (3.25 \text{ mA})(20 \Omega)$$

$$V_{Z0} = 5.6 - (.00325)(20)$$

$$V_{Z0} = 5.535 \text{ V}$$

$$\text{Want } I_Z = 5 \text{ mA}$$

$$V = IR$$

$$R_s = ?$$


$$V_{Z0} = 5.535$$

$$I_s = 12 \text{ mA}$$

$$V_Z = V_{Z0} + I_Z R_Z$$

$$= 5.535 + (.00325)(20)$$

$$V_Z = 5.6$$

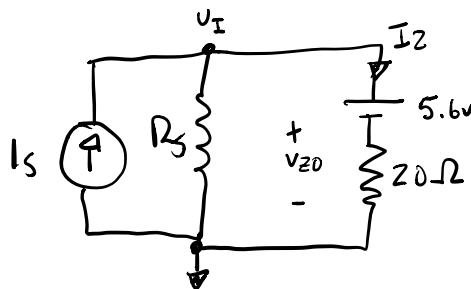

$$V_Z = 5.6$$

$$I_s = 12 \text{ mA}$$

$$I_Z = 5 \text{ mA}$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$5 \text{ mA} = \frac{5.535}{20 + R_s}$$

$$.1 + .005 R_s = 5.535$$


$$.005 R_s = 5.435$$

$$R_s = 1087 \Omega$$


$$R_s = 1.087 \text{ k}\Omega$$

Print Your Name _____

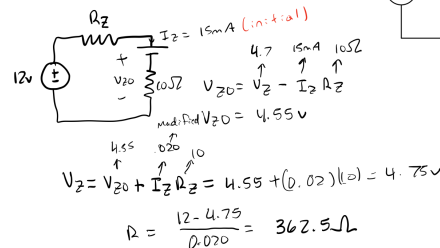4. [15 points] Consider the following circuit that contains a Zener diode. It is known that when the Zener voltage is 4.7 V, the Zener current is 15 mA. The incremental Zener resistance is 10 Ω . Find the value of V_{Z0} and design the resistor, R_s for a Zener current of 20 mA.



5

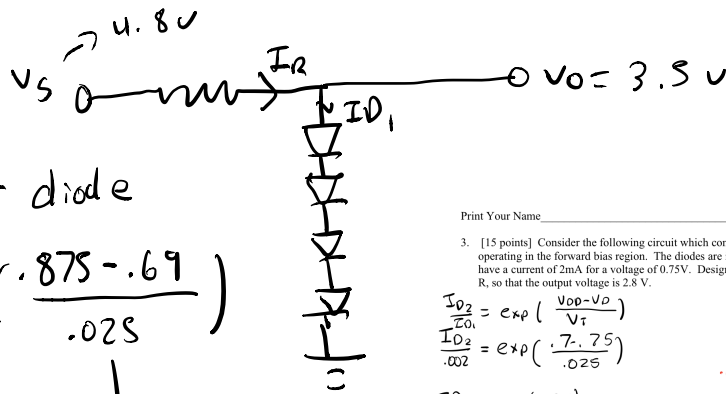

.875V per diode

$$\frac{I_{D2}}{I_{D1}} = \exp\left(\frac{.875 - .69}{.025}\right)$$



$$I_{D2} = .005 \exp\left(\right)$$

$$I_{D2} \xrightarrow{I_R} I_{D2} = 8.18 A$$

$$R = \frac{4.8 - 3.5}{8.18 A}$$

$$R = .158 \Omega$$

$$I_D = \frac{4.8 - .73V}{.158} \Rightarrow I_D = 25.76 A$$

Print Your Name _____

3. [15 points] Consider the following circuit which contains diodes operating in the forward bias region. The diodes are identical and have a current of 2mA for a voltage of 0.75V. Design the resistor, R, so that the output voltage is 2.8 V.

$$\frac{I_{D2}}{I_{D1}} = \exp\left(\frac{V_{D2} - V_{D1}}{V_T}\right)$$

$$\frac{I_{D2}}{.002} = \exp\left(\frac{.7 - .75}{.025}\right)$$

$$I_{D2} = .002(.135)$$

$$I_{D2} = .00027 A$$

$$R = \frac{8 - 2.8}{.00027 A} = 19.21 k\Omega$$

$$V_{D2} = 0.7$$

$$V_{D1} = 0.75$$

$$I_{D2} = I_{D1} \exp\left(\frac{V_{D2} - V_{D1}}{V_T}\right)$$

