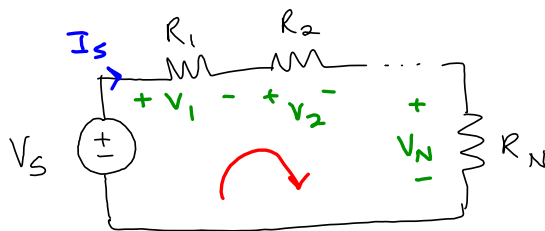


Quiz Wednesday, January 22nd

* Brute Force, Power *

20 min (Beginning of Class)

Resistors in Series :



by KVL:

$$V_S - V_1 - V_2 - \dots - V_N = 0$$

by Ohm's law:

$$V_1 = R_1 I_S$$

$$V_2 = R_2 I_S$$

\vdots

$$V_N = R_N I_S$$

$$V_S - I_S R_1 - I_S R_2 - \dots - I_S R_N = 0$$


$$V_S - I_S (R_1 + R_2 + \dots + R_N) = 0$$

$$V_S = I_S (R_1 + R_2 + \dots + R_N)$$

$$\text{let } R_{eq} = R_1 + R_2 + \dots + R_N$$


$$V_S = I_S R_{eq}$$

Equivalent ckt

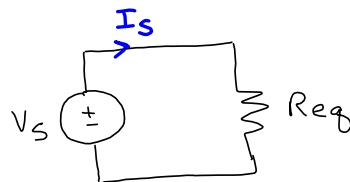

* that resistors in series combine via addition.

Resistors in Parallel

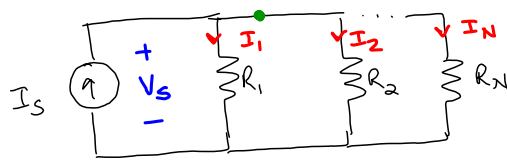

by KCL

$$I_s = I_1 + I_2 + \dots + I_N$$

by Ohm's law

$$I_1 = \frac{V_s}{R_1} \quad I_2 = \frac{V_s}{R_2} \quad \dots \quad I_N = \frac{V_s}{R_N}$$


$$I_s = \frac{V_s}{R_1} + \frac{V_s}{R_2} + \dots + \frac{V_s}{R_N}$$

$$I_s = V_s \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)$$

$$V_s = I_s \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$



$$\text{let } R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$

Eg ckt

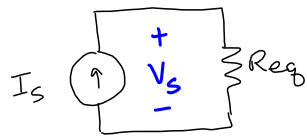

$$V_s = I_s R_{eq}$$

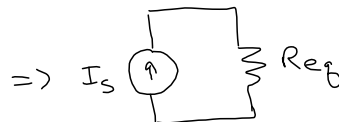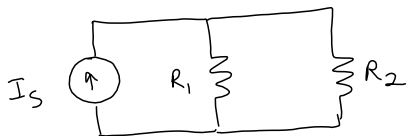* resistors in parallel combine as the inverse of the sum of the inverses.







$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$= \frac{1}{\frac{R_2 + R_1}{R_1 R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Case 1: $R_1 = 0, R_2$
 $R_{eq} = 0$

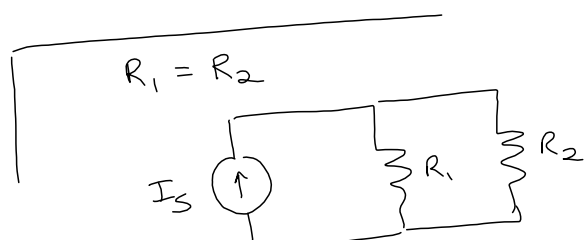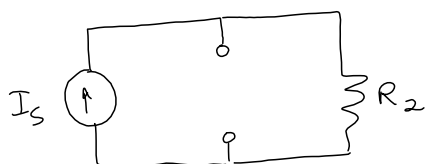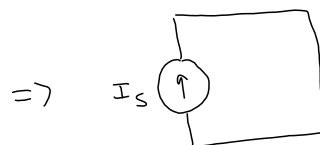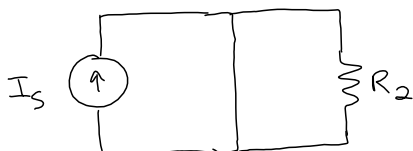Case 2: $R_1 \rightarrow \infty, R_2$
 $R_{eq} \rightarrow R_2$



more than two resistors in parallel

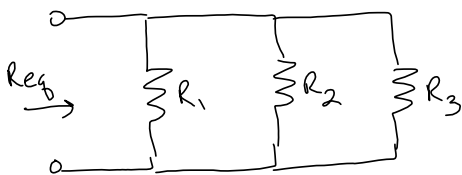


$$R_{eq} = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$



$$= \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$


$R_1 + R_2 + R_3 + \dots$ Series

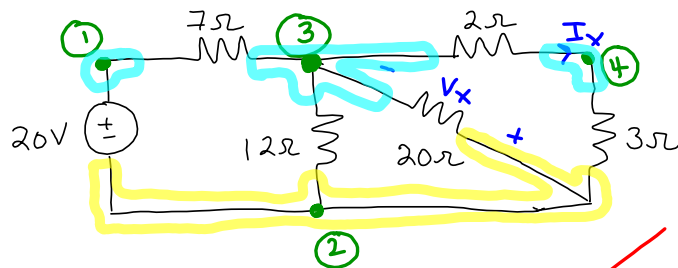$R_1 \parallel R_2 \parallel R_3 \parallel \dots$ Parallel



(A) at (4) $2 + 3 = 5\Omega$

$$I_x = -\frac{V_x}{5} = 1.2 \text{ A}$$

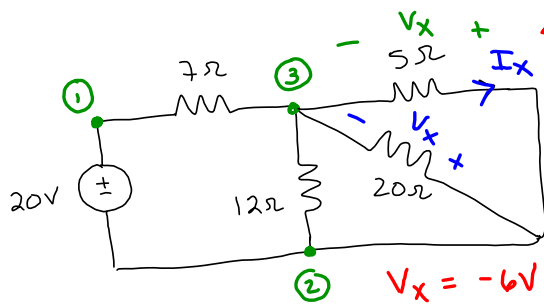

(B) between (2) + (3)


$$5 \parallel 20 \parallel 12 \quad *$$

$$5 \parallel 20 = \frac{100}{25} = 4$$

$$4 \parallel 12$$


$$4 \parallel 12 = \frac{48}{16} = 3\Omega$$

$$V_x = -6V$$

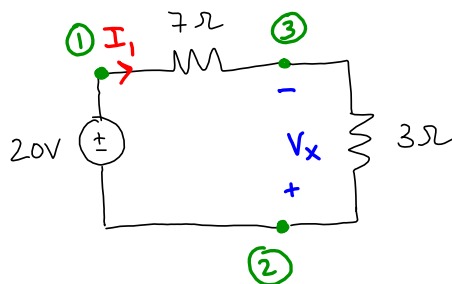


(C) at (3) $7 + 3 = 10\Omega$

$$V_x = 3(-I_1) = -6V$$

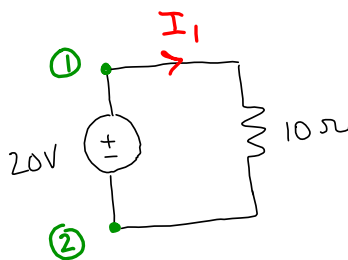





$$I_1 = \frac{20}{10} = 2 \text{ A}$$

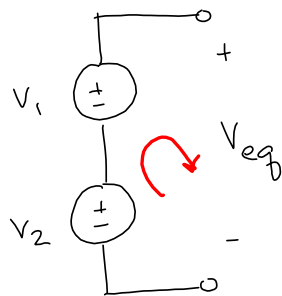

by KVL


$$V_2 + V_1 - V_{eq} = 0$$

$$V_{eq} = V_1 + V_2$$

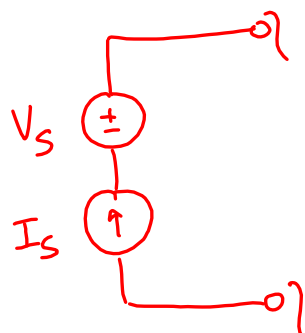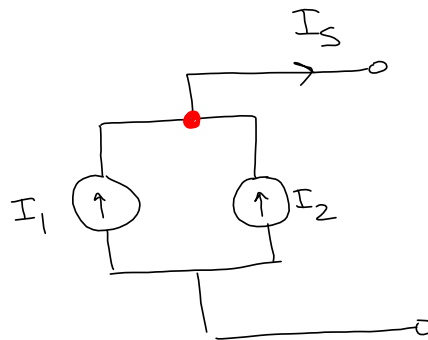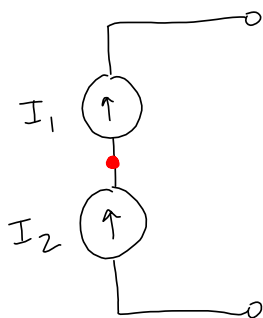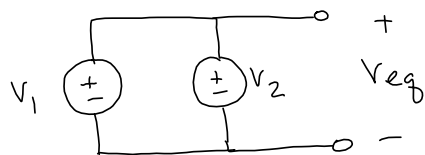

Voltage + Current Division

Voltage division/divider

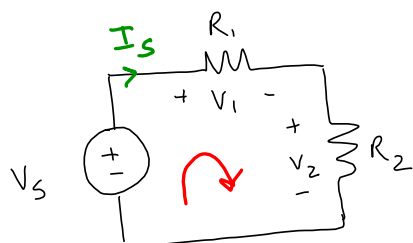

by KVL

$$V_S - V_1 - V_2 = 0$$

$$V_1 = I_S R_1$$

$$V_S = V_1 + V_2$$

$$V_2 = I_S R_2$$

$$V_S = I_S R_1 + I_S R_2$$