


Circuits Eq. Sheet

Natalie Tayya

Exam 2

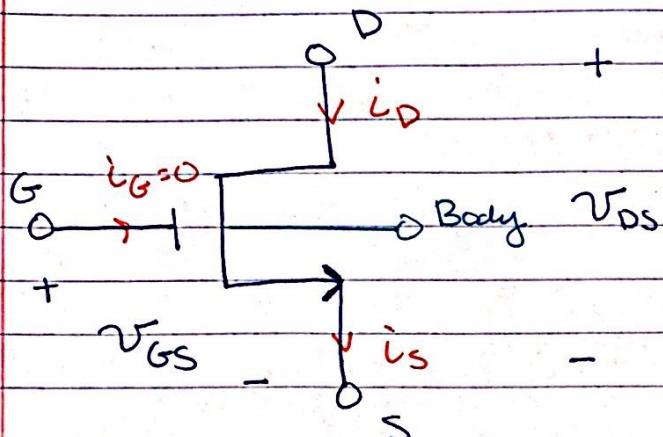(1)

- MOSFETS: NMOS. ★ see MOSFET Eq. Summary.



Symmetrical Device:

$$i_D = i_S$$

$$\text{so: } i_G = 0$$

$$4nCox, V_{tn} = V_t$$

Triode:

- ① $v_{GS} > V_t$, v_{DS} is very small

$$i_D = k'n \left(\frac{w}{l} \right) (v_{GS} - V_t) v_{DS}$$

$$v_{ds} = \frac{k'n \left(\frac{w}{l} \right) (v_{GS} - V_t)}{i_D}$$

- ② $v_{GS} > V_t$, v_{DS} is small

$$v_{DS} < (v_{GS} - V_t)$$

$$i_D = k'n \left(\frac{w}{l} \right) \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

Saturation Region:

$$v_{GS} > V_t$$

$$v_{DS} > v_{GS} - V_t \rightarrow$$


Edge of Saturation:

$$v_{DS} = v_{GS} - V_t$$

$$i_D = \frac{1}{2} k'n \left(\frac{w}{l} \right) (v_{GS} - V_t)^2$$

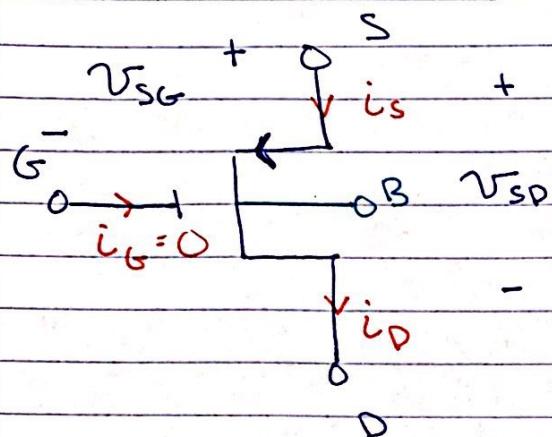(2)

- MOSFETs: PMOS \rightarrow also in MOSFET Eq. Summary



Symmetrical Device.

$$i_D = i_S$$

$$\text{so: } i_G = 0$$

$$V_{tP} < 0 \text{ so } |V_{tP}|$$

Triode:

$$\textcircled{1} \quad V_{SG} > |V_{tP}|, V_{SD} \text{ is very small}$$

$$i_D = k'_p \left(\frac{w}{l}\right) (V_{SG} - |V_{tP}|) V_{SD}$$

$$r_{ds} = \frac{1}{k'_p \left(\frac{w}{l}\right) (V_{SG} - |V_{tP}|)}$$

$$\textcircled{2} \quad V_{SG} > V_t, V_{SD} \text{ is small}$$

$$V_{SD} \ll V_{SG} - |V_{tP}|$$

$$i_D = k'_p \left(\frac{w}{l}\right) \left[(V_{SG} - |V_{tP}|) V_{SD} - \frac{1}{2} V_{SD}^2 \right]$$

Saturation:

$$V_{SG} > |V_{tP}|$$

Edge of saturation:

$$V_{SD} \geq V_{SG} - |V_{tP}| \rightarrow V_{SD} = V_{SG} - |V_{tP}|$$

$$i_D = \frac{1}{2} k'_p \left(\frac{w}{l}\right) (V_{SG} - |V_{tP}|)^2$$

- MOSFETs w/ Finite Output Resistance:

$$\lambda \sim \frac{1}{L} \quad V_A = \frac{1}{\lambda}$$


$$r_o = \frac{V_A}{I_D} = \frac{1}{2\lambda I_D} \quad * \text{Assume } \lambda=0 \text{ when no } V_A, \lambda, \text{ or } r_o \text{ values are given.}$$

$$I_D = \frac{1}{2} k' n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 (1 + 2V_{DS})$$

Original I_D eq.

- BJT Operation + DC Biasing:

npn:

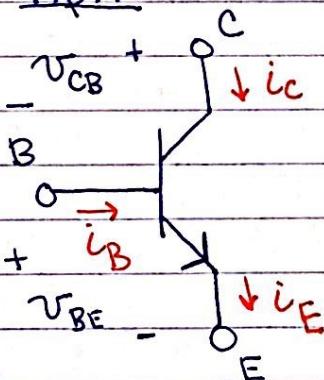

$$i_C = I_s \exp \left(\frac{V_{BE}}{V_T} \right)$$

$$i_B = \frac{i_C}{\beta}$$


$$i_E = i_B + i_C$$

$$i_C = \alpha i_E$$

$$\beta = \frac{\alpha}{\alpha-1} \quad \alpha = \frac{\beta}{\beta+1}$$

→ active: $V_{BE} > 0$ and $V_{CB} > -0.4V$

pnp:

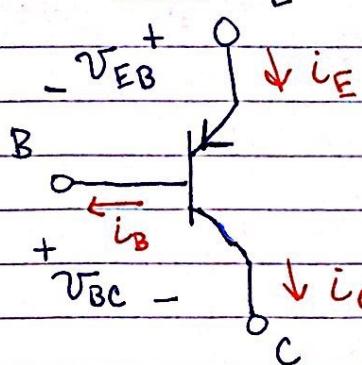

$$i_C = I_s \exp \left(\frac{V_{EB}}{V_T} \right)$$

$$i_E = i_C + i_B \quad i_B = \frac{i_C}{\beta}$$

$$i_C = \alpha i_E \quad * \alpha \text{ and } \beta \text{ are same}$$

active → $V_{EB} > 0$ and $V_{BC} > -0.4$

* See Note on Diode Eq. →

- Forward Bias Eq.: (Came back from diodes)

→ These equations were used in the diode forward bias lectures and the BJT forward bias lecture.

* Know how + when to use them.

General Forms:

$$\frac{I_a}{I_s} = \exp\left(\frac{V_a - V_i}{V_T}\right)$$

$$V_a - V_i = V_T \ln\left(\frac{I_a}{I_s}\right)$$

Example for BJT to find V_{BE2} :


$$V_{BE2} - V_{BE1} = V_T \ln\left(\frac{I_{C2}}{I_{C1}}\right)$$

1

1.

- MOSFETs + Amplifiers ★ I know how we are using prev. MOSFET Eq.

Always true: (Ohm's Law)

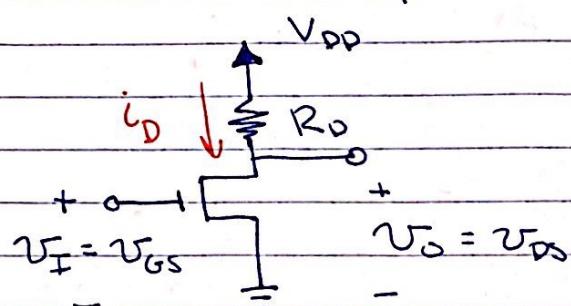

$$i_D = \frac{V_{DD} - V_{DS}}{R_D}$$

combined w/ MOSFET eqs.

- Cutoff: $V_{GS} < V_t$

$$i_D = 0$$

$$V_{DS} = V_{DD}$$

$$0 = \frac{V_{DD} - V_{DS}}{R_D}$$

$$\Rightarrow V_{DS} = V_{DD}$$

- Saturation: $(V_{DS} \geq V_{GS} - V_t)$

$$V_{DS} = V_{DD} - \frac{1}{2} R_D k'_n \left(\frac{w}{l}\right) (V_{GS} - V_t)^2$$

$R_D i_D$

- Triode: $(V_{DS} < V_{GS} - V_t)$

$$V_{DS} = \frac{V_{GS}}{1 + R_D k'_n \left(\frac{w}{l}\right) (V_{GS} - V_t)}$$

max $V_{GS} = V_{DD}$

$$V_{DS} = \frac{V_{DD}}{1 + R_D k'_n \left(\frac{w}{l}\right) (V_{DD} - V_t)}$$

- Edge of Saturation:

$$V_{GS} = V_t + \sqrt{1 + 2(R_D k'_n \left(\frac{w}{l}\right) V_{DD})} - 1$$

$R_D k'_n \left(\frac{w}{l}\right)$

(6)

- MOS Amplifier Voltage Gain + the Q-Point:

$$V_{GS} = V_{GSO} + v_{gs}(t)$$

$$V_{DS} = V_{DOS} + v_{ds}(t)$$

$$i_D = \underbrace{I_{DQ}}_{\substack{\text{DC-bias} \\ \text{point} \\ (\text{Q-point})}} + \underbrace{i_d(t)}_{\substack{\text{Small} \\ \text{Signal}}}$$

DC-bias Small
 point Signal
 (Q-point)

$$v_{ds} = A_v v_{gs}$$

↑ small signal volt. gain

$$A_v = -R_D k'n \left(\frac{w}{l}\right) (V_{GSO} - V_t)$$

* can pick resistors, transistors, and Q-point to get desired gain when designing.

- Small Signal Eq.:

$$i_d = k'n \left(\frac{w}{l}\right) [v_{gs} (V_{GSO} - V_t)]$$

$$g_m = \frac{i_d}{v_{gs}} = k'n \left(\frac{w}{l}\right) (V_{GSO} - V_t)$$

units $\left[\frac{A}{V}\right]$

$$A_v = -g_m R_D$$

Reminder: $r_o = \frac{V_A}{2I_{DQ}} = \frac{V_A}{I_{DQ}}$

* coupling capacitors act as open circuits for DC and as short circuits for AC.

(7)

- MOS Amps: * Combined w/ the Small sig. eqs.

$$R_{in} = \frac{V_i}{i_i}$$

$$V_i = \frac{R_{in}}{R_{in} + R_{sig}} \cdot V_{sig}$$


$$A_{v0} = \frac{V_0}{V_i} \quad |_{R_L \rightarrow \infty}$$

$$A_v = \frac{V_0}{V_i}$$

$$G_v = \frac{V_0}{V_{sig}}$$

- Common Source Amp: ("Source Grounded")

Given

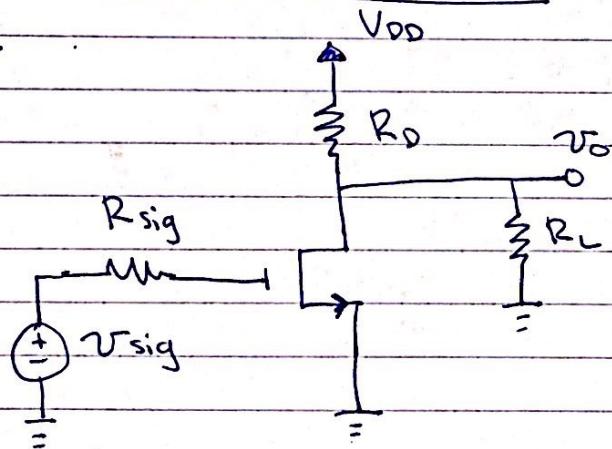


So $V_i = V_{sig}$
 $R_{in} = \infty \quad i_i = 0$

$$R_o = R_D \parallel r_o$$

$$A_{v0} = -g_m (r_o \parallel R_D)$$


$$A_v = -g_m (r_o \parallel R_D \parallel R_L)$$

$$G_v = -g_m (r_o \parallel R_D \parallel R_L)$$

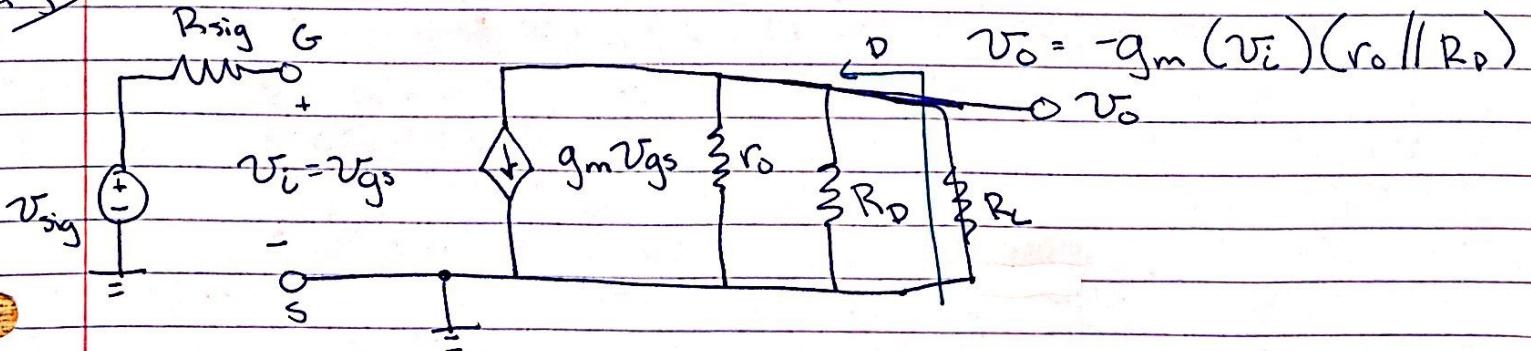Hybrid- π 

(8)

- Common Gate Amp: (gate grounded, v_i is @ source)

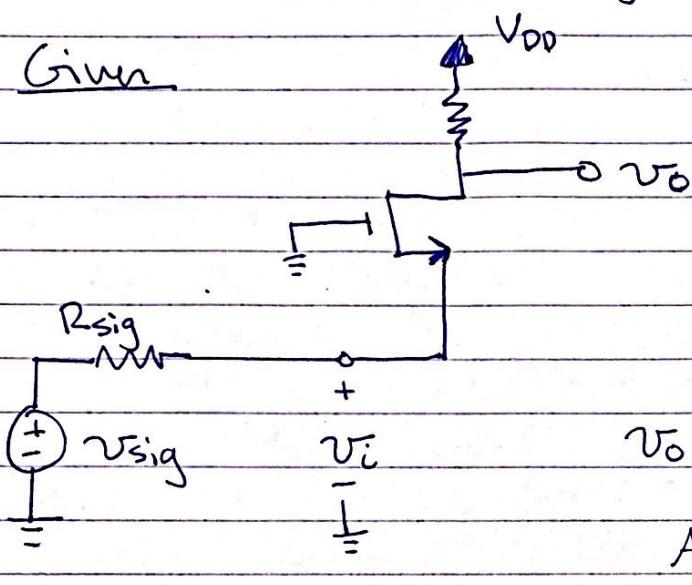Given

$$R_{in} = 1/g_m$$

$$R_o = R_d$$


$$v_{gs} = -v_i$$

$$v_0 = -g_m (R_d) (-v_i) = g_m R_d v_i$$

$$A v_0 = g_m R_d$$

T-model

$$A v = g_m (R_d \parallel R_L)$$

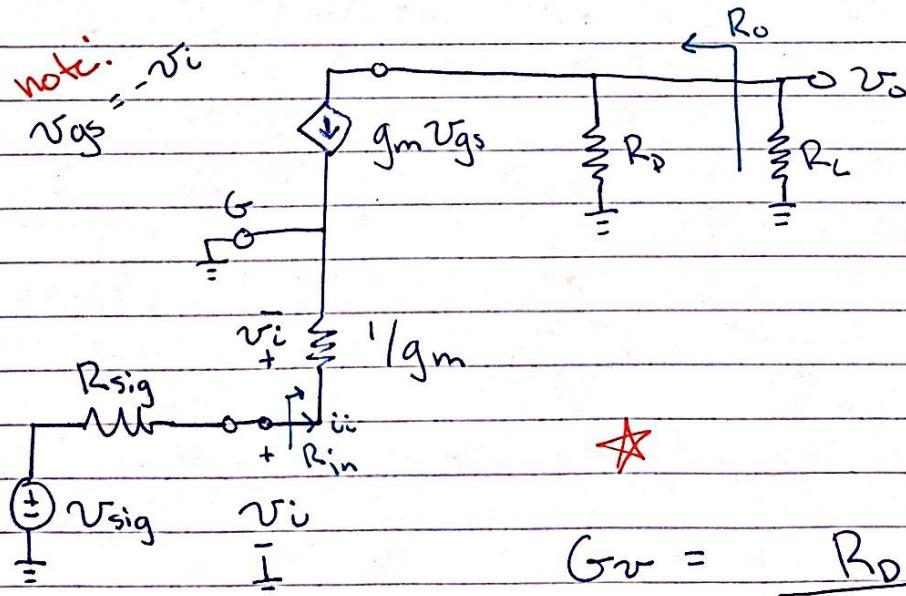

$$G_v = \frac{R_d \parallel R_L}{R_{sig} + 1/g_m}$$


or

$$G_v = \frac{R_d \parallel R_L}{R_{sig} + R_{in}}$$


(9)

Common Drain Amp: (voltage follower, V_i at gate)

Given

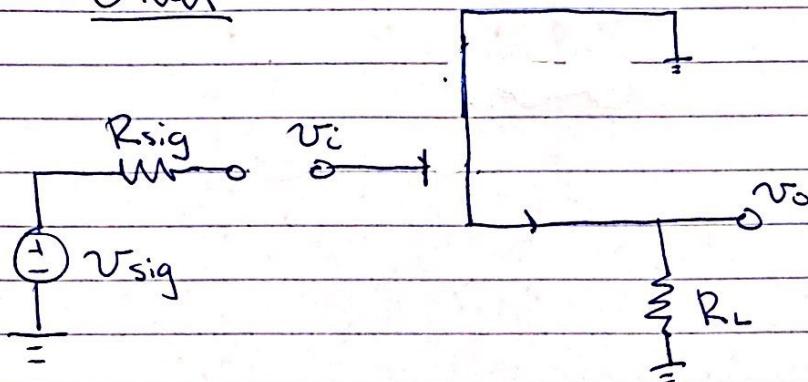

Model

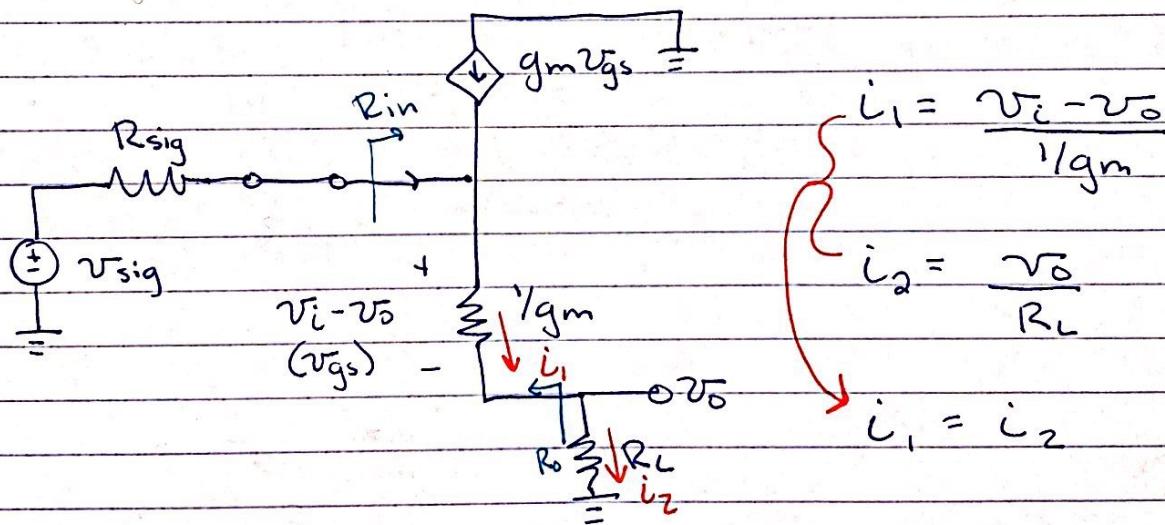

$$R_{in} = \infty$$

$$Av = \frac{V_0}{V_i} = \frac{R_L}{R_L + 1/g_m}$$

$$R_o = 1/g_m$$

$$G_v = \frac{V_0}{V_{sig}} = \frac{R_L}{R_L + 1/g_m}$$

$$Av_o = \left. \frac{V_0}{V_i} \right|_{R_L \rightarrow \infty} = 1$$

if R_L is $\gg 1/g_m$ then $G_v \approx 1$