
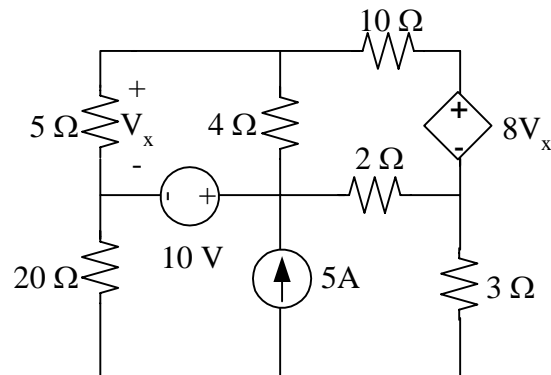


Extra Example of Brute Force Technique:

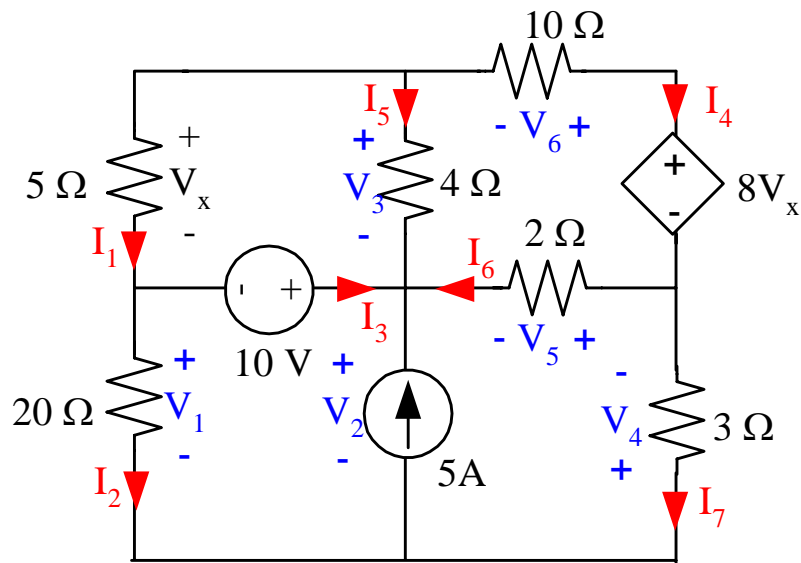
Solve for all the voltages, currents and power associated with each element.



Step 1: Label all the voltages and currents. (Note: I have labeled a few that violate the passive sign convention for resistors).



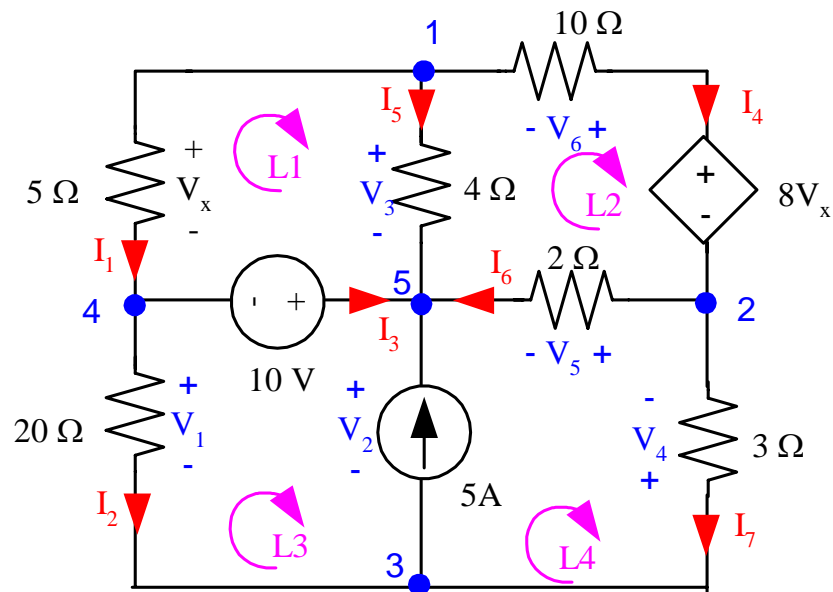Step 2: Identify and denote nodes and loops.



Step 3: Write KCL and KCL equations and Ohm' Law and Step 4: Simplify and Solve.

KCL (4 nodes)

N1:  $I_1 + I_4 + I_5 = 0$

N2:  $I_4 = I_6 + I_7$

N3:  $I_2 + I_7 = 5$

N4:  $I_1 = I_2 + I_3$

KVL (4 loops)

L1:  $V_x - V_3 - 10 = 0$

L2:  $V_3 + V_6 - 8V_x - V_5 = 0$

L3:  $V_1 + 10 - V_2 = 0$

L4:  $V_2 + V_5 + V_4 = 0$

Ohm's Law

$V_x = 5I_1$

$V_1 = 20I_2$

$V_3 = 4I_5$

$V_4 = 3(-I_7)$

$V_5 = 2I_6$

$V_6 = 10(-I_4)$

Simplify Equations and Solve

$I_1 + I_4 + I_5 = 0$

$I_4 - I_6 - I_7 = 0$

$I_2 + I_7 = 5$

$I_1 - I_2 - I_3 = 0$

$V_x - 4I_5 = 10$

$4I_5 - 10I_4 - 8V_x - 2I_6 = 0$

$20I_2 - V_2 = -10$

$V_2 + 2I_6 - 3I_7 = 0$

$5I_1 - V_x = 0$

Into a matrix:

$$\begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & -1 & -1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 1 & -1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -4 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & -10 & 4 & -2 & 0 & 0 & -8 \\ 0 & 20 & 0 & 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 2 & -3 & 1 & 0 \\ 5 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \\ I_7 \\ V_2 \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 5 \\ 0 \\ 10 \\ 0 \\ -10 \\ 0 \\ 0 \end{bmatrix}$$

Step 4: (continued)

Solutions:

$$\begin{aligned}
 I_1 &= -3.68\text{A} \\
 I_2 &= -0.26\text{A} \\
 I_3 &= -3.42\text{A} & V_1 &= 20I_2 = -5.20\text{V} \\
 I_4 &= 10.79\text{A} & V_3 &= 4I_5 = -28.40\text{V} \\
 I_5 &= -7.10\text{A} & V_4 &= 3(-I_7) = -15.78\text{V} \\
 I_6 &= -5.53\text{A} & V_5 &= 2I_6 = -11.06\text{V} \\
 I_7 &= 5.26\text{A} & V_6 &= 10(-I_4) = -107.90\text{V} \\
 V_2 &= 4.74\text{V} \\
 V_x &= -18.42\text{V}
 \end{aligned}$$

Step 5: Check using Power:

Element	Voltage (V)	Current (A)	Power (W)	Del/Abs
5 $\Omega$	-18.42	-3.68	67.79	Abs
4 $\Omega$	-28.4	-7.1	201.64	Abs
10 $\Omega$	-107.9	10.79	1164.24	Abs
2 $\Omega$	-11.06	-5.53	61.16	Abs
20 $\Omega$	-5.2	-0.26	1.352	Abs
3 $\Omega$	-15.78	5.26	83.00	Abs
10 V	10	-3.42	-34.2	Del
		<b>or</b>	<b>34.2</b>	<b>Abs</b>
5A	4.74	5	23.7	Del
8V <sub>x</sub>	-147.36	10.79	-1590.01	Abs
		<b>or</b>	<b>1590.01</b>	<b>Del</b>
sum of power delivered			1613.71	
sum of power absorbed			1613.38	
				Checks!!