

Circuits Cheat Sheet

Natalie Taggart^①

Exam 1

• Amplifiers

• Gain

$$A_v = \frac{v_o}{v_i} \left(\frac{V}{V} \right) \quad A_i = \frac{i_o}{i_i} \left(\frac{A}{A} \right) \quad A_p = \frac{P_o}{P_i} = \frac{v_o i_o}{v_i i_i} \left(\frac{W}{W} \right)$$

in dB

$$A_v \text{ or } A_i = 20 \log |A_{v \text{ or } i}|$$

$$A_p = 10 \log |A_p|$$

• Power Balance:

✓ d.s. in amp.

$$P_{dc} + P_i = P_L + P_{loss}$$

$$\frac{P_L}{P_{dc}} \times 100 = \% \text{ efficiency.}$$

• Standard Amp.

(Amp. Models concept lec)

$$\frac{v_o}{v_i} = A_{vo} \left(\frac{R_L}{R_L + R_o} \right) \left(\frac{R_i}{R_s + R_i} \right)$$

• Ideal Op-Amps

$$v_o = A(v_+ - v_-)$$

① Draws zero input current: $i_- = i_+ = 0 \text{ A}$

② v_o is not a func. of i_o : $R_o = 0$

③ Open loop gain is inf: $v_+ = v_-$

④ Inf. Common Mode Rejection: $v_o = 0$

⑤ Inf. Bandwidth: A is not a func. of freq.

• Non-Ideal Op-Amps (Finite A)

inverting: $\frac{v_o}{v_i} = \frac{-R_2/R_1}{1 + \frac{1}{A} \left(1 + \frac{R_2}{R_1} \right)}$

non-inverting: $\frac{v_o}{v_i} = \frac{(1 + R_2/R_1)}{1 + \frac{1}{A} \left(1 + \frac{R_2}{R_1} \right)}$

This is the one where you make tables

★ Know how to Draw all Op-Amp Configs.

★ Know how to Solve w/ Pots or dividers.

• Inverting Op-Amps

Closed Loop Gain:

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \rightarrow G = -\frac{R_2}{R_1}$$

$$R_i = \frac{v_i}{i_i} = R_1$$

$$R_o = 0$$

$$i_1 = \frac{v_i}{R_1}$$

$$i_2 = \frac{0 - v_o}{R_2}$$

★ Know how to Design an Op-Amp → see ex. lec.

• Weighted Summer

$$v_o = v_{o1} + v_{o2} + v_{o3}$$

$$v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \frac{R_f}{R_3} v_3 \dots$$

$$i_f = \frac{v_{o\max}}{R_f} \quad (?)$$

• Non-Inverting Op-Amps (Rev. V.S.P.)

$$R_i = \frac{v_i}{i_i} = \infty$$

$$R_o = 0$$

$$G = 1 + \frac{R_2}{R_1}$$

• Voltage Follower

$$R_i = \infty$$

$$R_o = 0$$

$$v_o = v_i$$

Difference Amplifier:

$$v_o = v_{o1} + v_{o2}$$

$$v_o = A_{cm} v_{icm} + A_d v_{id}$$

$$v_{o1} = \left(-\frac{R_2}{R_1} \right) v_{i1}$$

$$v_{o2} = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) v_{i2}$$

$$v_{i1} = v_{icm} - \frac{1}{2} v_{id}$$

ICM = common mode

$$v_{i2} = v_{icm} + \frac{1}{2} v_{id}$$

ID = differential

• Common Mode Rejection Ratio:

$$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right| \quad (dB)$$

★ if A_{cm} is zero (ideal) then $CMRR = \infty$.

$$A_{cm} = \frac{-R_2}{R_1} + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right)$$

$$A_d = \frac{1}{2} \left(\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) \right)$$

★ When $A_{cm} = 0$:

$$A_d = \frac{R_2}{R_1}$$

When true
 $A_d = \frac{R_2}{R_1}$
 $R_1 = R_3$

$$R_{id} = 2R_1$$

$$R_2 = R_4$$

★ know how to solve when Rs have a % tolerance.

• Instrumentation Amplifier

$$v_o = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1} \right) v_{ID}$$

w/ R_2 mismatch:

$$\hookrightarrow v_o = \frac{R_4}{R_3} \left(1 + \frac{R_{21} + R_{22}}{R_1} \right) v_{ID}$$

$$v_{ID} = v_{I2} - v_{I1}$$

$$i_1 = \frac{v_{I1} - v_{o1}}{R_2}$$

★ Know how to solve w/ a Pot.

$$i_2 = \frac{v_{I2} - v_{o2}}{R_2}$$

$$i_x = \frac{v_{ID}}{2R_1}$$

• IDEAL DIODES

OFF: Reverse Bias Region: $v < 0$, $i = 0$

↳ looks like an open circuit

ON: Forward Bias Region: $v > 0$, $i > 0$

↳ looks like a short circuit

→ Assume Diode state + solve to check.

★ Know how to read both types of circs.

- Forward Bias Diodes

$$V_T = \frac{kT}{q}$$

$$V_T = 25 \text{ mV (room temp.)}$$

$$k = 8.62 \times 10^{-5} \text{ eV/K}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$i \approx I_s \exp\left(\frac{v}{nV_T}\right)$$

$$\frac{I_2}{I_1} = \exp\left(\frac{V_2 - V_1}{V_T}\right)$$

$$V_2 - V_1 = V_T \ln\left(\frac{I_2}{I_1}\right)$$

- Modeling Diodes:

iterate: $I_D = \frac{V_{DD} - V_D}{R}$

constant drop: use \uparrow w/ $V_D = 0.7$ unless told otherwise

ideal: solve w/ $V_D = 0$.

- Zener Diodes

$$V_Z = V_{Z0} + I_Z r_Z \quad \text{or} \quad V_{Z0} = V_Z - I_Z r_Z$$

$$\Delta V_O = \frac{r_Z}{R + r_Z} (\Delta V_S)$$