

Quiz #2

Due Feb 22 at 9:51am

Points 100

Questions 4

Available Feb 22 at 9:40am - Feb 22 at 9:55am 15 minutes

Time Limit 12 Minutes

Instructions

The Quiz contains 4 questions worth 30/20/20/30 points.

This quiz was locked Feb 22 at 9:55am.

Attempt History

	Attempt	Time	Score
LATEST	Attempt 1	11 minutes	70 out of 100

Score for this quiz: **70** out of 100
Submitted Feb 22 at 9:50am
This attempt took 11 minutes.

Question 1

30 / 30 pts

For the function

$$y(t) = 2 \cdot e^{-t}$$

what is the value of the function

$$y(0.8 - \tau)$$

at time 0.2s ?

You Answered

1.1


Correct Answers

1.0976 (with margin: 0.001)

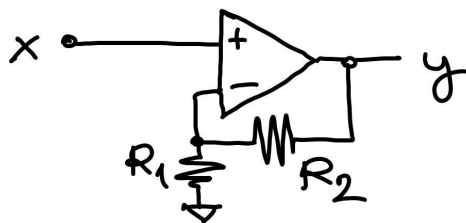Question 2

20 / 20 pts

what is the ratio of y/x for the following circuit, assuming $R_1=30K$ and $R_2=6K$.



Correct!

1.2


Correct Answers

1.2 (with margin: 0)

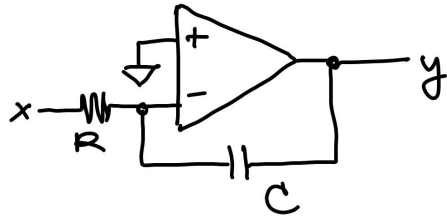Question 3

20 / 20 pts

What is the voltage y in Volts at time $t=0.5$ s if input x is connected to +3V at time $t=0$?
Assume $R=1M\Omega$ and $C=1\mu F$



Correct!

-1.5

Correct Answers

1.5 (with margin: 0)

-1.5 (with margin: 0)

Question 4

0 / 30 pts

What is Laplace transform of the function

$$u(t) - u(t - 2)$$

enter the formula with no spaces. Please use parentheses as necessary and the following symbols

^ for exponentiation,

* for multiplication

You Answered

2*u

Correct Answers

 $(1 - e^{-2s})/s$ $(1/s) * (1 - e^{-2s})$ $1/s - e^{-2s}/s$

