



# EE 315 Module 2A Practice Problem Solutions

(1)

$$R_i = 80 \text{ k}\Omega$$

$$G = \frac{200}{80} = 2.5 \text{ V/V}$$


$$R_i = 15 \text{ k}\Omega$$

$$G = \frac{30}{15} = 2 \text{ V/V}$$

$$R_i = 40 \text{ k}\Omega$$

$$G = \frac{90}{40} = 2.25 \text{ V/V}$$

(2)

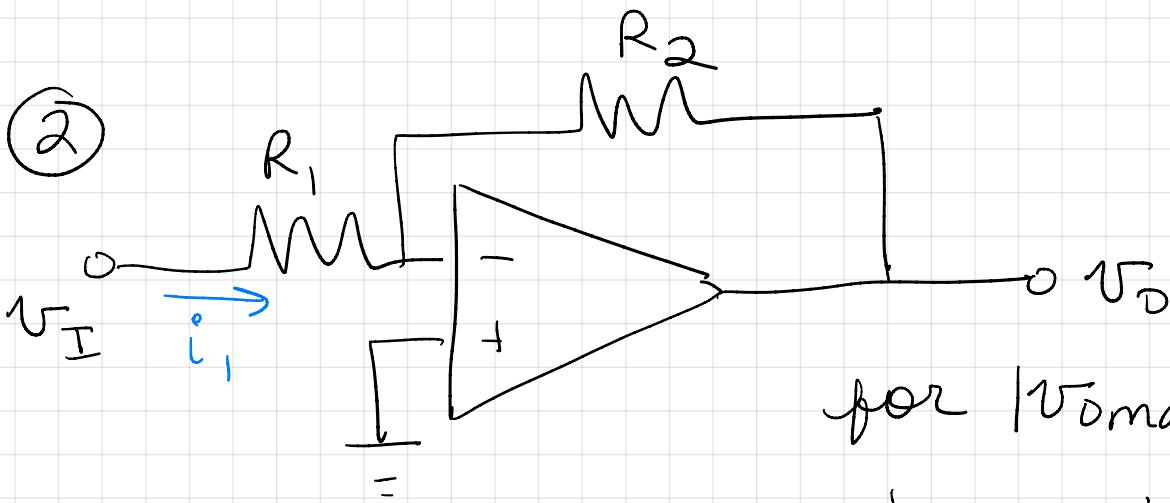

$$\text{for } |V_{o\max}| = 10 \text{ V}$$

$$|V_{i\max}| = \frac{10}{5} = 2 \text{ V}$$

$$i_{\max} = 50 \times 10^{-6} \text{ A}$$

$$i_{\max} = \frac{V_I}{R_1} = \frac{2}{R_1} = 50 \times 10^{-6}$$

$$G = -5 \frac{\text{V}}{\text{V}}$$

$R_1 = 40 \text{ k}\Omega$



$$-5 = -\frac{R_2}{R_1}$$

$$R_2 = 5R_1$$

$$R_2 = 200 \text{ k}\Omega$$

check  $R_2$  current

$$\left| \frac{0 - V_{max}}{200 \times 10^3} \right| \leq 50 \mu\text{A}$$

$$\left| \frac{-10}{200 \times 10^3} \right| = 50 \mu\text{A}$$

okay!

③ for standard inverting configuration

$$G = -\frac{R_2}{R_1}$$

$$\text{max } R = 100 \text{ k}\Omega$$

$$R_i = R_1$$

$$G = -1000 \text{ V/V}$$


$$R_i = 10 \text{ k}\Omega$$

$$1000 = \frac{R_2}{R_1} 100 \text{ k}\Omega$$

$$R_1$$

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega$$

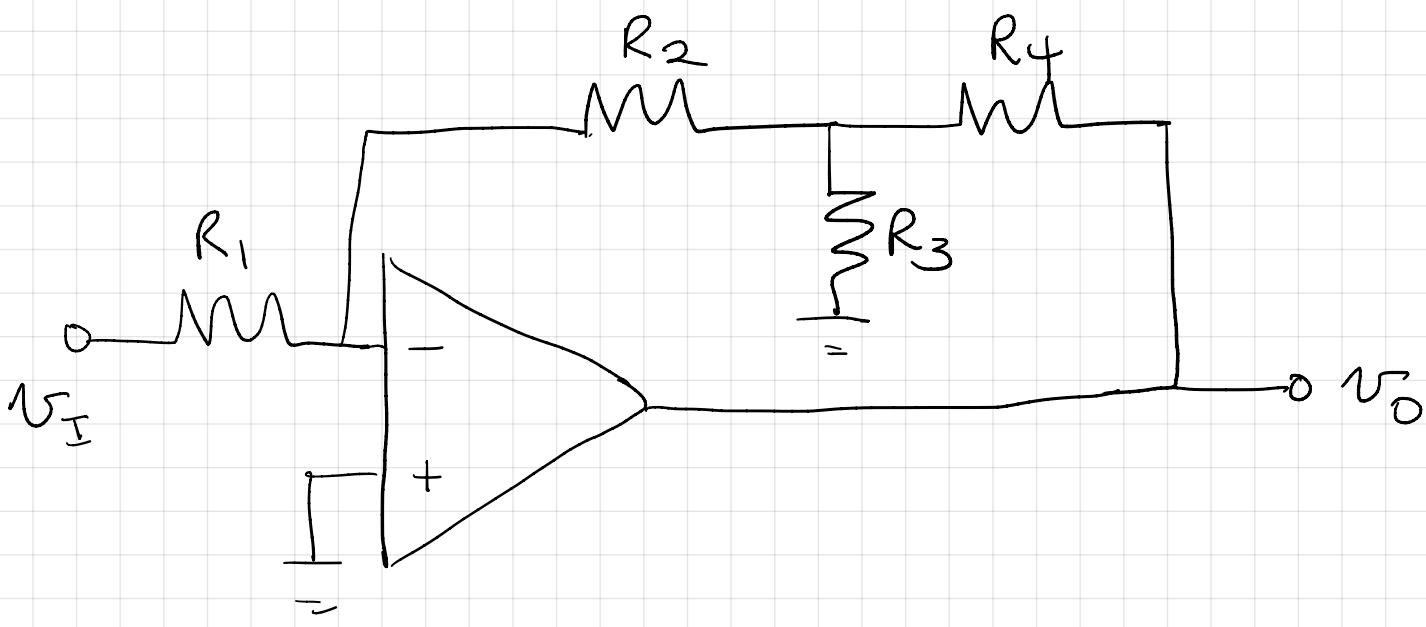

$$\frac{V_O}{V_I} = -\frac{R_2}{R_1} \left( \frac{R_4}{R_2} + \frac{R_4}{R_3} + 1 \right)$$

let  $R_1 = R_2 = R_4 = 100 \text{ k}\Omega$

$$\frac{V_O}{V_I} = -\frac{100}{100} \left( \frac{100}{100} + \frac{100 \times 10^3}{R_3} + 1 \right) = -1000$$

$$2 + \frac{100 \times 10^3}{R_3} = 1000$$


$R_3 = 100 \text{ k}\Omega$

$$\frac{100 \times 10^3}{R_3} = 998$$

$R_3 = 100.20 \Omega$

④

$$v_o = -2v_1 - 8v_2$$

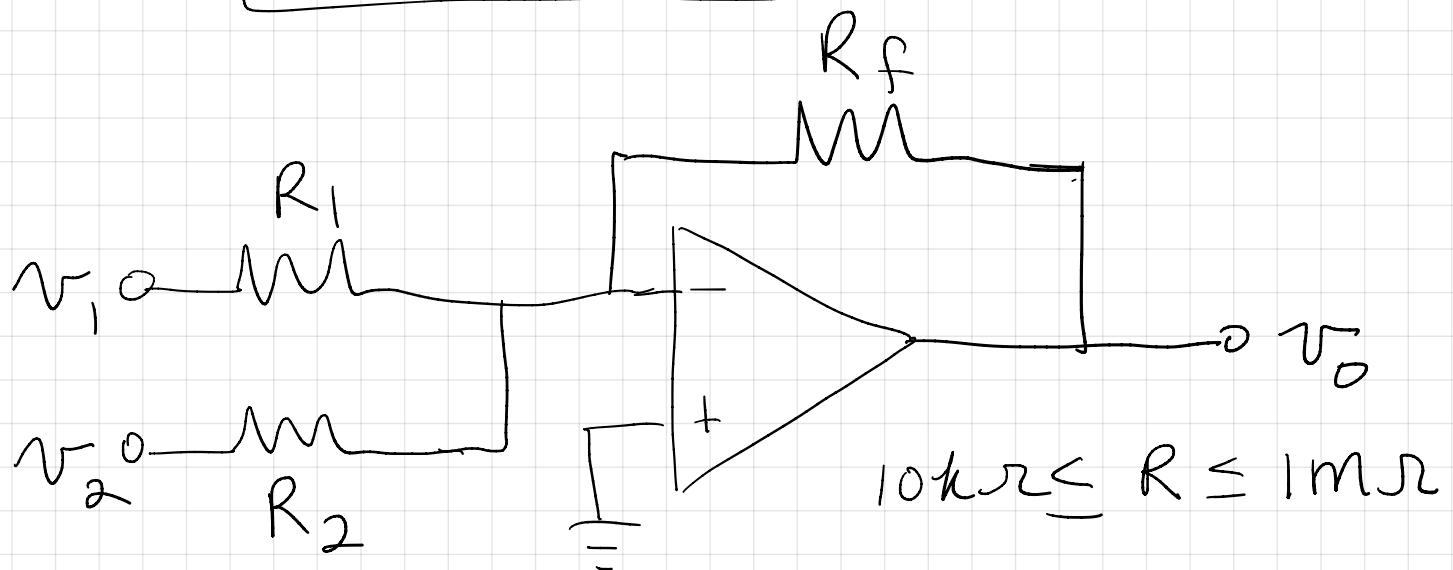

$$v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2$$

$$\frac{R_f}{R_1} = 2$$

$$\frac{R_f}{R_2} = 8$$

let

$$R_f = 400k\Omega$$


$$R_1 = \frac{R_f}{2} = 200k\Omega$$

$$R_2 = \frac{R_f}{8} = 50k\Omega$$

4

b.

$$V_0 = -12V_1 - 3V_2 + 2V_3$$

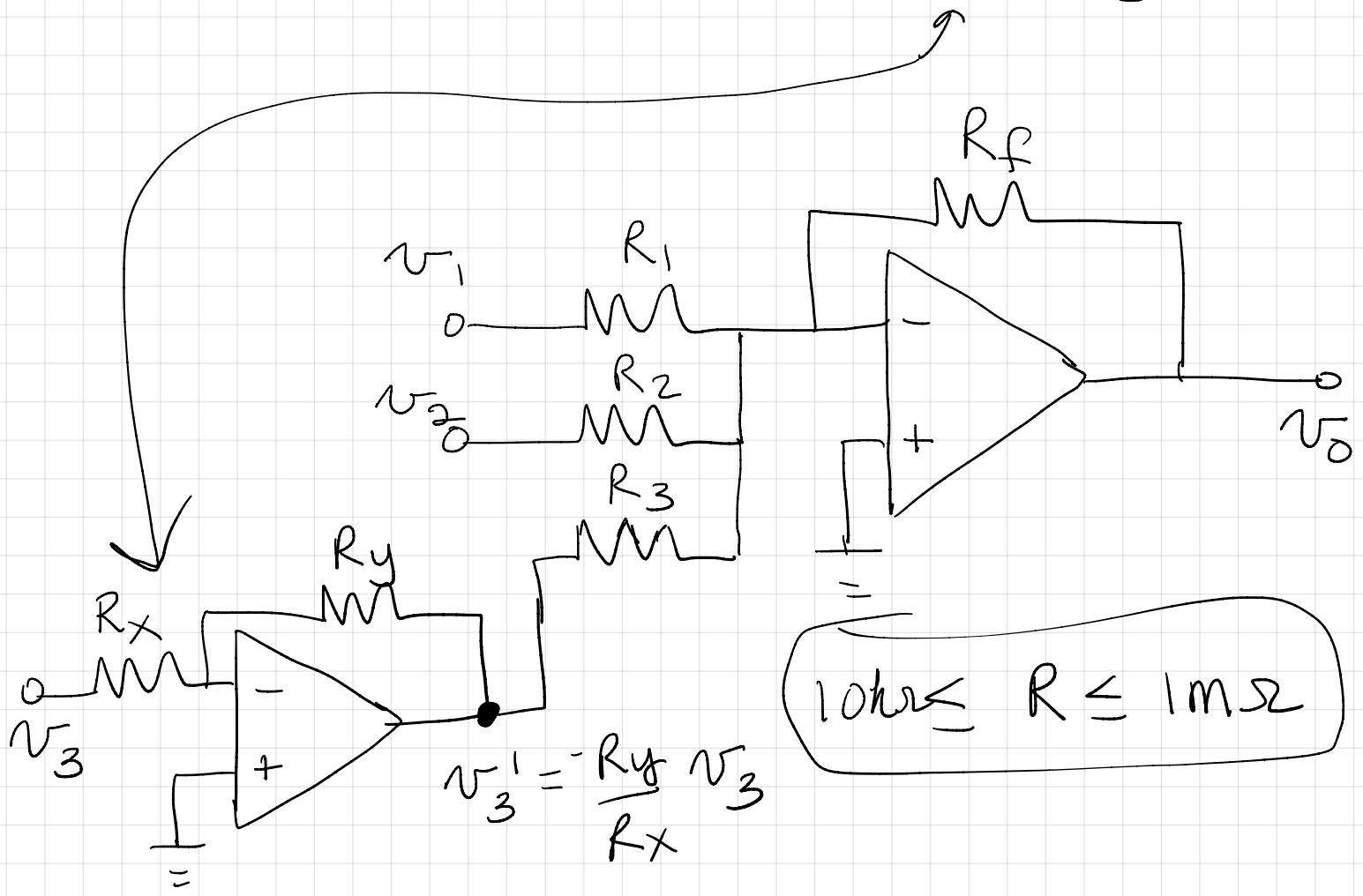

$$V_0 = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3^-$$

$$V_0 = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} \cdot \frac{R_Y}{R_X} V_3$$

$$\frac{R_f}{R_1} = 12$$

$$\frac{R_f}{R_2} = 3$$

$$\frac{R_Y}{R_X} \frac{R_f}{R_3} = 2$$

$$\text{let } R_f = 600 \text{ k}\Omega$$

$$R_y = 10 \text{ k}\Omega$$

$$R_x = 10 \text{ k}\Omega$$

$$R_3 = \frac{R_y \cdot R_f}{R_x / 2}$$

$$R_3 = 300 \text{ k}\Omega$$


$$R_1 = \frac{R_f}{12}$$

$$R_2 = \frac{R_f}{3}$$

$$R_1 = 50 \text{ k}\Omega$$


$$R_2 = 200 \text{ k}\Omega$$

⑤

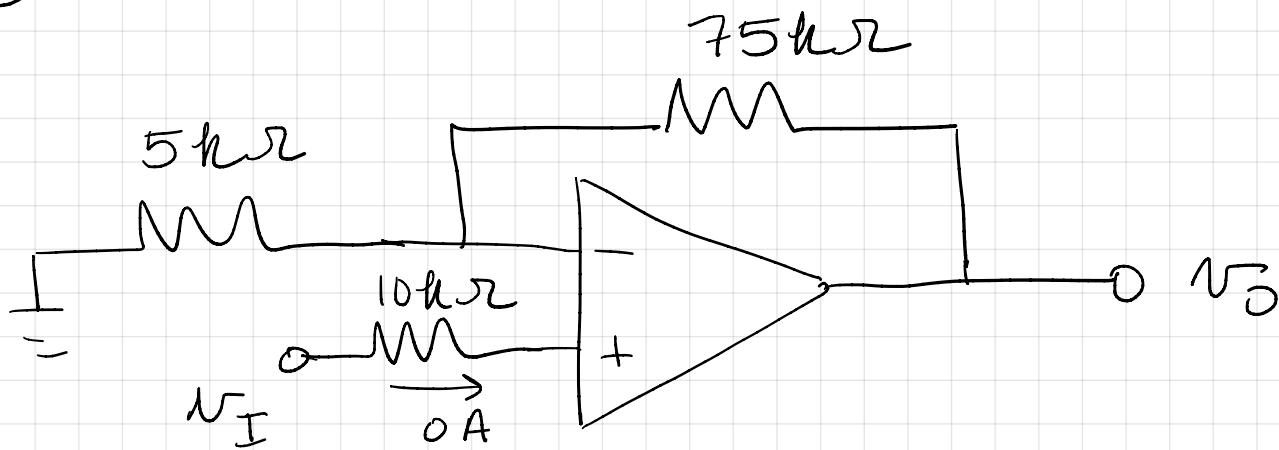

$$R_i = \infty$$

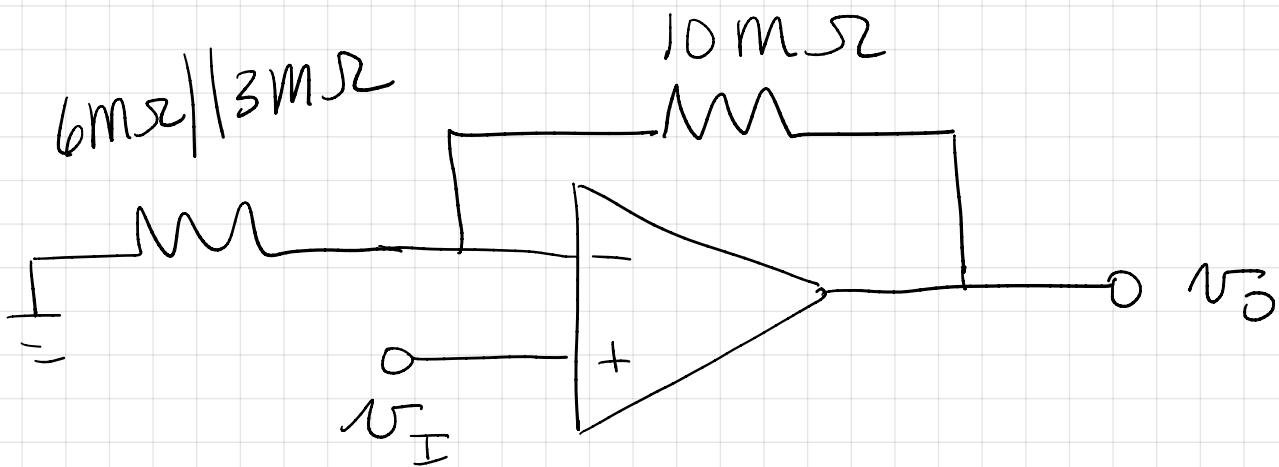
$$G = 1 + \frac{75}{5} = 16 \text{ V/V}$$



$$R_i = \infty \quad G = 1 + \frac{10}{2} = \frac{6\text{ V}}{\text{V}}$$

⑥ (to control gain)
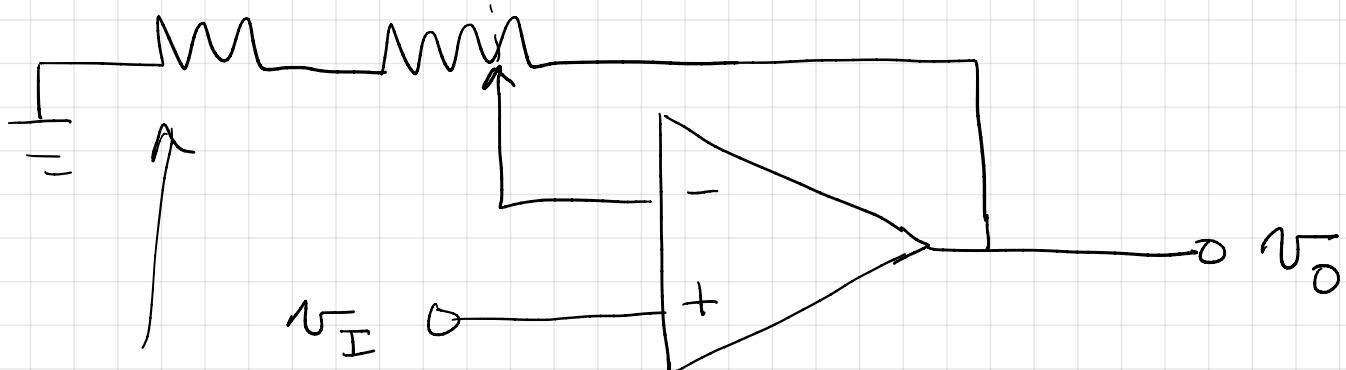
$$R_A = 10x \text{ k}\Omega, 10(1-x)\text{k}\Omega$$



add a fixed

resistor that prevents the gain from  
going to infinity

when  $x=0$  (max gain)       $x=1$  (min gain)

$$R_1 = R_A$$

$$R_2 = 0$$

$$R_2 = 10\text{k}\Omega$$

$$R_1 = R_A + 10\text{k}\Omega$$

$$G = 11 \text{ V/V}$$

$$G = 1$$

$$G = 1 + \frac{R_2}{R_1} = 11$$

$$\frac{R_2}{R_1} = 10$$

$$\frac{10k\Omega}{R_A} = 10$$

$$R_A = 1k\Omega$$

7.

inverting amp

$$\begin{aligned} R_2 &= 100k\Omega \\ R_1 &= 5k\Omega \end{aligned} \quad \left. \begin{array}{l} \text{choose these} \\ \text{at random} \end{array} \right\}$$

ideal :  $G = -\frac{R_2}{R_1} = -20V/V$

finite :  $G = \frac{-R_2 / R_1}{1 + \frac{1}{A} \left( 1 + \frac{R_2}{R_1} \right)}$

A (V/V)

100	- 16.53
1,000	- 19.59
10,000	- 19.96
100,000	- 19.996
1,000,000	- 19.9996

G (V/V)



looking at this range

A changes by a factor of 1000

G changes by a factor of 1.02


pretty stable ya!

Cont non-inverting

ideal  $R_2 = 100k\Omega$  } again  
 $R_1 = 5k\Omega$  } chose random

$$\frac{V_O}{V_I} = 1 + \frac{R_2}{R_1} = 21 \text{ V/V}$$
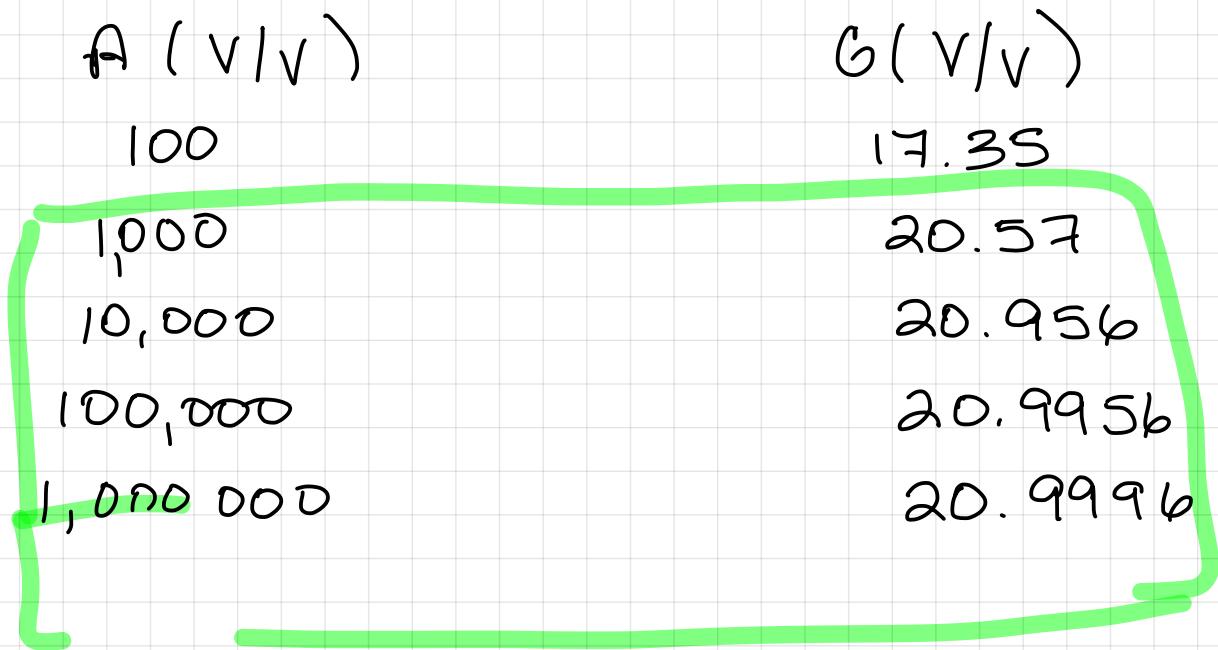
$$\text{ideal } G = \frac{1 + R_2/R_1}{1 + \frac{1 + R_2/R_1}{A}}$$



a

Looking at this range  
A changes by a factor of 1000

G changes by a factor of 1.02

pretty stable ya!

