
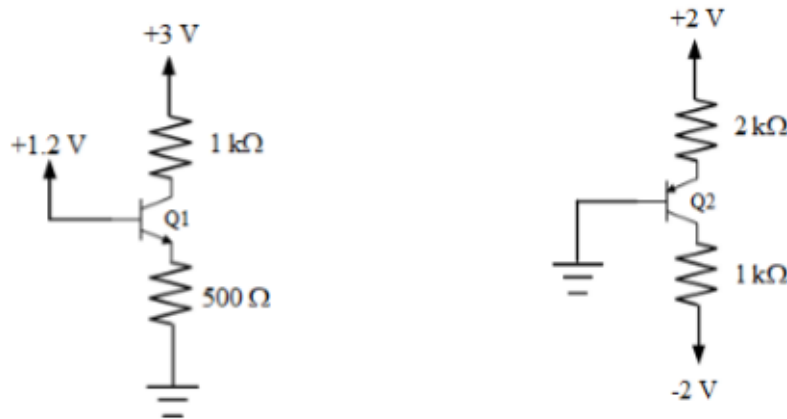


Practice Problems Module 5

1. For an npn BJT, the voltage $v_{BE}=0.74\text{ V}$ for $i_C=9.5\text{mA}$. What i_C for $v_{BE}=0.714\text{ V}$?
2. For a given BJT, $i_B=0.010\text{mA}$ and $i_C=0.6\text{mA}$. What are I_S , β , α , and i_E ?
3. A BJT has $I_S=5\times 10^{-15}\text{ A}$ and β fall in the range of 50 to 500. If the BJT operates in the active mode with $v_{BE} = 0.64\text{V}$, find the expected range of the collector, base, and emitter currents.
4. For Q_1 and Q_2 below, find the collector, base, and emitter currents for $\beta=50$ and $|V_{BE}|=0.8\text{V}$. What is the mode of operation for each circuit?

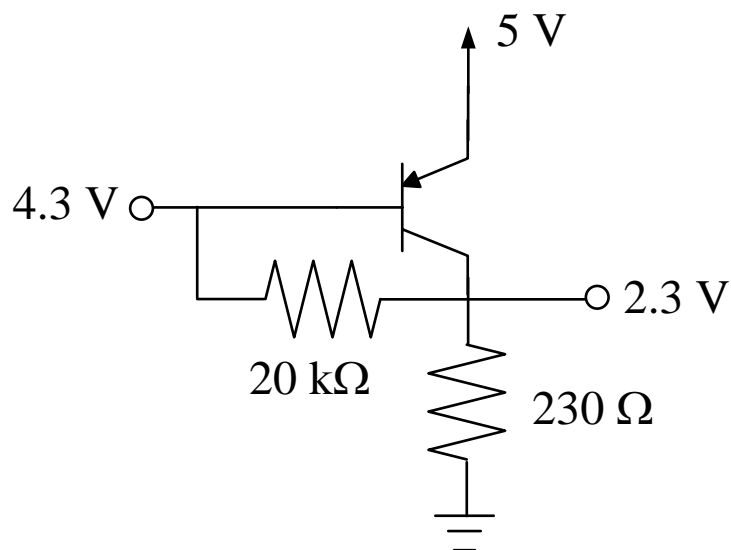

5. For the pnp transistor circuit below, find I_C and β .



6. For the following transistor, find the collector, base, and emitter currents and the collector and emitter voltages for the case where $\beta=100$ and β being very large. Assume $V_{BE}=0.7$ V. Do this for each of the following base voltages: $V_B=0$ V, $V_B=1$ V, and $V_B=2$ V.

