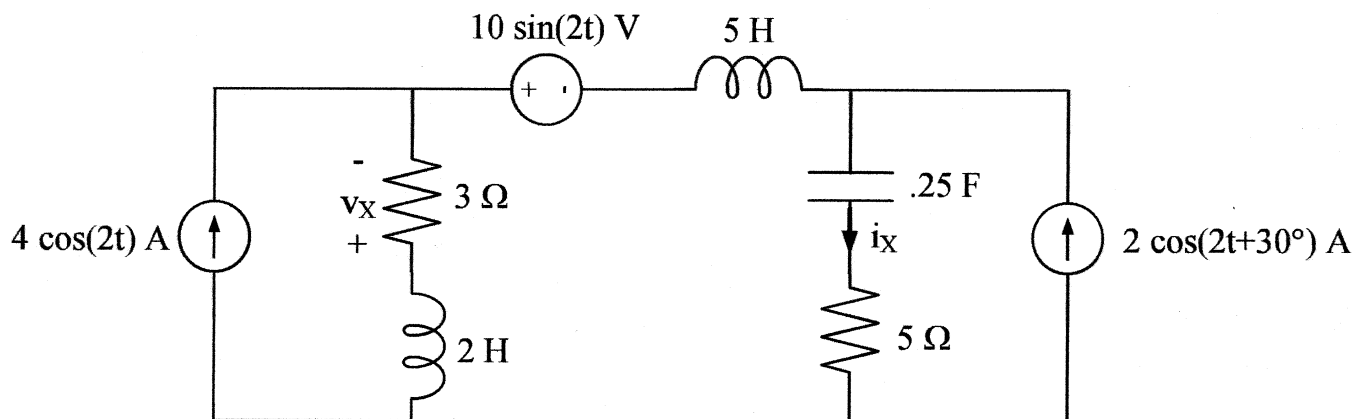


Quiz 4 - 20 points

- Convert the circuit from the time domain to the frequency domain.
- Using either nodal or mesh analysis, solve for the phasor current, I_x , and the phasor voltage V_x .
- What is the time domain current, $i_x(t)$ and the time domain voltage, $v_x(t)$? (Note: only the real parts of the time domain current/voltage are required.)
- Find the average power, P , delivered by each source and absorbed by each impedance.

Legible and logical work please!!

a) sources

- $4 \cos(2t) \text{ A} \rightarrow 4 \angle 0^\circ \text{ A}$
- $10 \sin(2t) \text{ V} \rightarrow 10 \angle -90^\circ \text{ V}$
- $2 \cos(2t+30^\circ) \text{ A} \rightarrow 2 \angle 30^\circ \text{ A}$


impedances

- $3 \Omega \rightarrow 3 \Omega$
- $5 \Omega \rightarrow 5 \Omega$
- $2 \text{ H} \rightarrow j\omega L = j2 \cdot 2 = j4 \Omega$
- $10 \angle -90^\circ \text{ V} \rightarrow j10 \Omega$

$\omega = 2 \text{ rad/s}$

$$5 \text{ H} = j \cdot 5 \cdot 2 = j10 \Omega$$

$$.25 \text{ F} = j / 2 \cdot .25$$

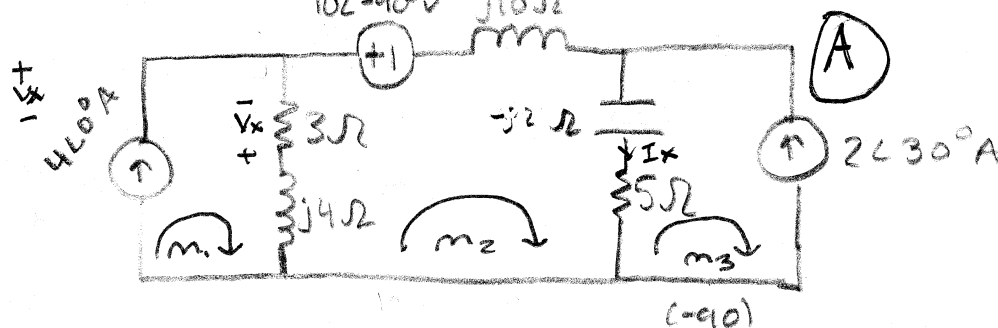

Known

$I_1 = 4 \angle 0^\circ \text{ A}$

$I_3 = 2 \angle 30^\circ \text{ A}$

$V_x = 3(I_2 - I_1)$

$V_x = 3(I_2 - 4)$

$$-j4(I_1 - I_2) - 3(I_2 - I_1) - 10 \angle -90^\circ - j10(I_2) + (j \frac{1}{2})(I_2 - I_3) - 5(I_2 - I_3) = 0$$


$$-j4(I_2 - 4) - 3(I_2 - 4) + 10j - j10(I_2) + 0.5j(I_2 + (\sqrt{3} + j)) - 5(I_2 + (\sqrt{3} + j)) = 0$$

$$-j4I_2 - 3I_2 - j10I_2 - 0.5I_2 - 5I_2 + 16j + 12 + 10j - 0.5 + 0.866j - 5\sqrt{3} - 5j = 0$$

$$I_2(-8 - 13.5j) + 16j + 12 + 10j - 0.5 + 0.866j - 5\sqrt{3} - 5j = 0$$

$$I_2(-8 - 13.5j) + 2.84 + 21.866j = 0 \Rightarrow I_2 = 1.29 + 0.55j$$

B

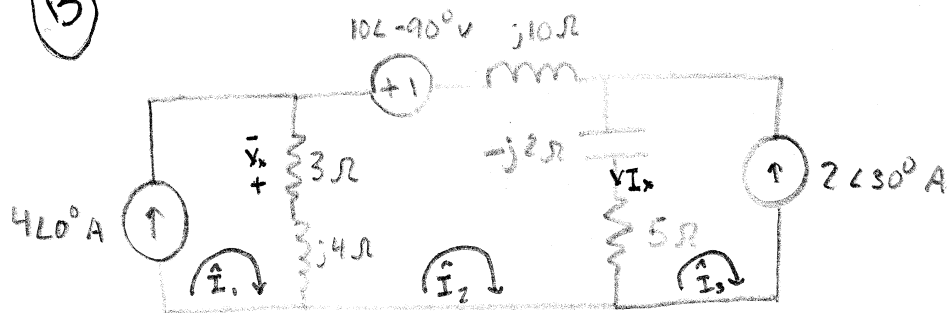

Know:

$$I_x = I_2 - I_3$$

$$V_x = 3(I_2 - I_3)$$

$$I_1 = 4\angle 0^\circ$$

$$I_3 = -2\angle 30^\circ = 2\angle -150^\circ$$

$$KVL: -(3+j4)(I_2 - I_1) - 10\angle -90^\circ - (5-j2)(I_2 - I_3) - j10I_2 = 0$$

$$-3I_2 - j4I_2 - 5I_2 + j2I_2 \overset{-j10I_2}{=} 10\angle -90^\circ + (3+j4)(-I_1) + (5-j2)(-I_3)$$

$$I_2(-8-j12) = -10j + (3+j4)(-4) + (5-j2)(\sqrt{3}+ji)$$

$$I_2(-8-j12) = -10j + (3+j4)(-4) + (5-j2)(\sqrt{3}+ji)$$

$$I_2(-8-j12) = -1.33 - 24.46j$$

$$I_2 = 1.46 + 0.86j$$

$$I_2 = 1.69 \angle 30.55^\circ$$

$$I_x = (1.69 \angle 30.55^\circ) - (2 \angle -150^\circ) = 3.69 \angle 30.255^\circ$$

$$V_x = 3((1.69 \angle 30.55^\circ) - (2 \angle -150^\circ)) = 11.09 \angle 30.255^\circ$$

~~$$I_x = (2.47 \angle -5.76^\circ) - (2 \angle -150^\circ) = 4.26 \angle 10.18^\circ$$~~

~~$$V_x = 3((2.47 \angle -5.76^\circ) - (4 \angle 0^\circ)) = 4.69 \angle -170.87^\circ$$~~

C

$$i_x(t) = 3.69 \cos(2t + 30.255^\circ) A$$

$$v_x(t) = 11.09 \cos(2t + 30.255^\circ) V$$

①

0.3234 - 163.015

• Sources

• $4\angle 0^\circ \text{ A}$: $P = (V_{rms})(I_{rms})\cos(0 - 0^\circ)$

$P = (4)(4)\cos(0)$

$P = 16 \text{ w del}$

• $10\angle -90^\circ$: $P = (V_{rms})(I_{rms})\cos(-90 - 30.55)$

$P = (10)(1.64)\cos(-90 - 30.55)$

$P = -8.6 \text{ w abs, } 8.6 \text{ w del}$

• $2\angle 30^\circ \text{ A}$: $P = (V_{rms})(I_{rms})\cos(30 + 150)$

$P = (2)(2)\cos(30 + 150)$

$P = -4 \text{ w abs, } 4 \text{ w del}$

28.6 w del

• Impedances

• 3Ω : $P = 3(I_1 - I_2)^2$

$3(14 - 1.64)^2 = 16.0083 \text{ w abs}$

• $j4\Omega$: $P = 0$

• $-j2\Omega$: $P = 0$

• $j10\Omega$: $P = 0$

• 5Ω : $P = 5(I_3 - I_2)^2$

$= 5(2 - 1.64)^2 = 0.4805 \text{ w abs}$

16.4805 w abs

$-(3 + j4)(I_2 - I_1) - 10\angle -90^\circ - j10 - (5 - j2)(I_2 - I_3)$

$-(3 + j4)(I_2 - I_1) - (5 - j2)(I_2 - I_3) - j10I_2 = 10\angle -90^\circ$

$(-3 - j4)(I_2 - I_1) + (-5 + j2)(I_2 - I_3) - j10I_2 = 10\angle -90^\circ$

$-3I_2 - 4jI_2 - 5I_2 + j2I_2 - j10I_2 + (-3 - j4)(-I_1) + (-5 + j2)(-I_3) = 10\angle -90^\circ$

$I_2(-8 - j12) = 10\angle -90^\circ - (-3 - j4)(-I_1) - (-5 + j2)(-I_3)$

$I_2(-8 - j12) = 10\angle -90^\circ + (3 + j4)(I_1) + (5 - j2)(I_3)$

$I_2(-8 - j12) = -10j + (3 + j4)(4) + (5 - j2)(-\sqrt{3} - j)$