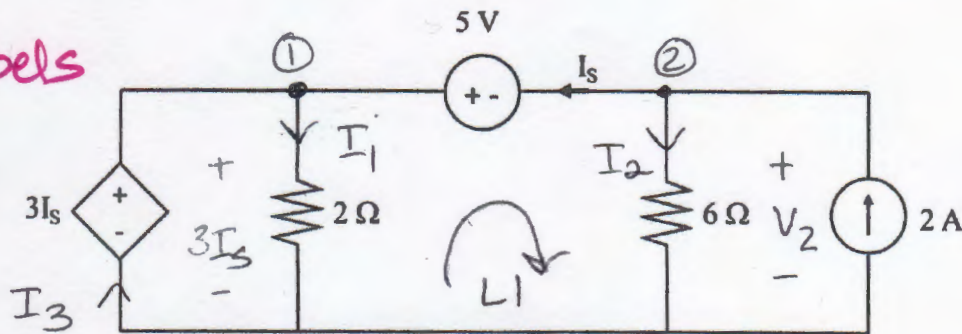


Key / Solution

1. Consider the following circuit. Using Brute Force, solve for all the voltages and currents in the circuit and then find the power delivered by each source and absorbed by each resistor.

Circuit labels
+2pts



KCL

$$I_s + I_3 = I_1 \quad +2pts$$

$$2 = I_2 + I_s \quad +2pts$$

KVL

$$3I_s - 5 - V_2 = 0 \quad +2pts$$

Ohm's Law

$$3I_s = 2I_1$$

$$V_2 = 6I_2$$

+2pts

+2pts

+1pt each

$$2I_1 - 5 - 6I_2 = 0$$

$$2I_1 - 6I_2 = 5$$

$$2 = I_2 + 0.667I_1$$

$$0.667I_1 + I_2 = 2$$

$$I_1 = 2.833A$$

$$I_2 = 0.11A$$

$$I_s = 1.889A$$

$$V_2 = 0.667V$$

$$I_3 = 0.944A$$

+3pts
math

$$\sum P_{del} = 16.13W$$

$$\sum P_{abs} = 16.13W$$



P: $3I_sA$	P: $2A$	P: $5V$	P: 2Ω	P: 6Ω
5.35W D	1.33W D	9.44W D	16.04 W, A	0.074 W, Abs

$$P = 3I_s \cdot I_3$$

$$P = 2V_2$$

$$P = 5I_s$$

$$P = I_1^2 \cdot 2$$

$$P = I_2^2 \cdot 6$$