
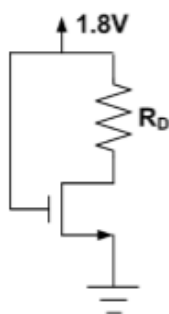


## EE 315 Module 4 Practice Problems

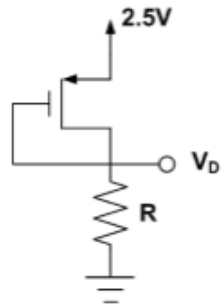1. An NMOS transistor is characterized as follows:  $V_{DS}=0.1V$ ,  $V_t=1.5V$ ,  $k'_n= 25 \mu A/V^2$ , and  $W/L = 10$ . Find the drain current for  $V_{GS}=0V$ ,  $1V$ ,  $2V$ , and  $3V$ .
2. An NMOS transistor is characterized as follows:  $V_{DS}=3.3V$ ,  $V_t=1.V$ ,  $k'_n= 37.5 \mu A/V^2$ , and  $W/L = 10$ . Find the drain current for  $V_{GS}=0V$ ,  $1V$ ,  $2V$ , and  $3V$ .
3. Identify the region of operation and the drain current for an NMOS transistor where the  $k'_n= 25 \mu A/V^2$ ,  $V_t=1V$  and  $W/L = 10$ .
  - a.  $V_{GS}=5V$  and  $V_{DS}=6V$
  - b.  $V_{GS}=0V$  and  $V_{DS}=6V$
  - c.  $V_{GS}=2V$  and  $V_{DS}=-0.5V$
4. An NMOS transistor has  $V_t=0.8V$ ,  $k'_n= 0.05 \text{ mA}/V^2$ , and  $W/L = 2$ . The device is biased at  $V_{GS}=2.5 V$ . Calculate the drain current and the resistance  $r_O$  for  $V_{DS}=2V$  and  $10V$  for
  - a.  $\lambda=0$
  - b.  $\lambda=0.02$
  - c.  $V_A=35V$
5. A PMOS transistor has  $k'_p= 0.1 \text{ mA}/V^2$ ,  $W/L = 2$ ,  $V_t= -2V$  and  $V_{SG}= 3V$ . Find the region of operation and the drain current for:
  - a.  $V_{SD}=0.5V$
  - b.  $V_{SD}=2V$
  - c.  $V_{SD}=5V$
6. Consider the following NMOS circuit where  $V_t=0.5V$ ,  $k'_n= 0.4 \text{ mA}/V^2$ , and  $W/L = 5$ . If the circuit operates at the edge of saturation with a drain current of  $1mA$ , find the resistor,  $R_D$ .



7. Consider the following PMOS circuit where  $V_t=-0.6V$ ,  $k'_p= 250 \mu A/V^2$ , and  $L = 0.25\mu m$ . find the values required for  $W$  and  $R$  such that the drain current is  $0.8mA$  and the drain voltage is  $1.5V$ .



8. Find the labeled voltages and currents in the following circuit where  $V_{tn} = +1V$ ,  $V_{tp} = -1V$ ,  $k'_n = 20 \mu A/V^2$ ,  $k'_p = 8 \mu A/V^2$  and  $W/L = 3$  (for both n and p-type transistors).

