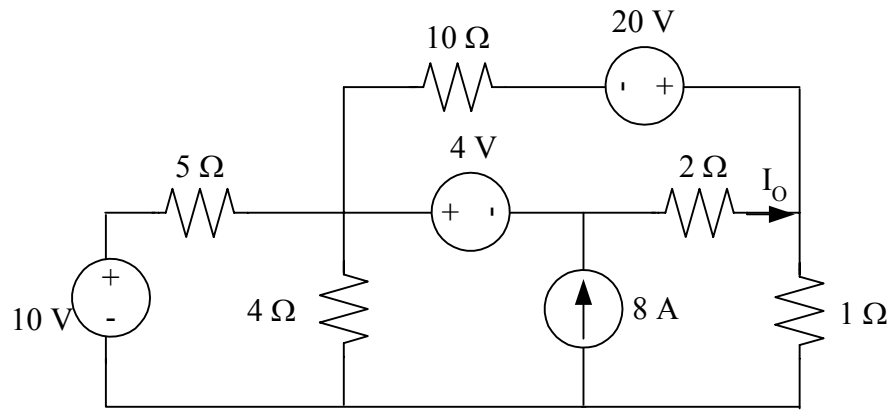


Nodal Analysis Examples:

1. Use nodal analysis to solve for the current  $I_O$  and the power delivered by the 4V source.



2. Use nodal analysis to find  $I_O$  and the power delivered by the 2A source.

