

→ perfectly match resistors

$R_1 - R_4$  have 1% tolerance

\* message expression to  
look at the tolerances.

$$200k\Omega \pm 1\% (200k\Omega)$$

$$200k\Omega (1 \pm 0.01)$$

$$2k\Omega (1 \pm 0.01)$$

↗ 1%

Now...

want to know worst case ACM

Numerator large

Denominator small

as opposed to  $\infty$

$N_{I_1}$



$N_{I_2}$

$N_0$

$N_{I_1}$

$N_o$

$N_{I_2}$

Design instrumentation amplifier

$$A_d = 2 \text{ V/V to } 1000 \text{ V/V}$$

