

Cover Page

CPE 324-02: Intro to Embedded Computer System

Lab 6

FIFO Memory

Submitted by: Nolan Anderson

Date of Experiment: 04/09/2021

Report Deadline: 04/13/2021

1. Introduction:

1.1 - What is to be studied, what is the purpose, and how is this purpose accomplished?


The purpose of Lab 6 is to expand our knowledge of FIFO memory by using newly developed code and code from previous labs. To do this, we first need to study FIFO memory, Fibonacci sequence, and a simple up counter (see section 2). We will accomplish this by writing code in varying difficulty, with phase 2 being the most in depth. We will also display the output of all the code (section 4) and go over phase 3 with a short demonstration video. Section 6 will contain all the new code developed in the lab.

2. Experiment Description

2.1 Theory, analysis, and purpose:

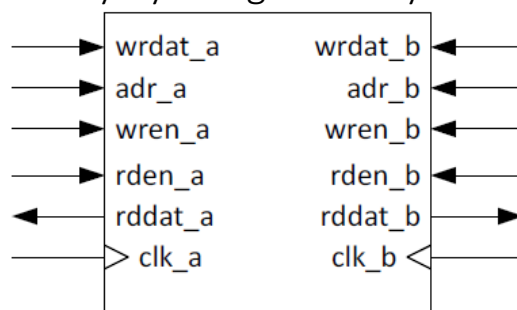
2.1.1 FIFO Memory

FIFO (first in first out) memory chips are good for applications where the devices operate at different speeds. You can temporarily store values for future processing so that you cover all your data. In this lab, we build our FIFO memory by using Memory Building blocks:



This is simply the block ram portion, however, and more implementation needs to be created to store and extract this data. We do this by creating FIFO Micro-Architecture. This is implemented in more detail in the Appendix, but a general overview can be seen

below.

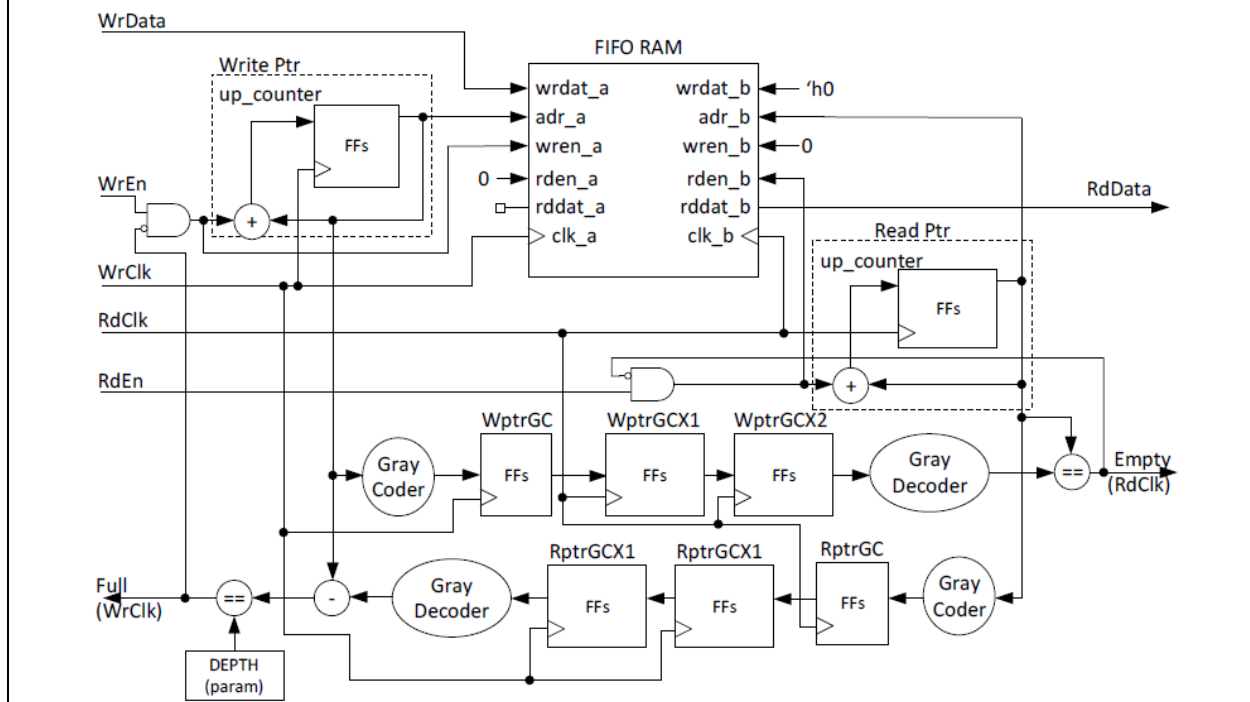

2.1.2 Fibonacci Sequence

The Fibonacci sequence is what we are storing in our FIFO ram. The general formula for this sequence is as follows: $F_n = F_{n-1} + F_{n-2}$. As you can see this data will grow very quickly. Continually, we can see this implemented in the appendix.


2.1.3 Up Counters

A general up counter will be used to increment through our Fibonacci sequence in phase 3. What is different about this up counter, however, is the fact that it will reset once the value gets to be too large for the DE10 lite to output, since we only have a 6-segment display. Even with displaying in hex, these values become very large.

2.1.4 Top Level Design

The top-level design for this program can also be found in the appendix. This file allows for the DE10 Lite board to display all the first 36 values of the Fibonacci sequence. A general overview can be seen

below.

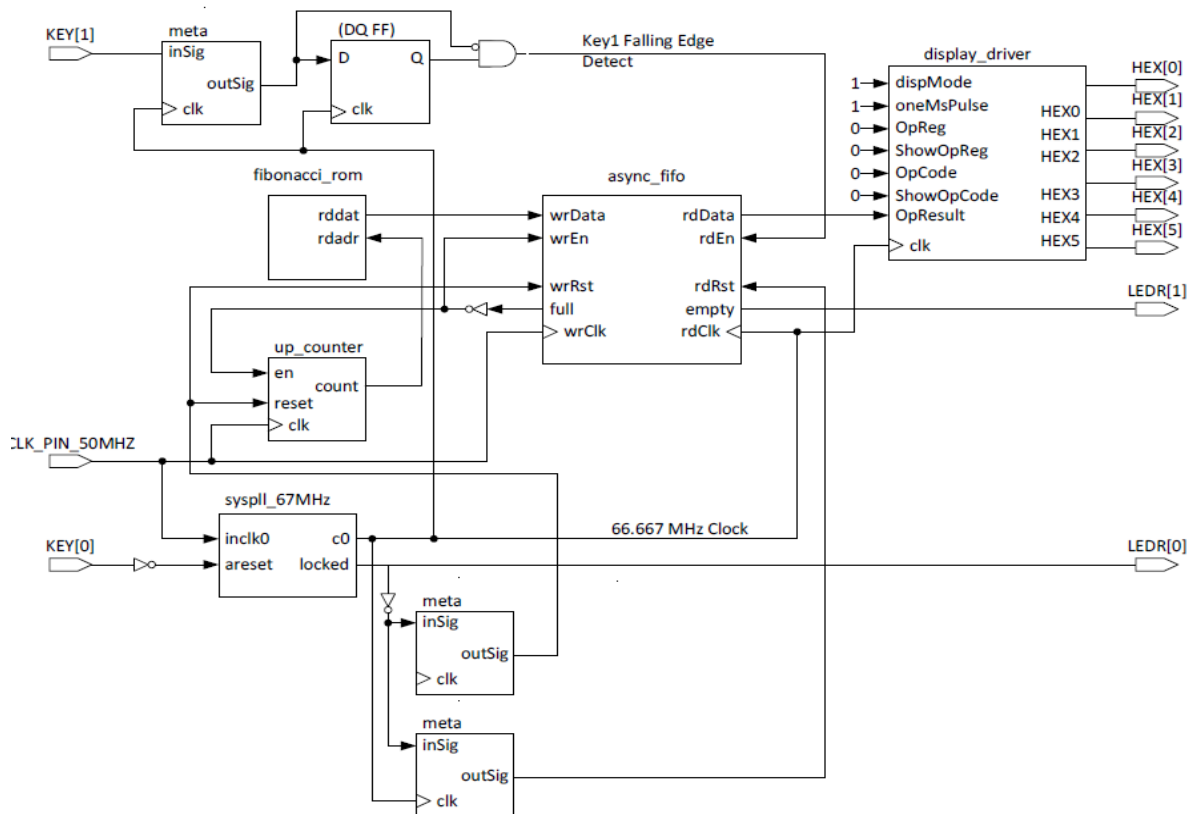

As you can see, this top-level file will introduce and use much of the code that we have already developed throughout this lab including the display_driver and meta from labs 3 and 4, and also the generated syspll file.

2.2 Design and implementation procedure:

All the design models can be found in the section 2.1, and the implementation procedure can be found in the appendix.

3. Demonstration

3.1 Implementation method:

See the appendix for the code I used.

3.2 Video Link:

Video is uploaded to provided link.

4. Experimental Results

4.1 Observations:

The results for the 3 phases can be seen in section 4.3. Overall, the results are as expected when comparing to theoretical values and operations.

4.2 Post lab questions:

1. Run through the entire 36 entries of the Fibonacci sequence stored in the ROM and report the numbers on the lab report. What is the next value of the sequence? Will it fit in a 24-bit binary number space of the 6-digit hex display?

A graph of the outputs can be seen below. Yes, it can fit on the display but if you were to continue past 36 iterations, it would eventually not fit on the display.

	A	B	C	D
1	Clicks	Result	Clicks2	Result2
2	0	000000	19	001055
3	1	000001	20	001A6d
4	2	000001	21	002AC2
5	3	000002	22	00452F
6	4	000003	23	006FF1
7	5	000005	24	00b520
8	6	000008	25	012511
9	7	00000d	26	1dA31
10	8	000015	27	02FF42
11	9	000022	28	04d973
12	10	000037	29	07d8b5
13	11	000057	30	0Cb228
14	12	000090	31	148Add
15	13	0000E9	32	213d05
16	14	000179	33	35C7E2
17	15	000262	34	5704E7
18	16	0003db	35	8CCCC9
19	17	00063d	36	E3d1b0
20	18	000A18	37	000000

2. For generating the 66.667 MHz clock for the read-side of the FIFO:

a. What frequency does the VCO oscillate at?

66.67 Mhz

b. What is the clock division ratio on the 50 MHz input clock?

5000

```
defparam  
    altp11_component.bandwidth_type = "AUTO",  
    altp11_component.clk0_divide_by = 5000,  
    altp11_component.clk0_duty_cycle = 50,  
    altp11_component.clk0_multiply_by = 6667,  
    altp11_component.clk0_phase_shift = "0",  
    altp11_component.compensate_clock = "CLK0",  
    altp11_component.inclk0_input_frequency = 20000, ..
```

c. What is the divider for the VCO feedback path?

20000

d. The answers to 1b and 1c above must lead to the same frequency for the PLL to lock – do they? What frequency is it?

Yes. They both go to 66.67 Mhz

e. What is the division ratio from the VCO to the 66.667 MHz output clock?

1

3. The top-level module has two meta.v blocks drawn at the ~locked output of the system PLL. They are connected to the same inSig, so why are there two different ones? Where do the outputs of these blocks lead?

There are two in the top level because one is connected to the clock and the other is not. The One not connected to the clock is used for the reset of the up counter and the reset for the write reset. The one with the clock input is sent to the read reset, essentially if it times out then we reset the reading.

4. What is the reported device utilization with the original sdp_ram_infer.v block? This must include the number of logic elements, flip-flops, and dedicated RAM blocks and/or bits.

11,232 / 1677312 (Memory Bits) 1838 / 49760 (Total Logic Elements)

a. In Phase 3, after recording the device utilization numbers, the student is asked to modify the sdp_ram_infer.v file to include a reset to set the RAM contents to 0 for every address. What effect does this have on device utilization numbers? Does it have an adverse impact on meeting timing?

The device utilization numbers were a bit less when implementing it this way.

b. The other modification to sdp_ram_infer (besides resetting all contents) is to remove the 1-cycle latency between the RAM data array storage and the read-data output. Again in this scenario, report and remark on the ability for Quartus to map the RAM into the large, efficient Block RAMs, and whether device utilization and timing were negatively impacted.

Timing seems to be affected, but the device utilization is less. This is because it is not using as much of the device to implement the latency.

5. Try the following depths for the async_fifo block, and report on device utilization numbers. For the case where the depth of the FIFO is not a power-of-two, simulate it to ensure it works properly and then demonstrate that it performs the same as any other (power-of-two) option.

Output generated was the same

a. 32 - 11136 / 1677312

b. 128 - 13440 / 1677312


c. 10 - 10608 / 1677312

d. 512 - 22656 / 1677312


e. 2048 - 59520 / 1677312

4.3 Results

4.3.1 Phase 1 Output

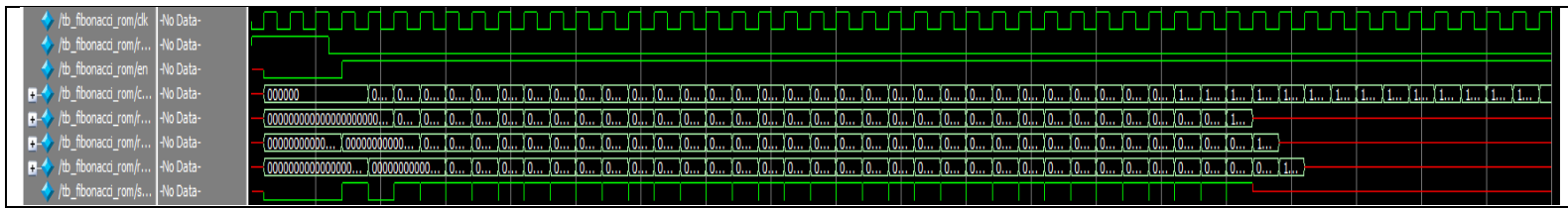

4.3.2 Phase 2 Output

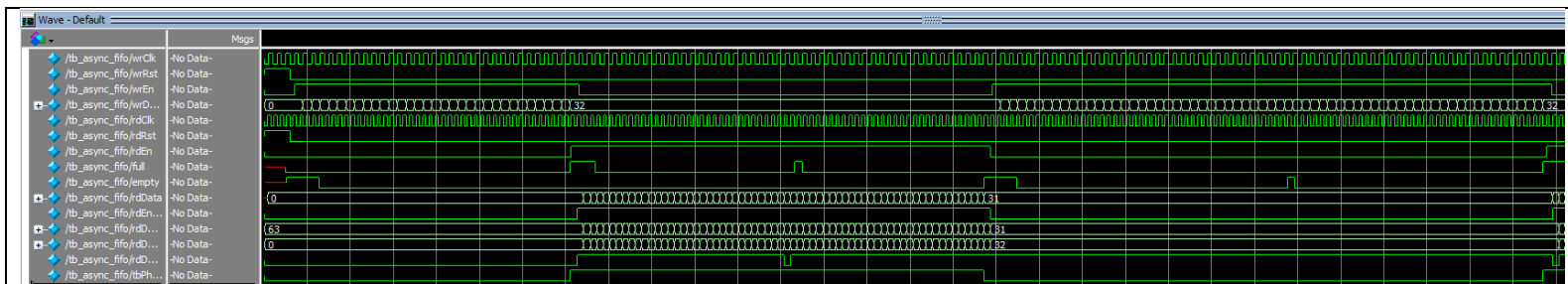

4.3.3 Phase 3 Output

The output for phase 3 can be seen in the demonstration video. The output for the hex display will be the first 36 numbers of the Fibonacci sequence.

5. Conclusions

5.1 - Results and lessons learned:

Overall, this lab was extremely difficult. Not due to the actual coding. The overall coding was not that bad, but the bug fixing, and wire checking took far too long to be acceptable for a 1 hour course. I did learn a lot, though.

6. Appendix

6.1 – Phase 1 Code:

```
// Nolan Anderson
// CPE324
// Lab 6 Phase 1 Fibonacci ROM

module fibonacci_rom (input  [5:0]  rdadr, output [23:0] rddat);

    reg [23:0] rom [0:35];
    integer i;

    initial begin
        rom[0] = 1; rom[1] = 1;
        for(i = 2; i < 35; i = i + 1) begin
            rom[i] = rom[i - 1] + rom[i - 2];
        end
    end

    assign rddat = rom[rdadr];
endmodule
```

```
// Nolan Anderson
// CPE324
// Lab 6 Phase 1 UP Counter
module up_counter #(parameter WIDTH, parameter TERM_CNT)
( input clk, reset, en, output reg [WIDTH-1:0] count);
always @(posedge clk)begin

if(reset)begin count = 0; end
else if(en) begin
    if(count == 2**(WIDTH)-1)begin count = 0; end
    else if (count == TERM_CNT)begin count = 0; end
    else begin count = count + 1; end
    end
end
endmodule
```

6.2 – Phase 2 Code:

```
// Nolan Anderson
// CPE324
// Lab 6 Phase 2 ASYNC Fifo
```



```

module async_fifo #(parameter WIDTH, parameter DEPTH)
(
    input          wrClk,
    input          wrRst,
    input          wrEn,
    input  [WIDTH-1:0] wrData,
    input          rdClk,
    input          rdRst,
    input          rdEn,
    output         full,
    output         empty,
    output  [WIDTH-1:0] rdData
);

    localparam DEPTH_LOG = $clog2(DEPTH);
    localparam PTR_WIDTH = (DEPTH == 2**DEPTH_LOG) ? DEPTH_LOG + 1 : DEPTH_LOG;

    wire w0, w1;
    and a0(w0, wrEn, ~full);
    wire [PTR_WIDTH - 1 : 0] WritePTR;
    and a1(w1, rdEn, ~empty);
    wire [PTR_WIDTH - 1 : 0] ReadPTR; // Read Address
    wire [DEPTH_LOG - 1 : 0] w2;      // GC Out Write
    wire [DEPTH_LOG - 1 : 0] w3;      // FF Out Write
    wire [DEPTH_LOG - 1 : 0] w4;      // META Out Write
    wire [DEPTH_LOG - 1 : 0] w5;      // GD OutWrite
    wire [DEPTH_LOG - 1 : 0] w6;      // GC Out Read
    wire [DEPTH_LOG - 1 : 0] w7;      // FF Out Write Read
    wire [DEPTH_LOG - 1 : 0] w8;      // Meta Out Read
    wire [DEPTH_LOG - 1 : 0] w9;      // GD Out Read

    up_counter #(.WIDTH(PTR_WIDTH), .TERM_CNT(2**(PTR_WIDTH)-1))
    Write_Ptr(
        .clk(wrClk),
        .reset(wrRst),
        .en(w0),
        .count(WritePTR)
    );

    up_counter #(.WIDTH(PTR_WIDTH), .TERM_CNT(2**(PTR_WIDTH)-1))
    Read_Ptr(
        .clk(rdClk),
        .reset(rdRst),
        .en(w1),

```

```

        .count(ReadPTR)
    );

    sdp_ram_infer #(.WIDTH(WIDTH), .DEPTH(DEPTH), .DEPTH_LOG(DEPTH_LOG))
    RAM(
        .wrClk(wrClk),
        .rdClk(rdClk),
        .rdRst(rdRst),
        .wrEn(w0),
        .wrDat(wrData),
        .wrAdr(WritePTR),
        .rdEn(w1),
        .rdAdr(ReadPTR),
        .rdDat(rdData)
    );

    gray_coder #(.WIDTH(DEPTH_LOG))
    write_coder(
        .binIn(WritePTR),
        .gcOut(w2)
    );

    DFF #(.WIDTH(DEPTH_LOG))
    WprtGC(
        .clk(wrClk),
        .D(w2),
        .Q(w3)
    );

    meta #(.DATA_WIDTH(DEPTH_LOG), .DEPTH(2))
    WptrGCX(
        .clk(rdClk),
        .in_sig(w3),
        .out_sig(w4)
    );

    gray_decoder #(.WIDTH(DEPTH_LOG))
    write_decoder(
        .gcIn(w4),
        .binOut(w5)
    );

    gray_coder #(.WIDTH(DEPTH_LOG))
    read_coder(
        .binIn(ReadPTR),

```

```

        .gcOut(w6)
    );

    DFF #(.WIDTH(DEPTH_LOG))
    RptrGC(
        .clk(rdClk),
        .D(w6),
        .Q(w7)
    );

    meta #(.DATA_WIDTH(DEPTH_LOG), .DEPTH(2))
    RptrGCX(
        .clk(wrClk),
        .in_sig(w7),
        .out_sig(w8)
    );

    gray_decoder #(.WIDTH(DEPTH_LOG))
    read_decoder(
        .gcIn(w8),
        .binOut(w9)
    );

    assign full = ((DEPTH) == (WritePTR - w9)) ? 1 : 0;
    assign empty = (ReadPTR == w5) ? 1 : 0;

endmodule

```

6.3 – Phase 3 Code:

```

// Nolan Anderson
// CPE324
// Lab 6 Phase 3 Top Level File
`define ENABLE_CLOCK1
`define ENABLE_HEX0
`define ENABLE_HEX1
`define ENABLE_HEX2
`define ENABLE_HEX3
`define ENABLE_HEX4
`define ENABLE_HEX5
`define ENABLE_KEY
`define ENABLE_LED
`define ENABLE_SW

```

```

`define ENABLE_GPIO

module DE10_LITE_Golden_Top(

    /////////////// ADC CLOCK: 3.3-V LVTTL ///////////////
`ifdef ENABLE_ADC_CLOCK
    input                ADC_CLK_10,
`endif

    /////////////// CLOCK 1: 3.3-V LVTTL ///////////////
`ifdef ENABLE_CLOCK1
    input                MAX10_CLK1_50,
`endif

    /////////////// CLOCK 2: 3.3-V LVTTL ///////////////
`ifdef ENABLE_CLOCK2
    input                MAX10_CLK2_50,
`endif

    /////////////// SDRAM: 3.3-V LVTTL ///////////////
`ifdef ENABLE_SDRAM
    output                [12:0]    DRAM_ADDR,
    output                [1:0]    DRAM_BA,
    output                DRAM_CAS_N,
    output                DRAM_CKE,
    output                DRAM_CLK,
    output                DRAM_CS_N,
    inout                [15:0]    DRAM_DQ,
    output                DRAM_LDQM,
    output                DRAM_RAS_N,
    output                DRAM_UDQM,
    output                DRAM_WE_N,
`endif

    /////////////// SEG7: 3.3-V LVTTL ///////////////
`ifdef ENABLE_HEX0
    output                [7:0]    HEX0,
`endif
`ifdef ENABLE_HEX1
    output                [7:0]    HEX1,
`endif
`ifdef ENABLE_HEX2
    output                [7:0]    HEX2,
`endif
`ifdef ENABLE_HEX3
    output                [7:0]    HEX3,
`endif

```

```

`ifndef ENABLE_HEX4
    output        [7:0]      HEX4,
`endif
`ifndef ENABLE_HEX5
    output        [7:0]      HEX5,
`endif

    //////////// KEY: 3.3 V SCHMITT TRIGGER ////////////
`ifndef ENABLE_KEY
    input         [1:0]      KEY,
`endif

    //////////// LED: 3.3-V LVTTL ////////////
`ifndef ENABLE_LED
    output        [9:0]      LEDR,
`endif

    //////////// SW: 3.3-V LVTTL ////////////
`ifndef ENABLE_SW
    input         [9:0]      SW,
`endif

    //////////// VGA: 3.3-V LVTTL ////////////
`ifndef ENABLE_VGA
    output        [3:0]      VGA_B,
    output        [3:0]      VGA_G,
    output        VGA_HS,
    output        [3:0]      VGA_R,
    output        VGA_VS,
`endif

    //////////// Accelerometer: 3.3-V LVTTL ////////////
`ifndef ENABLE_ACCELEROMETER
    output        GSENSOR_CS_N,
    input         [2:1]      GSENSOR_INT,
    output        GSENSOR_SCLK,
    inout         GSENSOR_SDI,
    inout         GSENSOR_SDO,
`endif

    //////////// Arduino: 3.3-V LVTTL ////////////
`ifndef ENABLE_ARDUINO
    inout         [15:0]     ARDUINO_IO,
    inout         ARDUINO_RESET_N,
`endif

```

```

        ////////////////////////////////////////////////// GPIO, GPIO connect to GPIO Default: 3.3-V LVTTL //////////////////////////////////
`ifdef ENABLE_GPIO
    inout          [35:0]      GPIO
`endif
);

//=====
// REG/WIRE declarations
//=====
wire notButton0, clk67, a1, w0, w1, w2, w3, w6, w8, lock, buttonPress;
assign notButton0 = ~KEY[0];
localparam WIDTH = 24;
localparam DEPTH = 36;
wire [WIDTH-1:0] w4;
wire [WIDTH-1:0] w5;
wire [WIDTH-1:0] w7;
assign LEDR[0] = lock;

//=====
// Structural coding
//=====

meta #(.DATA_WIDTH (1), .DEPTH (2))
meta_1(
    .clk (clk67),
    .in_sig (KEY[1]),
    .out_sig (w0)
);

D_Flip_Flop #( .WIDTH(WIDTH))
RptrGC(
    .clk(clk67),
    .D(w0),
    .Q(w1)
);

and a0(a1,~w0,w1);

syspll pll66 (
    .areset(notButton0),
    .inclk0 (MAX10_CLK1_50),
    .c0      (clk67),
    .locked (lock)
);

```

```

meta #(.DATA_WIDTH (1),.DEPTH (2))
meta_sys1(
    .clk (clk67),
    .in_sig (~lock),
    .out_sig (w2)
);

meta #(.DATA_WIDTH (1), .DEPTH (2))
meta_sys2(
    .clk (clk67),
    .in_sig (~lock),
    .out_sig (w3)
);

up_counter #(.WIDTH(WIDTH), .TERM_CNT(DEPTH))
Write_Ptr(
    .clk(MAX10_CLK1_50),
    .reset(w2),
    .en(~w6),
    .count(w4)
);

fibonacci_rom fib_rom(
    .rdadr(w4),
    .rddat(w5)
);

async_fifo #(.WIDTH(WIDTH),.DEPTH(DEPTH))
a_fifo(
    .wrClk(MAX10_CLK1_50),
    .wrRst(w2),
    .wrEn(~w6),
    .wrData(w5),
    .rdClk(clk67),
    .rdRst(w3),
    .rdEn(a1),
    .full(w6),
    .empty(LED_R[1]),
    .rdData(w7)
);

display_driver hex_leds (
    .clk          (clk67),
    .dispMode     (1'b1),

```

```
.oneMsPulse (1'b1),  
.OpReg      (1'b0),  
.ShowOpReg  (1'b0),  
.OpCode     (1'b0),  
.ShowOpCode (1'b0),  
.OpResult   (w7),  
.HEX0       (HEX0),  
.HEX1       (HEX1),  
.HEX2       (HEX2),  
.HEX3       (HEX3),  
.HEX4       (HEX4),  
.HEX5       (HEX5)  
);  
  
endmodule
```