

Prelab 2

Nolan Anderson

February 31, 2021

Part 1 – Integrator

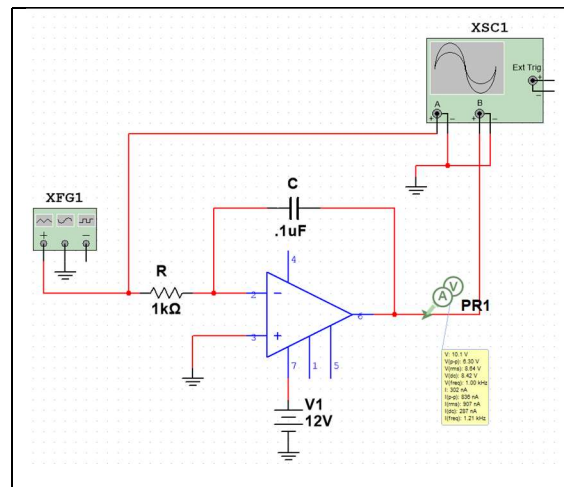


Figure 1: Integrator in Multisim

$R = 1\text{k}\Omega$, $C = 0.1\text{ }\mu\text{F}$, $f = 1\text{ kHz}$

$V_{IN} = 2\text{V}_{pp}$ sinusoidal, triangle, square

- a. Plot the input and output waveforms on the same graph for two complete cycles.
 - See Figures 2-4
- b. Comment on the gain and input-output phase relationship.
 - i. Figure 2 – Gain is 1.635 V/v – Input is sine and output is gain * cosx
 - ii. Figure 3 – Gain is 1.239 V/v – On max / min input, output is 0.
 - iii. Figure 4 – Gain is 2.472 V/v – When input changes direction, output is max / min.
 - iv. Figure 5 – Gain is 0.164 V/v – Input is out of phase wrt output.
 - v. Figure 6 – Gain is 0.133 V/v – On max / min input, output is 0.
 - vi. Figure 7 – Gain is 0.234 V/v – When the input is changing, output is max / min.
- c. Repeat for $C = 1\text{ }\mu\text{F}$ and compare to your results with $C = 0.1\text{ }\mu\text{F}$.
 - See Figures 5-7

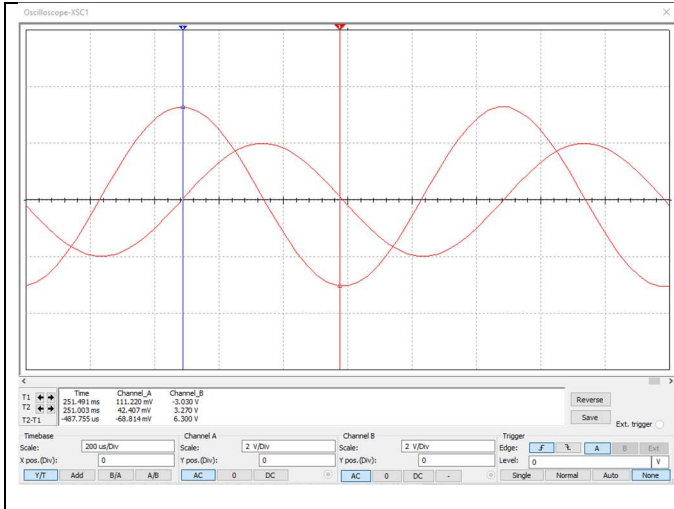


Figure 2: Integrator with sine wave $R = 1k\Omega$, $C = 0.1\mu F$

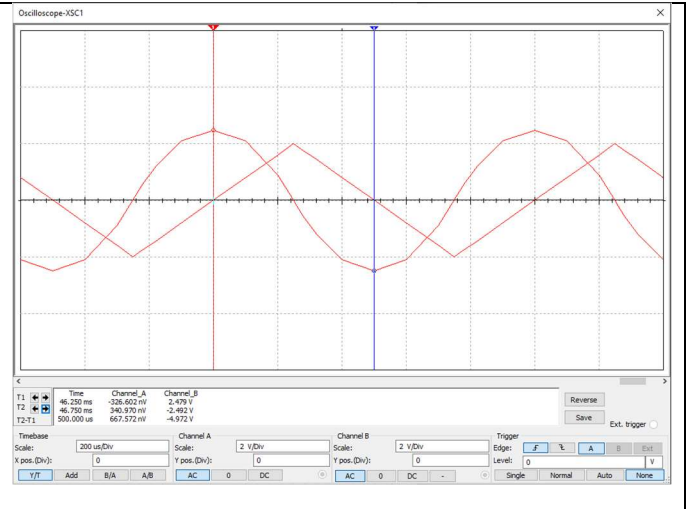


Figure 3: Integrator with triangle wave $R = 1k\Omega$, $C = 0.1\mu F$

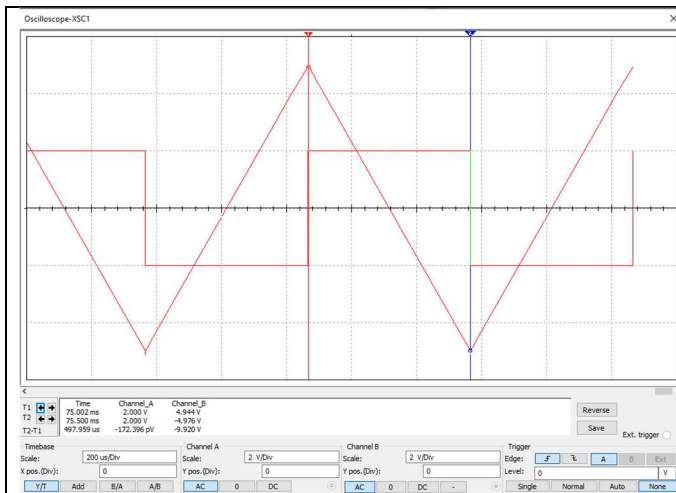


Figure 4: Integrator with square wave $R = 1k\Omega$, $C = 0.1\mu F$

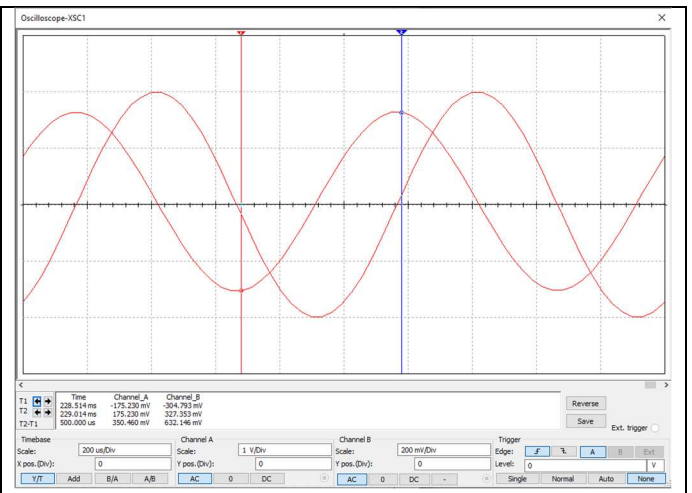


Figure 5: Integrator with sine wave $R = 1k\Omega$, $C = 1\mu F$

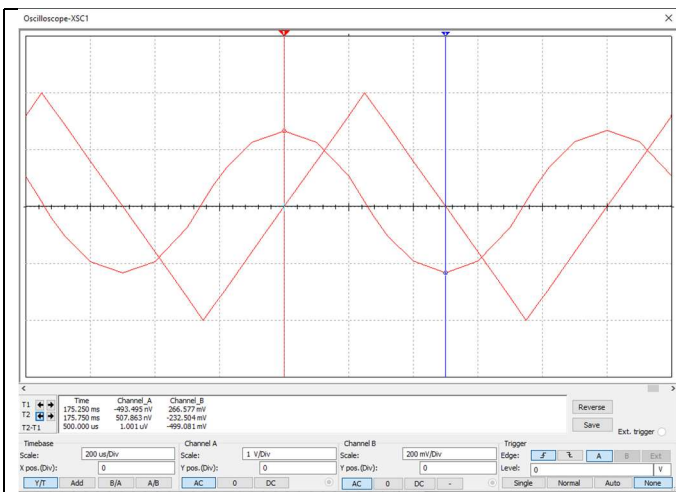


Figure 6: Integrator with triangle wave $R = 1k\Omega$, $C = 1\mu F$

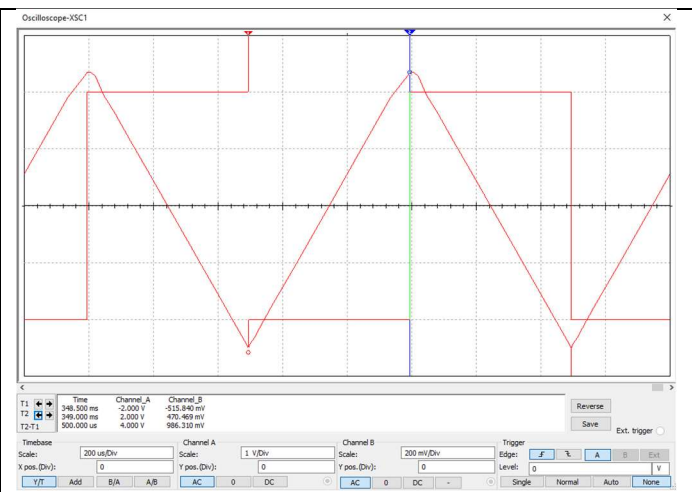


Figure 7: Integrator with square wave $R = 1k\Omega$, $C = 1\mu F$

Part 2 – Differentiator

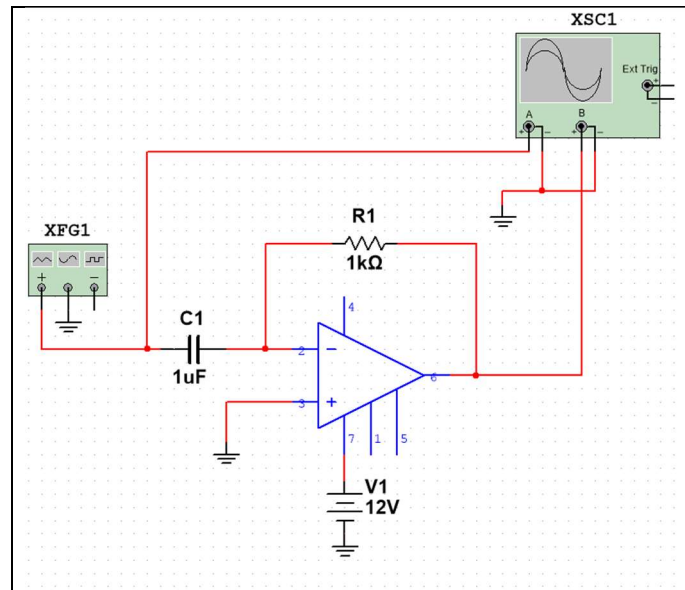


Figure 8: Differentiator in Multisim

$R = 1\text{k}\Omega$, $C = 0.1\text{ }\mu\text{F}$, $f = 1\text{ kHz}$

$V_{IN} = 2\text{Vpp}$ sinusoidal, triangle, square

- d. Plot the input and output waveforms on the same graph for two complete cycles.
 - See Figures 9-11
- e. Comment on the gain and input-output phase relationship.
 - i. Figure 9 – Gain is 0.73 V/v – When input is sin, output is $\text{gain} * \cos$
 - ii. Figure 10 – Gain is 1.07 V/v – When input inc / dec, output is damped oscillator.
 - iii. Figure 11 – Gain is 5.60 V/v – When input changes direction, output is max / min.
 - iv. Figure 12 – Gain is 5.41 V/v – The input is out of phase with output.
 - v. Figure 13 – Gain is 5.18 V/v – When input is at a minimum, output is decreasing.
 - vi. Figure 14 – Gain is 5.48 V/v – Output decreases as a reaction to the input gaining.
- f. Repeat for $C = 1\text{ }\mu\text{F}$ and compare to your results with $C = 0.1\text{ }\mu\text{F}$.
 - See Figures 12-14

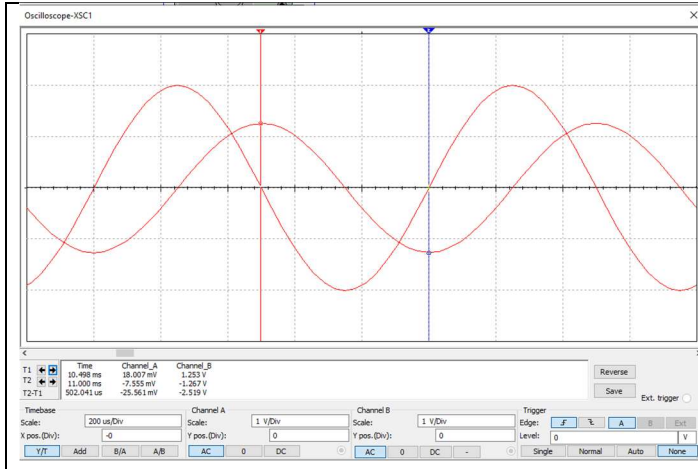


Figure 9: Differentiator with sine wave $R = 1\text{k}\Omega$, $C = 0.1\mu\text{F}$

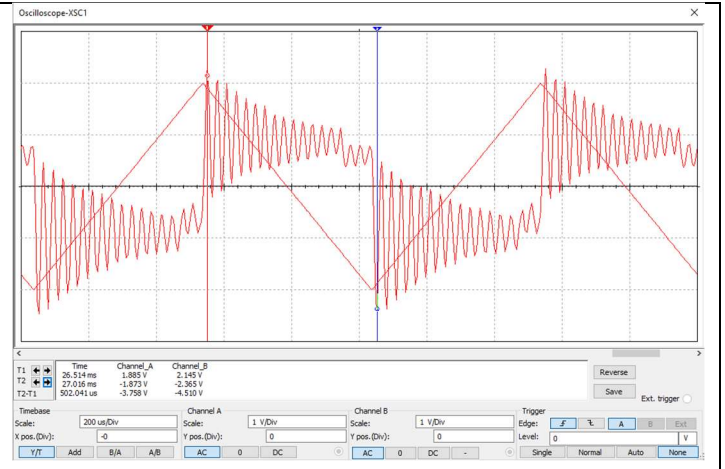


Figure 10: Differentiator with triangle wave $R = 1\text{k}\Omega$, $C = 0.1\mu\text{F}$

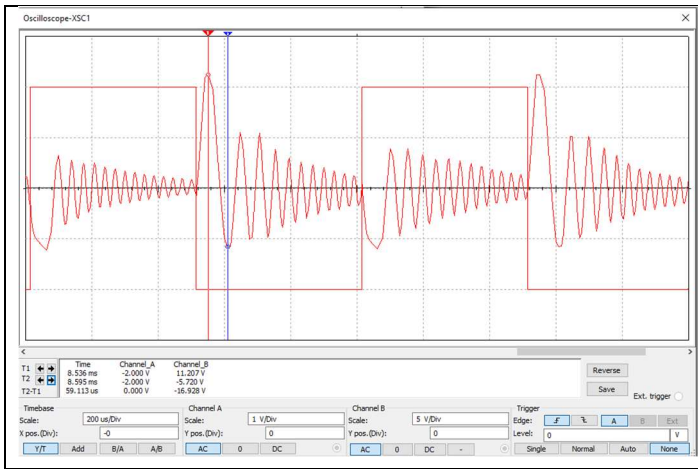


Figure 11: Differentiator with square wave $R = 1\text{k}\Omega$, $C = 0.1\mu\text{F}$

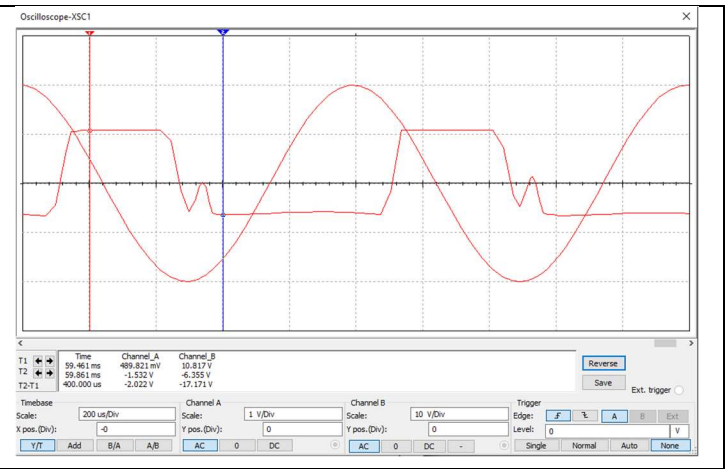


Figure 12: Differentiator with sine wave $R = 1\text{k}\Omega$, $C = 1\mu\text{F}$

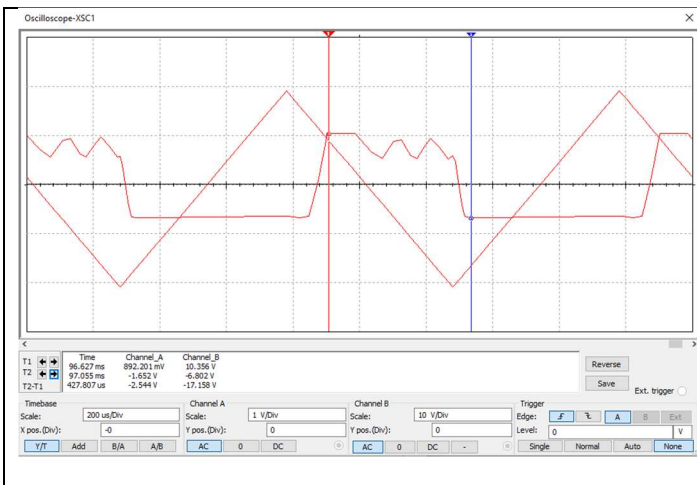


Figure 13: Differentiator with triangle wave $R = 1\text{k}\Omega$, $C = 1\mu\text{F}$

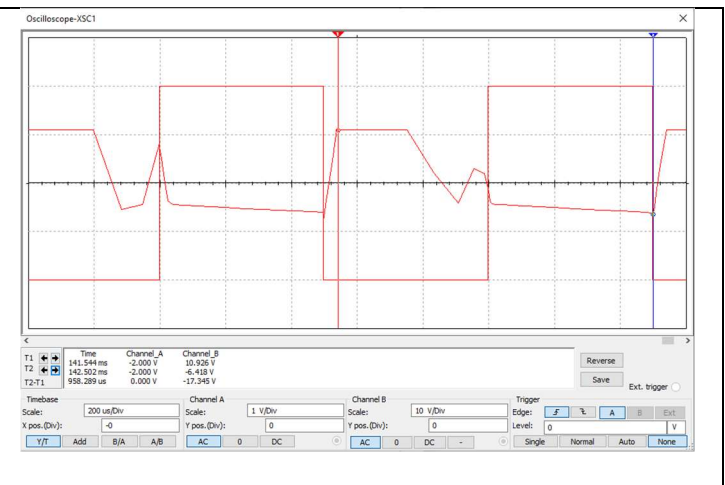


Figure 14: Differentiator with square wave $R = 1\text{k}\Omega$, $C = 1\mu\text{F}$

