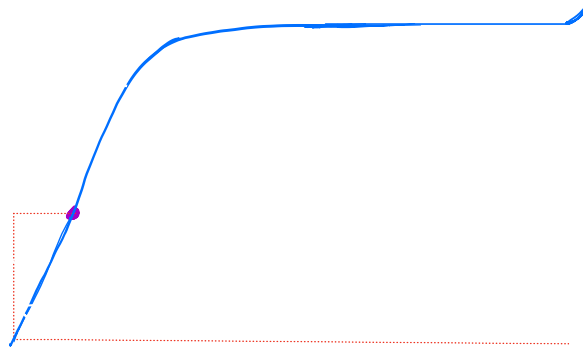


$I_z \checkmark$

I_z^* negative
 V_z^* negative

$I_z^* \wedge$

$-V_z -V_{z0} -V_{zk}$



V_{zk}

I_{zk}

I_{zT}

r_z

Example:

Example

Example:

Zener Diodes Examples

+
 V_o
-

a) Find V_o assume no load $R_L \rightarrow \infty$ and V_S is nominal 10V

b) Find change in V_o w/ respect to V_S

→ line regulation

→ output voltage change for a given $\pm 1\text{V}$

C) Find ΔV_o if we connect a load resistor that draws 1mA away from the Zener Diode

d) Find ΔV_o for $R_L = 2\text{k}\Omega$

e) $R_L = 500 \Omega$

→ Zener Diode is no longer
in breakdown

f) What is the minimum R_L value such that we are
on the edge of breakdown?

knee voltage
|