

Digital Hardware Design Fundamentals

Electrical and Computer Engineering


Finite State Machine Representation &
Verilog



Sequential Networks

- Have memory (state)
 - Present state depends not only on the current input, but also on all previous inputs (history)
 - Future state depends on the current input and state
 
$$X = x_1 \ x_2 \dots x_n$$
$$Q = Q_1 \ Q_2 \dots Q_k$$
$$Z = z_1 \ z_2 \dots z_m$$




$$Z(t) = F(X(t), Q(t))$$

$$Q(t^+) = G(X(t), Q(t))$$

Flip-flops are commonly used as storage devices:
D-FF, JK-FF, T-FF

Mealy Sequential Networks

 
General model of Mealy Sequential Network



$$Q(t^+) = G(X(t), Q(t)) \quad Z(t) = F(X(t), Q(t))$$

 - (1) X inputs are changed to a new value
- (2) After a delay, the Z outputs and next state appear at the output of CM (input of State Register)
- (3) The next state is clocked into the state register and the state changes

An Example: 8421 BCD to Excess3 BCD Code Converter



X (inputs)				Z (outputs)			
t3	t2	t1	t0	t3	t2	t1	t0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

State Graph

BCD to Excess3 Code Converter

X/Z


t₀ -----



State Graph

BCD to Excess3 Code Converter


X/Z

 

State Graph

BCD to Excess3 Code Converter


X/Z

 

State Graph

BCD to Excess3 Code Converter


X/Z

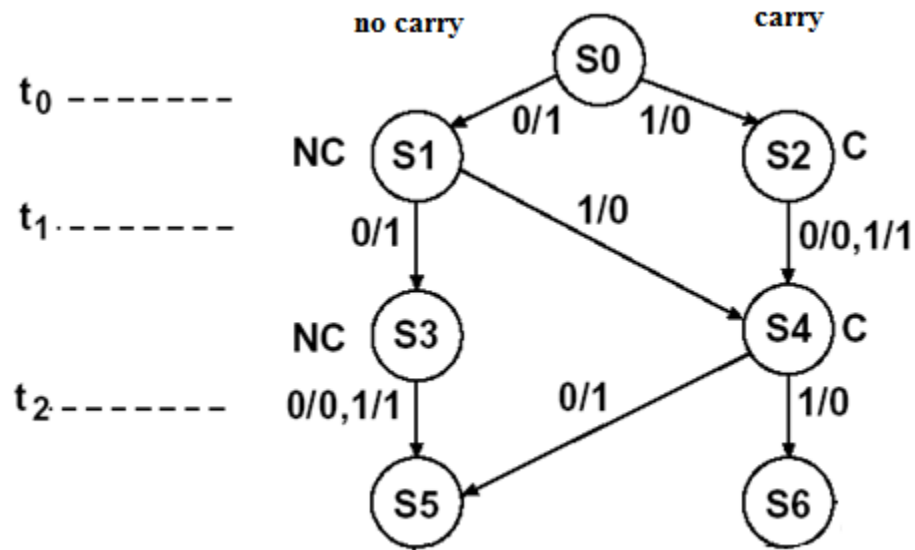


State Graph

BCD to Excess3 Code Converter

X/Z

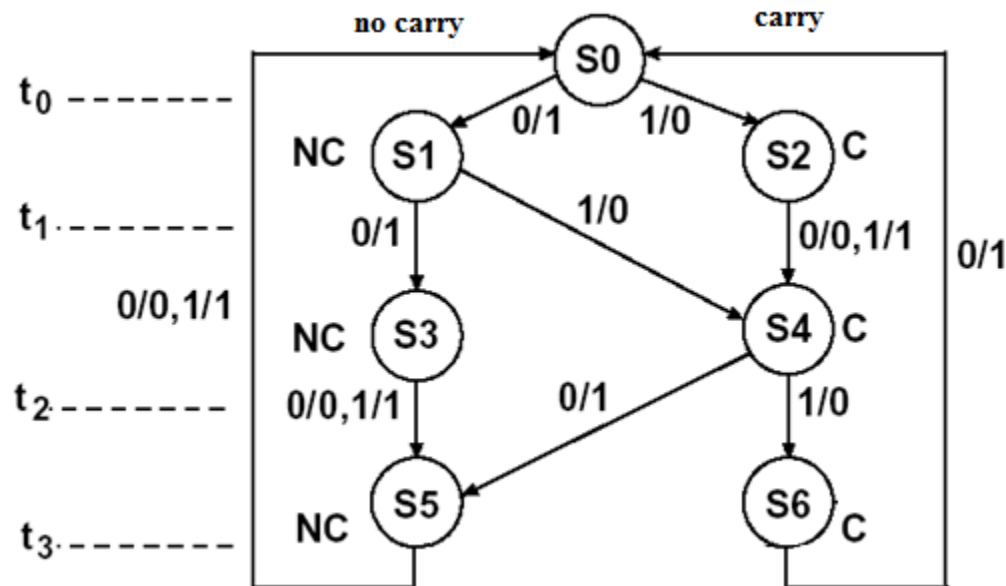

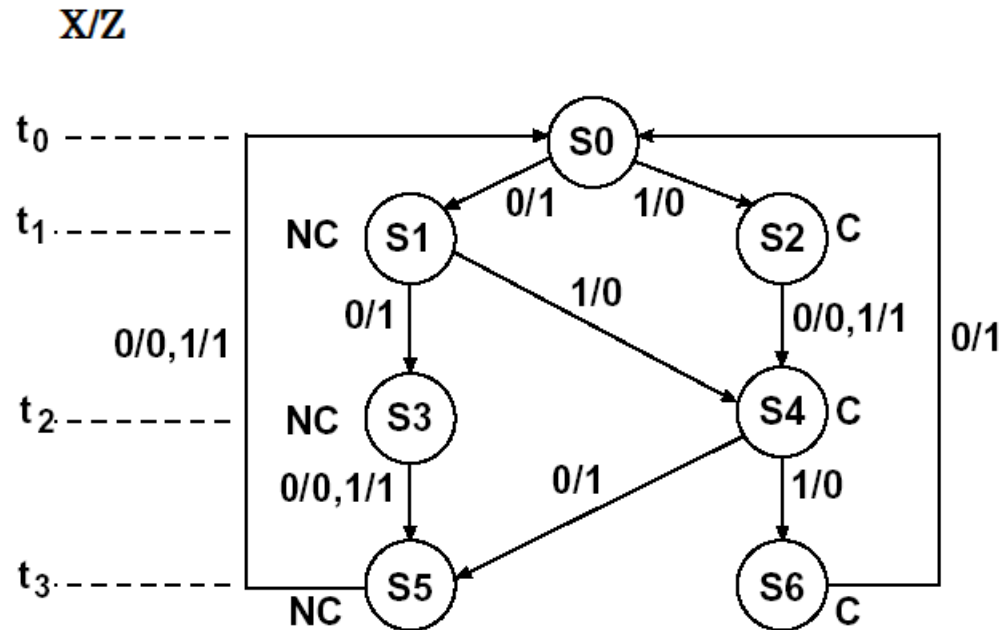State Graph and Table for BCD to Excess3 Code Converter



PS	NS		Z	
	X = 0	X = 1	X = 0	X = 1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S0	S0	0	1
S6	S0	—	1	—

Behavioral Verilog HDL Model


8421 BCD to Excess3 Code Converter (Mealy FSM)

```
// bcd to excess 3 converter
// Mealy Implementation
// Behavioral Model
module bcd_ex3_mealy(input X,CLK,output reg Z);
    reg [2:0] State=0,Nextstate=0;

    // Combinational Network
    always @ (State,X)
        case (State)
            0 : if (!X) begin Nextstate=1; Z=1; end
                else begin Nextstate=2; Z=0; end
            1 : if (!X) begin Nextstate=3; Z=1; end
                else begin Nextstate=4; Z=0; end
            2 : if (!X) begin Nextstate=4; Z=0; end
                else begin Nextstate=4; Z=1; end
            3 : if (!X) begin Nextstate=5; Z=0; end
                else begin Nextstate=5; Z=1; end
            4 : if (!X) begin Nextstate=5; Z=1; end
                else begin Nextstate=6; Z=0; end
            5 : if (!X) begin Nextstate=0; Z=0; end
                else begin Nextstate=0; Z=1; end
            6 : if (!X) begin Nextstate=0; Z=1; end
                else begin Nextstate=0; Z=1'b?; end
            default : begin Nextstate=0; Z=0;end
        endcase

    // State Reg Portion of Design
    always @ (posedge CLK)
        State=Nextstate;

endmodule
```

 

PS	NS		Z	
	X = 0	X = 1	X = 0	X = 1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S0	S0	0	1
S6	S0	-	1	-

Two always sections:

- the first represents the combinational network;
- the second represents the state register

State Assignment Rules

- I. States which have the same next state (NS) for a given input should be given adjacent assignments (look at the columns of the state table).
- II. States which are the next states of the same state should be given adjacent assignments (look at the rows).
- III. States which have the same output for a given input should be given adjacent assignments.

- I. (1,2) (3,4) (5,6) (in the X=1 column, S₁ and S₂ both have NS S₄;
in the X=0 column, S₃ & S₄ have NS S₅, and S₅ & S₆ have NS S₀)
- II. (1,2) (3,4) (5,6) (S₁ & S₂ are NS of S₀; S₃ & S₄ are NS of S₁;
and S₅ & S₆ are NS of S₄)
- III. (0,1,4,6) (2,3,5)

PS	NS		Z	
	X = 0	X = 1	X = 0	X = 1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S0	S0	0	1
S6	S0	—	1	—

State Assignment Rules

- I. States which have the same next state (NS) for a given input should be given adjacent assignments (look at the columns of the state table).
- II. States which are the next states of the same state should be given adjacent assignments (look at the rows).
- III. States which have the same output for a given input should be given adjacent assignments.

- I. (1,2) (3,4) (5,6) (in the X=1 column, S₁ and S₂ both have NS S₄;
in the X=0 column, S₃ & S₄ have NS S₅, and S₅ & S₆ have NS S₀)
- II. (1,2) (3,4) (5,6) (S₁ & S₂ are NS of S₀; S₃ & S₄ are NS of S₁;
and S₅ & S₆ are NS of S₄)
- III. (0,1,4,6) (2,3,5)

PS	NS		Z	
	X = 0	X = 1	X = 0	X = 1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S0	S0	0	1
S6	S0	—	1	—

		Q1	
		0	1
Q2 Q3	00	S0	S1
	01		S2
	11	S5	S3
	10	S6	S4

Transition Table

PS	NS		Z		Q1Q2Q3	Q1*Q2*Q3*		Z	
	X=0	X=1	X=0	X=1		X=0	X=1	X=0	X=1
S0	S1	S2	1	0	000	100	101	1	0
S1	S3	S4	1	0	100	111	110	1	0
S2	S4	S4	0	1	101	110	110	0	1
S3	S5	S5	0	1	111	011	011	0	1
S4	S5	S6	1	0	110	011	010	1	0
S5	S0	S0	0	1	011	000	000	0	1
S6	S0	-	1	-	010	000	xxx	1	x
					001	xxx	xxx	x	x

S0 = 000, S1 = 100, S2 = 101, S3 = 111, S4 = 110, S5 = 011, S6 = 010

K-maps

		XQ ₁			
		00	01	11	10
Q ₂ Q ₃	00	1	1	1	1
	01	X	1	1	X
	11	0	0	0	0
	10	0	0	0	X

$$D_1 = Q_1^+ = Q_2'$$

		XQ ₁			
		00	01	11	10
Q ₂ Q ₃	00	0	1	1	0
	01	X	1	1	X
	11	0	1	1	0
	10	0	1	1	X

$$D_2 = Q_2^+ = Q_1$$

		XQ ₁			
		00	01	11	10
Q ₂ Q ₃	00	0	1	0	1
	01	X	0	0	X
	11	0	1	1	0
	10	0	1	0	X

$$D_3 = Q_3^+ = Q_1Q_2Q_3 + X'Q_1Q_3' + XQ_1'Q_2'$$

		XQ ₁			
		00	01	11	10
Q ₂ Q ₃	00	1	1	0	0
	01	X	0	1	X
	11	0	0	1	1
	10	1	1	0	X

$$Z = X'Q_3' + XQ_3$$

Data Flow Representation Verilog HDL

8421 BCD to Excess3 Code Converter (Mealy FSM)

```
// bcd to excess 3 converter
// Mealy Implementation
// Data Flow Model
module bcd_ex3_mealy(input X,CLK,output Z);

    reg Q1=0,Q2=0,Q3=0;

    // FF State Update Portion of design
    // Active only on rising edge of clock
    always @(posedge CLK)
        begin
            Q1 <= ~Q2;
            Q2 <= Q1;
            Q3 <= (Q1 & Q2 & Q3) | (~X & Q1 & ~Q3) | (X & ~Q1 & ~Q2);
        end

    // Output Equation -- Continuous Assignment that is
    // a function only of the state variables Q1,Q2,Q3
    assign Z = (~X & ~Q3) | (X & Q3);

endmodule
```

$$Q_1^+ = Q_2'$$

$$Q_2^+ = Q_1$$

$$Q_3^+ = Q_1Q_2Q_3 + X'Q_1Q_3' + XQ_1'Q_2'$$

$$Z = X'Q_3' + XQ_3$$

Schematic Realization


8421 BCD to Excess3 Code Converter (Mealy FSM)

$$Q_1^+ = Q_2'$$

$$Q_2^+ = Q_1$$

$$Q_3^+ = Q_1Q_2Q_3 + X'Q_1Q_3' + XQ_1'Q_2'$$

$$Z = X'Q_3' + XQ_3$$

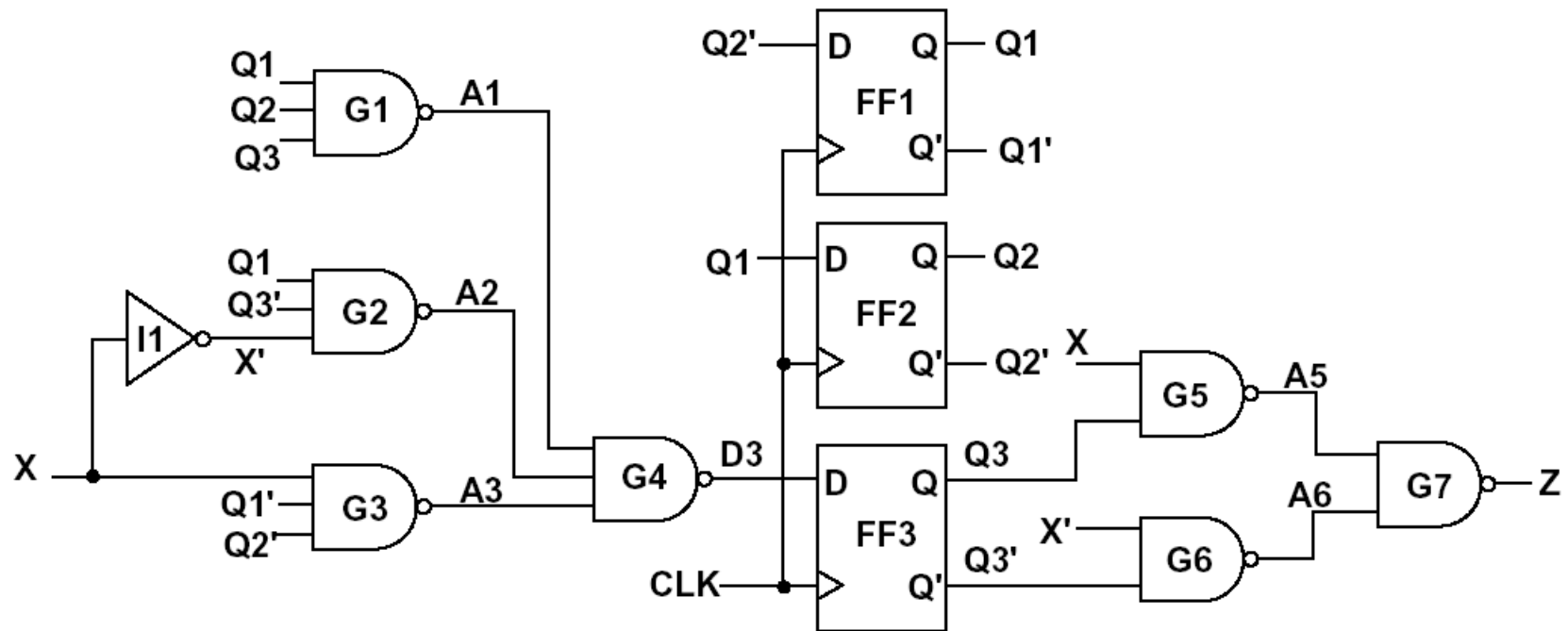

Structural Representation Verilog HDL

8421 BCD to Excess3 Code Converter (Mealy FSM)

```
// bcd to excess 3 converter
// Mealy Implementation
// Structural Model
module bcd_ex3_mealy(input X,CLK,output Z);
    wire A1,A2,A3,A5,A6,D3,Q1,Q1_N,Q2,Q2_N,Q3
```

```
    not I1(X_N,X);
    nand G1(A1,Q1,Q2,Q3);
    nand G2(A2,Q1,Q3_N,X_N);
    nand G3(A3,X,Q1_N,Q2_N);
    nand G4(D3,A1,A2,A3);
    nand G5(A5,X,Q3);
    nand G6(A6,X_N,Q3_N);
    nand G7(Z,A5,A6);
```

```
    d_ff FF1(CLK,Q2_N,Q1,Q1_N);
    d_ff FF2(CLK,Q1,Q2,Q2_N);
    d_ff FF3(CLK,D3,Q3,Q3_N);
```


```
endmodule
```

```
// basic rising edge D flip-flop module
module d_ff(input clk,d, output reg q, output q_n);
```

```
    initial q=0;
```

```
    always @(posedge clk)
        q = d;
```



```
    assign q_n = ~q;
endmodule
```

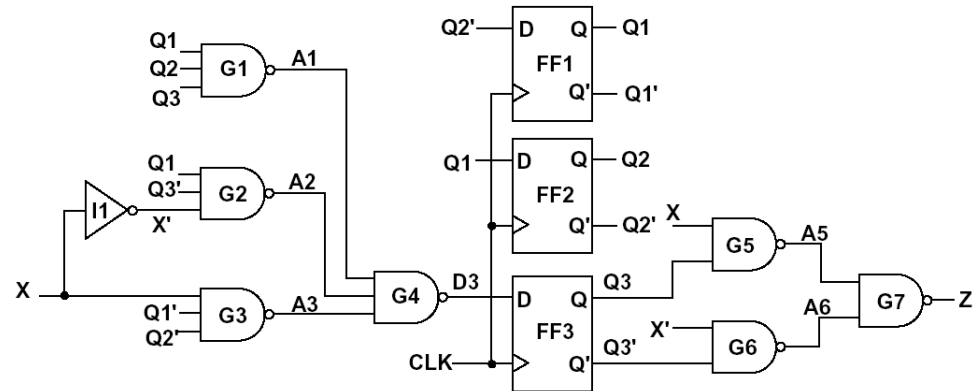

Sequential Network Timing


- Code converter
 - $X = 0010_1001 \Rightarrow$
 $Z = 1110_0011$

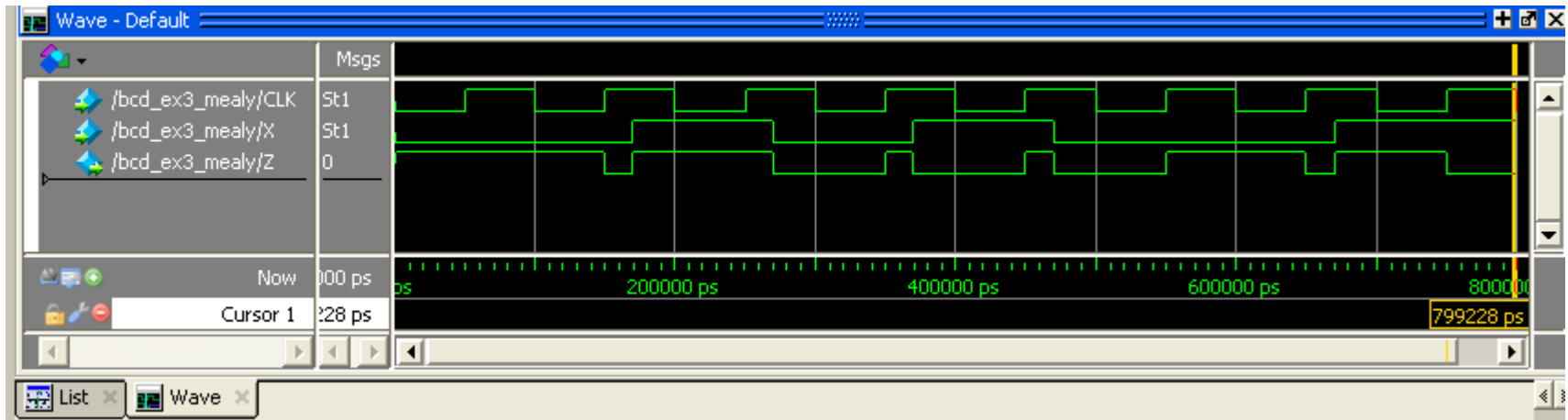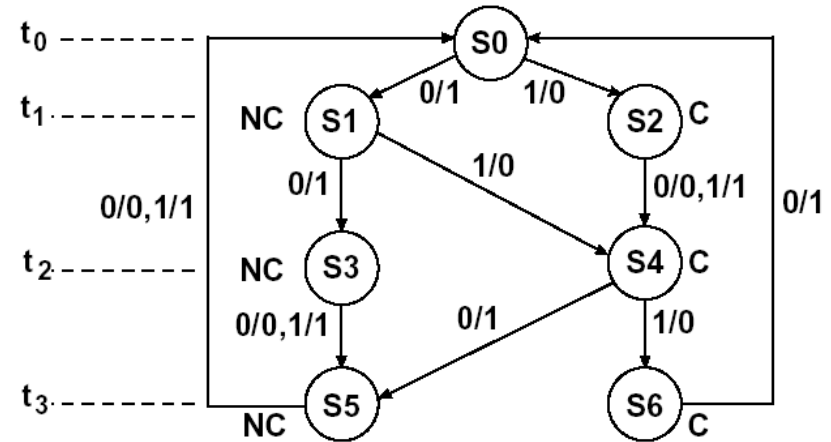Changes in X are not synchronized with active clock edge \Rightarrow glitches (false output), e.g. at t_b




Sequential Network Timing (cont'd)

 Timing diagram assuming a propagation delay
of 10 ns for each flip-flop and gate
(State has been replaced with the state of three flip-flops)



Review: Mealy Sequential Networks

 


$$Q(t^+) = G(X(t), Q(t)) \quad Z(t) = F(X(t), Q(t))$$

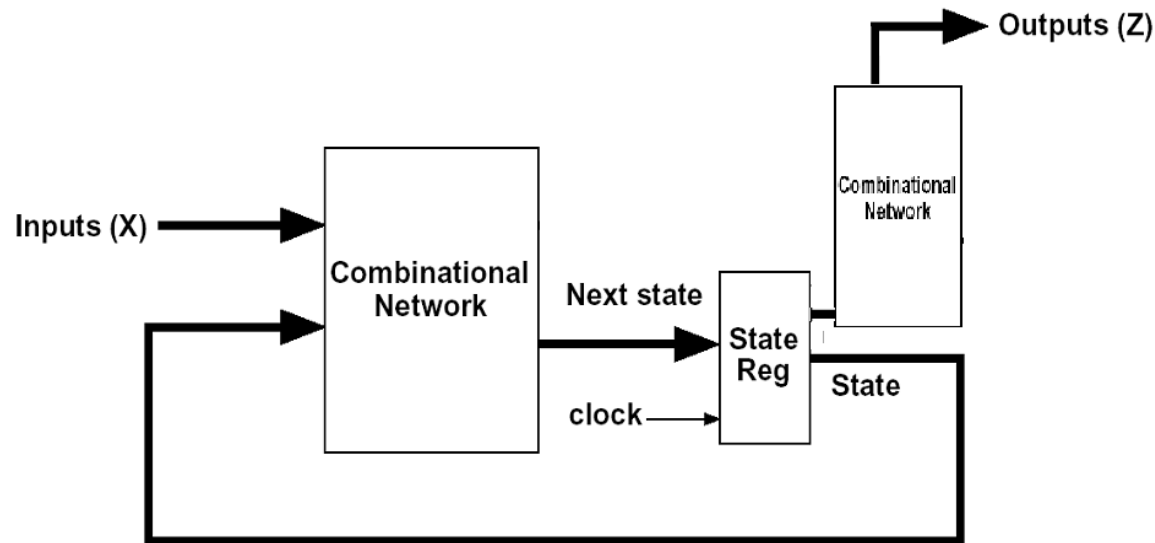- (1) X inputs are changed to a new value
- (2) After a delay, the Z outputs and next state appear at the output of CN (input of state register)
- (3) The next state is clocked into the state register and the state changes

Moore Sequential Networks

General model of Moore Sequential Network



- (1) X inputs are changed to a new value
- (2) The next state is clocked into the state registers
- (3) The outputs appear which are a function of the current state only (not the inputs)


General Model of Moore Sequential Machine

Outputs depend only on present state!

$$X = x_1 x_2 \dots x_n$$

$$Q = Q_1 Q_2 \dots Q_k$$

$$Z = z_1 z_2 \dots z_m$$

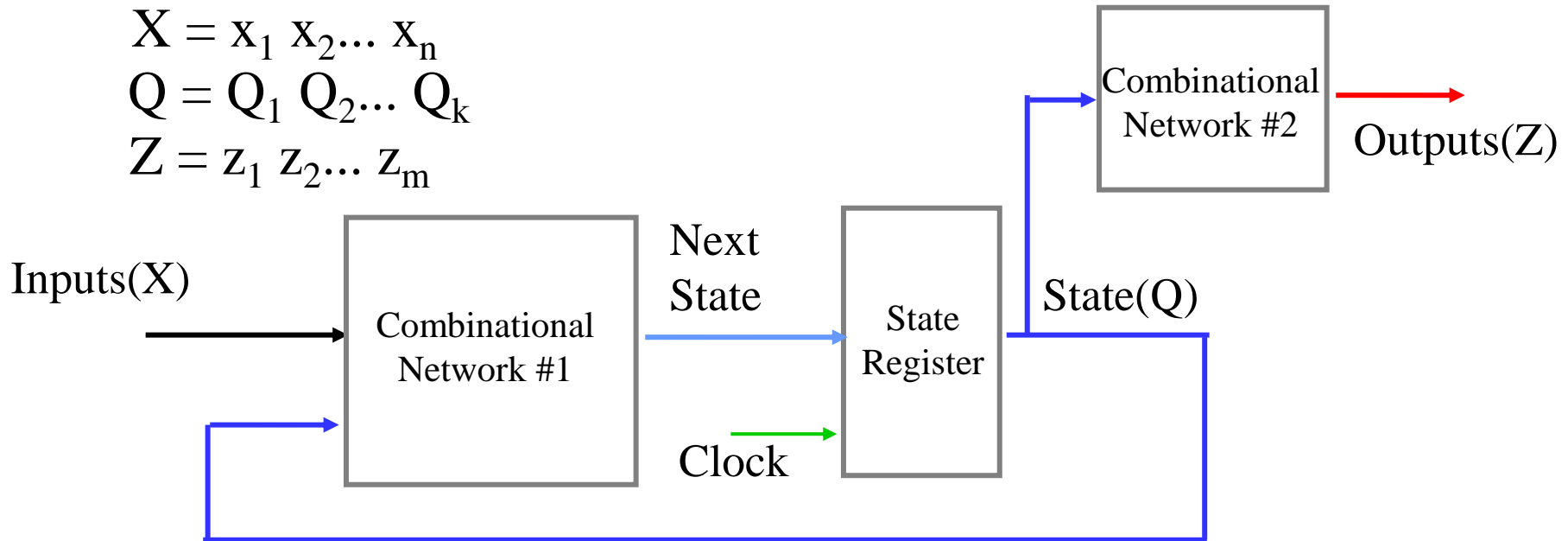


$$Q(t^+) = G(X(t), Q(t))$$

$$Z(t) = F(Q(t))$$

 
- (1) X inputs are changed to a new value
- (2) After a delay, the output of CN appears on the inputs of the state register
- (3) The next state is clocked into the state register resulting in a possible change in state, and possible new Z outputs appear after a CN delay

An Example: 8421 BCD to Excess3 Code Converter




X (inputs)				Z (outputs)			
t3	t2	t1	t0	t3	t2	t1	t0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0


Moore Machine

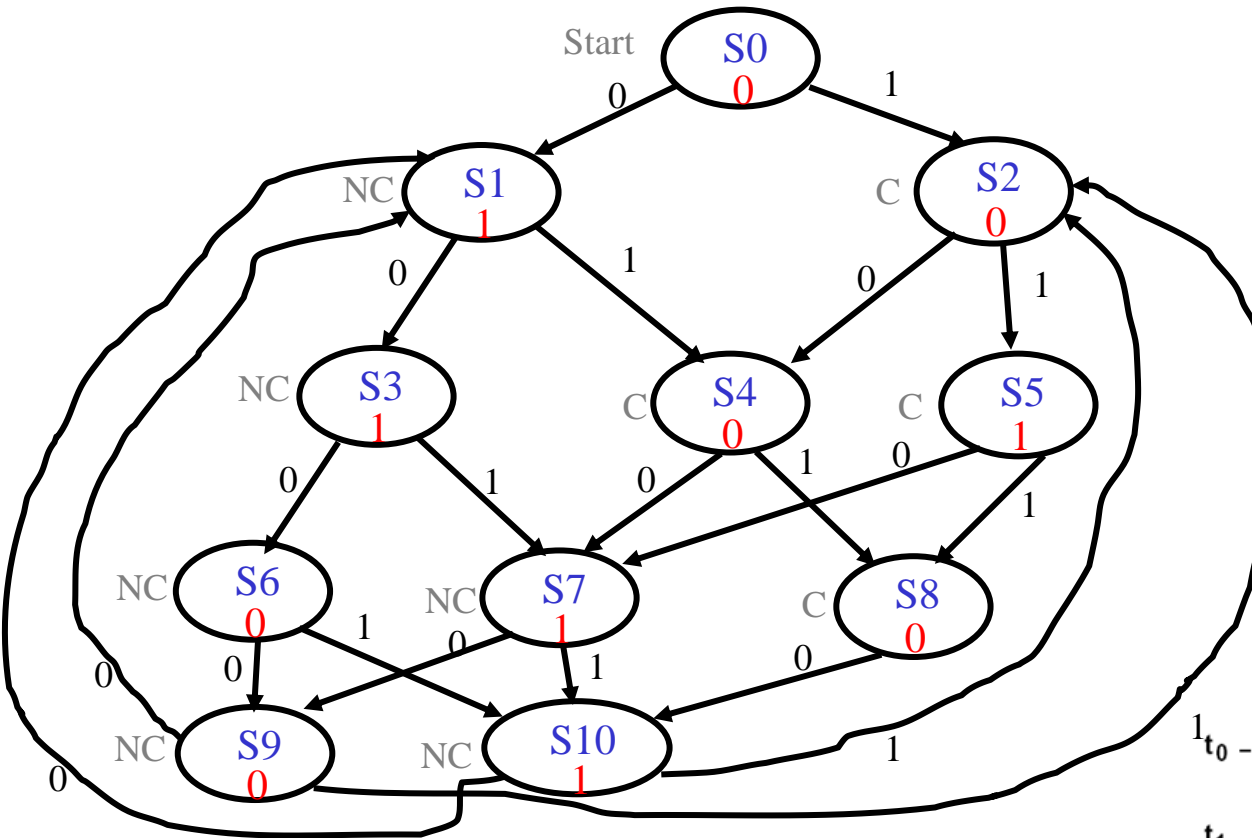

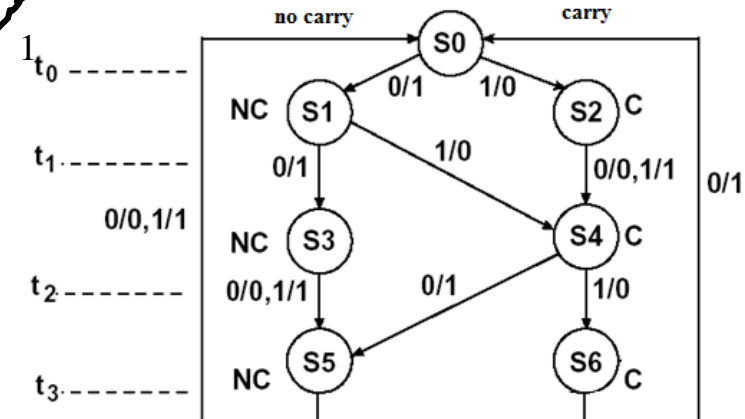Note: state S0 could be eliminated (S0 == S9), if S9 was start state!



Moore Machine

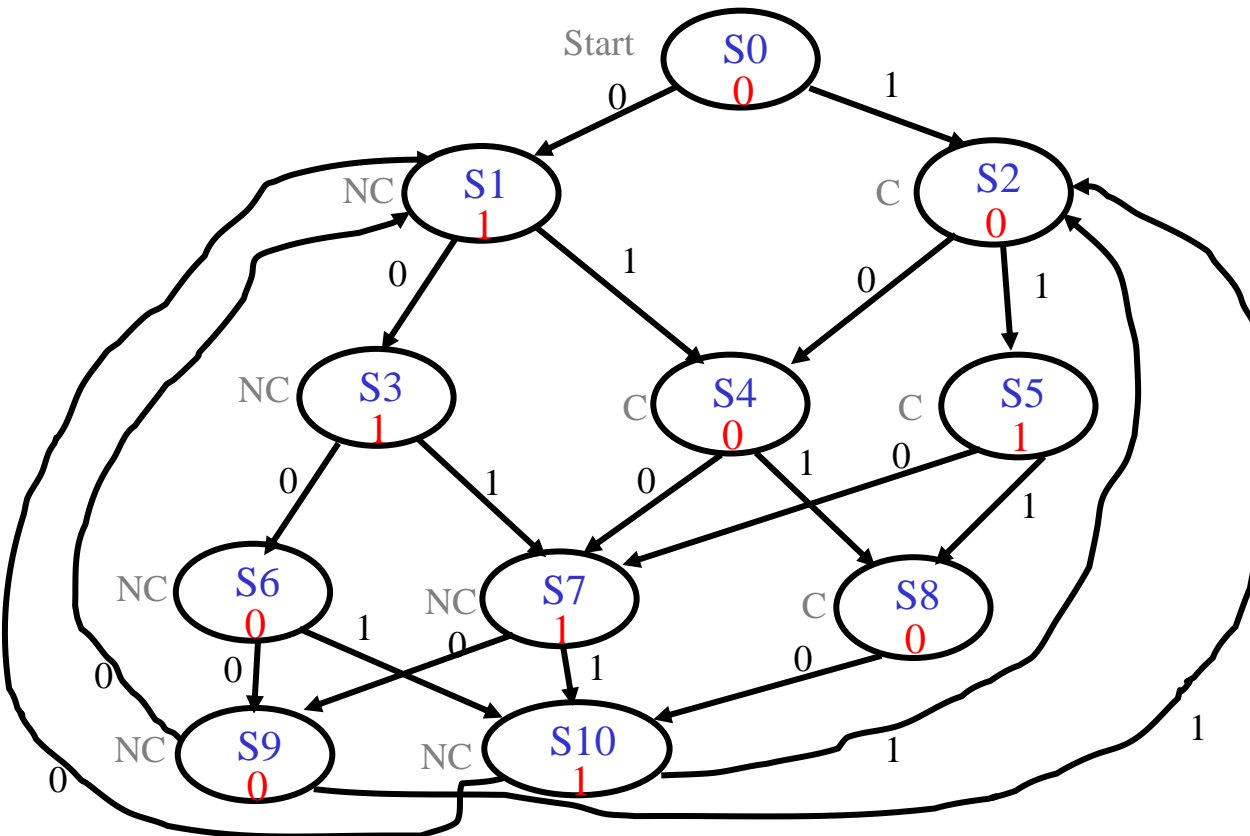

Note: state S0 could be eliminated
(S0 == S9), if S9 was start state!


PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1

FSM Timings


Differences between Mealy and Moore

- $X = 0010_1001 \Rightarrow Z = 1110_0011$

Mealy


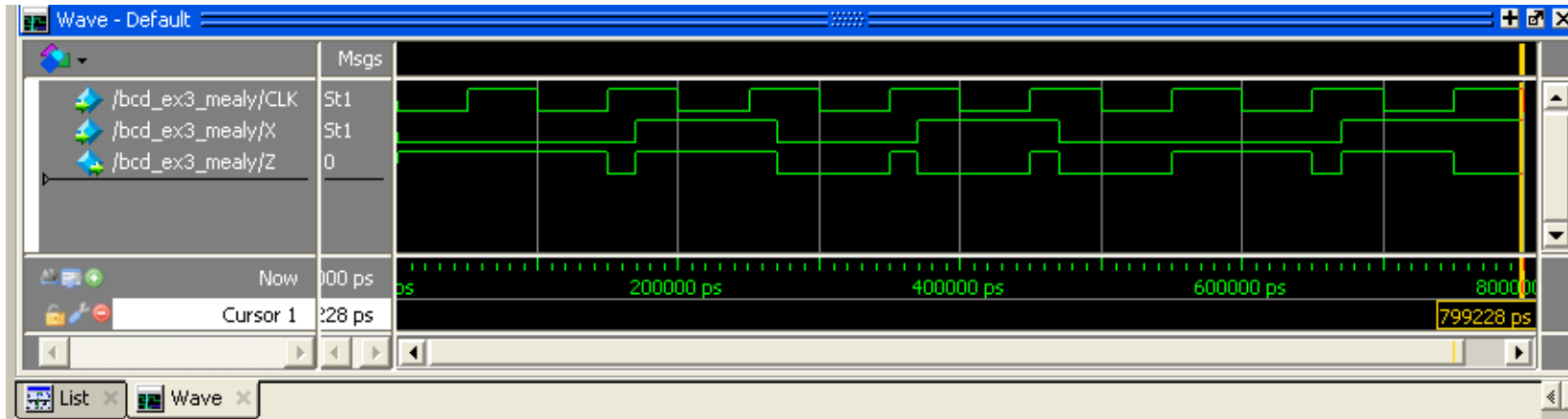


Moore

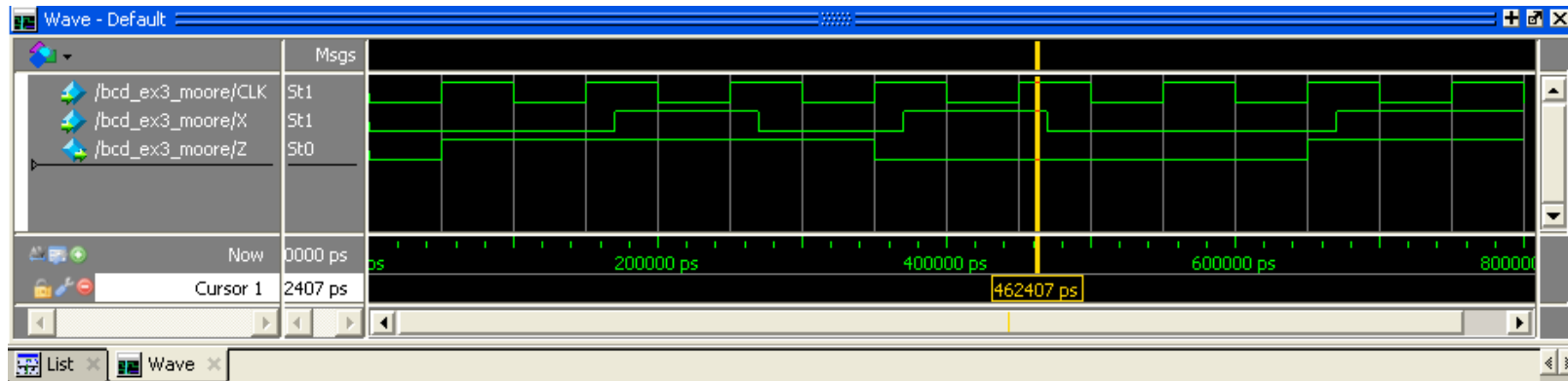

Behavioral Verilog HDL Model

 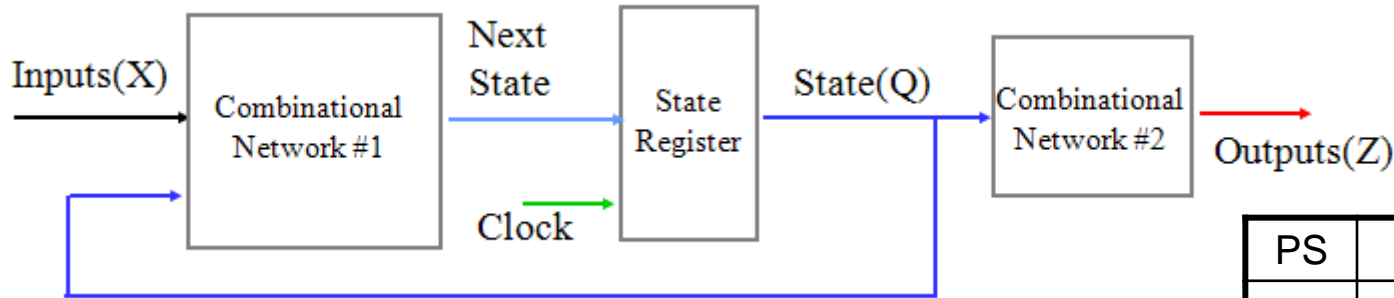8421 BCD to Excess3 Code Converter (Moore FSM)



```
// bcd to excess 3 converter
// Moore Implementation
// Behavioral Model
module bcd_ex3_moore(input X,CLK,output reg Z);
```

```
    reg [3:0] State=0,Nextstate=0;
```

```
    *
    *
    *
```


```
endmodule
```

PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1

Behavioral Verilog HDL Model

8421 BCD to Excess3 Code Converter (Moore FSM)

PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1

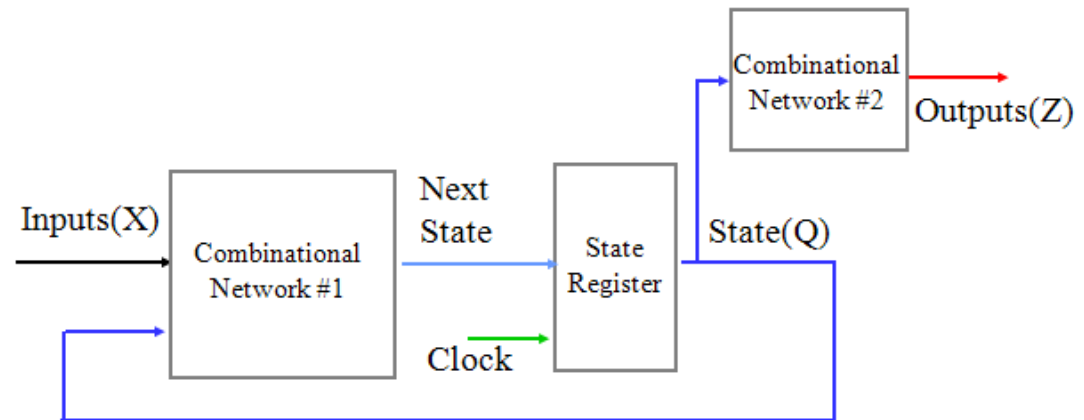

Behavioral Verilog HDL Model

8421 BCD to Excess3 Code Converter (Moore FSM)


PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1

```
// combinational Network #1
always @ (State,X)
    case (State)
        0 : if (!X) Nextstate=1;
            else Nextstate=2;
        1 : if (!X) Nextstate=3;
            else Nextstate=4;
        2 : if (!X) Nextstate=4;
            else Nextstate=5;
        3 : if (!X) Nextstate=6;
            else Nextstate=7;
        4 : if (!X) Nextstate=7;
            else Nextstate=8;
        5 : if (!X) Nextstate=7;
            else Nextstate=8;
        6 : if (!X) Nextstate=9;
            else Nextstate=10;
        7 : if (!X) Nextstate=9;
            else Nextstate=10;
        8 : Nextstate=10;
        9 : if (!X) Nextstate=1;
            else Nextstate=2;
        10: if (!X) Nextstate=1;
            else Nextstate=2;
        default : Nextstate=0;
    endcase
```

Behavioral Verilog HDL Model

8421 BCD to Excess3 Code Converter (Moore FSM)

PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1

 


```

// combinational Network #2
always @ (State)
  case (State)
    0 : Z=0;
    1 : Z=1;
    2 : Z=0;
    3 : Z=1;
    4 : Z=0;
    5 : Z=1;
    6 : Z=0;
    7 : Z=1;
    8 : Z=0;
    9 : Z=0;
    10: Z=1;
    default : Z=0;
  endcase
  
```

Behavioral Verilog HDL Model

8421 BCD to Excess3 Code Converter (Moore FSM)

PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1

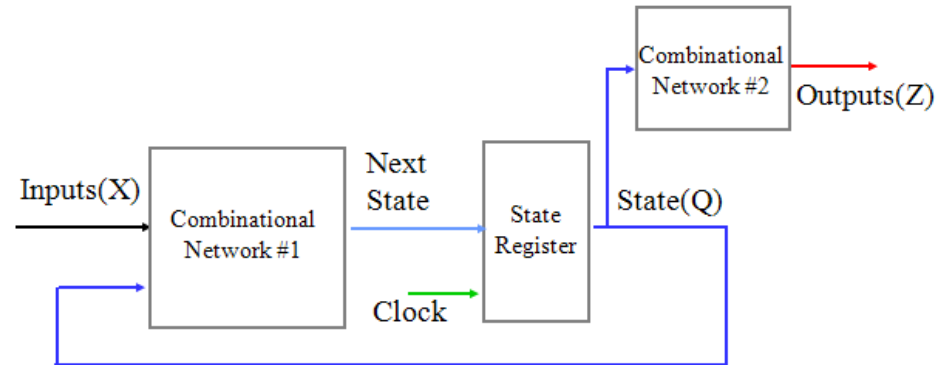

```
// State Reg Portion of Design
always @ (posedge CLK)
    State=Nextstate;
```


ModelSim™ Waveform

Behavioral 8421 BCD to Excess3 Code Converter (Moore FSM)


- $X = 0010_1001 \Rightarrow Z = 1110_0011$

- add wave CLK X Z

- force CLK 0 0 ns, 1 50 ns -r 100 ns

- force X 0 0 ns, 1 170 ns, 0 270 ns, 1 370 ns, 0 470 ns, 1 670 ns

- run 800 ns

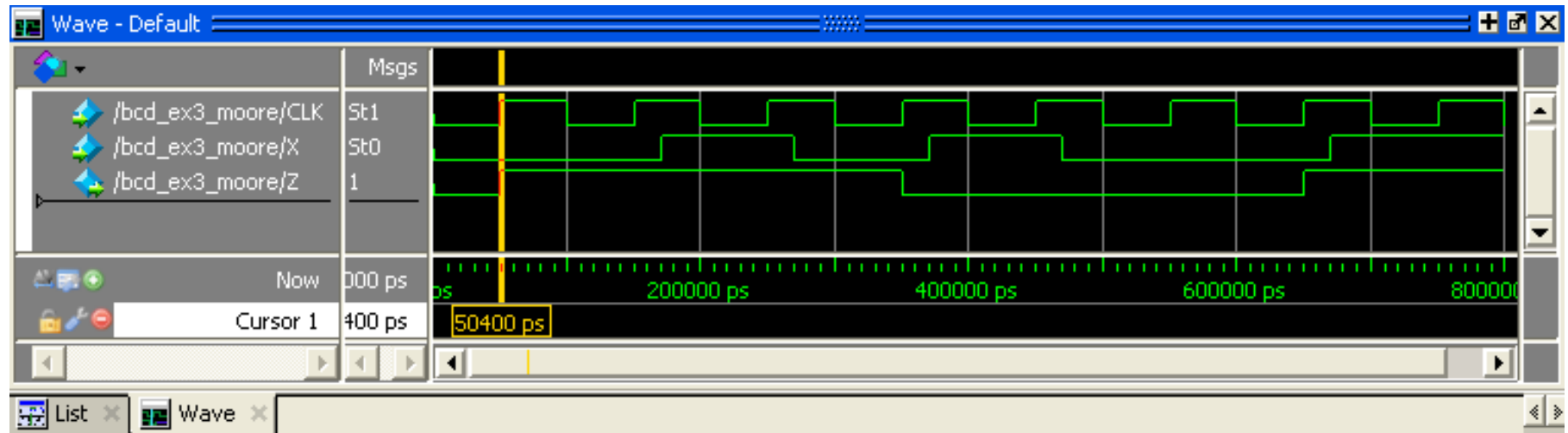

One-hot State Encoding

```
// bcd to excess 3 converter
// Moore Implementation
// Data Flow Model -- one hot state assignment
module bcd_ex3_moore(input X,CLK,output Z);
    // flip flop outputs
    reg Q0=1,Q1=0,Q2=0,Q3=0,Q4=0,Q5=0,Q6=0,Q7=0,Q8=0,Q9=0,Q10=0;

    // FF State Update Portion of design
    // Active only on rising edge of clock
    always @(posedge CLK)
        begin
            Q0 <= 0;
            Q1 <= (Q0 & ~X) | (Q9 & ~X) | (Q10 & ~X);
            Q2 <= (Q0 & X) | (Q9 & X) | (Q10 & X);
            Q3 <= Q1 & ~X;
            Q4 <= (Q1 & X) | (Q2 & ~X);
            Q5 <= Q2 & X;
            Q6 <= Q3 & ~X;
            Q7 <= (Q3 & X) | (Q4 & ~X) | (Q5 & ~X);
            Q8 <= (Q4 & X) | (Q5 & X);
            Q9 <= (Q6 & ~X) | (Q7 & ~X);
            Q10 <= (Q6 & X) | (Q7 & X) | (Q8 & ~X);
        end

    // Output Equation -- Continuous Assignment that is
    // a function only of the state variables QA,QB,QC,QD
    assign Z = Q1 | Q3 | Q5 | Q7 | Q10;

endmodule
```

PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1


• $X = 0010_1001 \Rightarrow Z = 1110_0011$

• add wave CLK X Z

• force CLK 0 0 ns, 1 50 ns -r 100 ns

• force X 0 0 ns, 1 170 ns, 0 270 ns, 1 370 ns, 0 470 ns, 1 670 ns

• run 800 ns

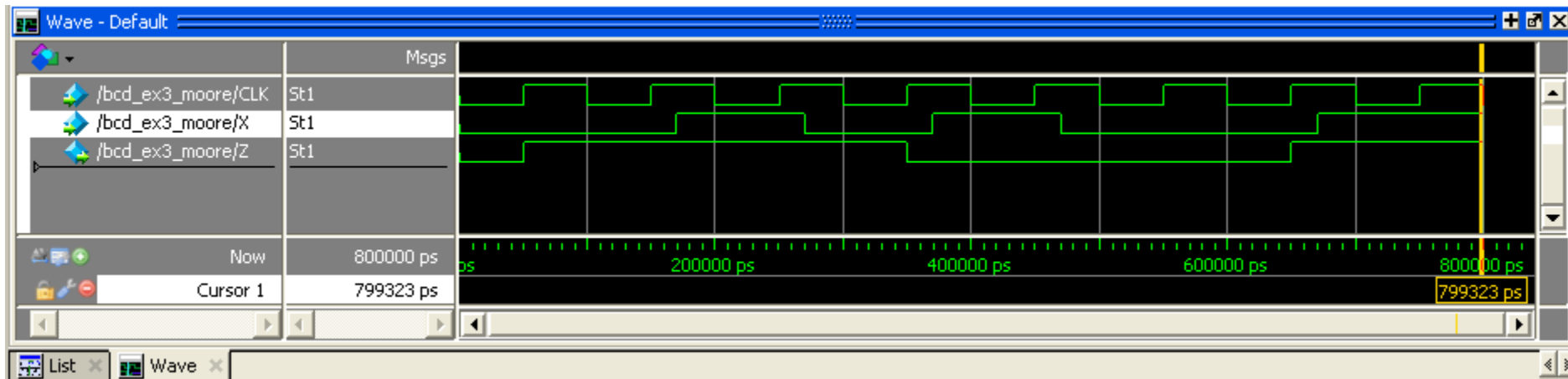

State Assignment Rules

- I. States which have the same next state (NS) for a given input should be given adjacent assignments (look at the columns of the state table).
 - II. States which are the next states of the same state should be given adjacent assignments (look at the rows).
 - III. States which have the same output for a given input should be given adjacent assignments.
-
- I. (1,2) (3,4) (5,6) (in the $X=1$ column, S_1 and S_2 both have NS S_4 ;
in the $X=0$ column, S_3 & S_4 have NS S_5 , and S_5 & S_6 have NS S_0)
 - II. (1,2) (3,4) (5,6) (S_1 & S_2 are NS of S_0 ; S_3 & S_4 are NS of S_1 ;
and S_5 & S_6 are NS of S_4)
 - III. (0,1,4,6) (2,3,5)

Moore State Table

Current state	Next state		Output	
	X=0	X=1		
S ₀	S ₁	S ₂	0	<u>Rule 1</u> (0, 9, 10) (4, 5) (6, 7)
S ₁	S ₃	S ₄	1	
S ₂	S ₄	S ₅	0	<u>Rule 2</u> (1, 2) (3, 4) (4, 5) (6, 7) (7, 8) (9, 10)
S ₃	S ₆	S ₇	1	
S ₄	S ₇	S ₈	0	<u>Rule 3</u> (1, 3, 5, 7, 10) (0, 2, 4, 6, 8, 9)
S ₅	S ₇	S ₈	1	
S ₆	S ₉	S ₁₀	0	
S ₇	S ₉	S ₁₀	1	
S ₈	S ₁₀	—	0	
S ₉	S ₁	S ₂	0	
S ₁₀	S ₁	S ₂	1	

state table

State Assignments

QA QB

QA QB	00	01	11	10
QC QD 00	S9	S10	S8	
01				S5
11		S1	S3	S4
10	S0	S2	S7	S6

Assignment Map

Assignments QA QB QC QD

$$S_0 = 0010$$

$$S_1 = 0111$$

$$S_2 = 0110$$

$$S_3 = 1111$$

$$S_4 = 1011$$

$$S_5 = 1001$$

$$S_6 = 1010$$

$$S_7 = 1110$$

$$S_8 = 1100$$

$$S_9 = 0000$$

$$S_{10} = 0100$$

Transition Diagram

	Current State				Next State								Output Z
	Q _A	Q _B	Q _C	Q _D	x=0				x=1				
	Q _A	Q _B	Q _C	Q _D	Q _A ⁺	Q _B ⁺	Q _C ⁺	Q _D ⁺	Q _A ⁺	Q _B ⁺	Q _C ⁺	Q _D ⁺	
s ₉	0	0	0	0	0	1	1	1	0	1	1	0	0
	0	0	0	1	-	-	-	-	-	-	-	-	-
s ₀	0	0	1	0	0	1	1	1	0	1	1	0	0
	0	0	1	1	-	-	-	-	-	-	-	-	-
s ₁₀	0	1	0	0	0	1	1	1	0	1	1	0	1
	0	1	0	1	-	-	-	-	-	-	-	-	-
s ₂	0	1	1	0	1	0	1	1	1	0	0	1	0
s ₁	0	1	1	1	1	1	1	1	1	0	1	1	1
	1	0	0	0	-	-	-	-	-	-	-	-	-
s ₅	1	0	0	1	1	1	1	0	1	1	0	0	1
s ₆	1	0	1	0	0	0	0	0	0	1	0	0	0
s ₄	1	0	1	1	1	1	1	0	1	1	0	0	0
s ₈	1	1	0	0	0	1	0	0	-	-	-	-	0
	1	1	0	1	-	-	-	-	-	-	-	-	-
s ₇	1	1	1	0	0	0	0	0	0	1	0	0	1
s ₃	1	1	1	1	1	0	1	0	1	1	1	0	1

Resulting Boolean Equations

If we make Flip-Flop next state Equations a function of Q_A, Q_B, Q_C, Q_D

$$Q_A^+ = m_6, m_7, m_9, m_{11}, m_{15}$$
$$Q_B^+ = m_0 + m_2 + m_4 + m_9 + m_{11} + m_{12} + m_7\bar{X} + m_{10}X + m_{14}X + m_{15}X$$
$$Q_C^+ = m_0 + m_2 + m_4 + m_7 + m_{15} + m_6\bar{X} + m_9\bar{X} + m_{11}\bar{X}$$
$$Q_D^+ = m_6 + m_7 + m_0\bar{X} + m_2\bar{X} + m_4\bar{X}$$

don't cares
 $m_1, m_3, m_5, m_8, m_{13}$

We can use map Entered variables in next state equations

Flip-flop Q_A

		Q_A^+			
		$Q_C Q_D$			
		00	01	11	10
$X \begin{array}{c} 1 \\ \diagdown \\ 0 \end{array}$	$Q_A Q_B$				
	00	\diagdown	-	-	\diagdown
	01	\diagdown	-	1	1
	11	-	-	1	\diagdown
	10	-	1	1	\diagdown
		-	1	1	\diagdown

$$Q_A^+ =$$

Flip-flop Q_A

		Q_A^+			
		$Q_C Q_D$			
		00	01	11	10
X	$Q_A Q_B$	00	01	11	10
	00	-	-	-	-
	01	-	-	1	1
	11	-	-	1	-
	10	-	1	1	-
		-	1	1	-

$$Q_A^+ = Q_D$$

Flip-flop Q_A

Q_A^+

		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00	-	-	-	-
	01	-	-	1	1
	11	-	-	1	-
	10	-	1	1	-

$X \begin{matrix} 1 \\ 0 \end{matrix}$

$$Q_A^+ = Q_D + Q_A' Q_B Q_C$$

Flip-flop Q_A

		Q_A^+			
		$Q_C Q_D$			
		00	01	11	10
$X \begin{matrix} 1 \\ 0 \end{matrix}$	$Q_A Q_B$ 00	-	-	-	-
	01	-	-	1	1
	11	-	-	1	-
	10	-	1	1	-

$$Q_A^+ = Q_D + Q_A' Q_B Q_C$$

Flip-flop Q_B

		Q_B^+			
		$Q_C Q_D$			
		00	01	11	10
$X \begin{array}{l} 1 \\ 0 \end{array}$	$Q_A Q_B$ 00	$\begin{array}{c} 1 \\ 1 \end{array}$	$\begin{array}{c} - \\ - \end{array}$	$\begin{array}{c} - \\ - \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$
	01	$\begin{array}{c} 1 \\ 1 \end{array}$	$\begin{array}{c} - \\ - \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$	
	11	$\begin{array}{c} - \\ 1 \end{array}$	$\begin{array}{c} - \\ - \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$
	10	$\begin{array}{c} - \\ - \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$

$Q_B^+ =$

Flip-flop Q_B

		Q_B^+			
		$Q_C Q_D$			
		00	01	11	10
X \ $\begin{matrix} 1 \\ 0 \end{matrix}$	$Q_A Q_B$ 00	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} - \\ - \end{matrix}$	$\begin{matrix} - \\ - \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$
	01	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} - \\ - \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$	
	11	$\begin{matrix} - \\ 1 \end{matrix}$	$\begin{matrix} - \\ - \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$
	10	$\begin{matrix} - \\ - \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$

$Q_B^+ = Q_C'$

Flip-flop Q_B

Q_B^+

$Q_C Q_D$

$Q_A Q_B$

X

	00	01	11	10
00	1	-	-	1
01	1	-	1	
11	1	-	1	1
10	-	1	1	1

$Q_B^+ = Q_C' + Q_A' Q_B'$

Flip-flop Q_B

Q_B^+

$Q_C Q_D$		Q_B^+			
		00	01	11	10
$Q_A Q_B$	00	1 1	- -	- -	1 1
	01	1 1	- -	1 1	
	11	- 1	- -	1 1	1 1
	10	- -	1 1	1 1	1 1

$Q_B^+ = Q_C' + Q_A' Q_B' + Q_A X$

Flip-flop Q_B

		Q_B^+			
		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00	1 1	- -	- -	1 1
	01	1 1	- -	- 1	- -
	11	- 1	- -	1 1	1 1
	10	- -	1 1	1 1	1 1

$$Q_B^+ = Q_C' + Q_A' Q_B' + Q_A X +$$

$$Q_A' Q_D X'$$

Flip-flop Q_B

Q_B^+

$Q_C Q_D$		00	01	11	10
$Q_A Q_B$	00	1 1	- -	- -	1 1
	01	1 1	- -	1 1	
	11	- 1	- -	1 1	1 1
	10	- -	1 1	1 1	1 1

$X \begin{matrix} 1 \\ 0 \end{matrix}$

$$Q_B^+ = Q_C' + Q_A' Q_B' + Q_A X + Q_A' Q_D X' + \textcolor{red}{Q_B' Q_D}$$

Flip-flop Q_B

Q_B^+

$Q_C Q_D$		Q_B^+			
		00	01	11	10
$Q_A Q_B$	00	1 1	- -	- -	1 1
	01	1 1	- -	1 1	
	11	- 1	- -	1 1	1 1
	10	- -	1 1	1 1	1 1

$X \begin{matrix} 1 \\ 0 \end{matrix}$

$$Q_B^+ = Q_C' + Q_A' Q_B' + Q_A X + Q_A' Q_D X' + Q_B' Q_D$$

Flip-flop Q_C

		Q_C^+				
		$Q_C Q_D$	00	01	11	10
X $\begin{matrix} 1 \\ 0 \end{matrix}$	$Q_A Q_B$	00	$\begin{matrix} 1 \\ 1 \end{matrix}$	-	-	$\begin{matrix} 1 \\ 1 \end{matrix}$
	01	$\begin{matrix} 1 \\ 1 \end{matrix}$	-	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$	
	11	-	-	$\begin{matrix} 1 \\ 1 \end{matrix}$		
	10	-	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$		

$Q_C^+ =$

Flip-flop Q_C

		Q_C^+			
		$Q_C Q_D$	00	01	11
$Q_A Q_B$	00	$\begin{array}{c} \diagup 1 \\ 1 \diagdown \end{array}$	-	-	$\begin{array}{c} \diagup 1 \\ 1 \diagdown \end{array}$
	01	$\begin{array}{c} \diagup 1 \\ 1 \diagdown \end{array}$	$\begin{array}{c} - \\ - \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$	$\begin{array}{c} \diagup 1 \\ 1 \diagdown \end{array}$
	11	$\begin{array}{c} \diagup - \\ - \diagdown \end{array}$	$\begin{array}{c} - \\ - \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$	$\begin{array}{c} \diagup - \\ - \diagdown \end{array}$
	10	$\begin{array}{c} \diagup - \\ - \diagdown \end{array}$	$\begin{array}{c} - \\ - \end{array}$	$\begin{array}{c} 1 \\ 1 \end{array}$	$\begin{array}{c} \diagup - \\ - \diagdown \end{array}$

$$Q_C^+ = Q_D X'$$

Flip-flop Q_C

		Q_C^+			
		$Q_C Q_D$	00	01	11
$Q_A Q_B$	00	$\begin{array}{c} 1 \\ 1 \end{array}$	-	-	$\begin{array}{c} 1 \\ 1 \end{array}$
	01	$\begin{array}{c} 1 \\ 1 \end{array}$	-	1	1
	11	-	-	1	
	10	-	1	1	

$$Q_C^+ = Q_D X' + Q_A' Q_B'$$

Flip-flop Q_C

		Q_C^+				
		$Q_C Q_D$	00	01	11	10
$Q_A Q_B$	00	<div><div></div><div>1</div><div>1</div></div>	-	-	-	<div><div></div><div>1</div><div>1</div></div>
	01	<div><div></div><div>1</div><div>1</div></div>	-	-	1	1
	11	-	-	-	1	-
	10	-	-	1	1	-

$$Q_C^+ = Q_D X' + Q_A' Q_B' + Q_A' Q_C'$$

Flip-flop Q_C

		Q_C^+				
		$Q_C Q_D$	00	01	11	10
$X \begin{matrix} 1 \\ 0 \end{matrix}$	$Q_A Q_B$	00	$\begin{matrix} 1 \\ 1 \end{matrix}$	-	-	$\begin{matrix} 1 \\ 1 \end{matrix}$
	01	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} - \\ - \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$	$\begin{matrix} 1 \\ 1 \end{matrix}$
	11	-	-	-	$\begin{matrix} 1 \\ 1 \end{matrix}$	-
	10	-	-	$\begin{matrix} 1 \\ 1 \end{matrix}$	-	-

$$Q_C^+ = Q_D X' + Q_A' Q_B' + Q_A' Q_C' + Q_B Q_D$$

Flip-flop Q_C

		Q_C^+			
		$Q_C Q_D$	00	01	11
$Q_A Q_B$	00	$\begin{array}{c} \diagup \\ 1 \end{array}$	-	-	$\begin{array}{c} \diagdown \\ 1 \end{array}$
	01	$\begin{array}{c} 1 \\ \diagdown \end{array}$	-	$\begin{array}{c} 1 \\ \diagup \end{array}$	$\begin{array}{c} 1 \\ \diagdown \end{array}$
	11	-	-	$\begin{array}{c} 1 \\ \diagup \end{array}$	
	10	-	$\begin{array}{c} 1 \\ \diagup \end{array}$	$\begin{array}{c} 1 \\ \diagdown \end{array}$	

$$Q_C^+ = Q_D X' + Q_A' Q_B' + Q_A' Q_C' + Q_B Q_D + \textcolor{red}{Q_A' X'}$$

Flip-flop Q_C

$Q_C Q_D$ Q_C^+
 00 01 11 10

$Q_A Q_B$
 00
 01
 11
 10

$X \begin{matrix} 1 \\ 0 \end{matrix}$

00	1	-	-	1
01	1	-	1	1
11	-	-	1	-
10	-	1	1	-

$$Q_C^+ = Q_D X' + Q_A' Q_B' + Q_A' Q_C' + Q_B Q_D + Q_A' X'$$

Flip-flop Q_D

Q_D^+

		$Q_C Q_D$			
		00	01	11	10
$X \begin{matrix} 1 \\ 0 \end{matrix}$	$Q_A Q_B$				
	00	$\begin{matrix} \diagdown \\ 1 \end{matrix}$	$\begin{matrix} \diagdown \\ - \end{matrix}$	$\begin{matrix} \diagdown \\ - \end{matrix}$	$\begin{matrix} \diagdown \\ 1 \end{matrix}$
	01	$\begin{matrix} \diagdown \\ 1 \end{matrix}$	$\begin{matrix} \diagdown \\ - \end{matrix}$	$\begin{matrix} \diagdown \\ 1 \\ 1 \end{matrix}$	$\begin{matrix} \diagdown \\ 1 \\ 1 \end{matrix}$
	11	$\begin{matrix} \diagdown \\ - \end{matrix}$	$\begin{matrix} \diagdown \\ - \end{matrix}$	$\begin{matrix} \diagdown \\ \end{matrix}$	$\begin{matrix} \diagdown \\ \end{matrix}$
	10	$\begin{matrix} \diagdown \\ - \\ - \end{matrix}$	$\begin{matrix} \diagdown \\ \end{matrix}$	$\begin{matrix} \diagdown \\ \end{matrix}$	$\begin{matrix} \diagdown \\ \end{matrix}$
		$Q_D^+ =$			

Flip-flop Q_D

Q_D^+

		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00	1	-	-	1
	01	1	-	1	1
	11	-	-		
	10	-			

$Q_D^+ = Q_A' X'$

Flip-flop Q_D

Q_D^+

		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00	1	-	-	1
	01	1	-	1	1
	11	-	-		
	10	-	-		

$X \begin{matrix} 1 \\ 0 \end{matrix}$

$$Q_D^+ = Q_A'X' + Q_A'Q_BQ_C$$

Flip-flop Q_D

Q_D^+

		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00	1	-	-	1
	01	1	-	1	1
	11	-	-		
	10	-			

$X \begin{matrix} 1 \\ 0 \end{matrix}$

$$Q_D^+ = Q_A'X' + Q_A'Q_BQ_C$$

Output Z

		Z			
		$Q_C Q_D$			
$Q_A Q_B$		00	01	11	10
	00		-	-	
	01	1	-	1	
	11		-	1	1
	10	-	1		

Z=

Output Z

Z

$Q_A Q_B$ \ $Q_C Q_D$		Z			
		00	01	11	10
00			-	-	
01	1		-	1	
11			-	1	1
10	-		1		

$$Z = Q_C' Q_D$$

Output Z

		Z			
		$Q_C Q_D$			
$Q_A Q_B$		00	01	11	10
	00		-	-	
	01	1	-	1	
	11		-	1	1
	10	-	1		

$$Z = Q_C' Q_D + Q_A Q_B Q_C$$

Output Z

		Z			
		$Q_C Q_D$			
$Q_A Q_B$		00	01	11	10
	00		-	-	
	01	1	-	1	
	11		-	1	1
	10	-	1		

$$Z = Q_C'Q_D + Q_AQ_BQ_C + Q_A'Q_BQ_C'$$

Output Z

Z

$Q_A Q_B$ \ $Q_C Q_D$		$Q_C Q_D$			
		00	01	11	10
00			-	-	
01	1		-	1	
11			-	1	1
10	-		1		

$$Z = Q_C'Q_D + Q_AQ_BQ_C + Q_A'Q_BQ_C' + \textcolor{red}{Q_BQ_D}$$

Output Z


Z

$Q_A Q_B$ \ $Q_C Q_D$		$Q_C Q_D$			
		00	01	11	10
00			-	-	
01	1		-	1	
11			-	1	1
10	-		1		

$$Z = Q_C'Q_D + Q_AQ_BQ_C + Q_A'Q_BQ_C' + Q_BQ_D$$

Quartus II Schematic Realization

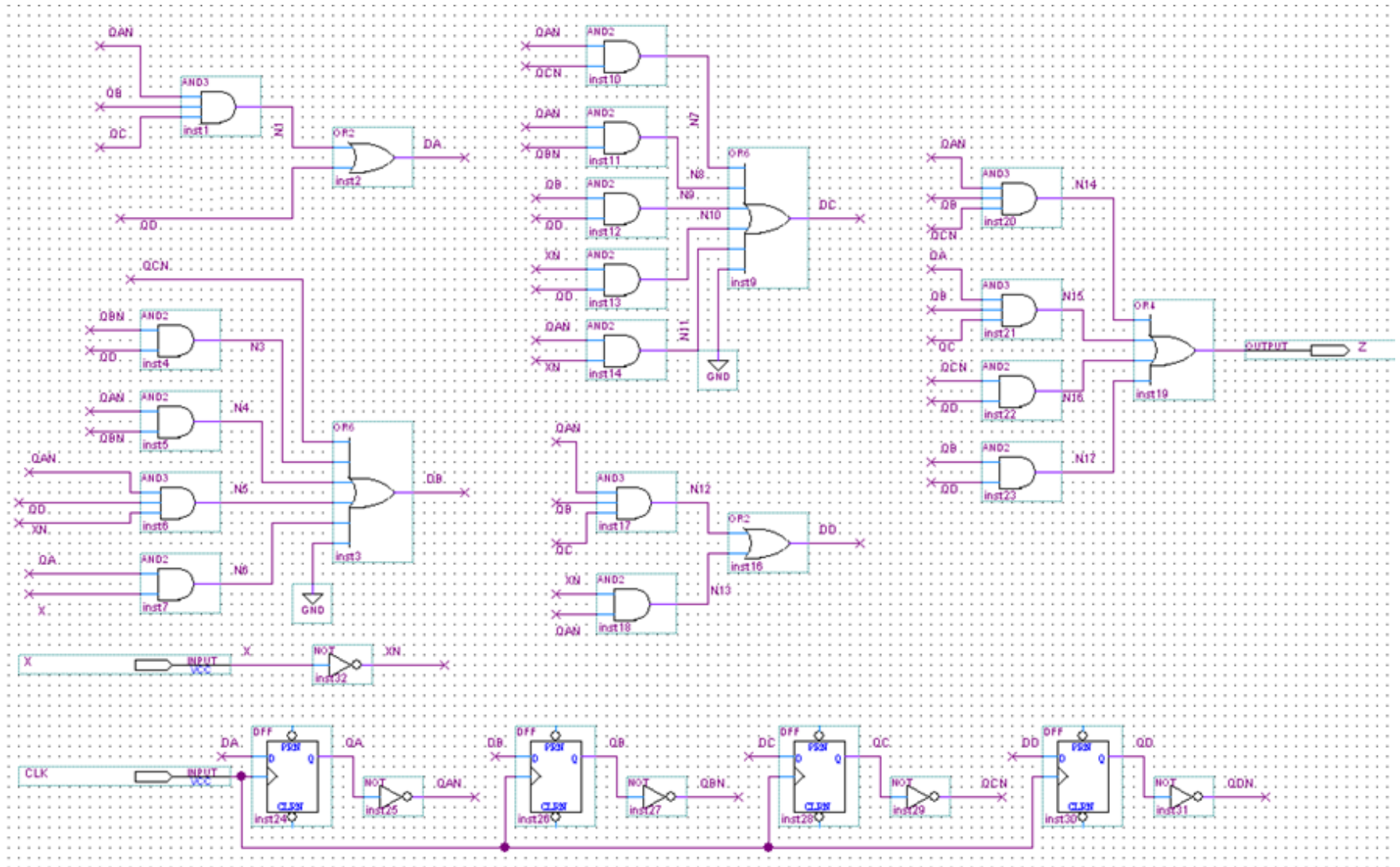8421 BCD to Excess3 Code Converter (Moore FSM)



Data Flow Representation Verilog HDL

8421 BCD to Excess3 Code Converter (Moore FSM)

```
// bcd to excess 3 converter
// Moore Implementation
// Data Flow Model
module bcd_ex3_moore(input X,CLK,output Z);

    reg QA=0,QB=0,QC=0,QD=0;

    // FF State Update Portion of design
    // Active only on rising edge of clock
    always @(posedge CLK)
        begin
            QA <= QD | (~QA & QB & QC);
            QB <= ~QC | (~QA & ~QB) | (QA & X) | (~QA & QD & ~X) | (~QB & QD);
            QC <= (QD & ~X) | (~QA & ~QB) | (~QA & ~QC) | (QB & QD) | (~QA & ~X);
            QD <= (~QA & ~X) | (~QA & QB & QC);
        end

    // Output Equation -- Continuous Assignment that is
    // a function only of the state variables QA,QB,QC,QD
    assign Z = (~QC & QD) | (QA & QB & QC) | (~QA & QB & ~QC) | (QB & QD);

endmodule
```

ModelSim™ Waveform

Data Flow 8421 BCD to Excess3 Code Converter (Moore FSM)

- $X = 0010_1001 \Rightarrow Z = 1110_0011$

- add wave CLK X Z
- force CLK 0 0 ns, 1 50 ns -r 100 ns
- force X 0 0 ns, 1 170 ns, 0 270 ns, 1 370 ns, 0 470 ns, 1 670 ns
- run 800 ns

