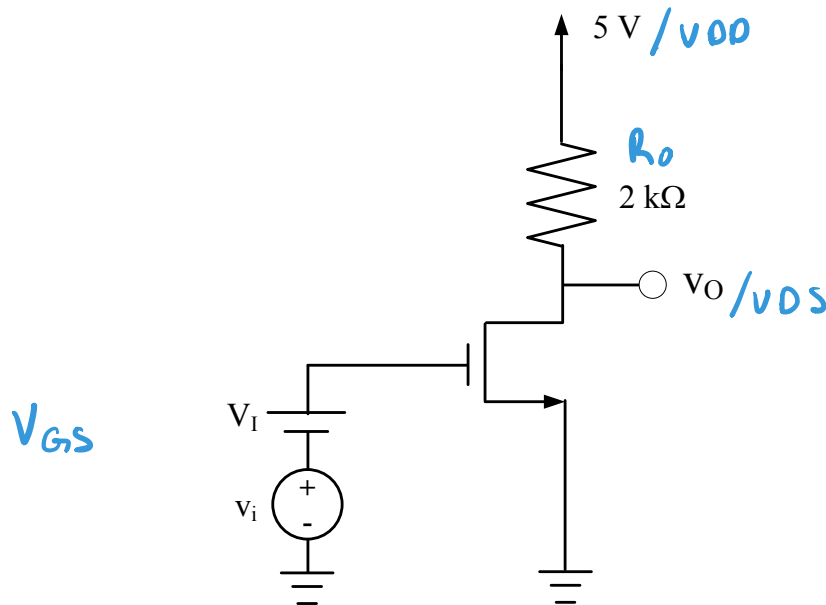


Print Your Name _____

1. [25 points] Consider the following circuit where $V_t = 1\text{V}$, and $k'_n(W/L) = 1\text{mA/V}^2$.



- a. [10 points] Find transition points A and B and plot the voltage transfer characteristic (VTC). Use the axes on the next page and label the plot clearly including each axis. Assume that $\lambda = 0$ for the DC biasing.

Point A: $V_I = V_t = 1\text{V}$
 $V_O = V_{DD} = 5\text{V}$

Point B:

$$V_O(V_{DS}) = V_I(V_{GS}) - V_t$$

$$V_I = V_{GS} = V_t + \frac{\sqrt{1 + 2(R_o k'_n \frac{W}{L} V_{DD})} - 1}{R_o k'_n \frac{W}{L}}$$

$$V_I = 2.791\text{V}$$

$$V_O = V_{DS} = V_I - V_t$$

$$V_O = 1.791\text{V}$$

Point C

$$V_{GS} = V_I = V_{DD} = 5\text{V}$$

$$V_{DS} = V_O = \frac{V_{GS}}{1 + R_o k'_n \frac{W}{L} (V_{GS} - V_t)}$$

$$V_O = \frac{5\text{V}}{1 + (1)(2)(5 - 1)}$$

$$V_O = 0.5556\text{V}$$



A: (5, 1)

B: (1.791, 2.791)

C: (0.5556, 5)

Print Your Name _____

1. [continued]

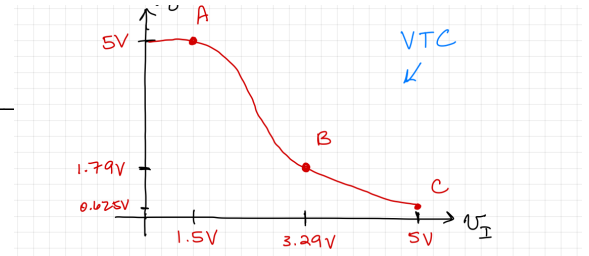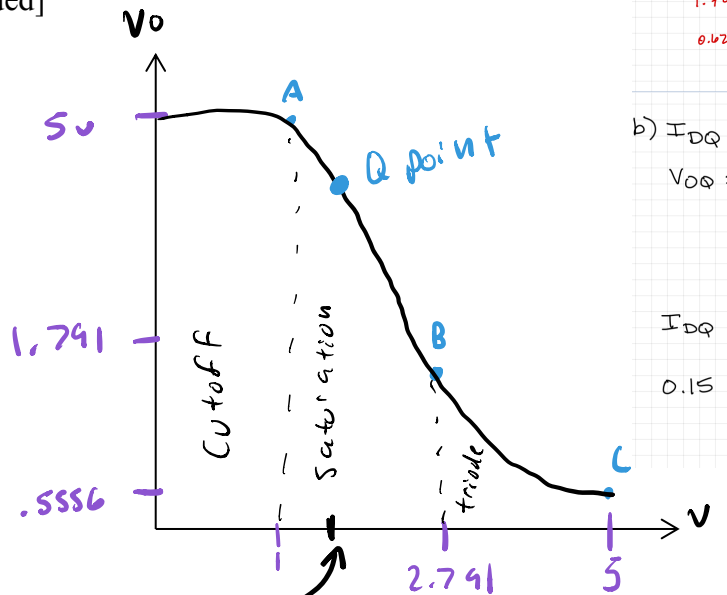

b) $I_{DQ} = 0.15 \text{ mA}$

$$V_{OQ} = V_{DSQ} = V_{DD} - I_{DQ} R_D$$

$$= 5 - (0.15)(10)$$

$$V_{OQ} = 3.5 \text{ V}$$

$$V_{IQ} = V_{GSQ}$$

$$I_{DQ} = \frac{1}{2} k'_n \frac{W}{L} (V_{IQ} - V_t)^2$$

$$0.15 = \frac{1}{2} (1.2) (V_{IQ} - 1.5)^2$$

$$V_{IQ} = 2.72 \text{ V}$$

b. [5 points] If $V_{GSQ} = 1.5 \text{ V}$ find V_{OQ} and I_{DQ} . Label the Q-point on the plot above.

$$V_{GSQ} = 1.5 \text{ V}$$

$$I_{DQ} = \frac{1}{2} k'_n \frac{W}{L} (V_{GSQ} - V_t)^2$$

$$I_{DQ} = \frac{1}{2} (1) (1.5 - 1)^2 = .125 \text{ mA}$$

$$V_{OQ} = V_{DD} - I_{DQ} R_D = 5 - (.125)(2) = 4.75 \text{ V}$$

$$Q \text{ point} = (1.5, 4.75)$$

c. [5 points] Draw the small signal model and find the voltage gain, v_o/v_i . Let $r_o = 200 \text{ k}\Omega$.


$$A_{v_o} = \frac{v_o}{v_i} = -g_m R_D$$

$$A_{v_o} = -\left(k'_n \frac{W}{L} (V_{GSQ} - V_t)\right) R_D$$

$$A_{v_o} = -\left(1(1.5 - 1)\right)(200000)$$

$$A_{v_o} = -.909 \text{ V}$$

$$\frac{r_o R_D}{r_o + R_D}$$

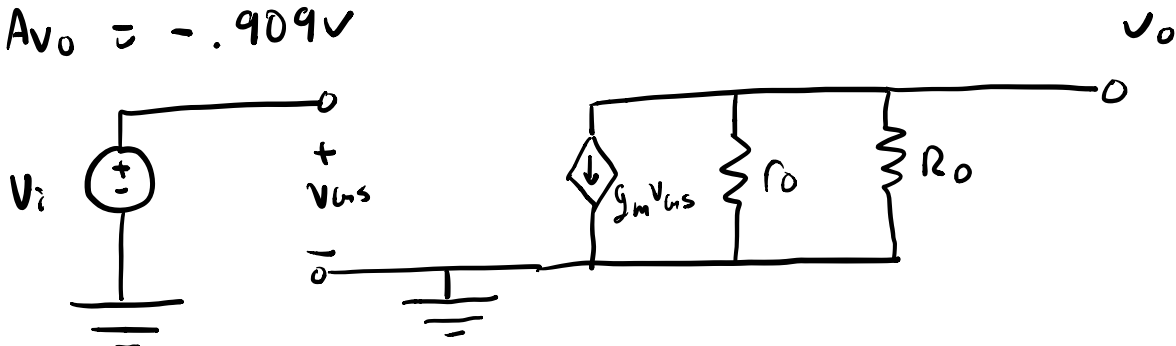

Print Your Name _____

$$V_{DSmin} = V_{GSmax} - V_t$$

$$V_{DSQ} - V_{DS} = V_{GSQ} + V_{GS} - V_t$$

$$|A_v| V_i = V_{GSQ} + V_i - V_t$$

$$-|A_v| V_i = V_i - V_t$$

$$V_i + |A_v| V_i = V_t$$

$$V_i = \frac{V_t}{1 + |A_v|}$$

$V_i = \frac{1.5}{1 + 3.3}$
 $V_i = 0.38V$
 large input signal and keep in saturation w/o distorting output

1. [continued]

- d. [5 points] What is the largest (peak) value of a sinusoid (small signal) that can be applied at the input such that the transistor remains in saturation?

$$V_{DSmin} = V_{GSmax} - V_t$$

$$V_{DSQ} - V_{DS} = V_{GSQ} + V_{GS} - V_t$$

$$V_{DSQ} - |A_v| V_i = V_{GSQ} + V_i - V_t$$

$$V_i = \frac{V_t}{1 + |A_v|}$$

\leftarrow given
 \leftarrow voltage gain.

$$V_i = \frac{1}{1 + 1.909}$$

$$V_i = 0.5238V$$

2. [10 points] A PMOS transistor has $V_t = -2V$, $k'_p(W/L) = 90 \mu A/V^2$, $V_{SG} = 4V$ and $V_{SD} = 3V$.

- a. [5 points] Calculate the drain current, I_D , and resistance, r_o , for: $\lambda = 0$

$$I_D = \frac{1}{2} k'_p \left(\frac{W}{L} \right) (V_{GS} - |V_t|)^2$$

$$I_D = \frac{1}{2} (90 \mu A/V^2) (4 - 2)^2$$

$$I_D = 180 \mu A \quad .000180A$$

$$r_o = \frac{1}{\lambda I_D} = \infty / \text{undefined.}$$

- b. [5 points] Calculate the drain current, I_D , and resistance, r_o , for: $V_A = 50V$

$$r_o = \frac{V_A}{I_D} = \frac{50}{.000180} = 277.7 k\Omega$$

$$\lambda = \frac{1}{V_A} = .02$$

$$I_D' = I_D (1 + .02 - 3) = -.356 mA$$

Metric Prefix	Symbol	Multiplier (Traditional Notation)	Exponential	Description
Yotta	Y	1,000,000,000,000,000,000,000,000	10^{24}	Septillion
Zetta	Z	1,000,000,000,000,000,000,000,000	10^{21}	Sextillion
Exa	E	1,000,000,000,000,000,000,000	10^{18}	Quintillion
Peta	P	1,000,000,000,000,000,000	10^{15}	Quadrillion
Tera	T	1,000,000,000,000,000	10^{12}	Trillion
Giga	G	1,000,000,000,000	10^9	Billion
Mega	M	1,000,000,000	10^6	Million
kilo	k	1,000	10^3	Thousand
hecto	h	100	10^2	Hundred
deca	da	10	10^1	Ten
base	b	1	10^0	One
deci	d	1/10	10^{-1}	Tenth
centi	c	1/100	10^{-2}	Hundredth
milli	m	1/1,000	10^{-3}	Thousandth
micro	μ	1/1,000,000	10^{-6}	Millionth
nano	n	1/1,000,000,000	10^{-9}	Billionth
pico	p	1/1,000,000,000,000	10^{-12}	Trillionth
femto	f	1/1,000,000,000,000,000	10^{-15}	Quadrillionth
atto	a	1/1,000,000,000,000,000,000	10^{-18}	Quintillionth
zepto	z	1/1,000,000,000,000,000,000,000	10^{-21}	Sextillionth
yocto	y	1/1,000,000,000,000,000,000,000,000	10^{-24}	Septillionth

Print Your Name _____

3. [20 points] You are given a common gate amplifier using an NMOS transistor for which $V_t = 0.8\text{V}$, $k'_n(W/L) = 2\text{mA/V}^2$, and $\lambda = 0$. The Q-point is at $V_{GSQ} = 1.5\text{V}$. There is a drain resistance, $R_D = 4.7\text{k}\Omega$ and a load resistance, $R_L = 10\text{k}\Omega$. The amplifier is driven by a signal source, v_{sig} , in series with a signal resistance, R_{sig} , $400\ \Omega$.

- a. [5 points] Find I_{DQ} and g_m .

$$I_{DQ} = \frac{1}{2} k'_n \frac{W}{L} (V_{GSQ} - V_t)^2 = \frac{1}{2} (2\text{mA}) (1.5 - 0.8)^2 = .49\text{mA}$$

$$I_{DQ} = .49\text{mA}$$

$$g_m = k'_n \frac{W}{L} (V_{GSQ} - V_t) = (2\text{mA}) (1.5 - 0.8) = 1.4$$

- b. [15 points] Draw the small-signal model (use the T-model). Label and solve for the input resistance, R_{in} , the output resistance, R_o , the open-loop voltage gain, A_{vo} , and the overall voltage gain, G_v . You must derive the equations for A_{vo} and G_v (i.e. don't just write equations from your cheat sheet).

$$R_{in} = 1/1.4 = 714.29\ \Omega$$

R_o

A_{vo}

G_v

$$G_v = \frac{R_o \parallel R_L}{R_{sig} + 1/g_m} = \frac{(4.7\text{k}\Omega \parallel 10\text{k}\Omega)}{400 + 714.29\ \Omega}$$


$$G_v = \frac{3197\ \Omega}{400 + 714.29} = 2.87$$

$$A_{vo} = g_m \cdot R_o = .0014(4.7\text{k}\Omega) = 6.58\text{V/V}$$

$$R_o = R_D = 4.7\text{k}\Omega$$

Print Your Name _____

3. [continued]

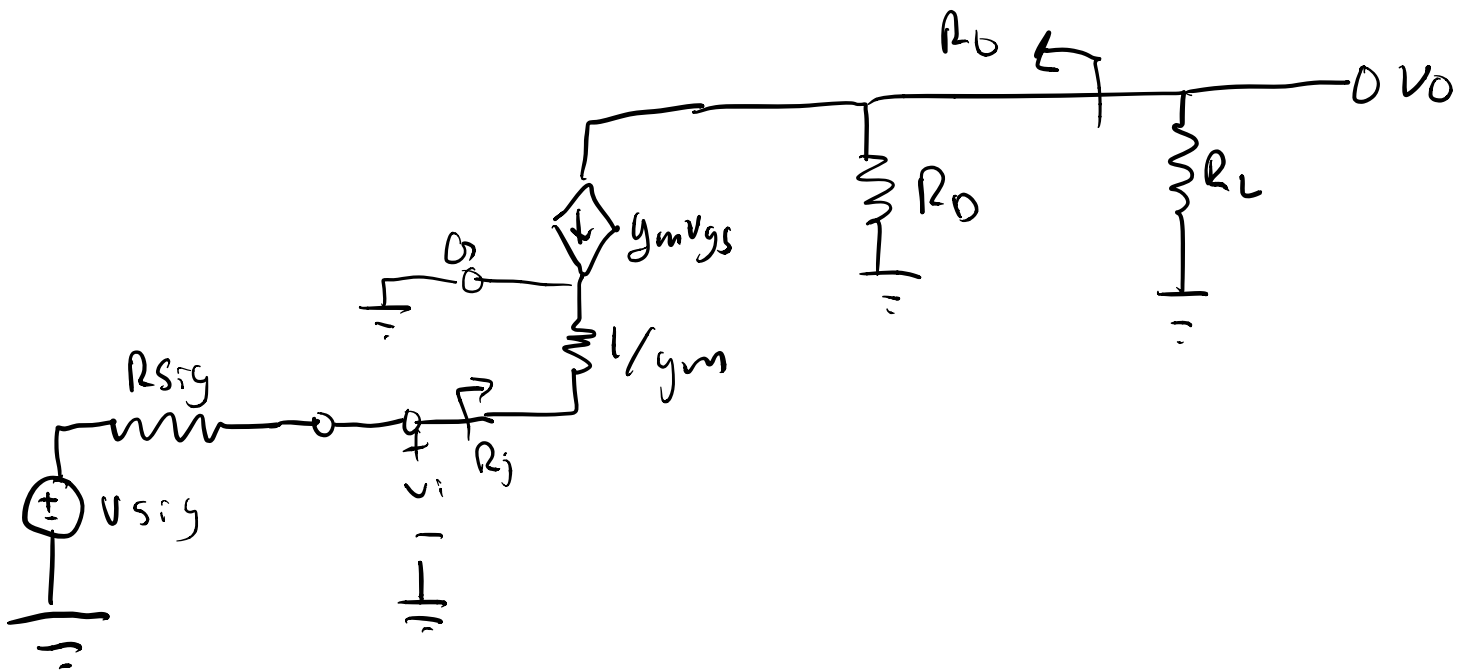

4. [10 points] Consider the circuit given where $V_t = -1.2\text{V}$, $k'_p(W/L) = 150 \mu\text{A/V}^2$, and $\lambda = 0$. Design the resistor, R , such that $V_{GS} = 2.1\text{V}$.


$$\begin{aligned} V_t &= V_{SG} = -1.2\text{V} \\ k'_n(W/L) &= 150 \mu\text{A/V}^2 \\ \lambda &= 0 \\ R &=? \\ V_{GS} &= 2.1\text{V} \end{aligned}$$

$$\begin{aligned} I_D &= \frac{1}{2} (150) (2.1 - 1.2)^2 \\ I_D &= 60.75 \mu\text{A} \end{aligned}$$

$$\begin{aligned} V_D &= V_S - V_{GS} \\ V_D &= 1.4\text{V} \end{aligned}$$

$$R = \frac{V_D}{I_D} = \frac{1.4}{60.75 \times 10^{-6}}$$

$$R = 23.05 \text{ k}\Omega$$

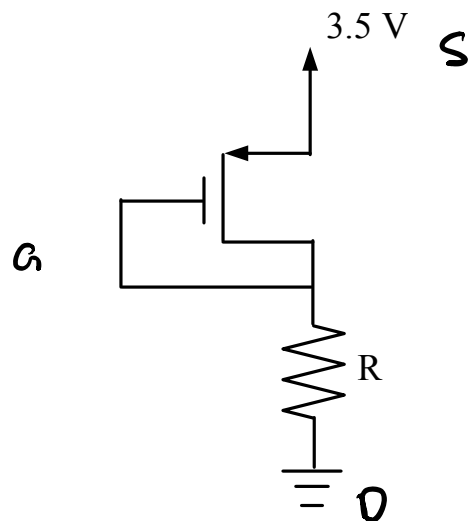

Print Your Name _____

5. [20 points] A common source amplifier is fed with a $0.5 \text{ M}\Omega$ source and connected to a $15 \text{ k}\Omega$ load. The MOSFET has $V_t = 1.5 \text{ V}$, $k'_n(W/L) = 2 \text{ mA/V}^2$, and $V_A = 30 \text{ V}$. The circuit is DC-biased at $I_{DQ} = 0.5 \text{ mA}$. The drain resistor is $8 \text{ k}\Omega$ and the load resistor is $10 \text{ k}\Omega$. Draw the small signal model and find the overall voltage gain, G_v , the output resistance, R_o , and the input resistance, R_{in} .

$0.5 \text{ M}\Omega$ source

$15 \text{ k}\Omega$ load

$V_t = 1.5 \text{ V}$ $k'_n \frac{W}{L} = 2 \text{ mA/V}^2$

G_v


R_o

R_{in}

$I_{DQ} = 0.5 \text{ mA}$

$R_D = 8 \text{ k}\Omega$

$R_L = 10 \text{ k}\Omega$

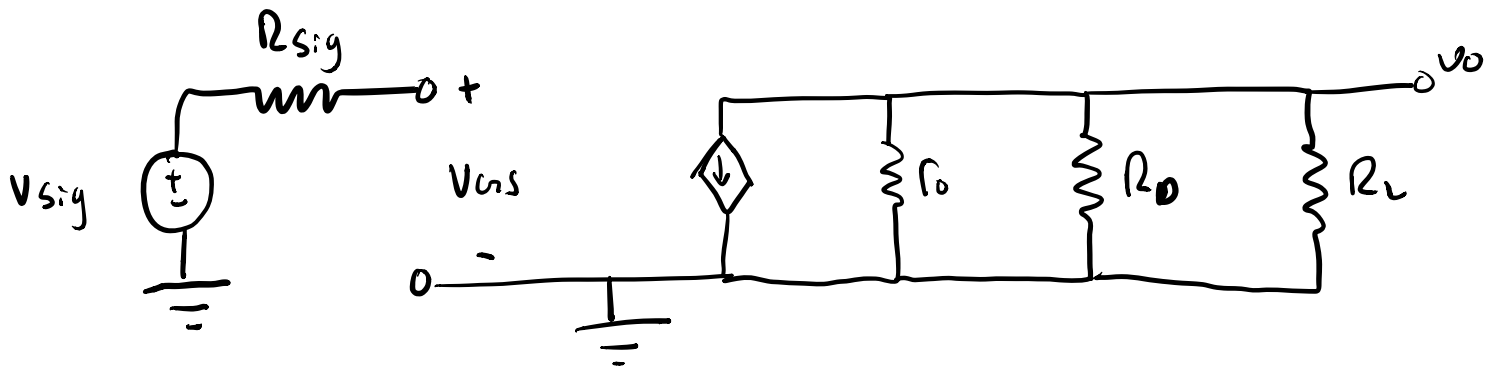

$$r_o = \frac{V_A}{I_{DQ}} = \frac{30}{0.5 \text{ mA}} = 60 \text{ k}\Omega$$

$$R_{in} = \infty$$

$$R_o = (r_o \parallel R_D) = 7.06 \text{ k}\Omega$$

$$V_{GSQ} = V_t + \sqrt{\frac{2I_{DQ}}{k'_n \frac{W}{L}}} = 2.207 \text{ V}$$

$$g_m = .002 (2.207 - 1.5)$$

$$g_m = .001414$$

$$G_v = -g_m (r_o \parallel R_D \parallel R_L)$$

$$G_v = -.001414 (60 \parallel 10 \parallel 8) = -5.85 \text{ V/V}$$

Print Your Name _____

6. [15 points] Find the V_{D1} and V_{D2} and design the resistor for a drain current of 1mA given that both MOSFETS have $V_t=1V$ and $k'_n W/L=5 \text{ mA/V}^2$.

$$\begin{aligned} V_{D1} &= ? & I_D &= 1 \text{ mA} \\ V_{D2} &= ? & V_t &= 1 \text{ V} \\ R &= ? & k'_n \frac{W}{L} &= 5 \text{ mA/V}^2 \end{aligned}$$

$$I_D = \frac{1}{2} (k'_n \frac{W}{L}) (V_{GS1} - V_t)^2$$

$$1 \text{ mA} = \frac{1}{2} (5 \text{ mA}) (V_{GS1} - 1)^2$$


$$\sqrt{1/(2.5)} + 1 = V_{GS1}$$

$$V_{GS1} = 1.632 \text{ V}$$

$$V_{GS1} = V_{D1} - V_{D2}$$

$$V_{D2} = 1.63 \text{ V}$$


$$V_{D1} = 3.26 \text{ V}$$

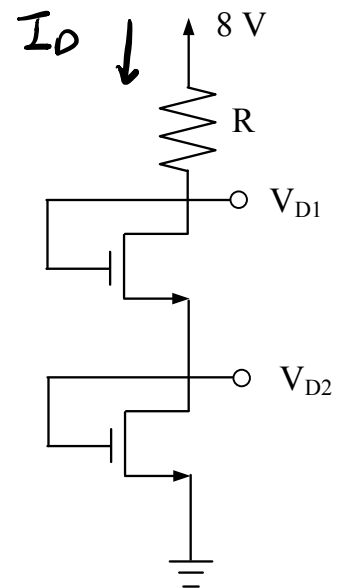

Print Your Name _____

7. [15 points] Given the following npn BJT with $V_{BE}=0.75$ V and $\alpha=.99$. What are the base, collector, and emitter currents?

$$V = 10 \text{ V}$$

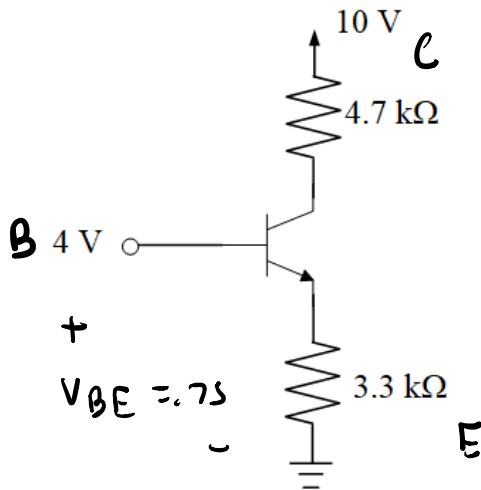

$$i_C = \alpha \cdot i_E = 975 \mu A$$

$$i_B = 985 \mu A - 975 \mu A = 10 \mu A$$

$$i_E = \frac{3.25}{3.3 \text{ k}\Omega} = 985 \mu A$$

$$V_E = 4 - 0.75 = 3.25 \text{ V}$$