

Lab 114 - 04: Quiz - ROTATIONAL DYNAMICS

---

PLEASE DO NOT WRITE ON PAGE AND RETURN IT TO YOUR INSTRUCTOR

---

Question 1: The plates of an **isolated** parallel plate capacitor with a capacitance  $C$  carry a charge  $Q$ . What is the capacitance of the capacitor if the **charge is increased to  $2Q$** ?

- (a)  $C/2$  (b)  $2C$  (c)  $C$  (d) none of these

Question 2: When the capacitor is **fully charged** in **DC** the current in the circuit is

- (a) maximum (b) minimum (c) somewhere in between maximum and minimum (d) zero

Question 3: Two **capacitors in series** that have the same charge density and same plate separation will always have the same

- (a) capacitance (b) voltage (c) charge (d) all of these on the list

Question 4: In an AC (sine-wave) domain, the time-series of the voltages **between the capacitor and the resistor** will ALWAYS be

- (a) exactly in phase (b) exactly  $180^\circ$  out of phase (c) exactly  $90^\circ$  out of phase (d) none of these

Question 5: In an AC (sine-wave) domain, the time-series of the voltages **between the capacitor and the entire circuit** will ALWAYS be

- (a) exactly in phase (b) exactly  $180^\circ$  out of phase (c) exactly  $90^\circ$  out of phase (d) none of these

Question 6: The **capacitance will increase** if one

- (a) increases the voltage (b) decreases the charge (c) increase the plate separation (d) none of these

Question 7: Consider a capacitor and resistor in series in AC (sine-wave) domain. Does the time-series of the **voltage** across the **capacitor** ever become zero?

- (a) no (b) yes

Question 8: One of the **major differences between DC and AC** (sine-wave) that when the circuit includes a **capacitor** is that

- (a) the capacitance depends on frequency (b) capacitor has resistance, but independent of frequency (c) capacitor has resistance, but dependent on frequency (d) none of this

Question 9: As AC (sine-wave) **frequency increases** in an RC in series, then the rms voltage **across the resistor**

- (a) approaches zero (b) approaches the RMS of the source (c) none of these on the list
- 

PLEASE DO NOT WRITE ON PAGE AND RETURN IT TO YOUR INSTRUCTOR

---