

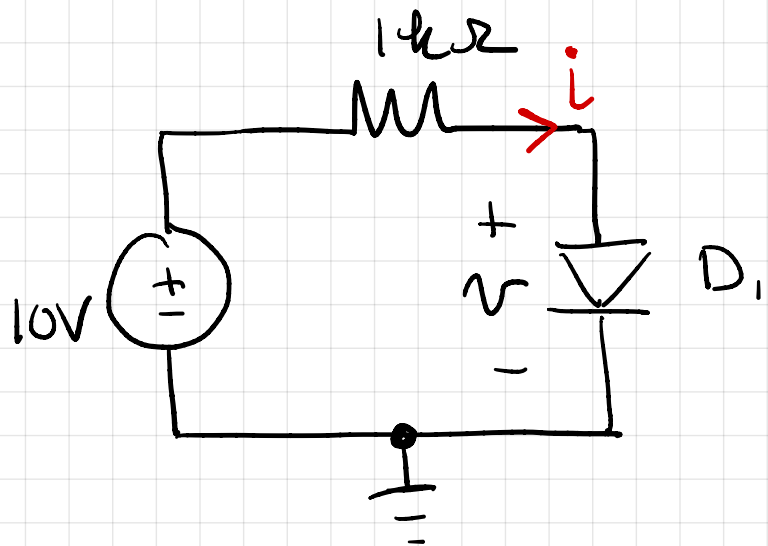
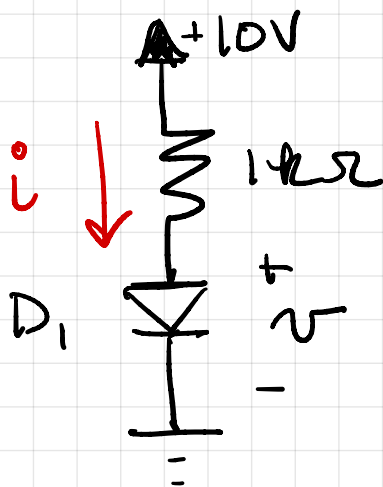
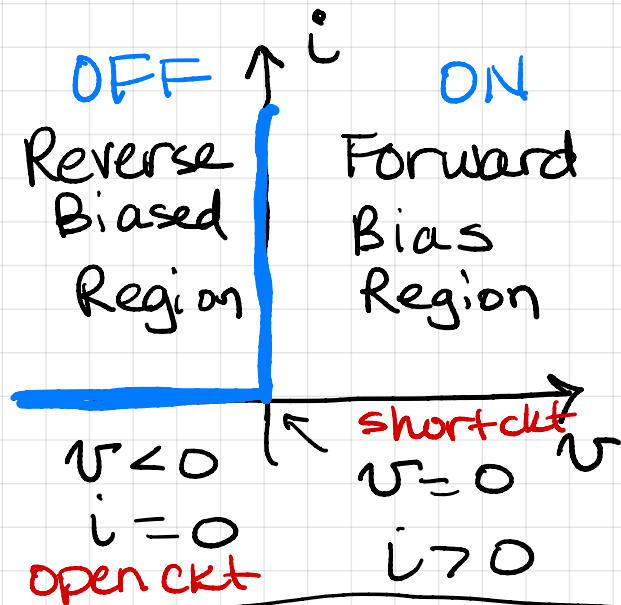


Ideal Diodes

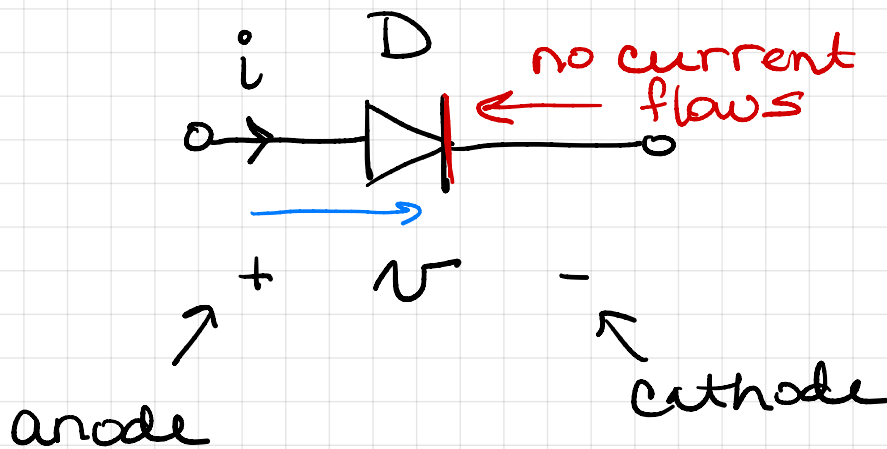diode is a switch that allows current to flow in one direction but not the other direction



Assume DI ON

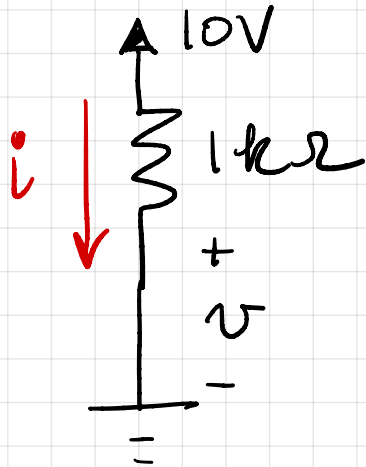


by ohm's law

$$i = \frac{10 - 0}{1 \times 10^3} = 10 \text{ mA}$$




Assume DI off

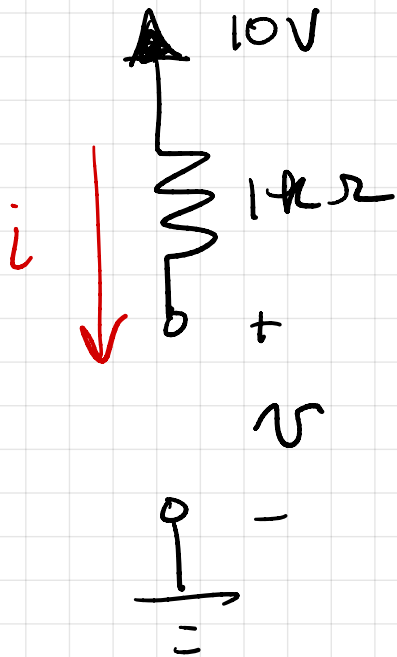


$$i = 0$$

$$v = +10 - 0 = 10 \text{ V}$$

since $v > 0$, DI is not off

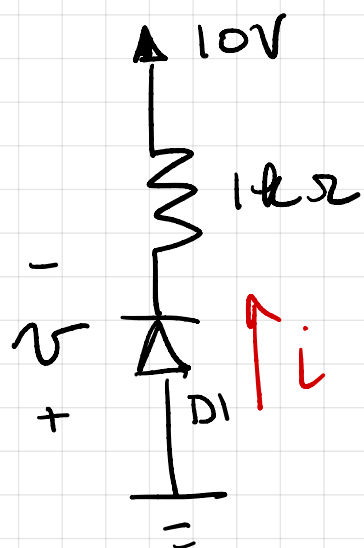





D1 is off

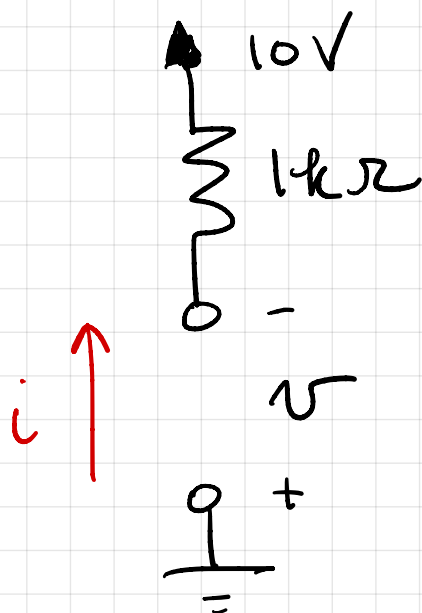

$$i = 0$$

$$v = 0 - 10$$

$$v = -10V$$

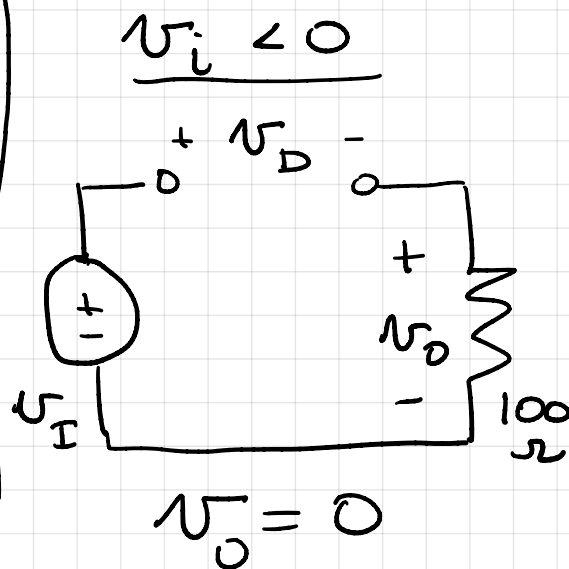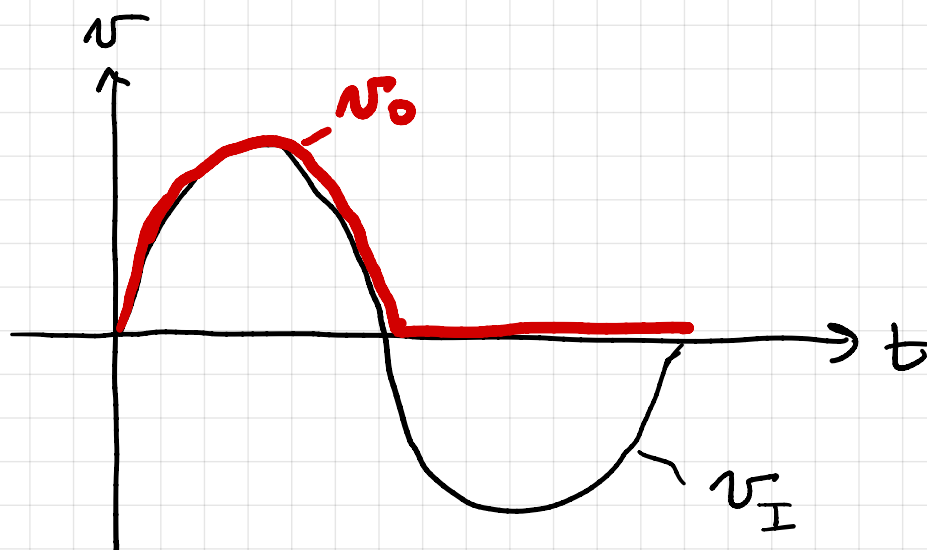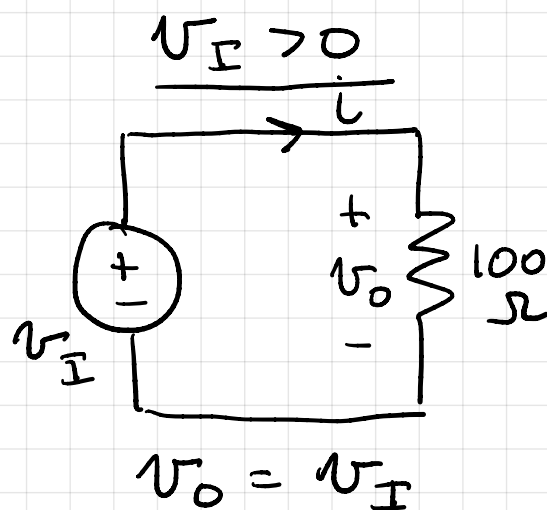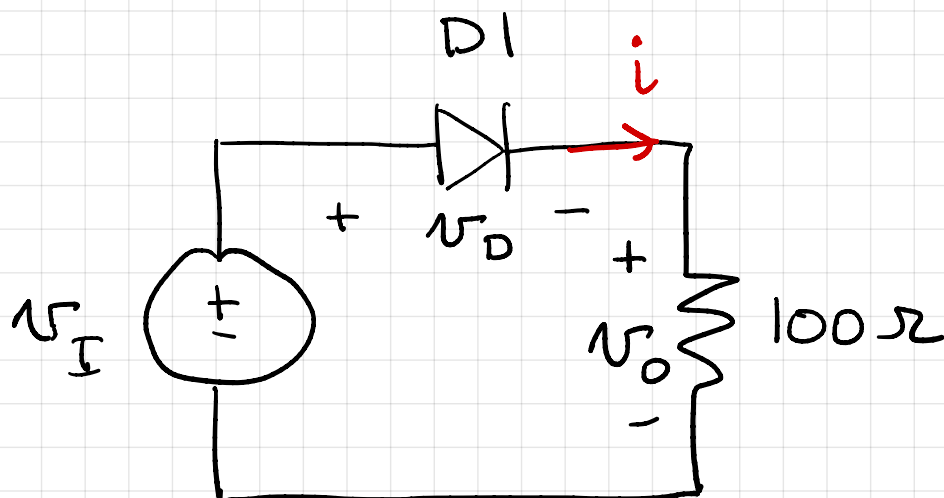

$$V_D = V_I \Rightarrow V_I \text{ is negative } \checkmark$$


Guesses

D_1, D_2 ON


D_1, D_2 OFF

D_1 ON, D_2 OFF

D_1 OFF, D_2 ON

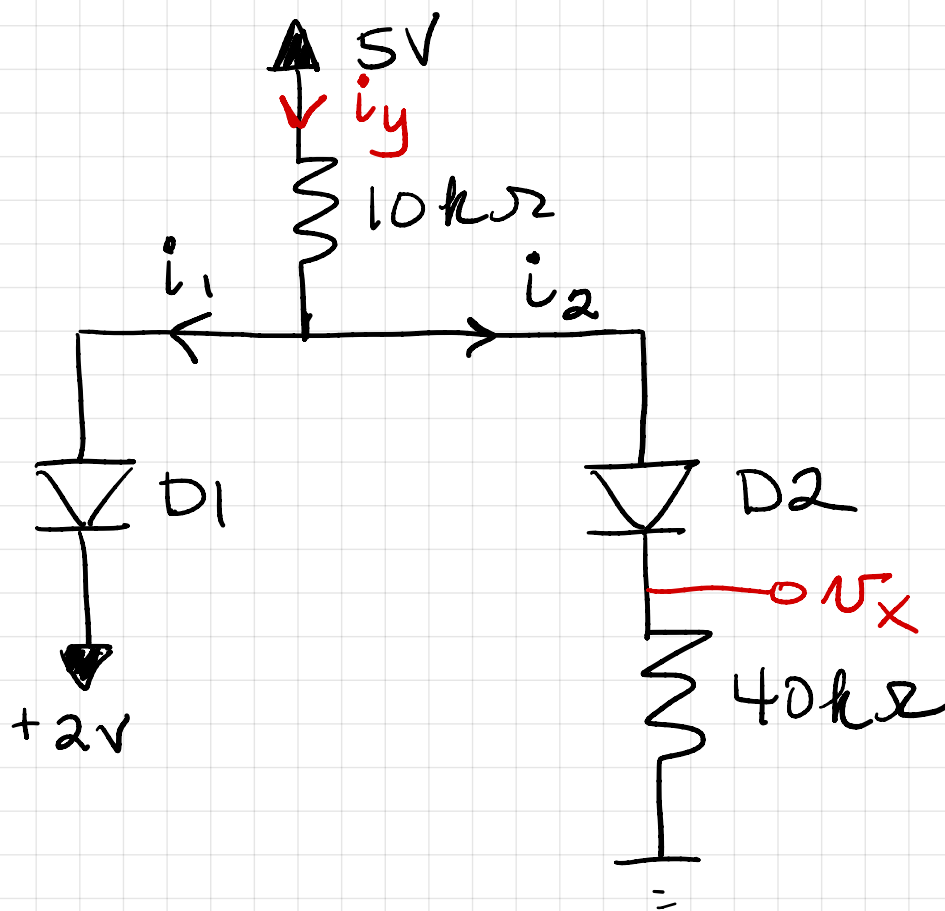

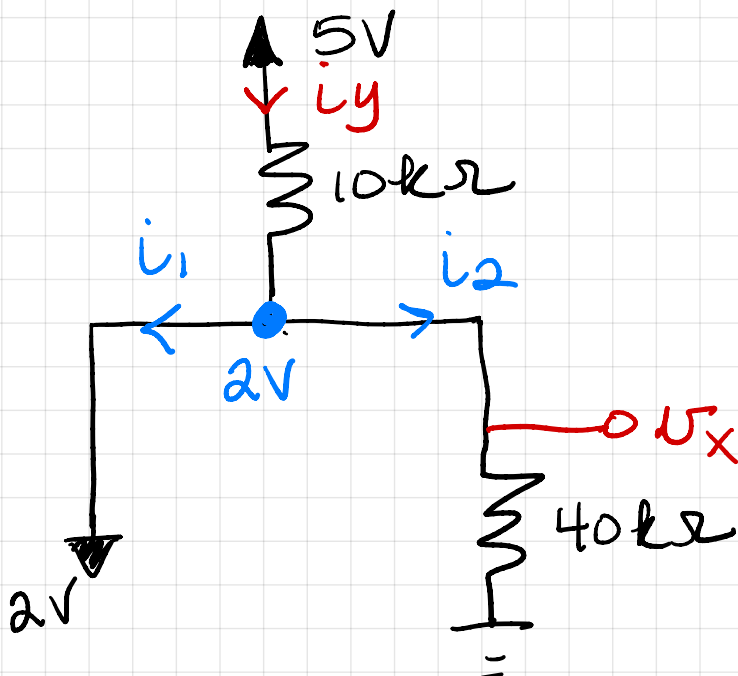Assume D_1, D_2 ON ($i_1 > 0$ & $i_2 > 0$)



$$i_y = \frac{5-2}{10 \times 10^3}$$

$$= 0.3 \text{ mA}$$

$$V_x = 2 \text{ V}$$

$$i_2 = \frac{v_x}{40 \times 10^3} = 0.05 \text{ mA}$$

by KCL: $i_y = i_1 + i_2$

$$i_1 = i_y - i_2$$

$$i_1 = 0.25 \text{ mA}$$

our assumption checks

$$\begin{aligned} v_x &= 2 \text{ V} \\ i_y &= 0.3 \text{ mA} \end{aligned}$$