
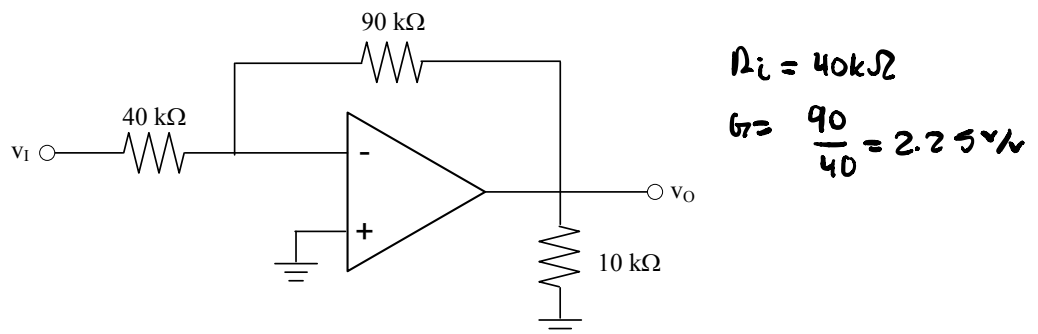
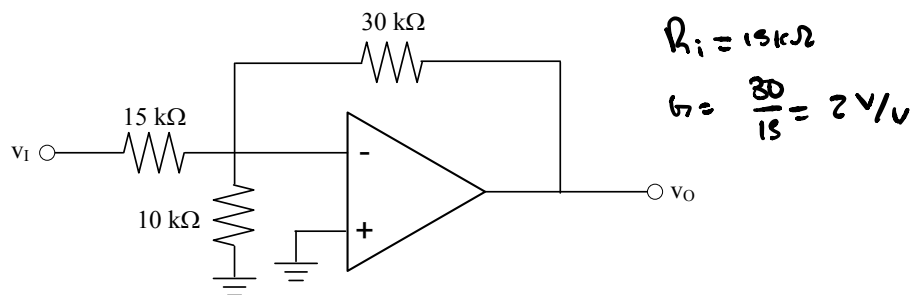


1	<input checked="" type="checkbox"/>	5	<input checked="" type="checkbox"/>
2	<input checked="" type="checkbox"/>	6	<input type="checkbox"/>
3	<input checked="" type="checkbox"/>	7	<input checked="" type="checkbox"/>
4	<input checked="" type="checkbox"/>		

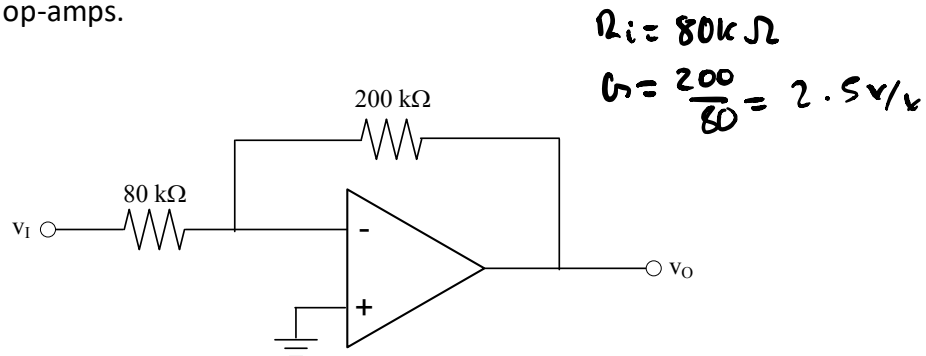1. For the following circuits, find the closed loop voltage gain and the input resistance. Assume ideal op-amps.



2. Design an ideal inverting amplifier with a closed loop gain of  $-5 \text{ V/V}$ . The output voltage is limited to  $-10 \text{ V} \leq v_O \leq 10 \text{ V}$ , and the maximum current in any resistor is limited to  $50 \mu\text{A}$ .
3. Using the standard inverting configuration with an ideal op-amp, design for a closed loop gain of  $-1000 \text{ V/V}$ . The maximum resistor value allowed is  $100 \text{ k}\Omega$ . What is the input resistance? Use the circuit with the T resistor feedback and the same maximum resistor value, design the circuit for the same closed-loop gain of  $-1000 \text{ V/V}$ . What is the input resistance for this circuit?

Handwritten calculations for problem 3:


$$G = -1000 \text{ V/V}$$

$$G = -\frac{R_2}{R_1}$$

$$1000 = \frac{R_2}{R_1}$$

$$R_i = R_1 = 10 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega$$

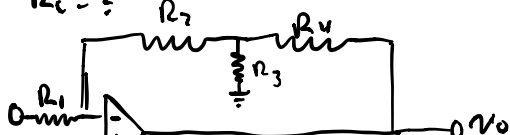

Handwritten calculation for the input resistance of the T-resistor feedback circuit:

$$\frac{v_i}{i_i} = -\frac{R_2}{R_1} \left( \frac{R_4}{R_3} + \frac{R_4}{R_2} + 1 \right)$$

$\frac{v_b}{v_z} = 1 \left( 1 + \frac{100 \times 10^3}{R_3} + 1 \right) \rightarrow R_i = 100k\Omega$   
 $1000 = 2 + \frac{100 \times 10^3}{R_3}$   
 $\frac{100 \times 10^3}{R_3} = 998 \quad R_3 = 100.20\Omega$

4. Design a weighted summer circuit for the following equations:


a.  $v_o = -2v_1 - 8v_2$

b.  $v_o = -12v_1 - 3v_2 + 2v_3$


Resistors should range between  $10k\Omega$  and  $1M\Omega$

5. For the following circuits, find the closed loop voltage gain and the input resistance.

Assume ideal op-amps.

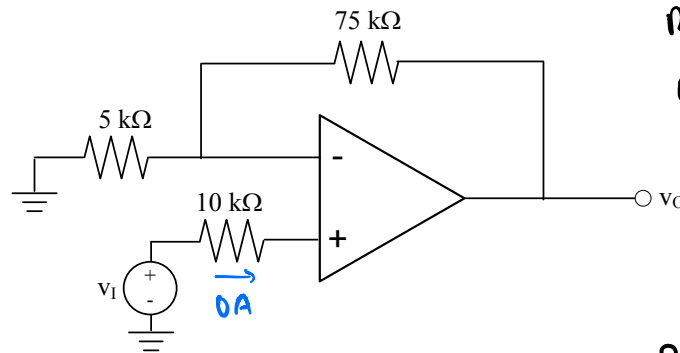

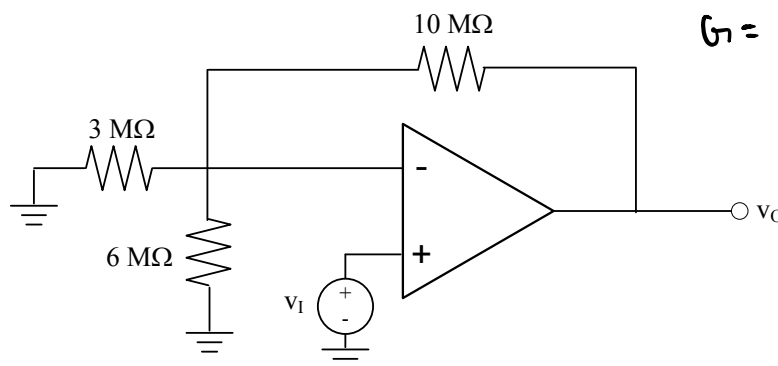$R_i = \infty$   
 $G = 1 + \frac{75}{5} = 16 \text{ V/V}$




$R_i = \infty$   
 $G = 1 + \frac{10}{2} = 6 \text{ V/V}$

6. We worked an example where a potentiometer was used to divide the resistance between  $R_1$  and  $R_2$  for a typical non-inverting amplifier configuration. We found that the range of gain was 1 to infinity. For this problem, consider how you might add a fixed resistor to the circuit to prevent the gain from increasing above 11 V/V. Draw the circuit and show how you calculated the new range of closed loop gain from 1 to 11 V/V.

7. ....

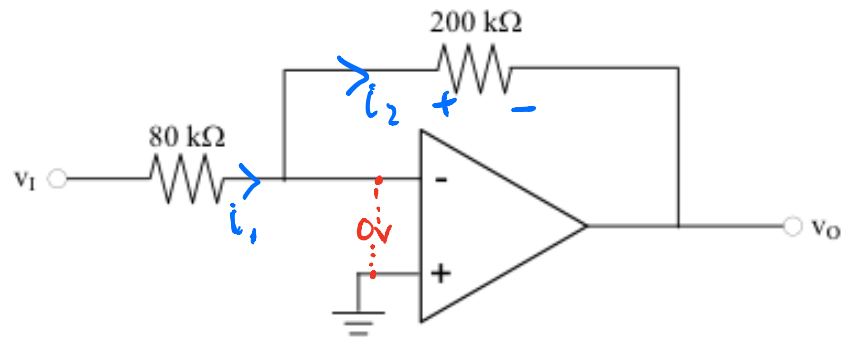1. For the following circuits, find the closed loop voltage gain and the input resistance.  
Assume ideal op-amps.



$$R_1 = 80 \text{ k}\Omega$$

$$R_2 = 200 \text{ k}\Omega$$


$v_O/v_I \equiv$  Closed loop gain

$$i_1 = \frac{v_I}{R_1}$$


$$i_2 = \frac{0 - v_O}{R_2}$$

$$\frac{v_I}{R_1} = -\frac{v_O}{R_2} \Rightarrow \frac{v_O}{v_I} = -\frac{R_2}{R_1} \quad \cdot \text{By KCL, } i_1 = i_2.$$
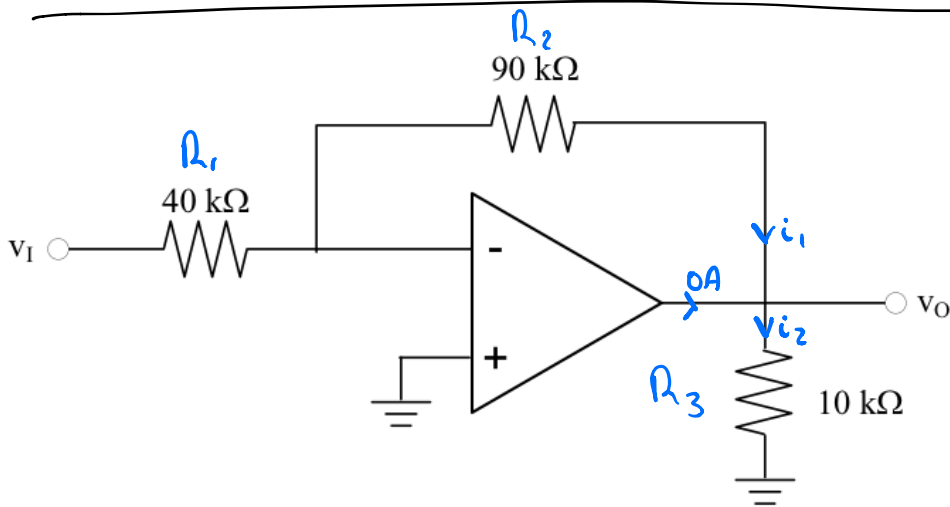
$$= -\frac{200 \text{ k}\Omega}{80 \text{ k}\Omega} = -2.5 \text{ V/V}; R_i = R_1 = 80 \text{ k}\Omega$$



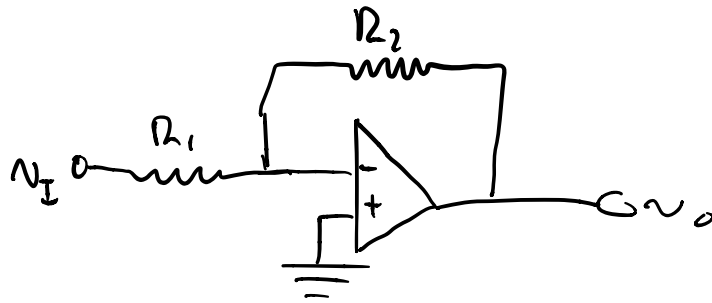2. Design an ideal inverting amplifier with a closed loop gain of  $-5V/V$ . The output voltage is limited to  $-10V \leq v_o \leq 10V$ , and the maximum current in any resistor is limited to  $50\mu A$ .



$$G = -5V/V$$

$$-10 \leq v_o \leq 10$$

$$i_{max} = 50\mu A$$

$$v_{o,max} = 10V$$

$$|v_{I,max}| = 10/5 = 2V$$

$$i_{max} = \frac{v_I}{R_1} = 2/R_1 = 50 \times 10^{-6}$$


$$R_1 = 40k\Omega$$

4. Design a weighted summer circuit for the following equations:

a.  $v_o = -2v_1 - 8v_2$

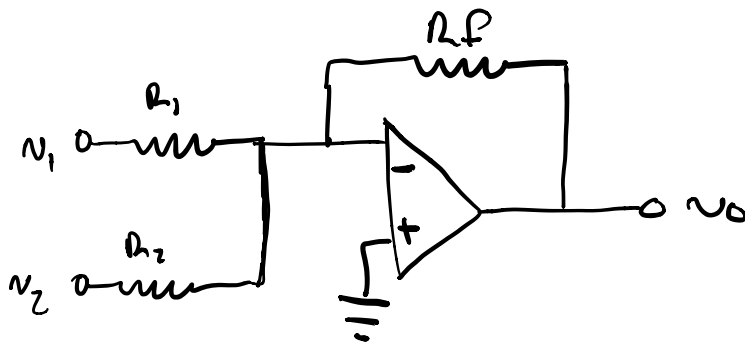b.  $v_o = -12v_1 - 3v_2 + 2v_3$

Resistors should range between  $10k\Omega$  and  $1M\Omega$




$$v_o = -2v_1 - 8v_2$$

$$10k\Omega \leq R \leq 1M\Omega$$

$$v_o = -\frac{R_F}{R_1}v_1 - \frac{R_F}{R_2}v_2; \quad \frac{R_F}{R_1} = 2 \quad \frac{R_F}{R_2} = 8$$

$$\text{Let } R_F = 400k\Omega \quad R_1 = \frac{R_F}{2} = 200k\Omega \quad R_2 = \frac{R_F}{8} = 50k\Omega$$

b)  $v_0 = -12v_1 - 3v_2 + 2v_3$

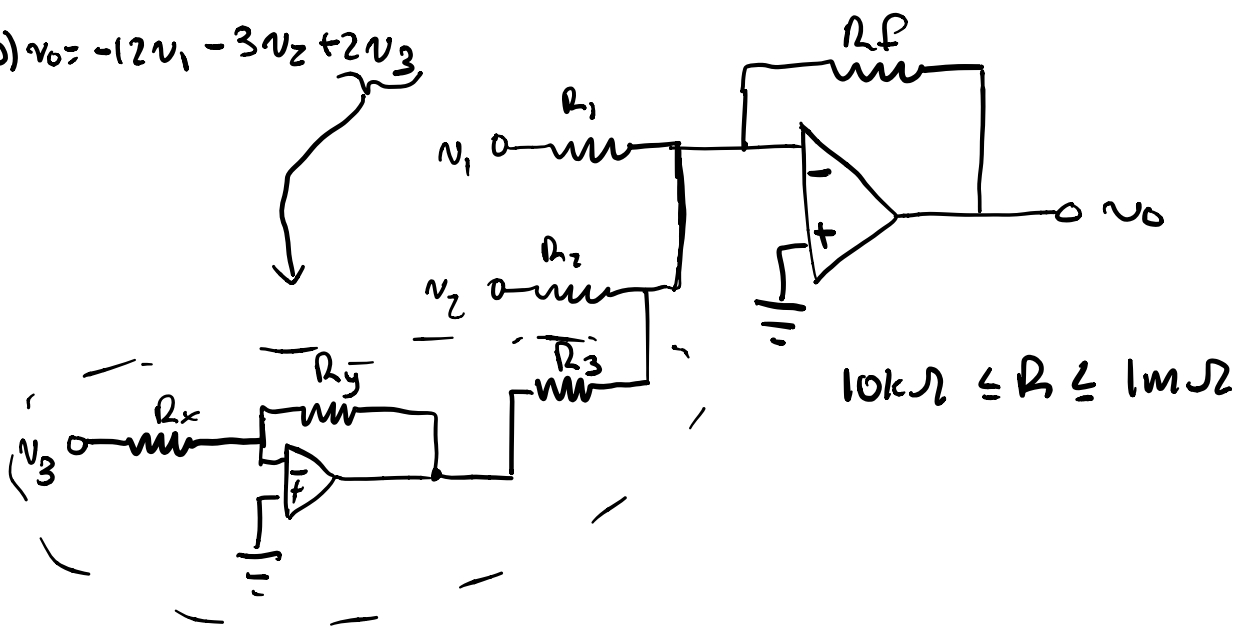

$$v_3' = -\frac{R_y}{R_x} v_3 \Rightarrow v_0 = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 - \frac{R_F}{R_3} v_3'$$


$$v_0 = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 + \frac{R_F}{R_3} \cdot \frac{R_y}{R_x} v_3 \quad \frac{R_F}{R_1} = 12 \quad \frac{R_F}{R_2} = 3 \quad \frac{R_y}{R_x} \frac{R_F}{R_3} = 2$$

$$\left. \begin{array}{l} \text{Let } R_F = 600 \text{ k}\Omega \\ R_y = 10 \text{ k}\Omega \\ R_x = 10 \text{ k}\Omega \end{array} \right\} R_3 = \frac{R_y}{R_x} \cdot \frac{R_F}{2} : R_3 = 300 \text{ k}\Omega$$

$$R_1 = \frac{R_F}{12} = 50 \text{ k}\Omega \quad R_2 = \frac{R_F}{3} = 200 \text{ k}\Omega$$

You can design these with different values, so as long as these values lie within the range, then it is a valid design.

$$v_0 = -5v_1 - 10v_2$$

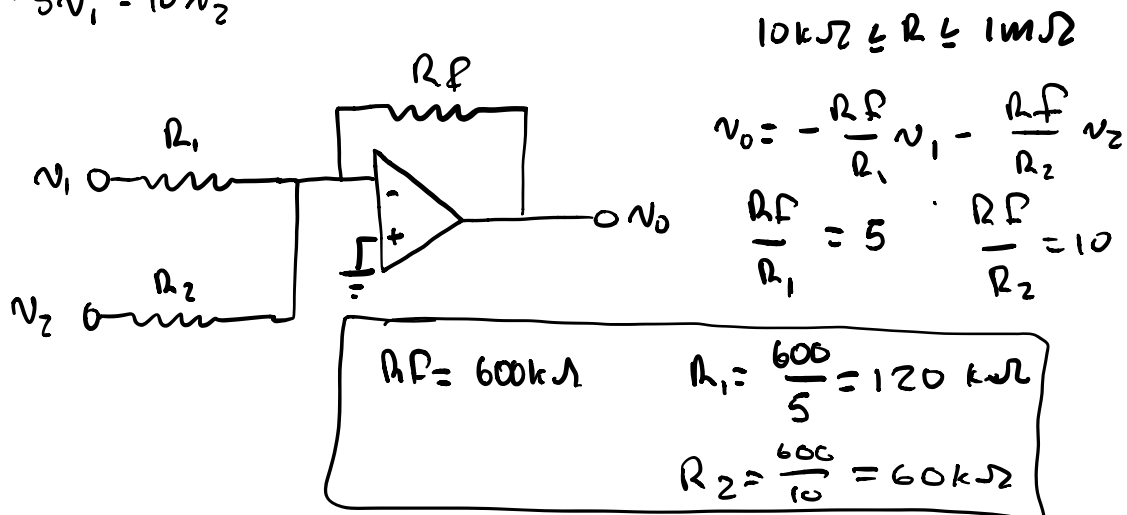

$$v_0 = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 \quad \frac{R_F}{R_1} = 5 \quad \frac{R_F}{R_2} = 10$$

$$R_F = 600 \text{ k}\Omega \quad R_1 = \frac{600}{5} = 120 \text{ k}\Omega$$

$$R_2 = \frac{600}{10} = 60 \text{ k}\Omega$$

7. For both the inverting and non inverting configurations, show how the closed loop gain varies if the op-amp has finite open loop gain of. 100, 1000, 10,000, 100,000, and 1,000,000.

**Inverting amp:**

$$\left. \begin{array}{l} R_2 = 100 \text{ k}\Omega \\ R_1 = 5 \text{ k}\Omega \end{array} \right\} \begin{array}{l} \text{Choose these} \\ \text{at random} \end{array}$$

$$\text{finite: } \frac{-R_2/R_1}{1 + 1/A (1 + R_2/R_1)}$$

$$\text{ideal: } G = -R_2/R_1 = -20 \text{ V/V}$$

A	G (V/V)
100	16.53
1000	19.59
10000	19.96
100000	19.996
1,000,000	19.9996

**Non-inverting**

$$\text{ideal: } \left. \begin{array}{l} R_2 = 100 \text{ k}\Omega \\ R_1 = 5 \text{ k}\Omega \end{array} \right\} \begin{array}{l} \text{Choose at} \\ \text{random} \end{array}$$

$$\frac{V_o}{V_I} = 1 + R_2/R_1 = 21 \text{ V/V}$$

non ideal	$G = \frac{1 + R_2/R_1}{1 + \frac{1 + R_2/R_1}{A}}$	A	G (V/V)
		100	17.35
		1000	20.57
		10,000	20.955
		100,000	20.995
		1,000,000	20.9996

## General notes


o Closed loop voltage gain:  $G = V_o/V_I$

o  $R_i = R_1$  in non-inverting

o  $V = I R$

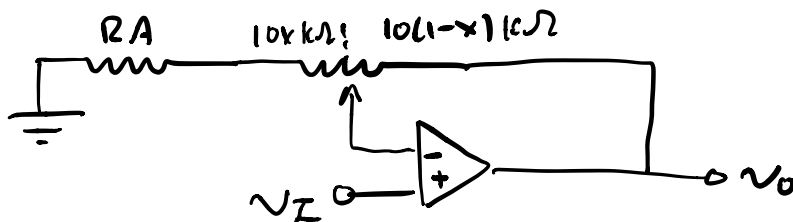6. We worked an example where a potentiometer was used to divide the resistance between  $R_1$  and  $R_2$  for a typical non-inverting amplifier configuration. We found that the range of gain was 1 to infinity. For this problem, consider how you might add a fixed resistor to the circuit to prevent the gain from increasing above 11 V/V. Draw the circuit and show how you calculated the new range of closed loop gain from 1 to 11 V/V.

$$1 \text{ V/V} \leq G \leq 11 \text{ V/V}$$



When  $x=0$  (max gain)

$$R_1 = R_A$$

$$R_2 = 10 \text{ k}\Omega$$

$$G = 11 \text{ V/V}$$

When  $x=1$  (min gain)

$$R_2 = 0$$

$$R_1 = 10 + R_A$$

$$G = 1$$

$$G = \frac{R_2}{R_1} + 1 = 11$$

$$\frac{R_2}{R_1} = 10 \approx \frac{10 \text{ k}\Omega}{R_A} = 10 \Rightarrow R_A = 1 \text{ k}\Omega$$