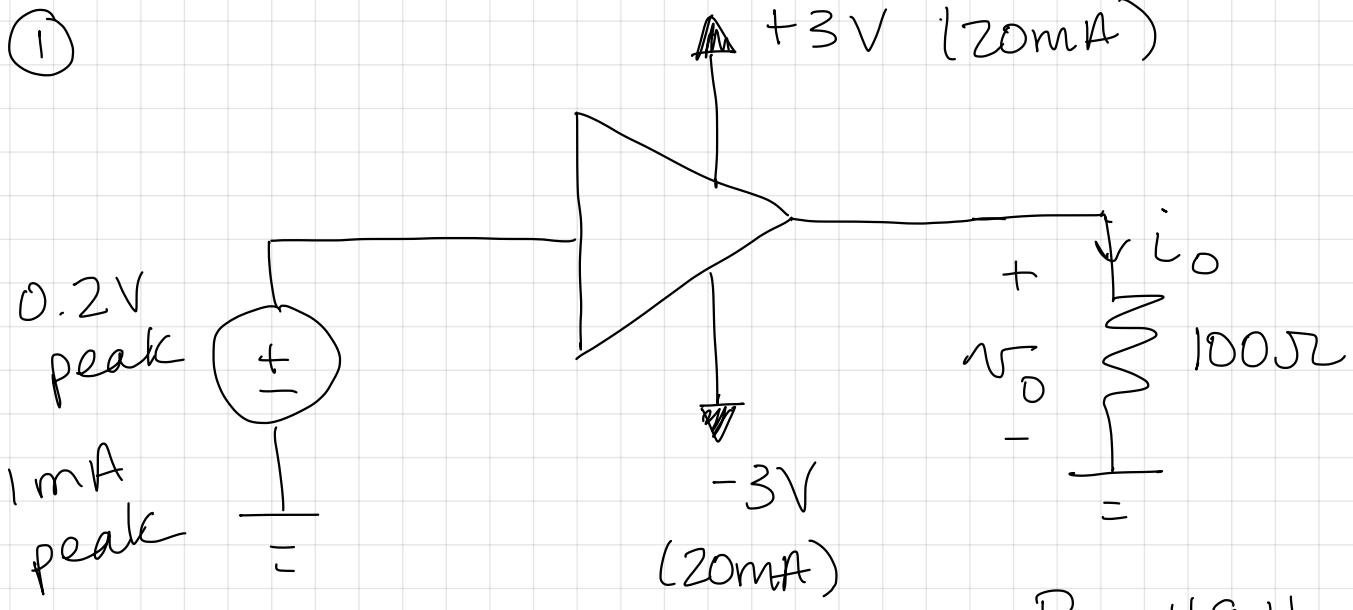


EE 315 HW #1 Solutions



$$P_o = \frac{V_o^2}{100} \quad V_o^2 = 100(48.4 \times 10^{-3})$$

$$V_o = 2.2 \text{ V}$$

$$i_o = \frac{V_o}{100} = 22.0 \text{ mA}$$

a)  $A_v = \frac{V_o}{V_i} = \frac{2.2}{0.2} = 11 \frac{\text{V}}{\text{V}}$  or  $20.83 \text{ dB}$

$$A_i = \frac{i_o}{i_i} = \frac{22 \times 10^{-3}}{1 \times 10^{-3}} = 22 \frac{\text{A}}{\text{A}}$$

or  $26.85 \text{ dB}$

$$A_p = \frac{P_o}{P_i} = \frac{V_o i_o}{V_i i_i} = \frac{(2.2)(22 \times 10^{-3})}{(1.2)(1 \times 10^{-3})}$$

$$A_p = 242 \frac{\omega}{\bar{\omega}} \text{ or } 23.84 \text{ dB}$$

b) \* now we have to deal w/ rms units or remember that average power is  $\frac{1}{2} V I$ .

$$P_{dc} + P_i = P_L + P_{diss}$$

$$P_{dc} = 3(20 \times 10^{-3})(2)$$

↑  
assume  
average  
values  
=

$$P_{dc} = 120 \text{ mW}$$

↑  
same  
as  $P_o$

there  
are  
2  
Supplies

$$P_o = \frac{1}{2} \left( \frac{V_o^2}{100} \right) = 24.2 \text{ mW}$$

$$P_i = \frac{P_o}{A_p} = \frac{24.2}{242} = 0.1 \text{ mW}$$

$$\eta = \frac{P_o}{P_{dc}} \times 100 = \frac{24.2}{120} \times 100$$

$$\eta = 20.17\%$$

c)  $P_{diss} = P_{dc} + P_i - P_o$

$$P_{diss} = 95.9 \text{ mW}$$

(2)

DC supplies	input at clipping	output $V_o$ at clipping
$\pm 2V$	$\pm 8.5 \text{ mV}$	$V_o = \pm 200(8.5 \times 10^{-3})$ $V_o = \pm 1.7V$
$\pm 5V$	$\pm 21.5 \text{ mV}$	$V_o = \pm 200(21.5 \times 10^{-3})$ $V_o = \pm 4.3V$
$\pm 10V$	$\pm 42.5 \text{ mV}$	$V_o = \pm 200(42.5 \times 10^{-3})$ $V_o = \pm 8.5V$

so: for  $\pm 2V$ ,  $-1.7V \leq V_o \leq 1.7V$

$\pm 5V$ ,  $-4.3V \leq V_o \leq 4.3V$

$\pm 10V$ ,  $-8.5V \leq V_o \leq 8.5V$

$$V_o = AV_I$$

$$A = 200V/V$$


Clipping occurs at :  $\sim 85\%$  of DC

$$\frac{1.7}{2} = 0.85 \quad ; \quad \frac{4.3}{5} = 0.86 \quad \text{Supply}$$

$$\frac{8.5}{10} = 0.85$$


---

③

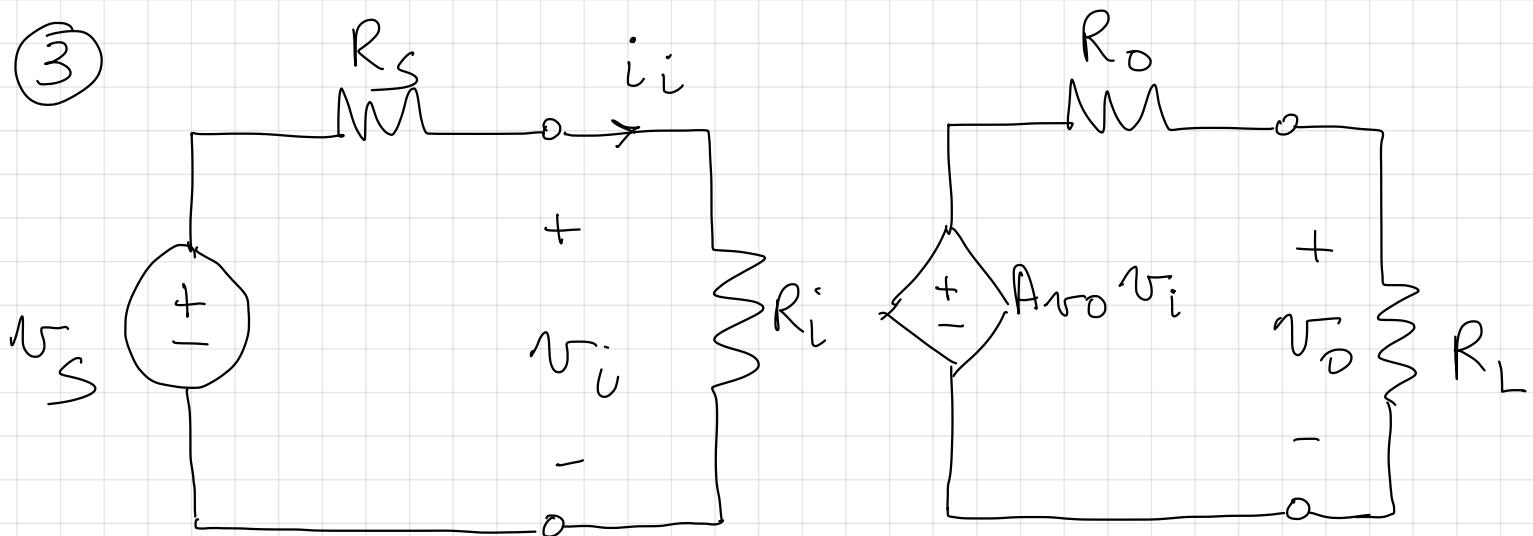

$$R_S = 200\text{k}\Omega \quad R_i = 1M\Omega \quad R_L = 150\Omega$$

$$v_S = 2\text{ V peak} \quad R_O = 40\Omega \quad A_{v_o} = 1\text{ V/V}$$

$$v_o = \frac{R_L}{R_L + R_O} (A_{v_o} v_i)$$

$$v_i = \frac{R_i}{R_i + R_S} v_S$$

$$V_o = \left( \frac{R_L}{R_L + R_o} \right) (A_{vo}) \left( \frac{R_i}{R_i + R_s} \right) V_S$$

$$\frac{V_o}{V_S} = \left( \frac{150}{150 + 40} \right) (1) \left( \frac{1 \times 10^6}{1 \times 10^6 + 200 \times 10^3} \right)$$

$$\frac{V_o}{V_S} = (0.789)(1)(0.833)$$

$$A_{vo} = \frac{V_o}{V_S} = 0.6575 \quad \text{V/V or } -3.64 \text{ dB}$$

means attenuation

$$V_o = 0.6575 \cdot (2) = 1.315$$

$$I_o = \frac{V_o}{R_L} = \frac{1.315}{150} = 8.77 \text{ mA}$$

$$I_i = \frac{V_S}{R_i + R_s} = \frac{2}{1.2 \times 10^6} = 1.67 \mu\text{A}$$

$$A_i = \frac{I_o}{I_i} = 5.25 \times 10^3 \text{ A/A or } 74.4 \text{ dB}$$

$$A_p = \frac{P_o}{P_s} = \frac{V_o i_o}{V_s i_s} = \frac{(1.315)(8.77 \times 10^{-3})}{(2)(1.67 \times 10^{-6})}$$

$$A_p = 3.45 \times 10^3 \frac{W}{W}$$

or 35.38 dB

I would also except :

$$A_p = \frac{P_o}{P_i} = \frac{V_o i_o}{i_i^2 (R_i)} = \frac{(1.315)(8.77 \times 10^{-3})}{(1.67 \times 10^{-6})^2 (1 \times 10^6)}$$


$$A_p = 4.14 \times 10^3 \frac{W}{W} \text{ or } 36.16 \text{ dB}$$




does not take into account  
the source resistance - it  
is pretty minimal.

4

$$V_S = 10 \text{ mV} \quad 40 \text{ dB} = 100 \text{ V/V} \quad 6 \text{ dB} = 2 \text{ V/V}$$

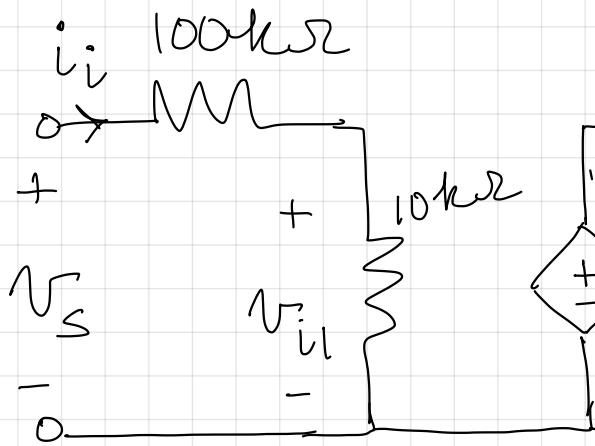

Amplifier 1

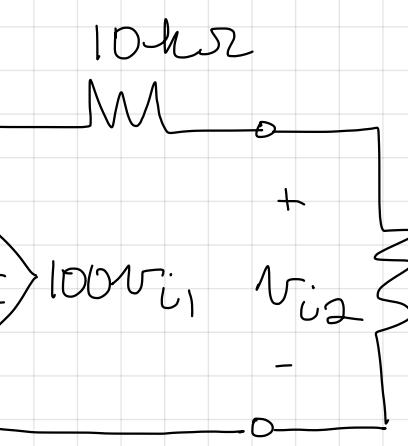

Amplifier 2

Solve for  $A_v$ ,  $A_i$ ,  $A_p$ 

$$\frac{V_o}{V_S} = \left( \frac{50}{50+20} \right) (2) \left( \frac{100 \times 10^3}{110 \times 10^3} \right) (100) \left( \frac{10 \times 10^3}{110 \times 10^3} \right)$$

$$= (0.714)(2)(0.909)(100)(0.0909)$$

$$\frac{V_o}{V_S} = 23.14 \frac{\text{V}}{\text{V}}$$

An

$$\frac{V_o}{V_S} = 23.14 (10 \times 10^{-3})$$

$$= 231.47 \text{ mV}$$

$$i_i = \frac{V_S}{110 \times 10^3} = \frac{10 \times 10^{-3}}{110 \times 10^3}$$

$$i_i = 9.09 \times 10^{-8} \text{ A}$$


$$i_o = \frac{V_o}{50} = 4.63 \text{ mA}$$

$$A_i = \frac{i_o}{i_i} = \frac{4.63 \times 10^{-3}}{9.09 \times 10^{-8}}$$

$$= 5.09 \times 10^4 \text{ A/A}$$

$$A_p = \frac{P_o}{P_s} = \frac{V_o i_o}{V_s i_i} = 1.18 \times 10^6 \frac{W}{W}$$

Now, let's switch the order:

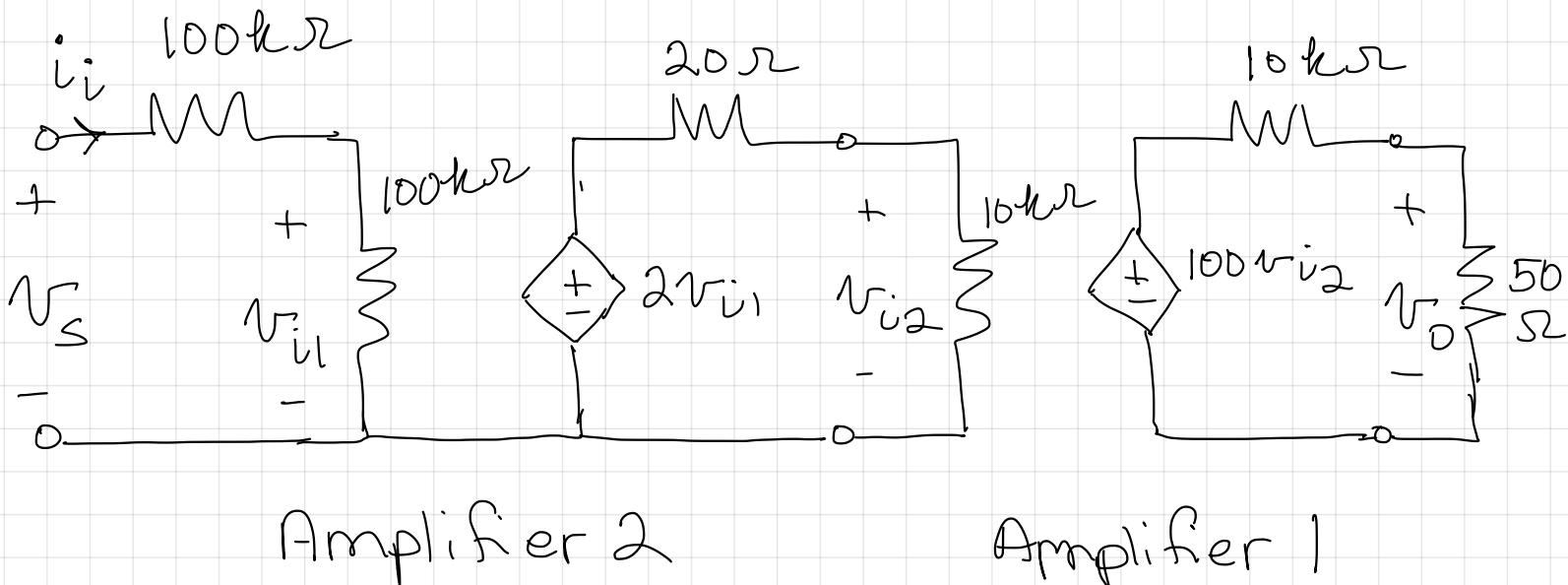

$$\frac{V_o}{V_s} = \left( \frac{50}{50 + 10 \times 10^3} \right) (100) \left( \frac{10 \times 10^3}{10 \times 10^3 + 20} \right) (2) \left( \frac{100 \times 10^3}{200 \times 10^3} \right)$$

$$= (0.005)(100)(0.998)(2)(0.5)$$

$$\frac{V_o}{V_s} = 0.5 \frac{V}{V}$$

$$V_o = 0.5 (10 \times 10^{-3})$$

$$V_o = 5 \text{ mV}$$

$$i_i = \frac{V_s}{200 \times 10^3} = 5 \times 10^{-8} \text{ A}$$

$$i_o = \frac{V_o}{50} = 0.1 \text{ mA}$$

$$A_i = \frac{i_o}{i_i} = 2,000 \text{ A/A}$$

$$A_p = \frac{V_o i_o}{V_s i_i} = 1,000 \text{ w/w}$$

<u>Compare</u>	A <sub>T</sub>	A <sub>i</sub>	A <sub>p</sub>
order Ampl, Amp 2	23.14 V/V	$5.09 \times 10^4$ A/A	$1.18 \times 10^6$ w/w
Amp 2, Amp 1	0.5 V/V	2000 A/A	1000 w/w

which is better?

It depends, I could make an argument for both.

Amp1, Amp2 : good Av but very high Ai & Ap - can the load handle it?

Amp2, Amp1 : Av is small - maybe too small depending on the application but Ai + Ap are pretty good.

My point here is that there is no "right" answer - it depends on the application and what is needed at the load.

And - don't simply pick a stage based on one factor. Based on lectures, you might have been tempted to just go w/ the high Ri as Amp stage 1 and low Ro as Amp stage 2,

that design plan is never  
a good one!

Get used to this!  
We are not in EE 213 land  
anymore!

gme



# EE 315 Module 2A Practice Problem Solutions

(1)

$$R_i = 80 \text{ k}\Omega$$

$$G = \frac{200}{80} = 2.5 \text{ V/V}$$


$$R_i = 15 \text{ k}\Omega$$

$$G = \frac{30}{15} = 2 \text{ V/V}$$

$$R_i = 40 \text{ k}\Omega$$

$$G = \frac{90}{40} = 2.25 \text{ V/V}$$

(2)

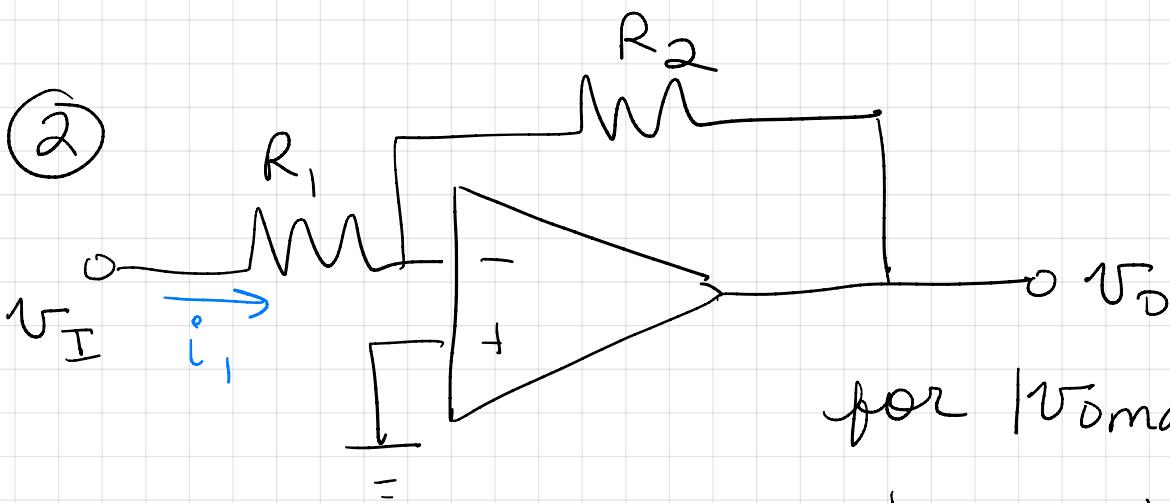

$$\text{for } |V_{o\max}| = 10 \text{ V}$$

$$|V_{i\max}| = \frac{10}{5} = 2 \text{ V}$$

$$i_{\max} = 50 \times 10^{-6} \text{ A}$$

$$-10 \text{ V} \leq V_o \leq 10 \text{ V}$$

$$G = -5 \frac{\text{V}}{\text{V}}$$

$$i_{\max} = \frac{V_I}{R_1} = \frac{2}{R_1} = 50 \times 10^{-6}$$

$R_1 = 40 \text{ k}\Omega$



$$-5 = -\frac{R_2}{R_1}$$

$$R_2 = 5R_1$$

$$R_2 = 200 \text{ k}\Omega$$

check  $R_2$  current

$$\left| \frac{0 - V_{max}}{200 \times 10^3} \right| \leq 50 \mu\text{A}$$

$$\left| \frac{-10}{200 \times 10^3} \right| = 50 \mu\text{A}$$

okay!

③ for standard inverting configuration

$$G = -\frac{R_2}{R_1}$$

$$\text{max } R = 100 \text{ k}\Omega$$

$$R_i = R_1$$

$$G = -1000 \text{ V/V}$$


$$R_i = 10 \text{ k}\Omega$$

$$1000 = \frac{R_2}{R_1} 100 \text{ k}\Omega$$

$$R_1$$

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega$$

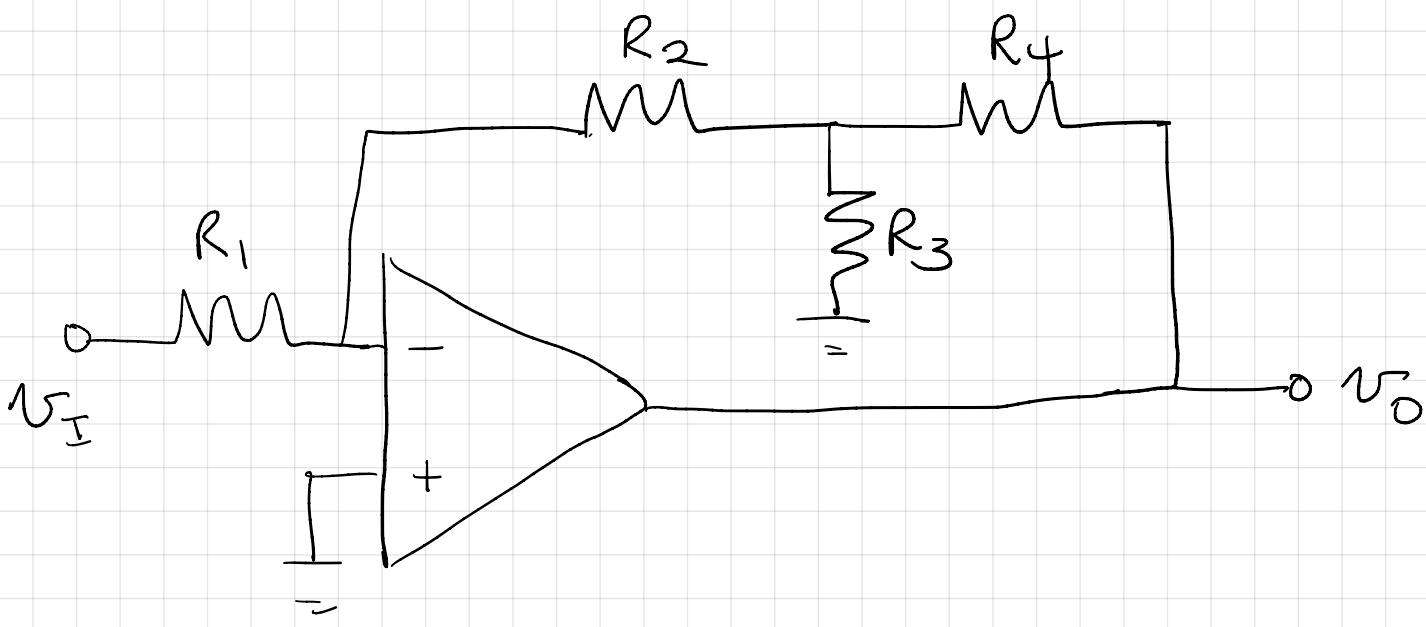

$$\frac{V_O}{V_I} = -\frac{R_2}{R_1} \left( \frac{R_4}{R_2} + \frac{R_4}{R_3} + 1 \right)$$

let  $R_1 = R_2 = R_4 = 100 \text{ k}\Omega$

$$\frac{V_O}{V_I} = -\frac{100}{100} \left( \frac{100}{100} + \frac{100 \times 10^3}{R_3} + 1 \right) = -1000$$

$$2 + \frac{100 \times 10^3}{R_3} = 1000$$


$R_i = 100 \text{ k}\Omega$

$$\frac{100 \times 10^3}{R_3} = 998$$

$R_3 = 100.20 \Omega$

④

$$v_o = -2v_1 - 8v_2$$

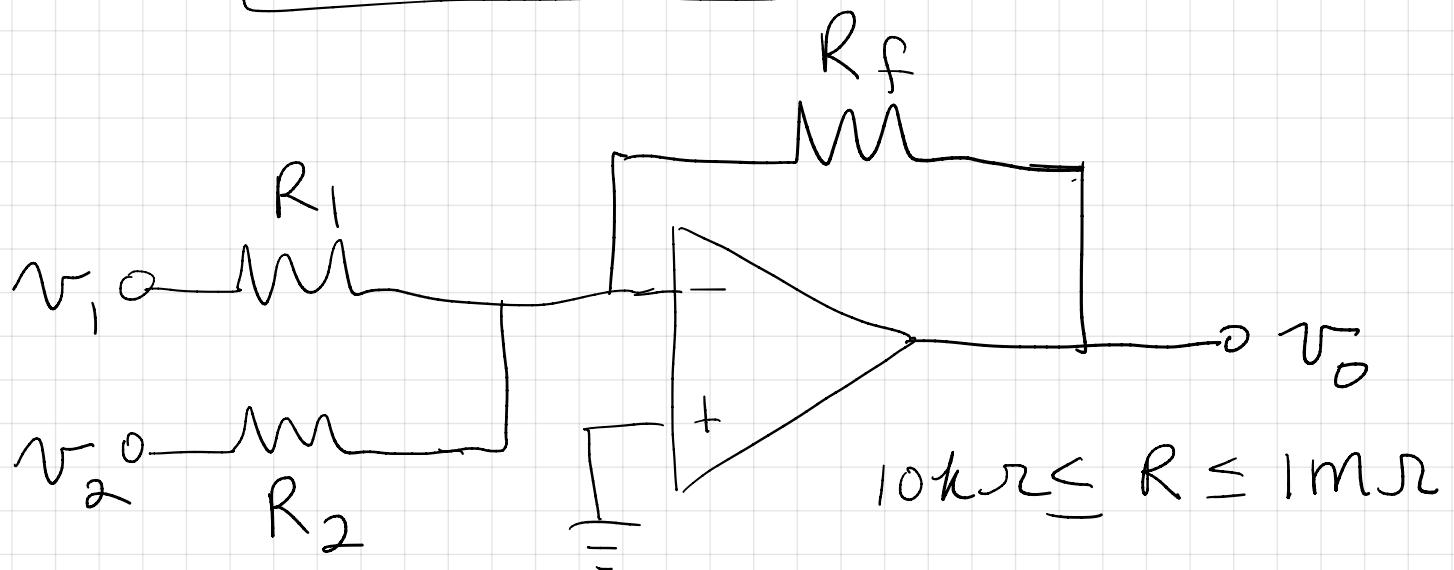

$$v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2$$

$$\frac{R_f}{R_1} = 2$$

$$\frac{R_f}{R_2} = 8$$

let

$$R_f = 400k\Omega$$


$$R_1 = \frac{R_f}{2} = 200k\Omega$$

$$R_2 = \frac{R_f}{8} = 50k\Omega$$

4

b.

$$v_o = -12v_1 - 3v_2 + 2v_3$$

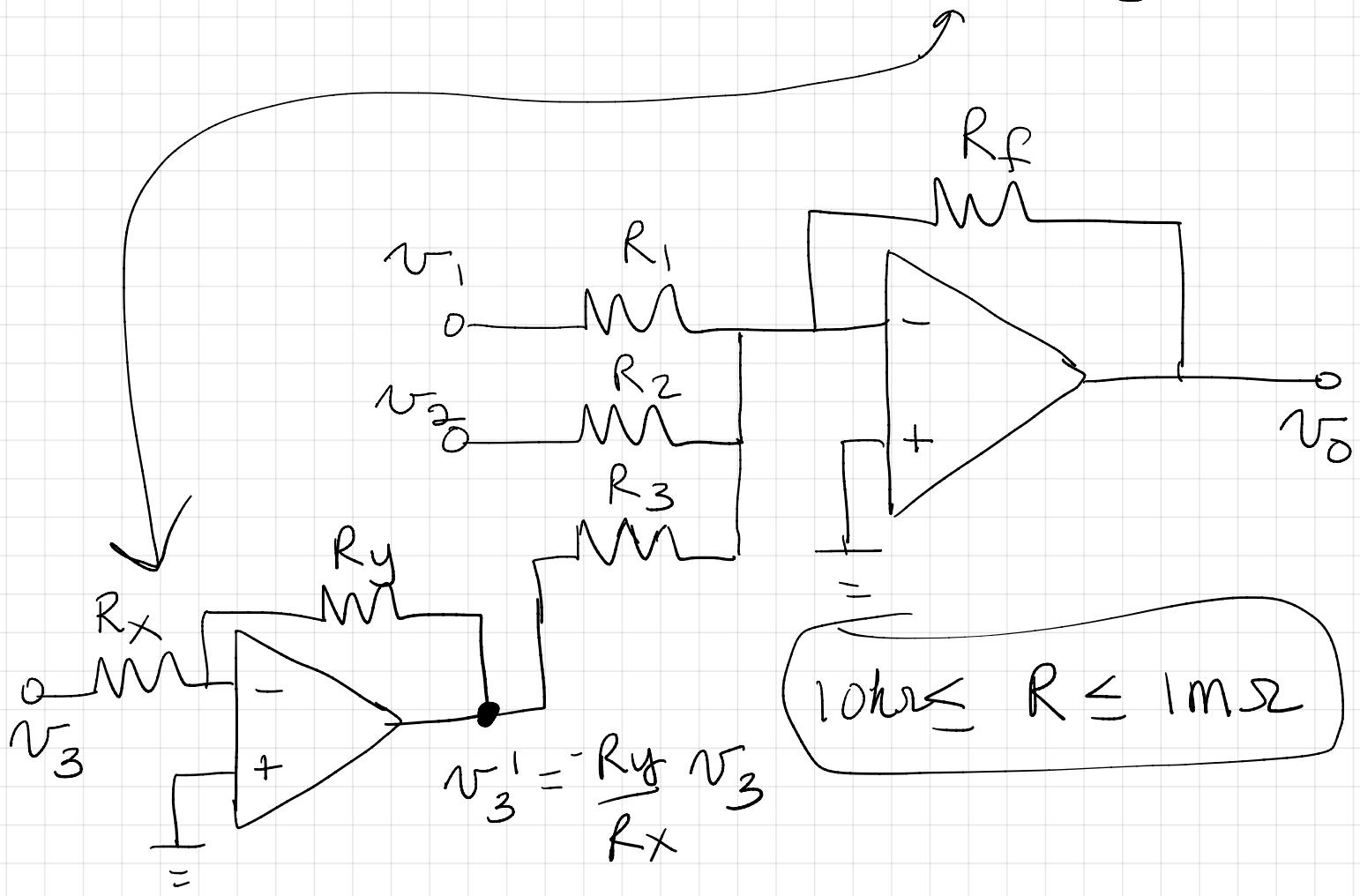

$$v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \frac{R_f}{R_3} v_3^{-1}$$

$$v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} \cdot \frac{R_y}{R_x} v_3$$

$$\frac{R_f}{R_1} = 12$$

$$\frac{R_f}{R_2} = 3$$

$$\frac{R_y}{R_x} \frac{R_f}{R_3} = 2$$

$$\text{let } R_f = 600 \text{ k}\Omega$$

$$R_y = 10 \text{ k}\Omega$$

$$R_x = 10 \text{ k}\Omega$$

$$R_3 = \frac{R_y \cdot R_f}{R_x / 2}$$

$$R_3 = 300 \text{ k}\Omega$$


$$R_1 = \frac{R_f}{12}$$

$$R_2 = \frac{R_f}{3}$$

$$R_1 = 50 \text{ k}\Omega$$


$$R_2 = 200 \text{ k}\Omega$$

⑤

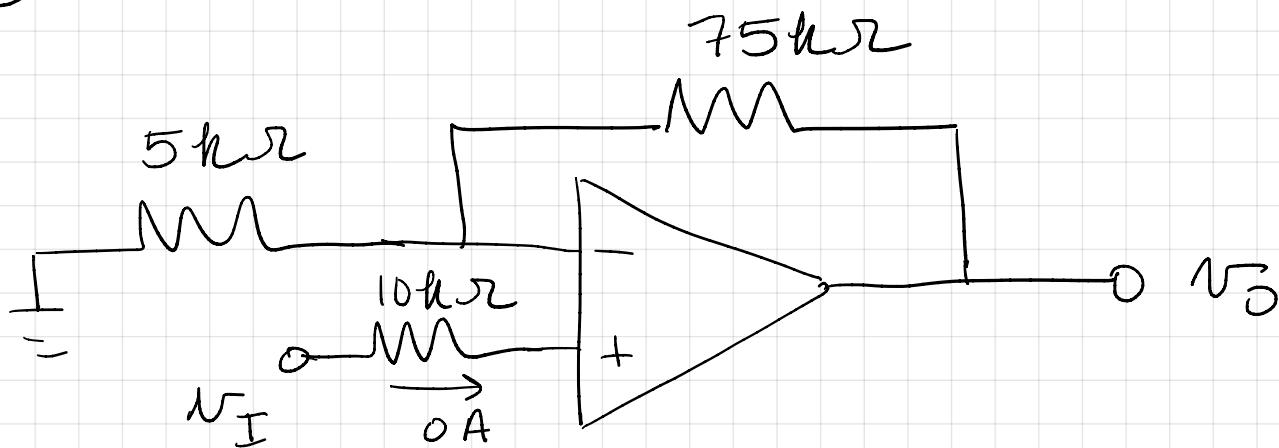

$$R_i = \infty$$

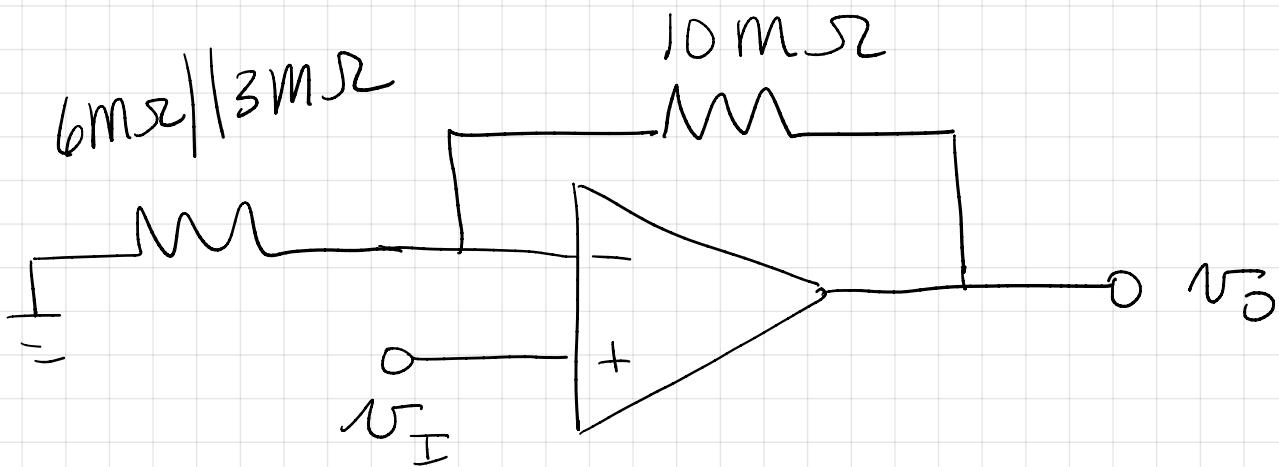
$$G = 1 + \frac{75}{5} = 16 \text{ V/V}$$



$$R_i = \infty \quad G = 1 + \frac{10}{2} = \frac{6\text{ V}}{\text{V}}$$

⑥ (to control gain)
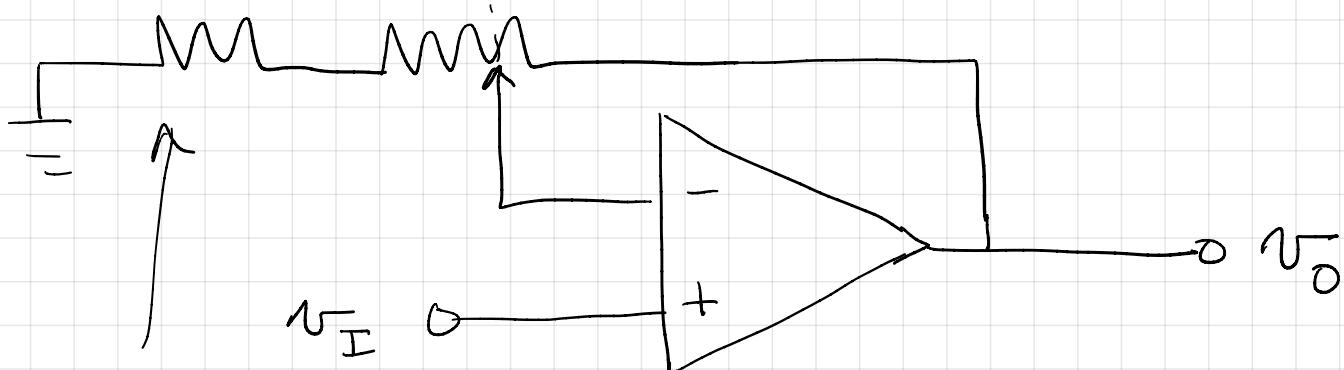
$$R_A = 10x \text{ k}\Omega, 10(1-x)\text{k}\Omega$$



add a fixed

resistor that prevents the gain from  
going to infinity

when  $x=0$  (max gain)       $x=1$  (min gain)

$$R_1 = R_A$$

$$R_2 = 0$$

$$R_2 = 10\text{k}\Omega$$

$$R_1 = R_A + 10\text{k}\Omega$$

$$G = 11 \text{ V/V}$$

$$G = 1$$

$$G = 1 + \frac{R_2}{R_1} = 11$$

$$\frac{R_2}{R_1} = 10$$

$$\frac{10k\Omega}{R_A} = 10$$

$$R_A = 1k\Omega$$

7.

inverting amp

$$\begin{aligned} R_2 &= 100k\Omega \\ R_1 &= 5k\Omega \end{aligned} \quad \left. \begin{array}{l} \text{choose these} \\ \text{at random} \end{array} \right\}$$

ideal :  $G = -\frac{R_2}{R_1} = -20V/V$

finite :  $G = \frac{-R_2 / R_1}{1 + \frac{1}{A} \left( 1 + \frac{R_2}{R_1} \right)}$

A (V/V)

100	- 16.53
1,000	- 19.59
10,000	- 19.96
100,000	- 19.996
1,000,000	- 19.9996

G (V/V)



looking at this range

A changes by a factor of 1000

G changes by a factor of 1.02


pretty stable ya!

Cont non-inverting

ideal  $R_2 = 100k\Omega$  } again  
 $R_1 = 5k\Omega$  } chose random

$$\frac{V_O}{V_I} = 1 + \frac{R_2}{R_1} = 21 \text{ V/V}$$
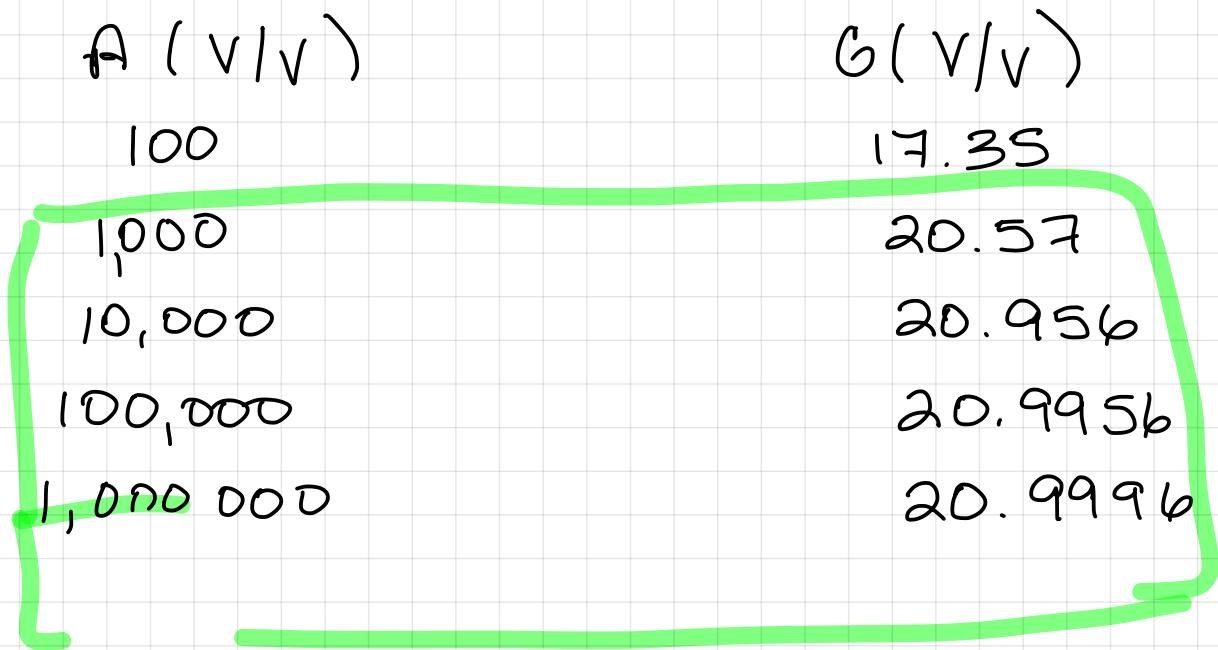
$$\text{ideal } G = \frac{1 + R_2/R_1}{1 + \frac{1 + R_2/R_1}{A}}$$



a

looking at this range

A changes by a factor of 1000

G changes by a factor of 1.02

pretty stable ya!



module  
2B practice  
problem  
solutions

① Difference Amp (assume ideal  
& matched  
resistors)

$$R_{id} = 2R_1 = 50\text{k}\Omega$$

$$\boxed{R_1 = 25\text{k}\Omega}$$

$$A_d = 50 = \frac{R_2}{R_1}$$

$$\boxed{R_2 = 1.25\text{M}\Omega}$$

for  $A_{cm} = 0$

$$\boxed{R_4 = R_2 = 1.25\text{M}\Omega}$$

$$\boxed{R_1 = R_3 = 25\text{k}\Omega}$$

② Since  $R_1 \neq R_3$   
 $R_2 \neq R_4$

$R_1 = 10\text{k}\Omega$   
 $R_2 = 55\text{k}\Omega$   
 $R_3 = 6\text{k}\Omega$   
 $R_4 = 58\text{k}\Omega$

$$A_{cm} = -\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right)$$

$$Ad = \frac{1}{2} \left( \frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right)\right)$$

$$A_{cm} = -\frac{55}{10} + \left(1 + \frac{55}{10}\right) \left(\frac{58}{6+58}\right)$$

$A_{cm} = 0.39 \text{ V/V}$

$$Ad = \frac{1}{2} \left( \frac{55}{10} + \left(1 + \frac{55}{10}\right) \left(\frac{58}{6+58}\right)\right)$$

$Ad = 5.70 \text{ V/V}$

$$CMRR = 20 \log \left| \frac{Ad}{A_{cm}} \right| = 23.29 \text{ dB}$$

$$(3) \quad Ad = \left( 1 + \frac{2R_2}{2R_1} \right) \left( \frac{R_4}{R_3} \right)$$

second gain stage

I didn't specify the size  
of the pot. I chose 100k $\Omega$

lots of possible designs!

$$\frac{R_4}{R_3} = 2 \frac{V}{V}$$

let

$$\boxed{\begin{aligned} R_4 &= 200\text{k}\Omega \\ R_3 &= 100\text{k}\Omega \end{aligned}}$$

$$2R_1 = R_f + 100\text{k}\Omega \quad \left\{ \begin{array}{l} \text{max: } R_f + 100\text{k}\Omega \\ \text{min: } R_f \end{array} \right.$$

$$Ad = \left( 1 + \frac{2R_2}{2R_1} \right)(2)$$

Ad = 5 for 2R<sub>1</sub> at max value

Ad = 500 for 2R<sub>1</sub> at min value

$$\left( 1 + \frac{2R_2}{R_f + 100\text{k}} \right)(2) = 5$$

$$\boxed{2R_2 = 1.5(R_f + 100 \times 10^3)}$$

$$\left(1 + \frac{2R_2}{R_f}\right)(2) = 500$$

$$2R_2 = 249 R_f$$



$$249 R_f = 1.5 R_f + 150 \times 10^3$$

$$247.5 R_f = 150 \times 10^3$$

$$R_f = 606.06 \Omega$$

$$R_2 = 75.45 k\Omega$$

(1)

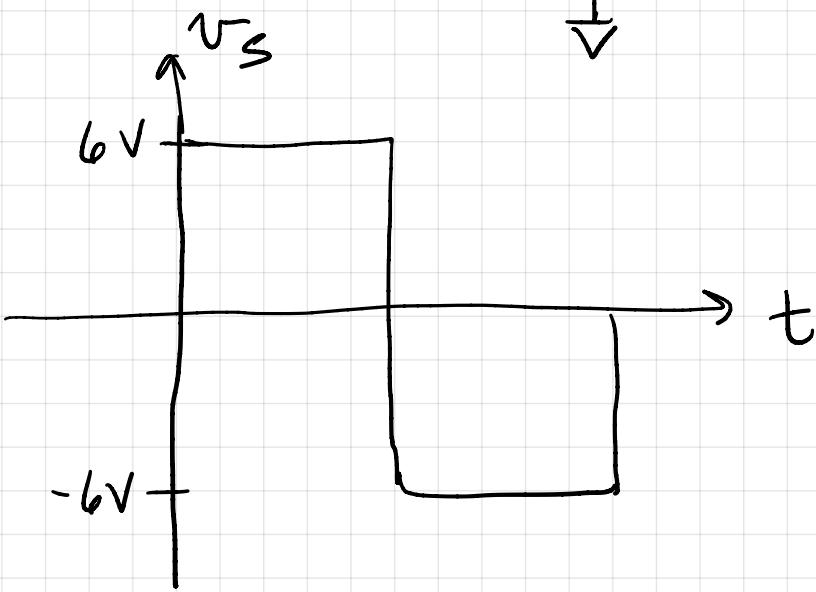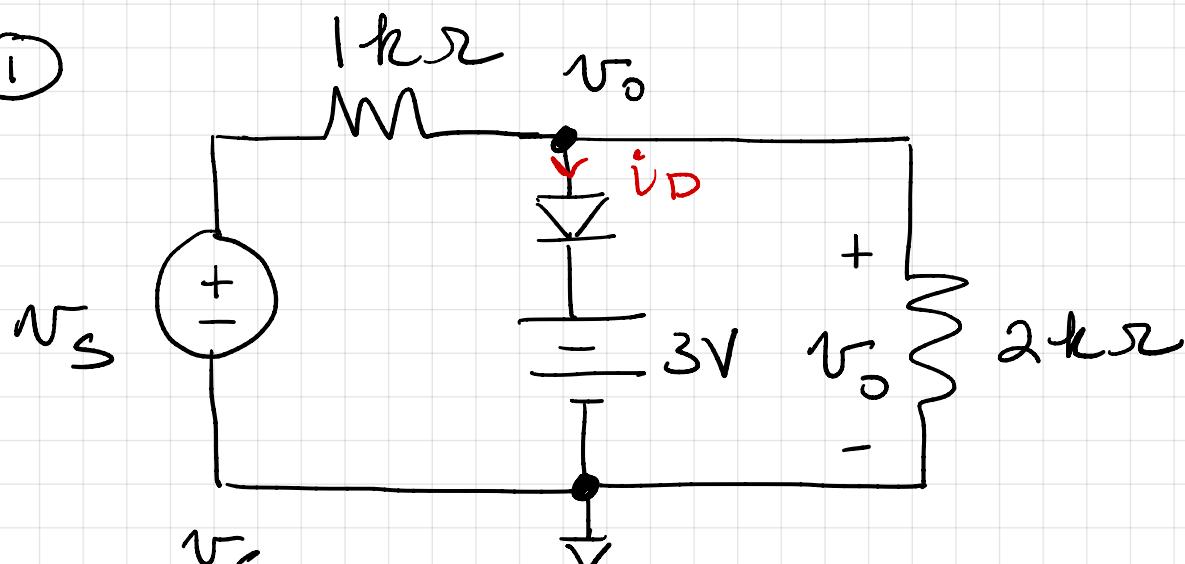

by modal analysis :

$$\frac{v_o - v_s}{1000} + i_D + \frac{v_o}{2000} = 0$$

$$i_D = \frac{v_s}{1000} - \left( \frac{v_o}{1000} + \frac{v_o}{2000} \right)$$

$$i_D = \frac{v_s}{1000} - \frac{v_o (1.5)}{1000}$$

$$i_D = v_S - 1.5 v_0 \text{ (mA)}$$

if diode is on :  $i_D > 0$

$$v_0 = 3V$$

there are two values of  $v_S$  :

$$v_S = +6V \text{ and } v_S = -6V$$

for  $v_S = 6V \Rightarrow$  assume diode on

$$v_0 = 3V, i_D = 6 - 1.5(3)$$

you!  
diode  
is on 

$$i_D = 1.5mA$$


for  $v_S = -6V \Rightarrow$  assume diode on

$$v_0 = 3V, i_D = -6 - 1.5(3)$$

Diode  
is off!   $i_D < 0$   
 $= -10.5mA$


When the diode is off

/

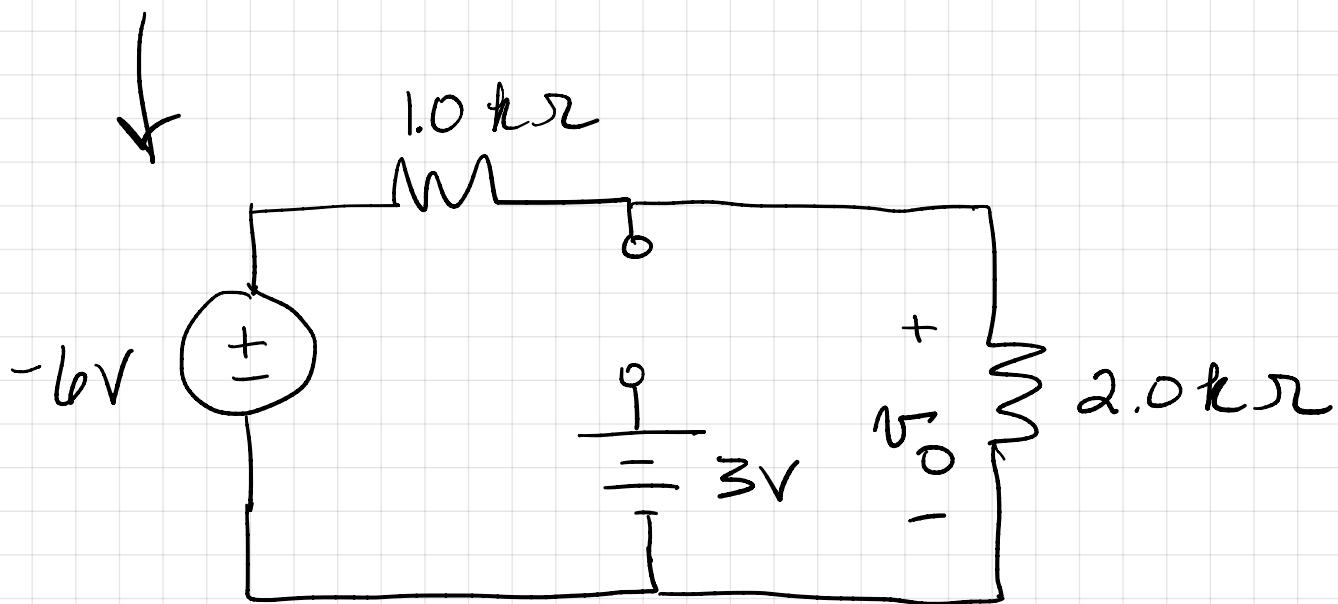

by voltage division
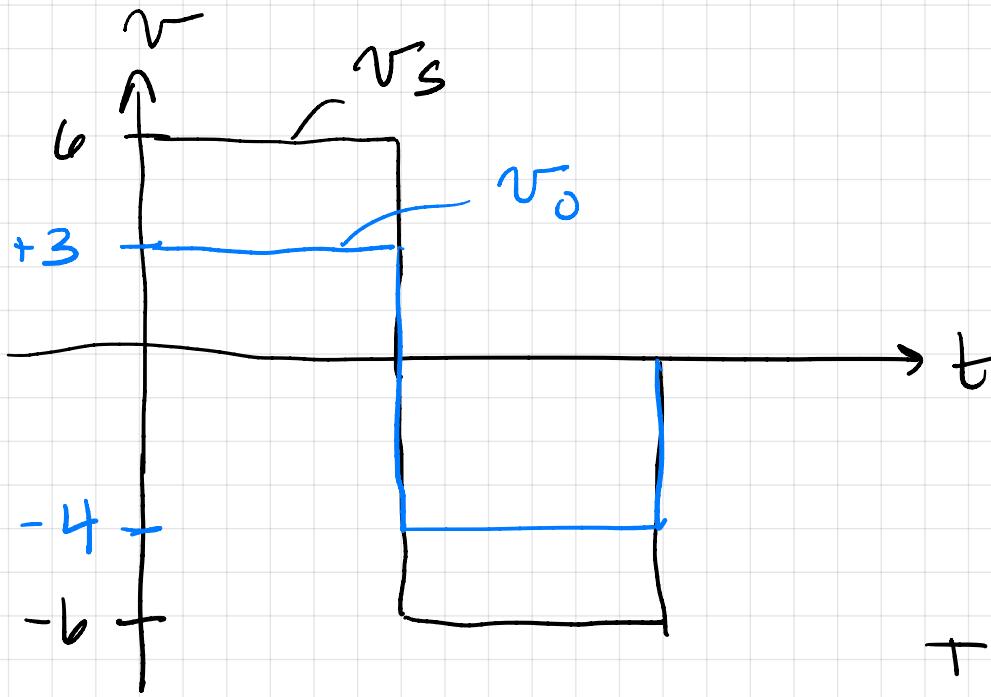
$$v_o = -6 \left( \frac{2}{3} \right) = -4\text{V}$$



$$\text{Average value} = \frac{1}{T_0} \int_0^{T_0} v_o(t) dt$$

$$V_0 = \frac{1}{T} \left[ \int_0^{T/2} 3 dt + \int_{T/2}^T -4 dt \right]$$


$$= \frac{1}{T} \left[ 3t \Big|_0^{T/2} + (-4t) \Big|_{T/2}^T \right]$$

$$= \frac{1}{T} \left( \frac{3T}{2} + (-4T + 2T) \right)$$


$$= \frac{1}{T} \left( -\frac{T}{2} \right)$$

$$\boxed{V_0 = -0.5 V}$$

(2)

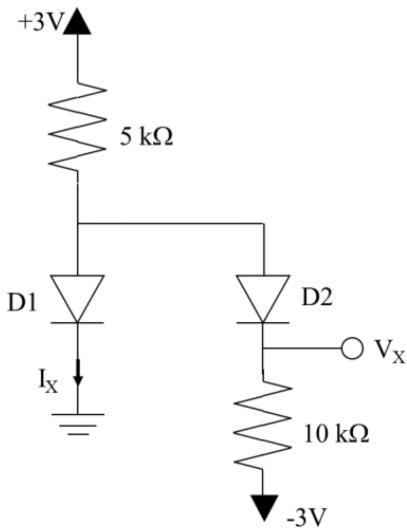

Assume both diodes are on.

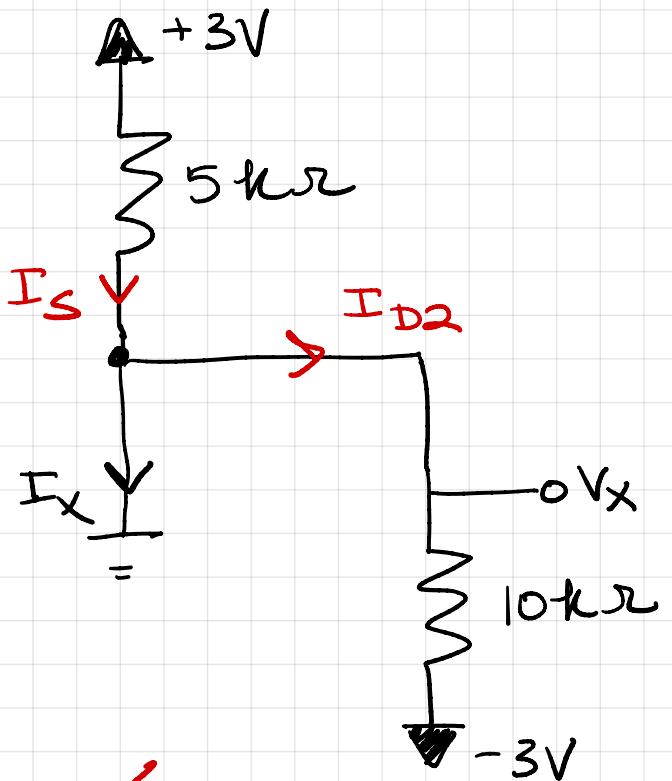

$$I_X \text{ & } I_{D2} > 0$$

$$V_x = 0V$$

$$I_{D2} = \frac{0 - (-3)}{10} = 0.3 \text{ mA} \quad \checkmark$$

$$I_S = \frac{3 - 0}{5} = 0.6 \text{ mA}$$

by KCL :

$$\begin{aligned} I_X &= I_S - I_{D2} \\ &= 0.6 - 0.3 \end{aligned}$$


$$I_X = 0.3 \text{ mA} \quad \checkmark$$

(3)

▼ -3V

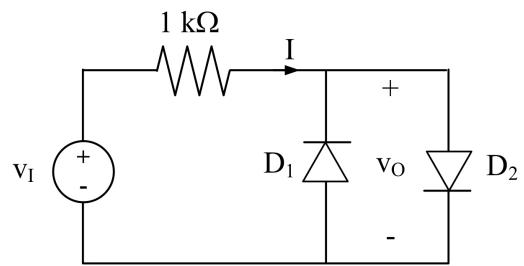3. For the following circuit,  $v_I = 10 \cos(t)$  volts.  
 Assume ideal diodes.

- For what values of  $v_I$  is diode 1 on?
- For what values of  $v_I$  is diode 2 on?
- What is the peak current value,  $I$  (magnitude only required).
- Plot the voltages,  $v_I$  and  $v_O$ .



a) D1 is on when  $v_I < 0$

$$I = -10 \text{ mA}$$

$$I < 0$$

$$v_O = 0V$$


b) D2 is on when  $v_I > 0$

$$I = +10 \text{ mA}$$

$$I > 0$$


$$v_O = 0V$$

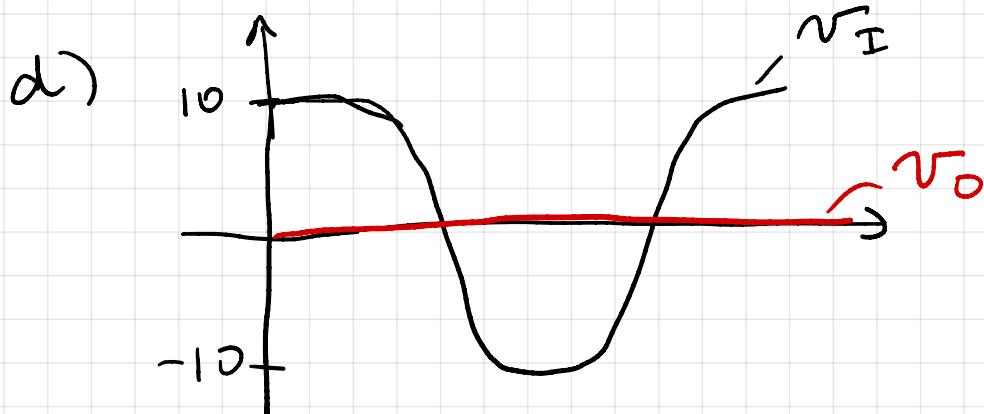c) peak current is  $\frac{10}{1000} = 10 \text{ mA}$



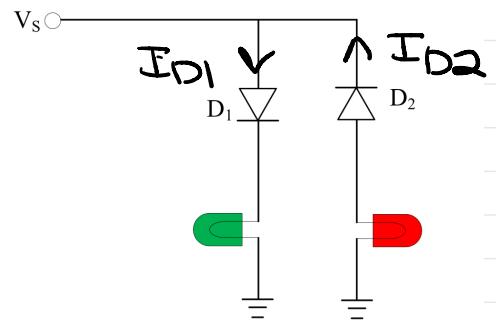4. Consider the following circuit. The voltage,  $V_s$ , can be either +3V, 0V, or -3V. The LED lights require +3 volts dropped across them in order to light up. Assume ideal diodes.

- What does  $V_s$  need to be for the green light (only) to be on?
- What does  $V_s$  need to be for the red light (only) to be on?
- Can both lights be on simultaneously?




a)  $V_s = 3V$

b)  $V_s = -3V$

c) no if  $V_s = 0$ , no current will flow.

(5)

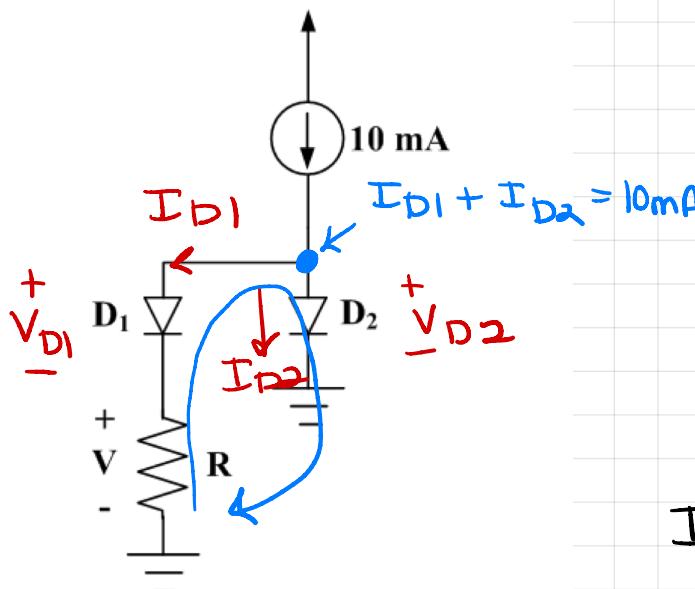

$$V = 80mV$$

$$R = \frac{V}{ID_1}$$

by KVL

$$V + V_{D1} - V_{D2} = 0$$

$$\begin{aligned} V_{D2} - V_{D1} &= V \\ &= 80mV \end{aligned}$$

$$\frac{ID_2}{ID_1} = \exp\left(\frac{V_{D2} - V_{D1}}{nV_T}\right)$$

$$\frac{ID_2}{ID_1} = \exp\left(\frac{80}{25}\right)$$

$$R = \frac{80}{0.392}$$

$$\frac{I_{D2}}{I_{D1}} = 24.53$$

$$I_{D2} = 24.53 I_{D1}$$


$$R = 204.24 \Omega$$

$$I_{D1} + I_{D2} = 10$$

$$25.53 I_{D1} = 10$$

$$I_{D1} = 0.392 \text{ mA}$$

⑥  $I_R = I_s - I_{D2}$

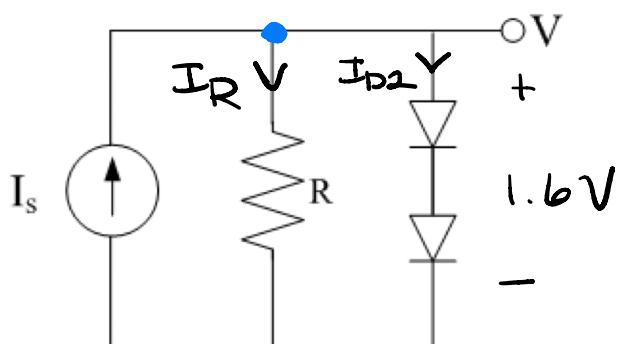

$$V = 1.6 \text{ V}$$

$$I_s = 100 \text{ mA}$$

$$\text{for } V_D = 0.7 \text{ V}$$

$$I_D = 1 \text{ mA}$$

diodes are identical, so each diode will provide  $\frac{1.6}{2} = 0.8 \text{ V}$

$$I_{D2} = I_{D1} \exp\left(\frac{V_{D2} - V_{D1}}{V_T}\right)$$

$$= (1) \exp\left(\frac{0.8 - 0.7}{25 \times 10^{-3}}\right) (\text{mA})$$


$$I_{D2} = 54.6 \text{ mA}$$

$$I_R = (100 - 54.6) = 45.4 \text{ mA}$$

$$R = \frac{1.4}{45.4 \times 10^{-3}}$$


$$R = 35.24 \Omega$$

7

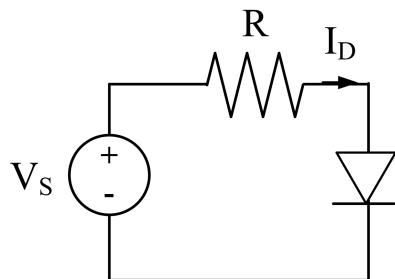

a) ideal


$$I_D = \frac{1}{200} = 5 \text{ mA}$$

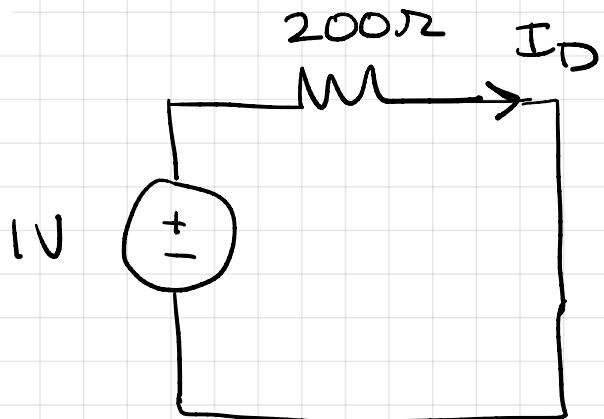

b) constant drop

$$I_D = \frac{1 - 0.75}{200}$$

$$I_D = 1.25 \text{ mA}$$

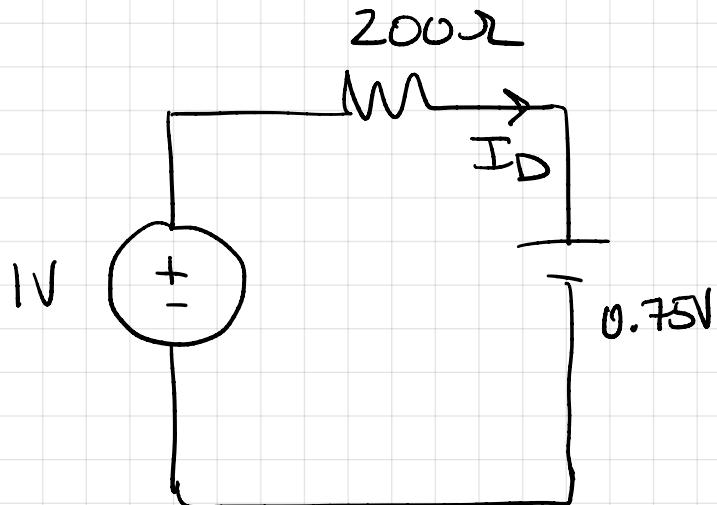

c) let  $V_{D_1} = 0.7 \text{ V}$

$$I_{D_2} = \frac{1 - 0.7}{200} = 1.5 \text{ mA}$$

$$(I_1, V_1) = (1 \text{ mA}, 0.7 \text{ V})$$

$$(I_2, V_2) = (1.5 \text{ mA}, 0.71 \text{ V}) \quad V_2 = V_1 + V_T \ln\left(\frac{I_2}{I_1}\right)$$
$$= 0.71 \text{ V}$$

---



$$I_{D_3} = \frac{1 - 0.71}{200} = 1.45 \text{ mA}$$

$$V_{D_3} = V_{D_2} + V_T \ln\left(\frac{I_{D_3}}{I_{D_2}}\right)$$
$$= 0.709 \text{ V}$$

$$I_{D_4} = \frac{1 - 0.709}{200} = 1.45 \text{ mA}$$


$$\boxed{I_D = 1.45 \text{ mA}}$$

8

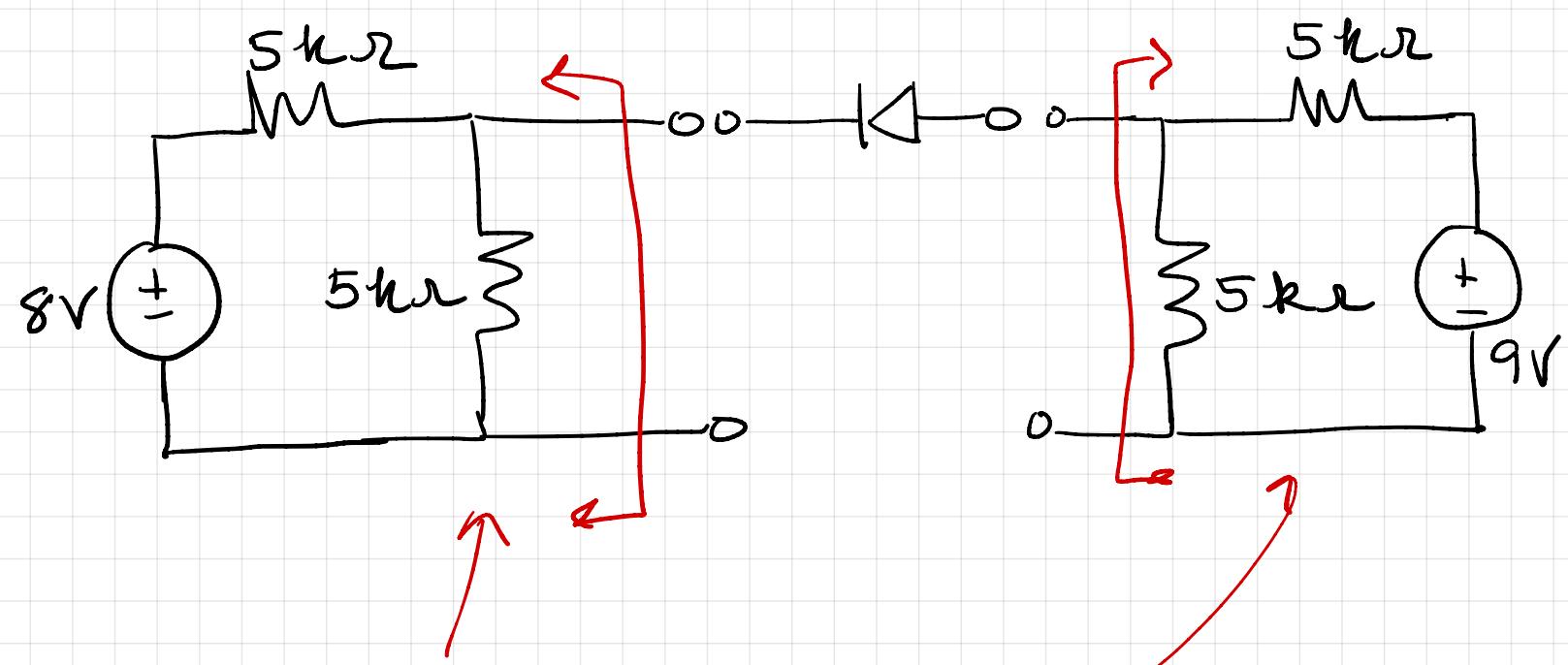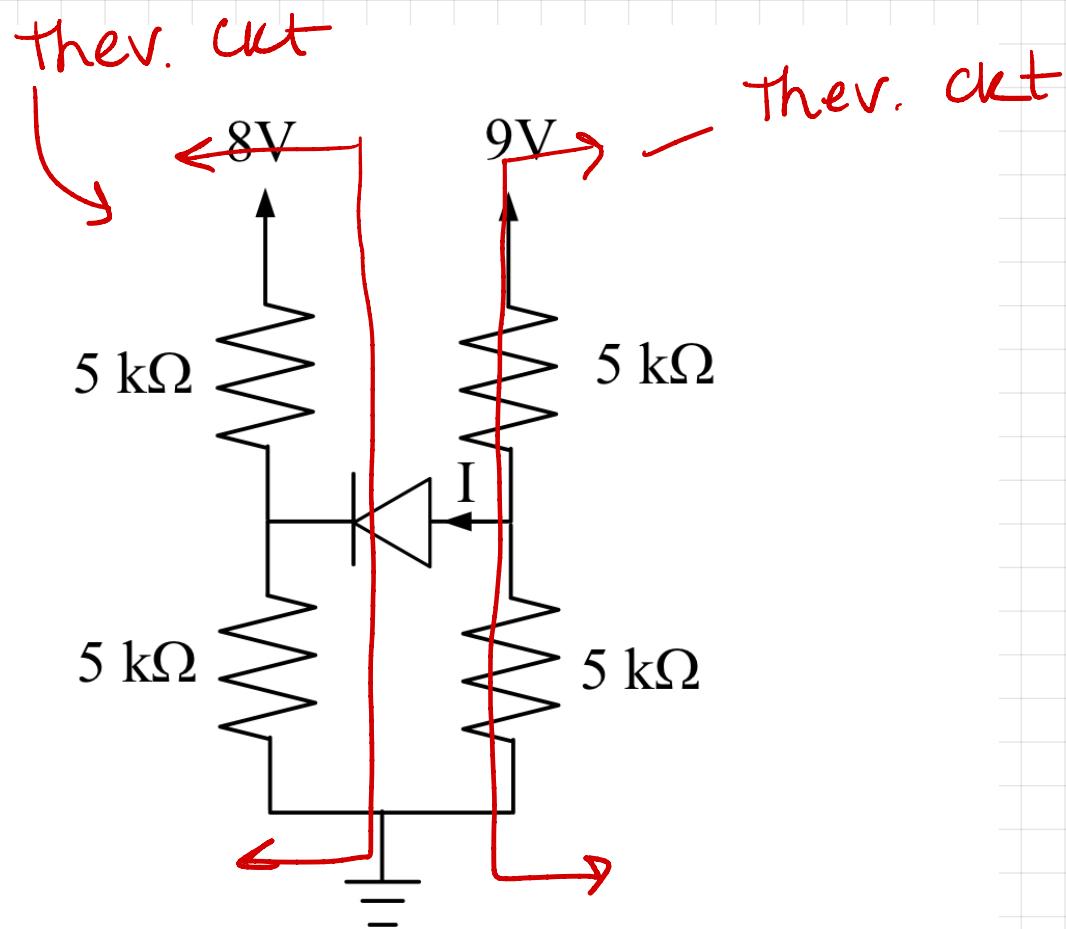

find  
ther. equivalent  
cuts

⑧ cont  $2.5\text{ k}\Omega$

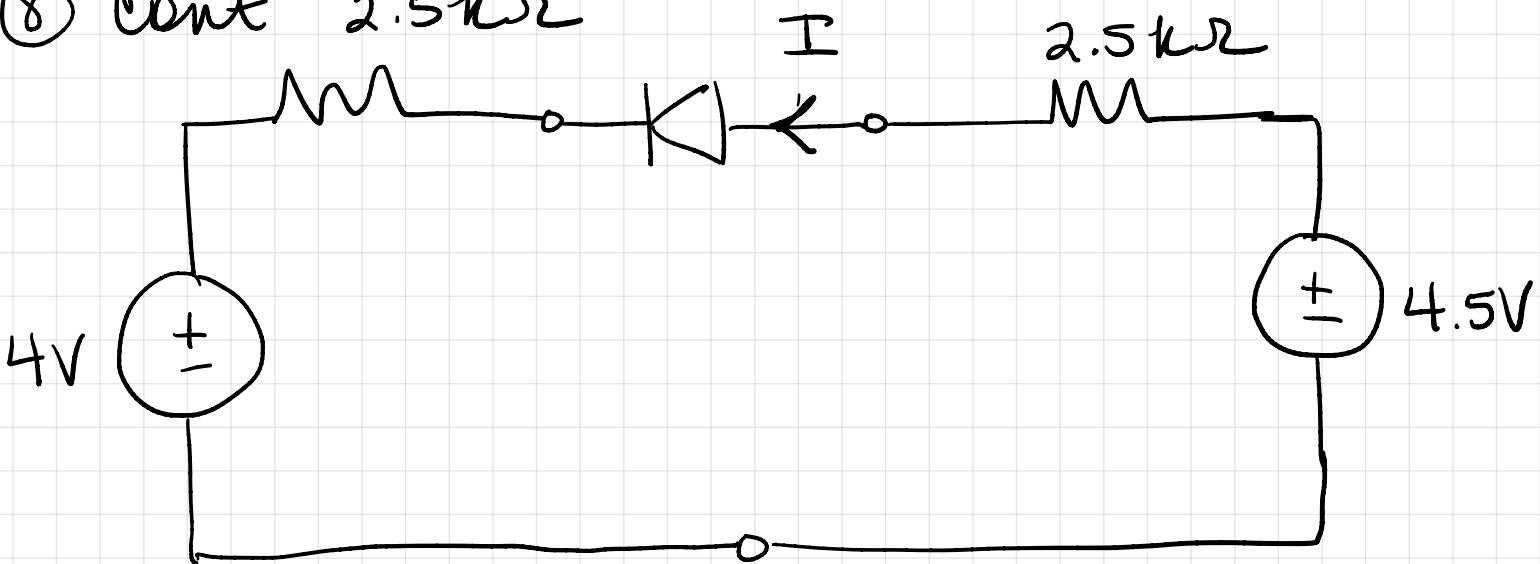

a) ideal

$$I = \frac{4.5 - 4}{5} = 0.1\text{ mA}$$

b) constant drop  $I = \frac{4.5 - 0.7 - 4}{5}$


$$I = -0.04\text{ mA}$$

current is negative

diode is off

$I = 0$ !

(9)

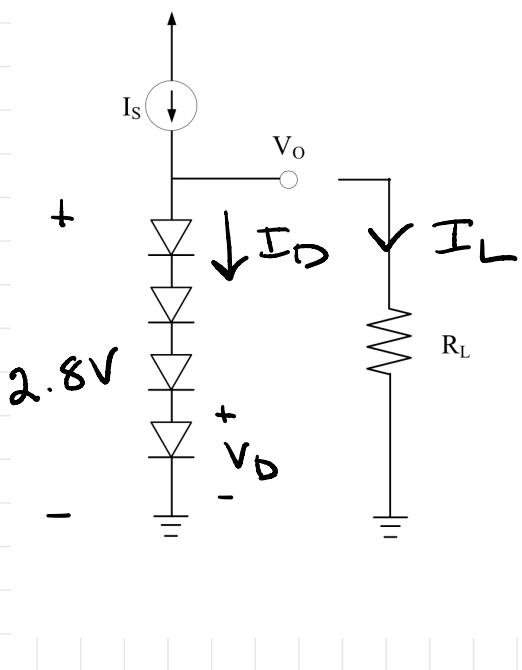sat current  $10^{-14} \text{ A}$  $I_s = ?$  for  $V_o = 2.8 \text{ V}$ 

diodes identical.

each diode has  $\frac{2.8}{4} \text{ V or } 0.7 \text{ V}$

$$I_D = (10^{-16})(\exp(0.7/0.025))$$

$$I_D = 0.145 \text{ mA} \quad (\text{no load})$$

$$\text{If } I_L = .1 \text{ mA}$$

$$I_D = I_s - I_L = .145 - 0.1$$

$$I_D = 0.045 \text{ mA}$$

$$V_D = V_T \ln\left(\frac{I_D}{10^{-16}}\right)$$



$$= 0.025 \ln\left(\frac{0.045 \times 10^{-3}}{10^{-16}}\right)$$

$$V_D = 0.671 \text{ V}$$

$$V_o = 4V_D = 2.68 \text{ V}$$

$$\boxed{\Delta V_o = 2.68 - 2.8 = -0.12 \text{ V}}$$

10

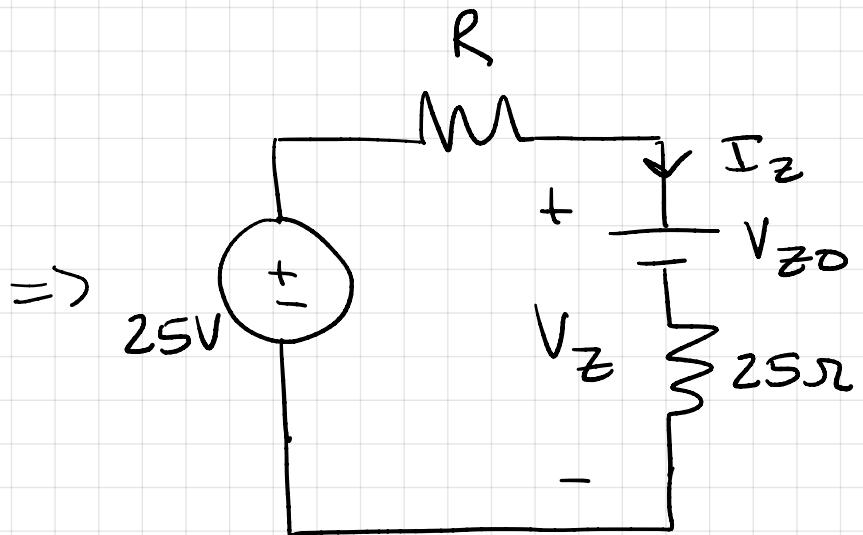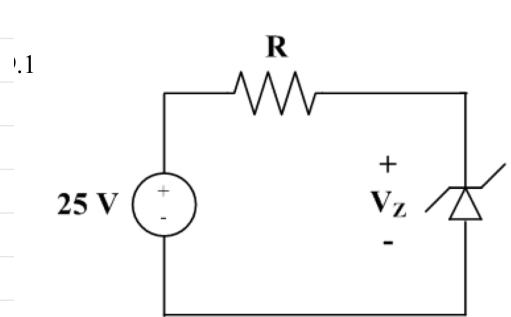

$$V_Z = 9.1V$$

$$I_Z = 3mA$$

$$\begin{aligned} V_{Z0} &= V_Z - I_Z r_Z \\ &= 9.1 - (.003)(25) \end{aligned}$$

$$V_{Z0} = 9.025V$$

for  $I_Z = 5mA$

$$V_Z = V_{Z0} + I_Z r_Z$$

$$V_Z = 9.025 + (.005)(25)$$

$$\boxed{V_Z = 9.15V}$$

$$R = \frac{25 - V_Z}{I_Z}$$

$$R = \frac{25 - 9.15}{5 \times 10^{-3}}$$

$$\boxed{R = 3.17 k\Omega}$$

# Module 4 - Assignment

pg 1

$$\textcircled{1} \quad V_{DS} = .1 \text{ V}$$

$$V_t = 1.5 \text{ V}$$

$$k'_n = 25 \mu\text{A}/\text{V}^2$$

$$V_{GS} = 0 \text{ V}$$

$$\frac{W}{L} = 10$$

$$V_{GS} < V_t \quad I_D = 0 \rightarrow \text{cut off}$$

$$V_{GS} = 1 \text{ V}$$

$$V_{GS} < V_t \quad I_D = 0 \rightarrow \text{cut off}$$

$$V_{GS} = 2 \text{ V}$$

$$V_{DS} < V_{GS} - V_t \quad \xrightarrow{\text{triode region}}$$

$$.1 < 2 - 1.5$$

$$I_D = k'_n \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$I_D = 25(10) \left[ (0.5)(.1) - \frac{1}{2} (.1)^2 \right]$$

$$I_D = 11.25 \mu\text{A}$$

$$V_{GS} = 3V$$

$$0.1 < 3 - 1.5$$

triode

$$I_D = 25(10) \left[ (1.5)(1) - \frac{1}{2} (1)^2 \right]$$

$$= 36.25 \mu A$$

(See my additional clarification note in the Module 4 lecture)

②  $V_{DS} = 3.3V$   $k'n = 37.5 \mu A/V^2$   
 $V_t = 1V$   $wL = 10$

$$V_{GS} = 0V \quad \text{cutoff} \quad I_D = 0$$

$$V_{GS} = 1V \quad \text{cutoff} \quad I_D = 0$$

$$V_{GS} = 2V \quad \text{Saturation}$$

$$V_{DS} > V_{GS} - V_t \quad I_D = \frac{1}{2} (k'n \frac{w}{L}) (V_{GS} - V_t)^2$$

$$3.3 > 2 - 1$$

$$I_D = \frac{1}{2} (37.5)(10)(1)^2$$

$$\boxed{I_D = 187.5 \mu A}$$

$$V_{GS} = 3V$$

saturation

$$V_{DS} > V_{GS} - V_t$$

$$3.3 > 3 - 1$$

$$\boxed{I_D = 750 \mu A}$$

③  $k'n = 25 \frac{\mu A}{V^2}$      $V_t = 1V$      $\frac{W}{L} = 10$

a)  $V_{GS} = 5V$      $V_{DS} = 6V$

$$V_{DS} > V_{GS} - V_t \Rightarrow \text{saturation}$$

$$I_D = \frac{1}{2} k'n \frac{W}{L} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} (25)(10)(4)^2$$

$$\boxed{I_D = 2mA} \quad \text{or } 2000 \mu A \quad \therefore$$

b)  $V_{GS} = 0$      $V_{DS} = 6V$

cutoff

$$I_D = 0$$

c)  $V_{GS} = 2V$

$$V_{DS} < 0$$

$$V_{DS} = -0.5V$$

cutoff

$$I_D = 0$$

$$\textcircled{4} \quad V_t = 0.8V$$

$$k'_n = 0.05 \frac{mA}{V^2}$$

$$\frac{w}{L} = 2$$

$$V_{DS} = 2.5V$$

$$\text{a) } \underline{x=0}$$

$$V_{DS} = 2V$$

$$V_{DS} = 10V$$

$$V_{DS} > V_{DS} - V_t$$

$$V_{DS} > V_{DS} - V_t$$

$$2 > 1.7$$

$$10 > 1.7$$

saturation

saturation

$$I_D = \frac{1}{2} k'_n \frac{w}{L} (V_{DS} - V_t)^2$$

$$I_D = 0.14mA$$

$$I_D = 0.14mA$$

$$\text{b) } \lambda = 0.02 V^{-1}$$

$$V_{DS} = 2V$$

$$V_{DS} = 10V$$

saturation

saturation

$$r_o = \frac{1}{\lambda I_D}$$

$$r_o = \frac{1}{\lambda I_D}$$

$$r_o = \frac{1}{(0.02)(0.14mA)}$$

$$r_o = 375.14 k\Omega$$

$$r_o = 375.14 k\Omega$$

$$I_D = \frac{1}{2} k_n \frac{W}{L} (V_{DS} - V_t)(1 + \lambda V_{DS})$$

$$\underline{I_D = 0.15 \text{ mA}}$$

$$I_D = 0.17 \text{ mA}$$

$$c) V_A = 35 \text{ V}$$

$$V_{DS} = 2 \text{ V}$$

$$r_o = \frac{V_A}{I_D}$$

still saturation  $V_{DS} = 10 \text{ V}$

$$r_o = 250 \text{ k}\Omega$$

$$r_o = 250 \text{ k}\Omega$$

$$I_D = 0.153 \text{ mA}$$

$$I_D = 0.19 \text{ mA}$$

$$⑤ k'_p = \frac{1 \text{ mA}}{V^2} \quad \frac{W}{L} = 2 \quad V_t = -2 \text{ V} \\ V_{SG} = 3 \text{ V}$$

$$a) V_{SD} = 0.5 \text{ V}$$

triode

$$V_{SD} < V_{SG} - |V_t|$$

$$0.5 \text{ V} < 1 \text{ V}$$

$$I_D = k'_p \frac{W}{L} \left[ (V_{SG} - |V_{tp}|) V_{SD} - \frac{1}{2} r_{SD}^2 \right]$$

$$= 0.75 \mu \text{A}$$

b)  $V_{SD} = 2V$

Saturation

$$V_{SD} > V_{SG} - |V_t|$$

$$I_D = \frac{1}{2} k' p \frac{W}{L} (V_{SG} - |V_t|)^2$$

$$I_D = 0.1 \text{ mA}$$


c)  $V_{SD} = 5V$

$$V_{SD} > V_{SG} - |V_t|$$

Saturation

$$I_D = 0.1 \text{ mA}$$

⑥

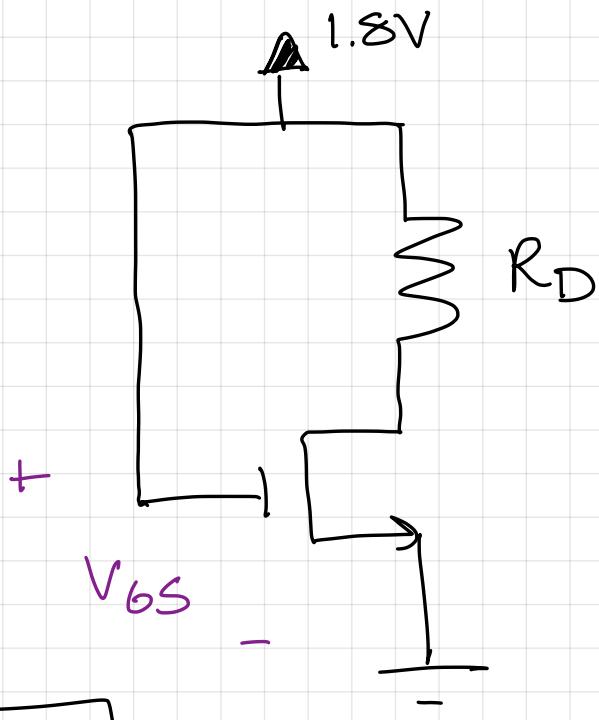

$$V_t = 0.5V$$

$$k'n = \frac{0.4 \text{ mA}}{\sqrt{V}}$$

$$\frac{W}{L} = 5$$

at edge of saturation

$$V_{DS} = V_{BS} - V_t$$

$$V_{BS} = 1.8V$$

$$V_{DS} = 1.8 - 0.5$$


$$V_D = 1.3V$$

$$V_{DS} = 1.3V$$

$$I_D = 1 \text{ mA}$$

$$R_D = \frac{1.8 - V_D}{I_D} = \frac{1.8 - 1.3}{1 \times 10^{-3}} = 0.5 \text{ k}\Omega$$

7

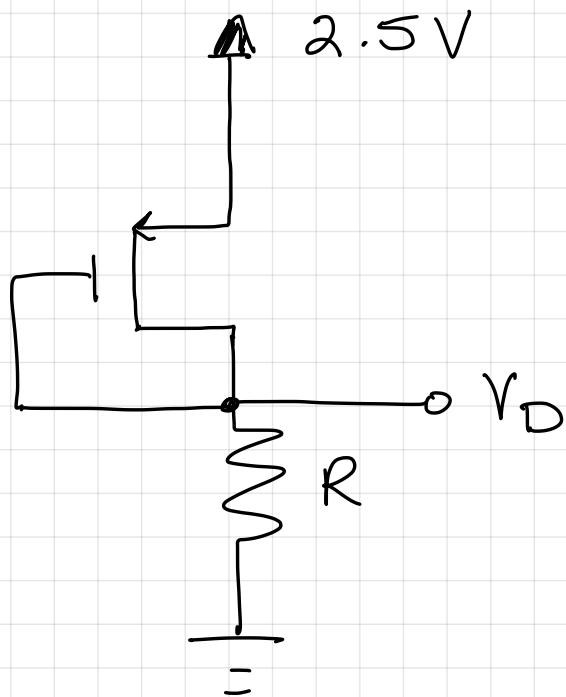

$$|V_t| = 0.6 \text{ V}$$

$$k'p = 250 \mu\text{A}/\text{V}^2$$

$$L = 0.25 \mu\text{m}$$

$$I_D = 0.8 \text{ mA}$$

$$V_D = 1.5 \text{ V}$$

gate & drain are tied together so device is in saturation.

$$V_D = V_G = 1.5 \text{ V}$$

$$V_{SG} = 2.5 - 1.5 = 1.0 \text{ V}$$


$$I_D = \frac{1}{2} k'p \frac{W}{L} (V_{SG} - |V_t|)^2$$

$$0.8 \times 10^{-3} = \frac{1}{2} (250 \times 10^{-6}) / \left( \frac{W}{0.25 \mu\text{m}} \right) (1 - 0.6)^2$$

$$\boxed{W = 10 \mu\text{m}}$$

$$R = \frac{V_D}{I_D} = \frac{1.5}{8 \times 10^{-3}} = 1.875 \text{ k}\Omega$$

(8)

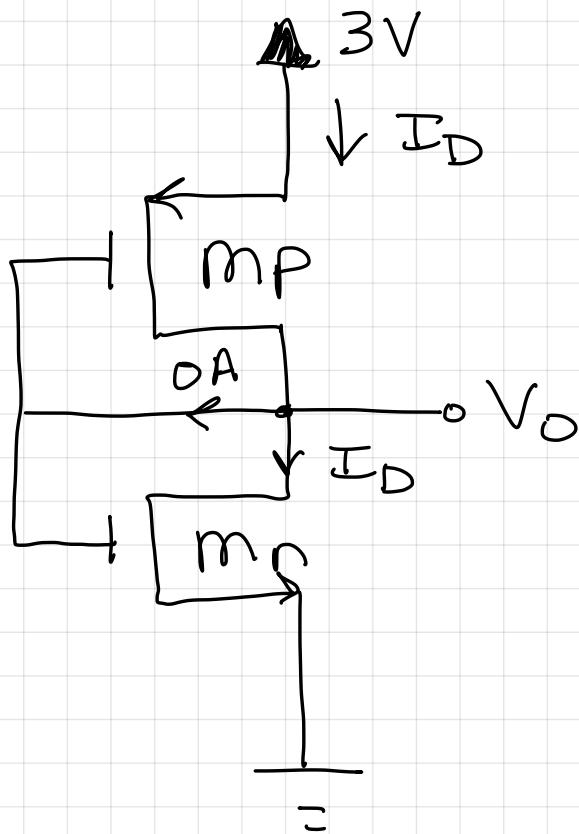

$$V_{tn} = |V_{tp}| = 1V$$

$$k'n = 20 \mu A/V^2$$

$$k'p = 8 \mu A/V^2$$

$$\frac{W}{L} = 3$$

Step 1: what mode is each device in?

for both devices: the drain and gate are tied together



Saturation

$$V_{Gsn} = V_O$$

$$V_{SGp} = 3 - V_O$$

(2) write current equations

$$I_{DP} = \frac{1}{2} k' p \left( \frac{w}{L} \right) (V_{SD} - |V_{TP}|)^2$$

$$I_{DN} = \frac{1}{2} k'n \left( \frac{w}{L} \right) (V_{DS} - V_{TN})^2$$

$$I_{DP} = \frac{1}{2} (8)(3)((3-V_0) - 1)^2$$

$$I_{DN} = \frac{1}{2} (20)(3)(V_0 - 1)^2$$

$$I_{DP} = I_{DN}$$

$$\frac{1}{2} (8)(3) (2 - V_0)^2 = \frac{1}{2} (20)(3) (V_0 - 1)^2$$

$$1.5 V_0^2 - V_0 - 1.5 = 0$$

two solutions

$$V_0 = 1.39V$$

$$V_0 = -0.72V$$

$$I_D = 4.56 \mu A$$

↑  
results  
in  
cutoff

# Practice Problems #5

1.  $V_{BE1} = 0.74 \text{ V}$        $V_{BE2} = 0.714 \text{ V}$

 $i_{C1} = 9.5 \text{ mA}$        $i_{C2} = \underline{\hspace{2cm}}$

$$\frac{i_{C2}}{i_{C1}} = \exp\left(\frac{V_{BE2} - V_{BE1}}{V_T}\right)$$

$$i_{C2} = (9.5) \left( \exp\left(\frac{.714 - .74}{.025}\right) \right)$$

$$\boxed{i_{C2} = 3.36 \text{ mA}}$$

2.  ~~$I_B$~~        $I_B = 0.01 \text{ mA}$   
 $I_C = 0.6 \text{ mA}$

$$I_E = I_C + I_B$$

$$\boxed{I_E = 0.61 \text{ mA}}$$

$$I_C = \alpha I_E$$

$$\alpha = \frac{I_C}{I_E} = 0.984$$

$$\boxed{\alpha = 0.984}$$

$$I_B = \frac{I_C}{\beta}$$

$$\beta = \frac{I_C}{I_B}$$

$$\boxed{\beta = 60}$$

$$3. \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$= 5 \times 10^{-15} \exp\left(\frac{.64}{.025}\right)$$

$$\boxed{I_C = 0.656 \text{ mA}}$$

$$I_B = \frac{I_C}{\beta} \Rightarrow \frac{.656 \times 10^{-3}}{50} \text{ to } \frac{.656 \times 10^{-3}}{500}$$
$$= 13.1 \mu\text{A} \text{ to } 1.31 \mu\text{A}$$


$$I_E = I_C + I_B$$

$$I_E \Rightarrow 0.669 \text{ mA} \text{ to } 0.657 \text{ mA}$$

(4)

$$\beta = 50$$

$$|V_{BE}| = 0.8V$$

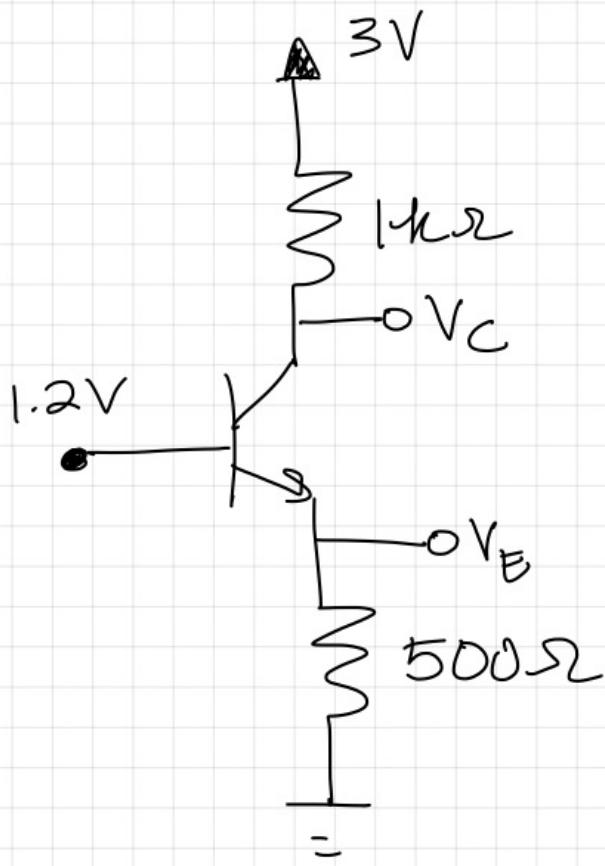

$$V_B = 1.2V$$

$$V_E = 0.4V$$

$$I_E = \frac{V_E}{500}$$

$$I_E = 0.8mA$$

$$\alpha = \frac{\beta}{\beta+1} = \frac{50}{51} = 0.98$$

$$I_C = \alpha I_E$$

$$I_C = 0.78mA$$

$$I_C = \frac{3 - V_C}{1k\Omega}$$


$$V_C = 2.22V$$

$$I_B = I_E - I_C$$

$$I_B = 0.02mA$$

$V_C > V_B > V_E \Rightarrow \text{active}$

④ cont

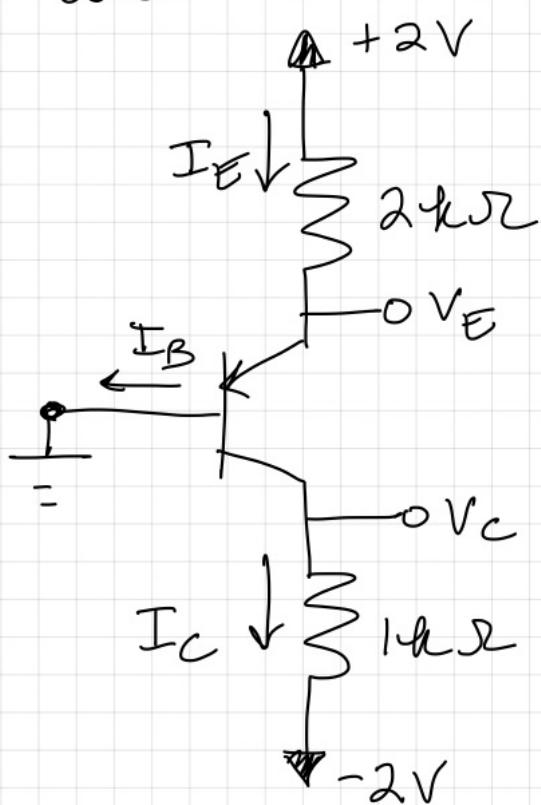

$$|V_{BE}| = 0.8V$$

$$\beta = 50$$

$$\boxed{V_B = 0}$$

$$V_E - V_B = 0.8V$$

$$\boxed{V_E = 0.8V}$$

$$I_E = \frac{2 - V_E}{2000}$$

$$\boxed{I_E = 0.6mA}$$

$$\frac{V_C + 2}{1000} = I_C \quad I_C = \alpha I_E = (0.98)(0.6)$$

$$V_C = -1.4V$$

$$\boxed{I_C = 0.59mA}$$


$$V_C < V_B < V_E$$

$\Downarrow$   
active  
 $\equiv$

$$I_B = I_E - I_C$$

$$\boxed{I_B = 0.01mA}$$

(5)

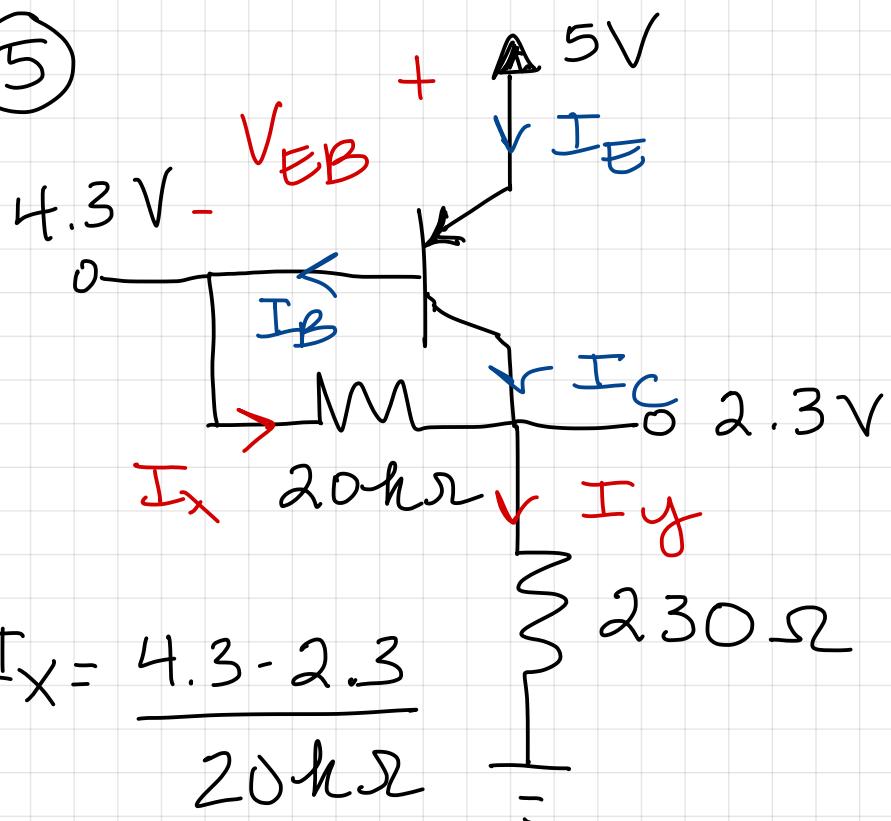

$$V_{EB} = 0.7V$$

Active

$$I_x = \frac{4.3 - 2.3}{20k\Omega} =$$

$$I_x = 0.1mA = I_B$$


$$\beta = \frac{I_C}{I_B}$$

$$I_y = \frac{2.3}{230} = 10mA$$

$$\boxed{\beta = 99}$$

$$\begin{aligned} I_C &= I_y - I_x \\ &= 9.9mA \end{aligned}$$

6

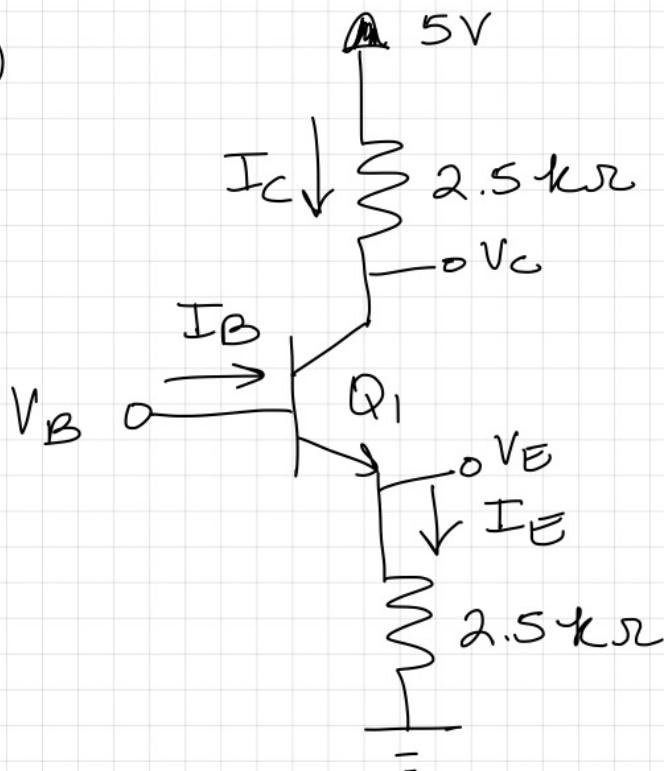

$$V_{BE} = 0.7V$$

$$V_E = V_B - V_{BE}$$

note:  
 $\beta \equiv \frac{\text{very}}{\text{large}}$

$$I_B = \frac{I_C}{\beta}$$

$$I_B \rightarrow 0$$

$$I_E \approx I_C$$

$$\beta = 100 \ (\alpha = 0.99)$$

$$V_B = 0$$

$$V_E = -0.7$$

$Q_1 \equiv$  cutoff

$$V_B = 1V$$

$$V_E = 0.3V$$

$$I_E = \frac{0.3}{2.5 \times 10^3} = 0.12mA$$

$$I_r = \alpha I_E = 0.119mA$$

$\beta \equiv \frac{\text{very}}{\text{large}}$

$$V_B = 0$$

$$V_E = -0.7V$$

$Q \equiv$  cut off

$$V_B = 1V$$

$$V_E = 0.3V$$

$$I_E = 0.12mA$$

$$I_C \approx 0.12mA$$

$$I_B \approx 0$$

$$I_B = I_E - I_C = 0.001 \text{ mA}$$

$$V_B = 2 \text{ V}$$

$$V_E = 1.3 \text{ V}$$

$$I_E = \frac{1.3}{2.5 \times 10^3} = 0.52 \text{ mA}$$

$$I_C = \alpha I_E = 0.515 \text{ mA}$$

$$I_B = 0.005 \text{ mA}$$

$$V_B = 2 \text{ V}$$


$$V_E = 1.3 \text{ V}$$

$$I_E = 0.52 \text{ mA}$$

$$I_C \approx 0.52 \text{ mA}$$

$$I_B \approx 0$$

(1)

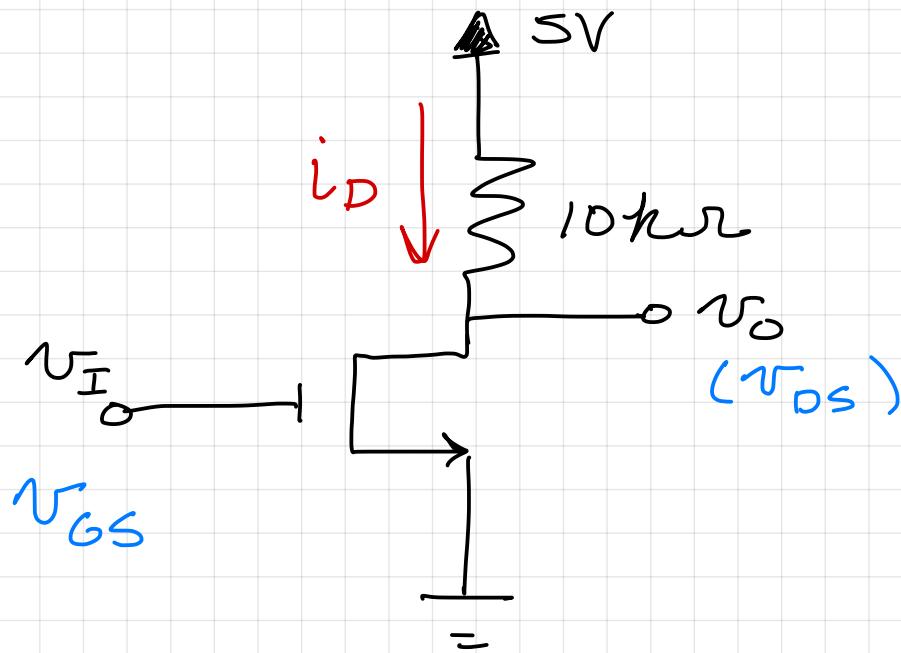

$$V_t = 1.5V$$

$$k_n' \frac{w}{L} = 0.2mA \frac{V^2}{V^2}$$

point A :  $V_I = V_t$  (cutoff)

$$V_o = V_{DD}$$

point B : edge of saturation

$$V_o = V_I - V_t$$

$\uparrow$                    $\uparrow$   
 $V_{DS}$                    $V_{GS}$

$$V_I = V_{GS} = V_t + \sqrt{1 + 2(R_D k_n' \frac{w}{L} V_{DD})} - 1$$

$R_D k_n' \frac{w}{L}$

$V_I = 3.29V$       or       $-1.29V$

$$V_O = V_{DS} = V_I - V_t$$

$$= 3.29 - 1.5$$

$$V_O = 1.79V$$

point C:

$$V_{GS} = V_I = V_{DD} = 5V$$


$$V_{DS} = V_D = \frac{V_{GS}}{1 + R_D k' n \frac{W}{L} (V_{GS} - V_t)}$$

$$V_O = V_{DS} = 0.625V$$

point A :  $(5V, 1.5V)$

point B :  $(1.79V, 3.29V)$

point C :  $(0.625V, 5V)$

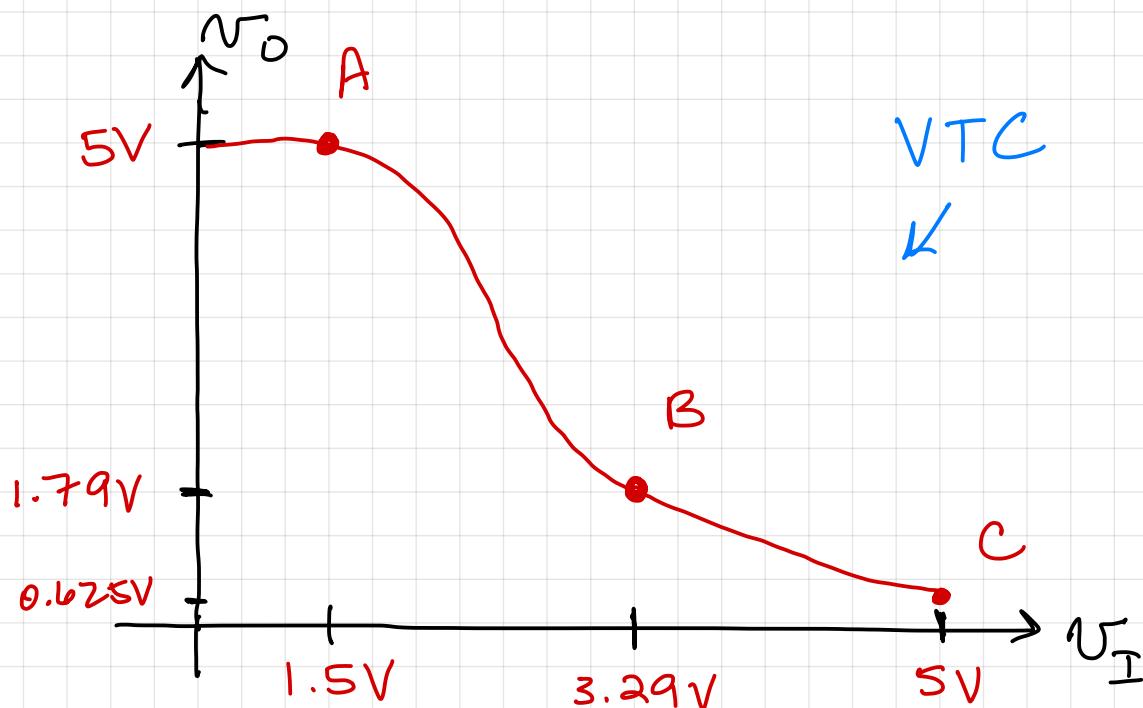

$$b) I_{DQ} = 0.15 \text{ mA}$$

$$V_{OQ} = V_{DSQ} = V_{DD} - I_{DQ} R_D$$

$$= 5 - (0.15)(10)$$

$$\boxed{V_{OQ} = 3.5 \text{ V}}$$


$$V_{IQ} = V_{GSQ}$$

$$I_{DQ} = \frac{1}{2} k'n \underbrace{\omega}_{L} (V_{IQ} - V_t)^2$$

$$0.15 = \frac{1}{2} (.2) (V_{IQ} - 1.5)^2$$

$$\boxed{V_{IQ} = 2.72 \text{ V}}$$

c)

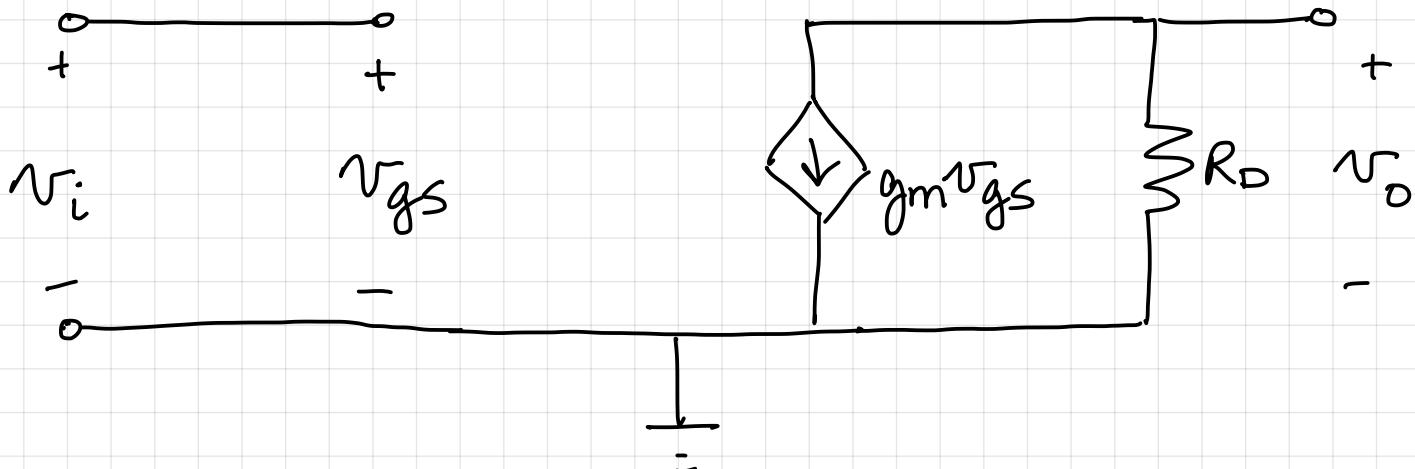

$$V_i = V_{gs}$$


$$A V_o = \frac{V_o}{V_i} = -g_m R_D$$

$$= - \left( k'n \underbrace{\omega}_L (V_{IQ} - V_t) \right) R_D$$

$$A_{VO} = - (0.2)(2.72 - 1.5)(10)$$

$$A_{VO} = -2.45 \text{ V/V}$$

(2)

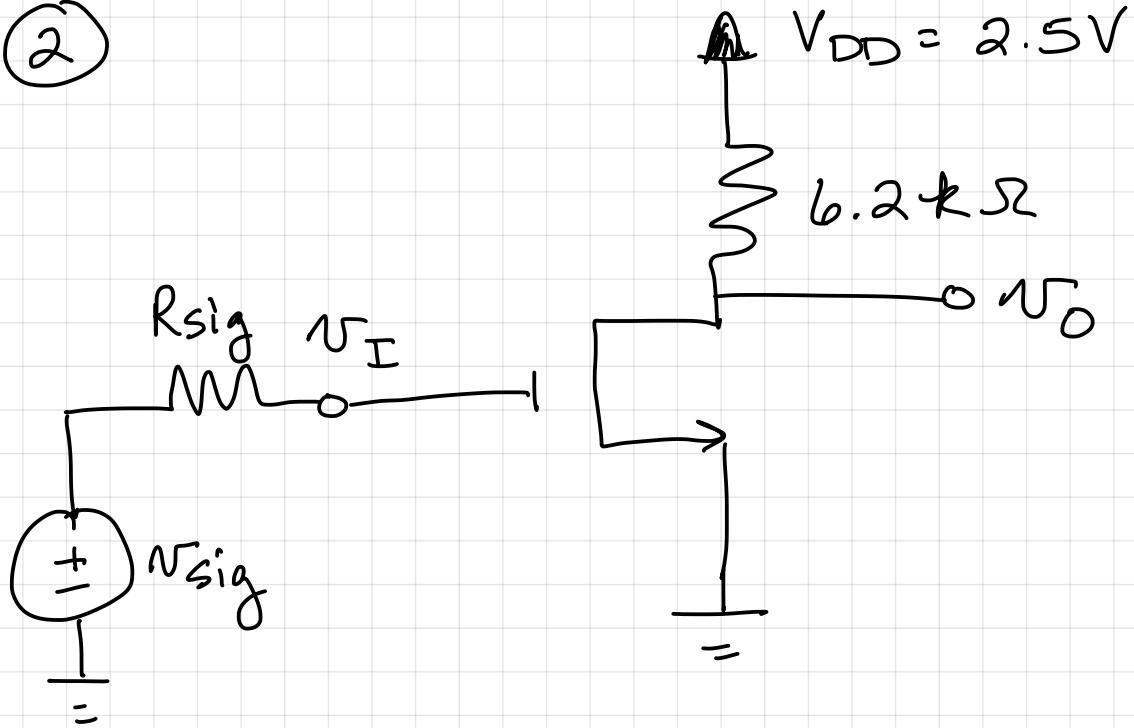

$$k'n = 0.4 \frac{\text{mA}}{\text{V}^2} \quad \frac{w}{L} = 10 \quad V_t = 0.4\text{V}$$

$$V_A = 10\text{V}$$

a)  $I_{DQ} = 0.2\text{mA} = \frac{1}{2} k'n \frac{w}{L} (V_{DSQ} - V_t)^2$

$$V_{DSQ} = 0.716\text{V}$$

$$V_{DSQ} = 2.5 - I_{DQ} R_D = 1.26\text{V}$$


$$b) R_{in} = \infty$$

$$g_m = k_r \frac{w}{L} (V_{BSQ} - V_t)$$

$$= 0.4(10)(0.716 - 0.4)$$

$$g_m = 1.264 \text{ mA/V}$$
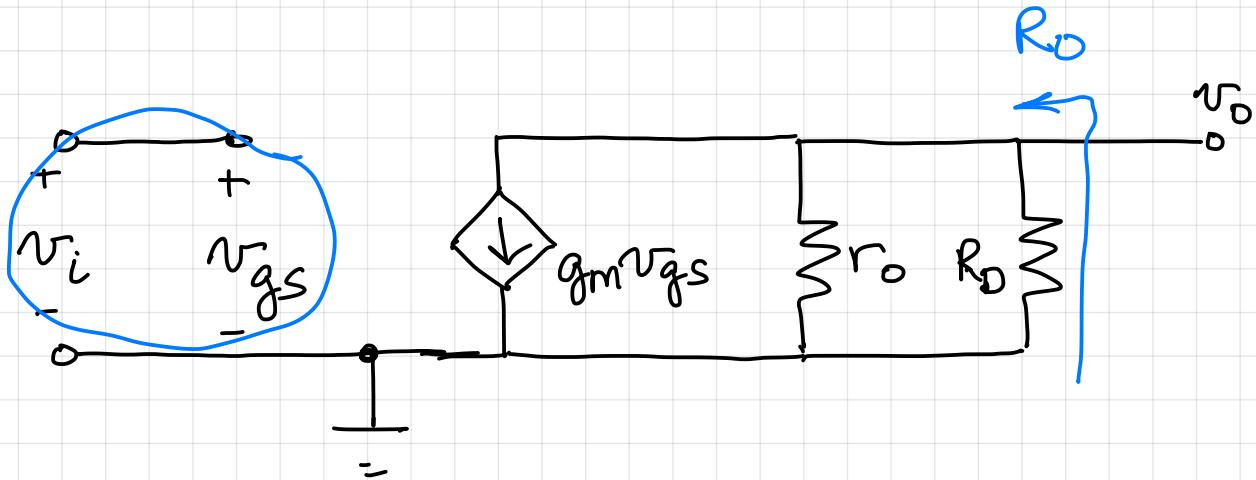
$$r_o = \frac{V_A}{I_{DQ}} = \frac{10}{.2 \times 10^{-3}} = 50 \text{ k}\Omega$$




$$R_o = r_o \parallel R_D = 50 \parallel 6.2 = 5.52 \text{ k}\Omega$$

$$A v_o = \frac{v_o}{v_i} = -g_m (r_o \parallel R_D)$$

$$= -1.264 (5.52)$$

$$= -6.98 \text{ V/V}$$

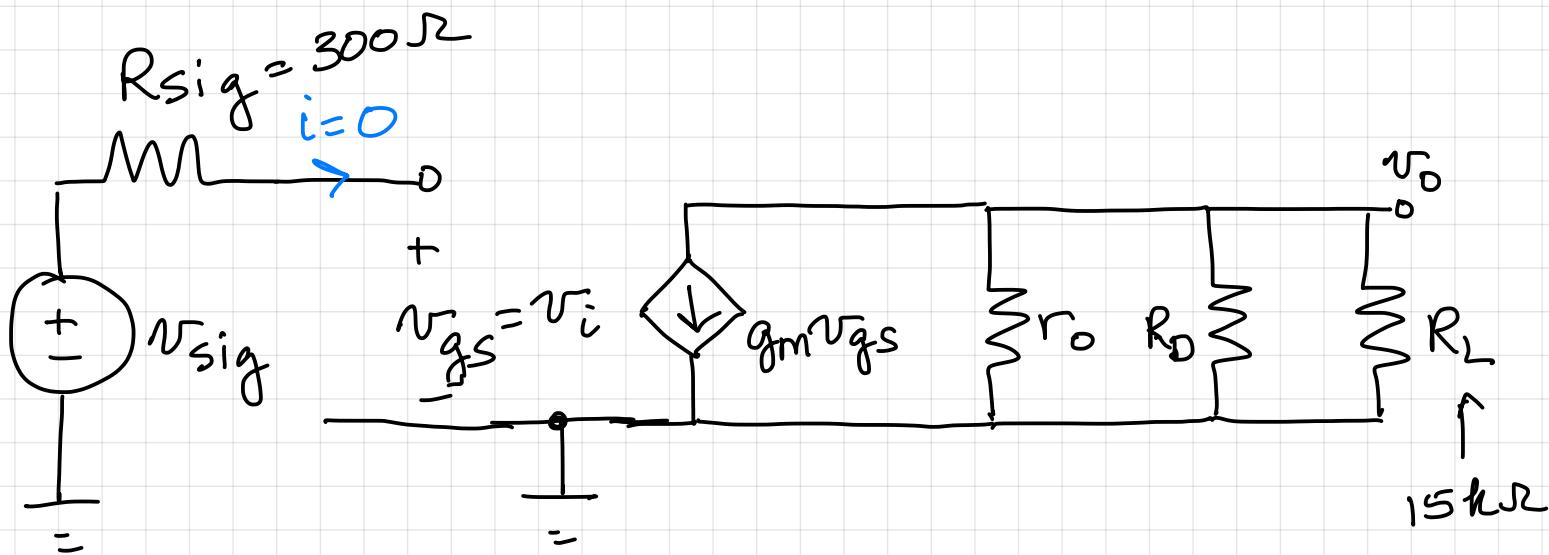

$$\begin{aligned}
 c) \quad A_v &= \frac{v_o}{v_i} = -g_m(r_o \parallel R_D \parallel R_L) \\
 &= -1.264 (50 \parallel 6.2 \parallel 15) \\
 A_v &= -5.1 \text{ V/V}
 \end{aligned}$$

a)

$$G_v = \frac{v_o}{v_{sig}} = -5.1 \text{ V/V}$$


$$(3) \quad g_m = \frac{4 \text{ mA}}{\text{V}}$$

$$R_D = 5 \text{ k}\Omega$$

$$R_L = 7.5 \text{ k}\Omega$$

$$R_{sig} = 500 \Omega$$
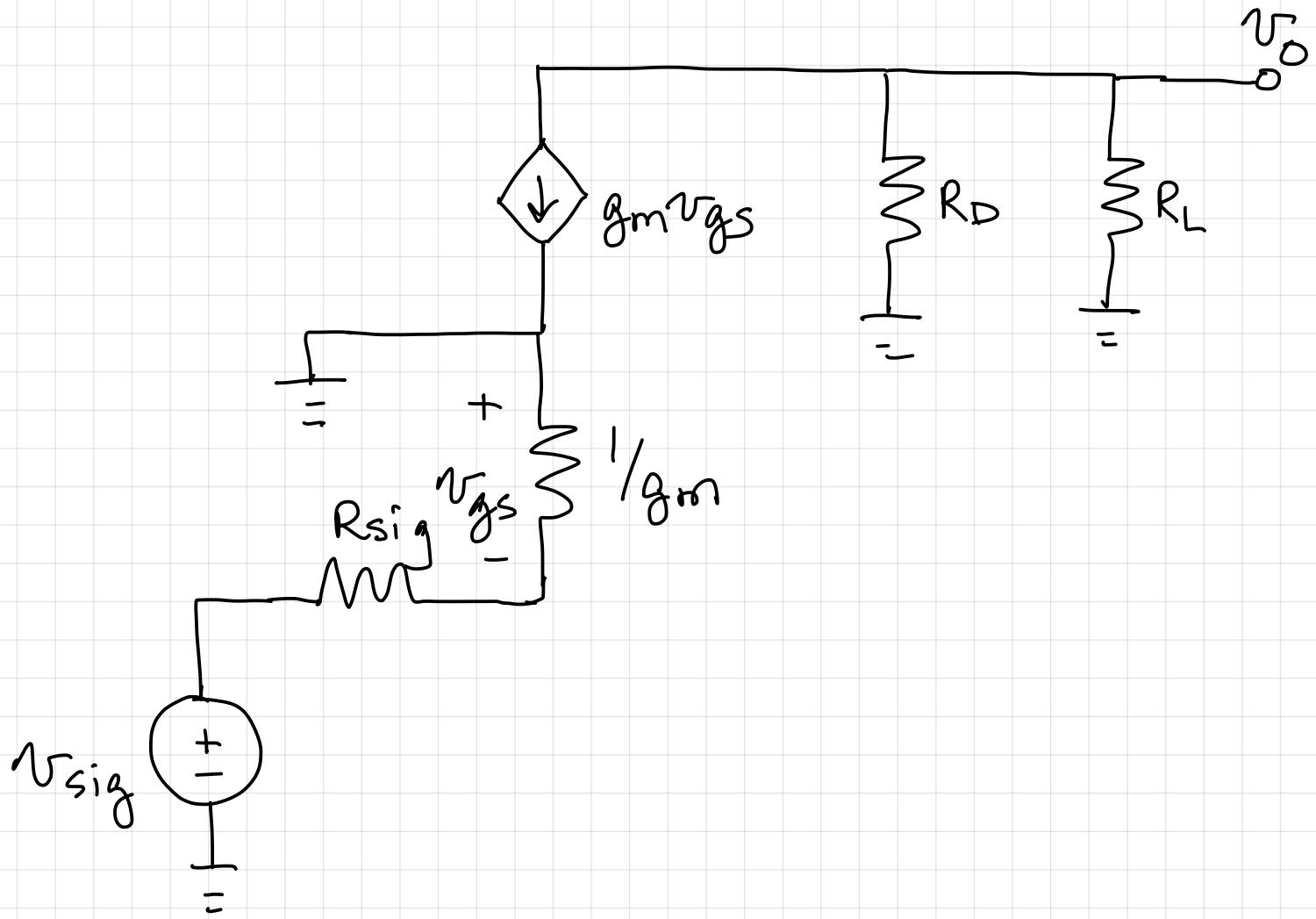
$$a) \quad R_{in} = \frac{1}{g_m} = \frac{1}{4 \times 10^{-3}} = 250 \Omega$$



$$G_v = \frac{(R_D || R_L)}{R_{sig} + \frac{1}{g_m}} = \frac{(5 || 7.5)}{500 + 250}$$

$$= \frac{3000}{750}$$

$$\boxed{G_v = 4 \text{ V/V}}$$

b)  $R_{in} = R_{sig}$  at the Q pt

what would the  $I_{DQ}$  need to change to.

$$R_{sig} = 500$$

$$R_{in} = 250 = \frac{1}{gm}$$

$$gm_1 = \frac{4mA}{V}$$

$$\frac{1}{gm} = 500$$

$$gm = 2 \frac{mA}{V}$$

$$I_{DQ} = \frac{1}{2} k'n \frac{w}{L} (V_{GSQ} - V_t)^2$$

$$gm = k'n \frac{w}{L} (V_{GSQ} - V_t)$$

$$gm = \frac{2 I_{DQ}}{(V_{GSQ} - V_t)}$$

$$(V_{GSQ} - V_t)^2 = \frac{2 I_{DQ}}{k'n w L}$$

$$(V_{GSQ} - V_t) = \sqrt{\frac{2 I_{DQ}}{k'n w L}}$$

$$g_m = \sqrt{2 k' n \frac{w}{L} I_{DQ}}$$

constant

$g_m$  reduces by a factor of  $\frac{1}{2}$

$I_{DQ}$  reduce by a factor  $\frac{1}{4}$

(4)  $\frac{CD}{k'n} = 0.1 \frac{mA}{V^2}$        $V_t = 0.6V$

$$V_{OSQ} = 0.85V$$

a)  $R_o = 300\Omega$  - what is  $\frac{w}{L}$

$$R_o = \frac{1}{g_m} = 300$$

$$g_m = 3.33 \frac{mA}{V} = k'n \frac{w}{L} (V_{OSQ} - V_t)$$

$$3.33 = .1 \left( \frac{w}{L} \right) (0.85 - 0.6)$$

$$\frac{w}{L} = 133.2$$

b)  $I_{DQ} = \frac{1}{2} k'n \frac{w}{L} (V_{OSQ} - V_t)^2$

$$I_{DQ} = \frac{1}{2} (.1)(133.2)(.85 - .6)^2$$

$$I_{DQ} = 0.416 \text{ mA}$$

c)  $R_L = 10k\Omega$  pot  $0 \rightarrow 10k\Omega$

$$G_V = \frac{R_L}{R_L + 1/g_m} = \frac{R_L}{R_L + 300}$$

for  $R_L = 0$   $G_V = 0$

$$R_L = 10k\Omega \quad G_V = 0.97 \text{ V/V}$$