


Small Signal Analysis

 → ignore since very small.

$$i_D = k'_n \frac{W}{L} [v_{gs}(v_{gsQ} - v_t)]$$

now v_{gs} and i_D are linearly related due to small signal.

$g_m \equiv$ mosfet trans conductance

$$A_v = -g_m R_D$$

Hybrid- π Small signal model

Example

① DC operating First

Find I_{DQ} ; V_{DSQ} ; V_{GSQ}

$I_{DQ} \downarrow$
 $\rightarrow 0$ $\begin{matrix} + \\ V_{DSQ} \\ - \end{matrix}$


$\begin{matrix} + \\ V_{GSQ} \\ - \end{matrix}$



② Small Signal analysis

o A + AC, DC voltage supply \rightarrow Ground.

o Capacitors will look like shorts.

 

$$R_G = 10\text{m}\Omega$$

o
G

$$R_D = 10\text{k}\Omega$$

o
P

$$R_L = 10\text{k}\Omega$$

S o

$$R_o \parallel R_D \parallel R_L$$

$$(47.2 \parallel 10 \parallel 10)$$

$$R_{eq} = 4.52 \text{ k}\Omega$$

$$A_v = -3.3 \checkmark$$

Finding input resistance

ii →

V_o

④ max swing.

\uparrow
 V_o

\uparrow
 V_i

→
larges input signal
and keep in saturation
w/o distorting output.

$$V_i = \frac{V_x}{1 + |A_v|}$$