

# CPE 322

## Digital Hardware Design Fundamentals


---

Electrical and Computer Engineering  
UAH

Algorithmic State Machine Notation



# Example: Faster Multiplier

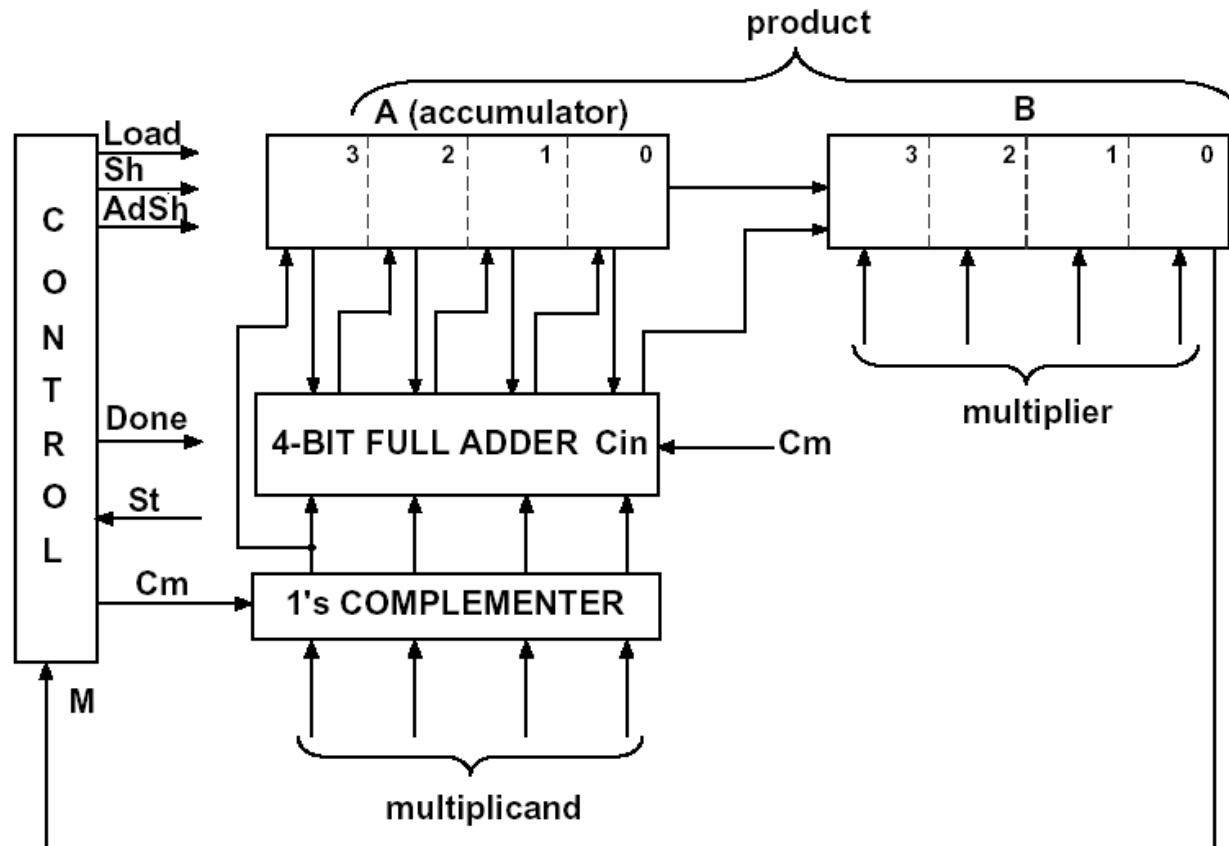


- Move wires from the adder outputs one position to the right => add and shift can occur at the same clock cycle

# Extended State Transition Graph

---


- Similarities to basic State Transition Graph
  - Nodes represent states
  - Arcs (or edges) represent transition between states
  - Labelling on arcs are Inputs/Outputs
- Differences with basic State Transition Graph
  - To reduce Clutter
    - Only Inputs that impact a transition from one state to another are present.
    - Only Outputs that are TRUE for a given transition are listed.
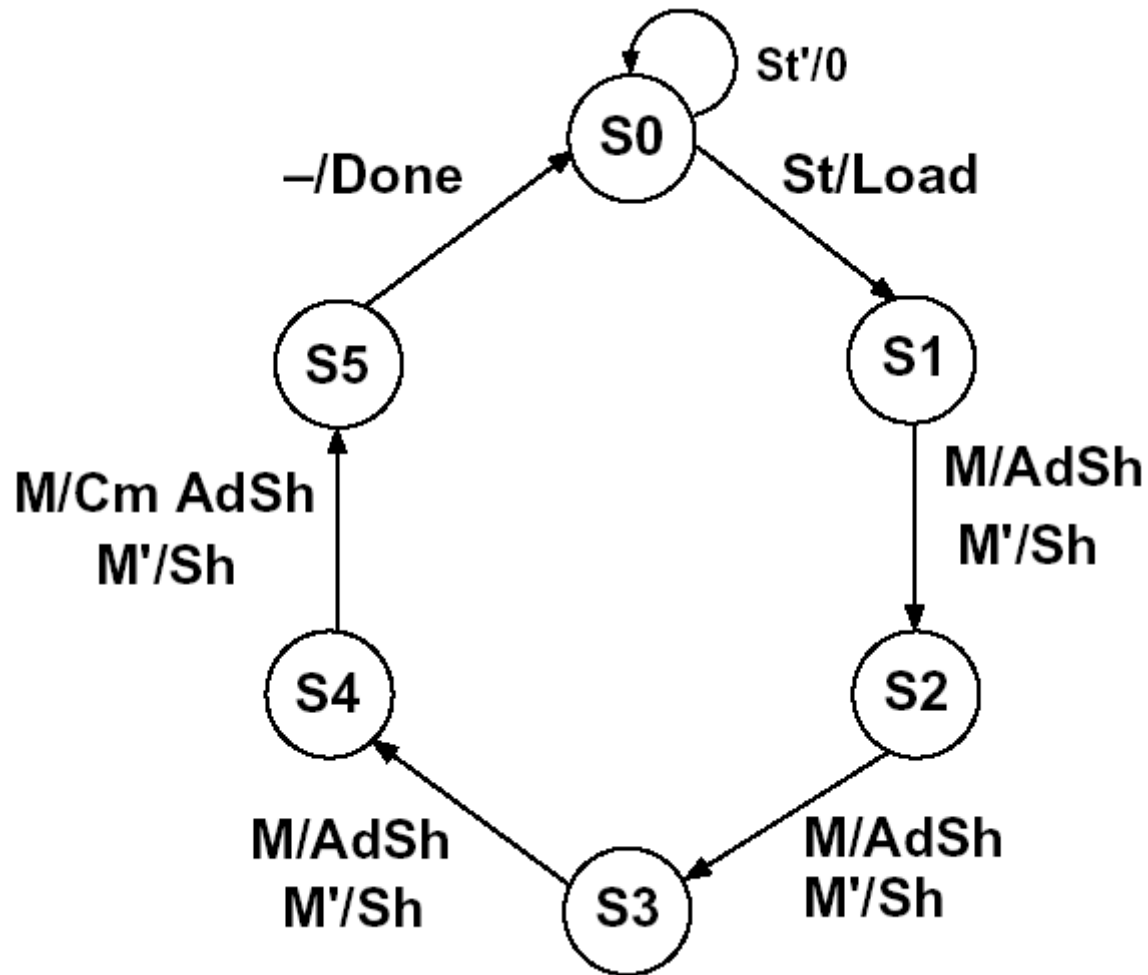
# Extended State Transition Graph for Multiplier


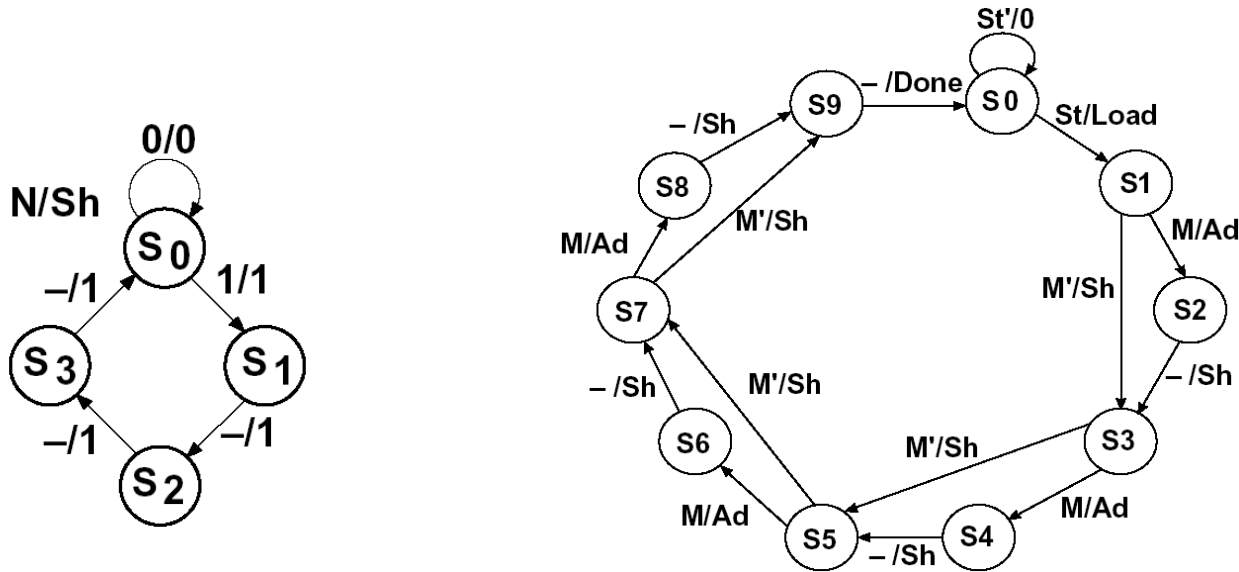
# Digital Design with ASM Charts

- State Transition Graphs are used to describe state machines controlling a digital system



- Alternative: use algorithmic state machine flowchart


# State Machine Charts

---

- ASM (*Algorithmic State Machine*) or simply a SM chart
  - Easier to understand the operation of digital system by examining of the ASM chart instead of equivalent state transition graph
  - ASM chart leads directly to hardware realization


# Components of ASM charts

---

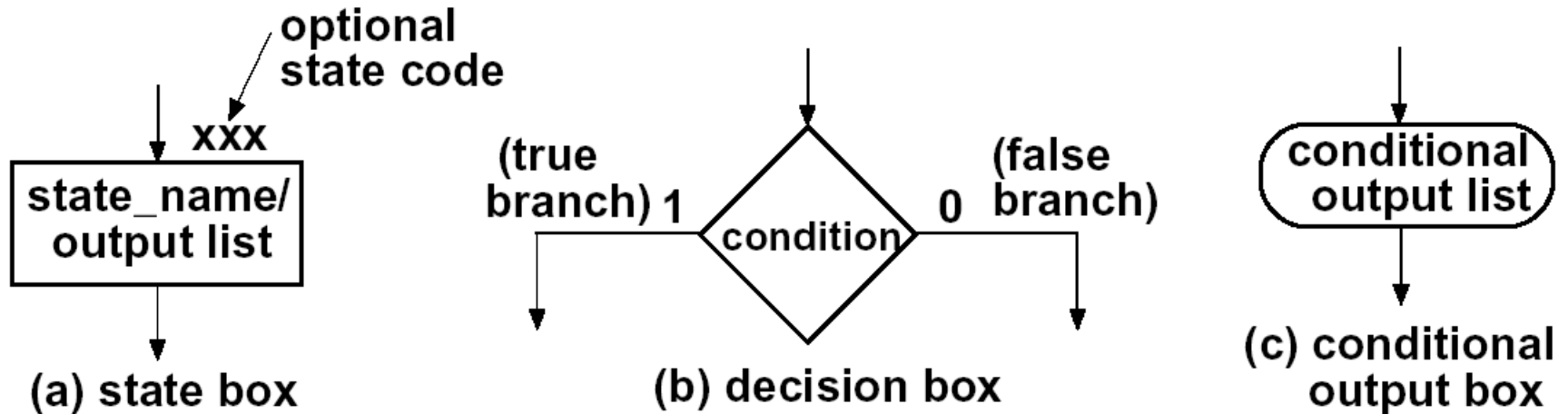

# ASM Blocks

ASM chart is constructed from SM blocks

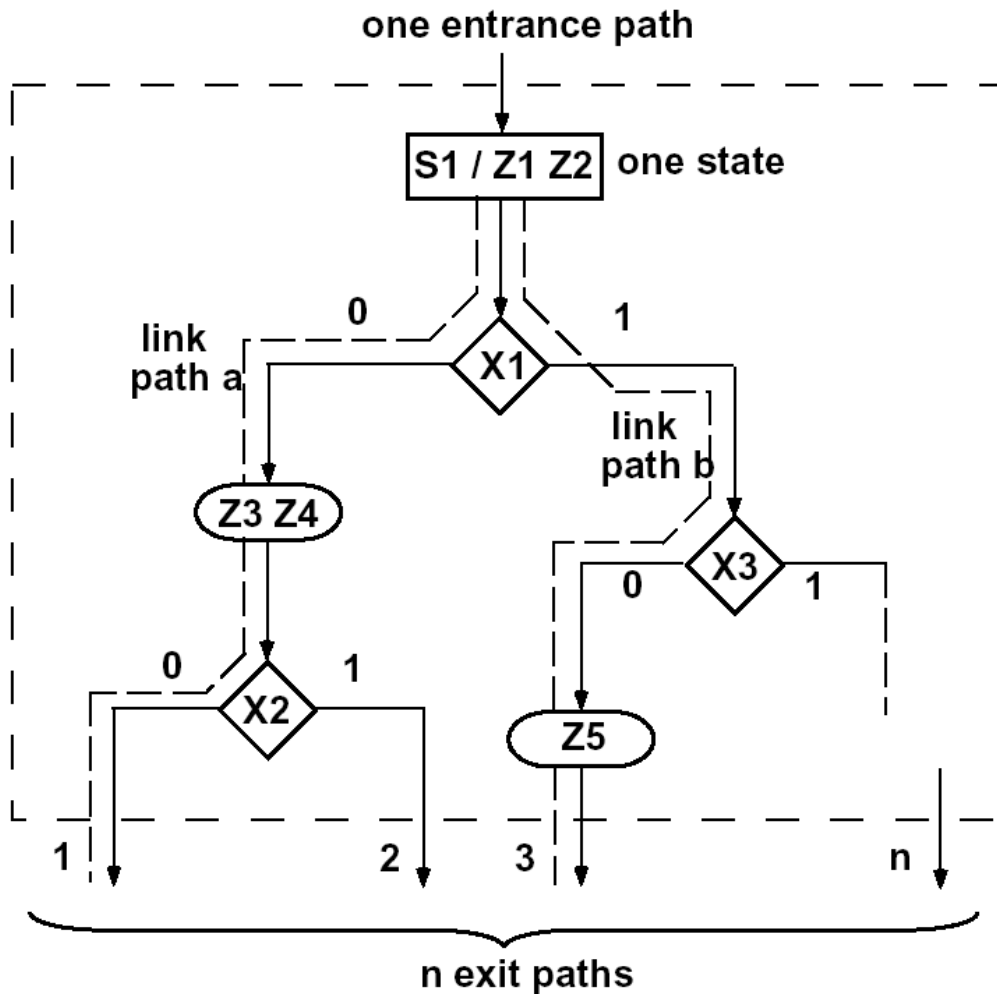

SM  
block

State S1 is entered =>

Z1 and Z2 become 1

if X1=0


Z3 and Z4 become 1

if X1=1 and X3=0


Z5 become 1



# Equivalent SM Blocks

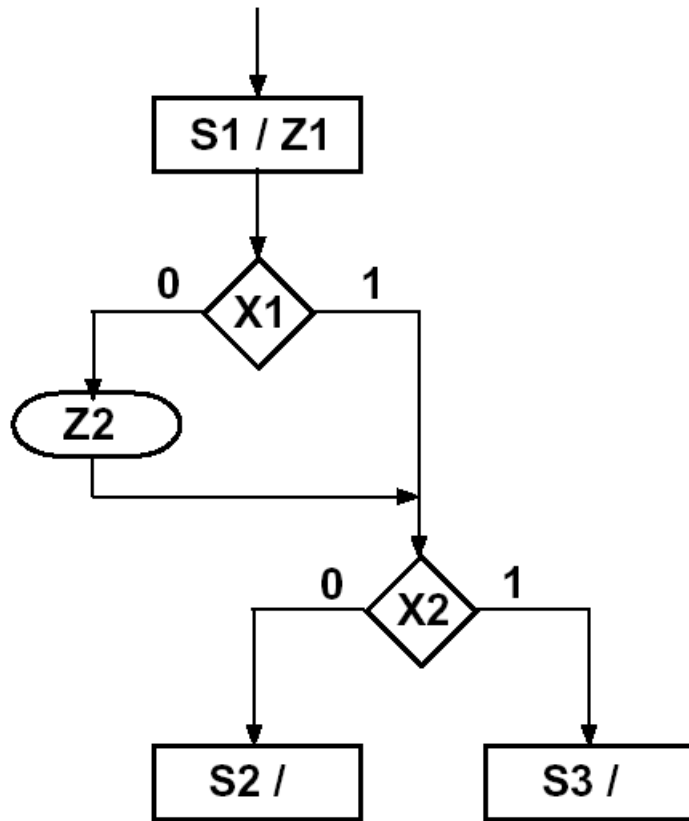


(a)

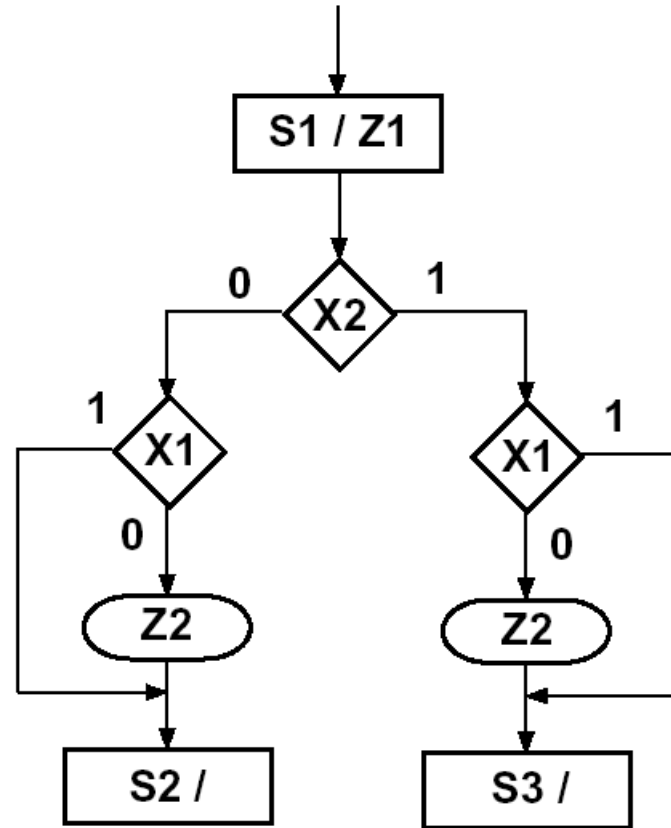


(b)
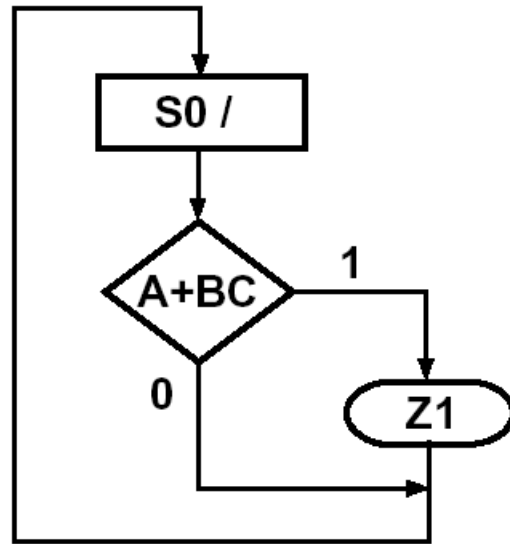
# Equivalent ASM Charts for Comb Networks




(a)

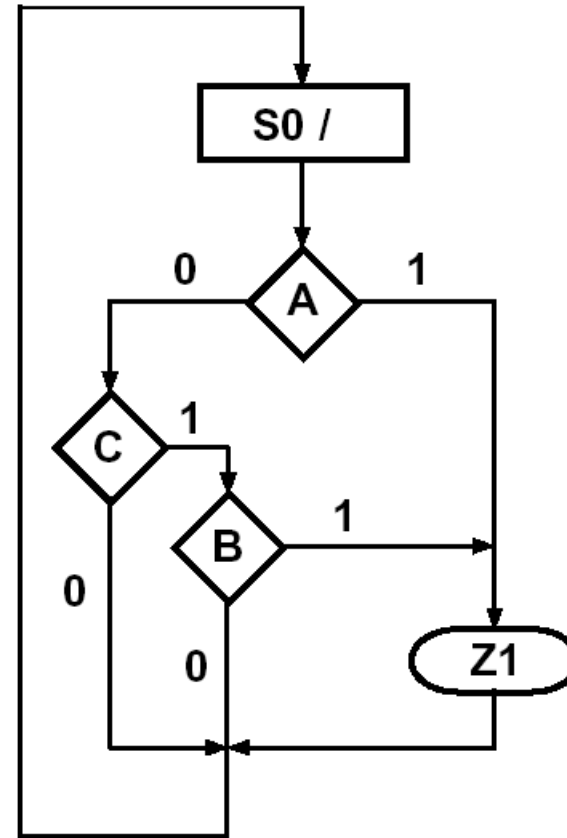


(b)

# Block with Feedback

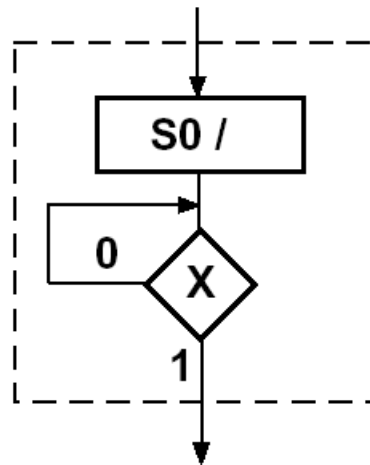


(a) incorrect

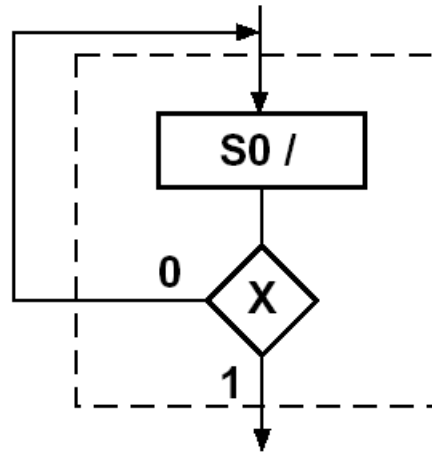


(b) correct

# Equivalent ASM Blocks


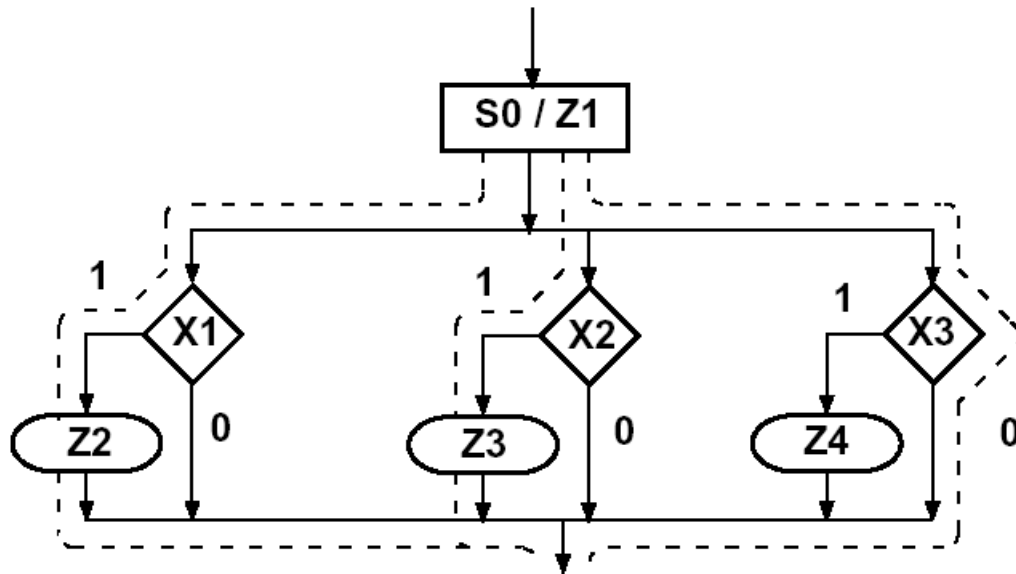


(a) Parallel form

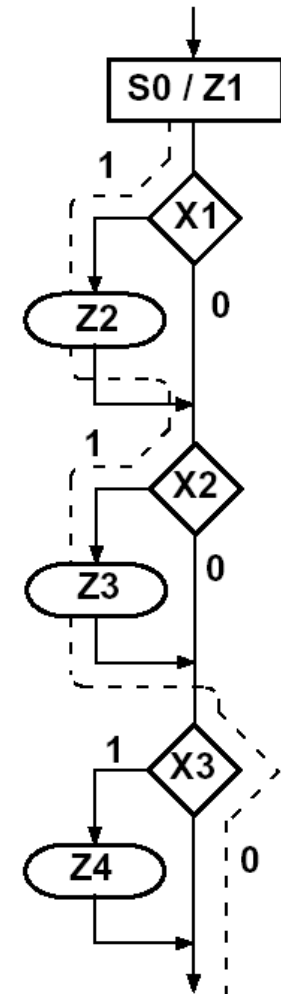



(b) Serial form
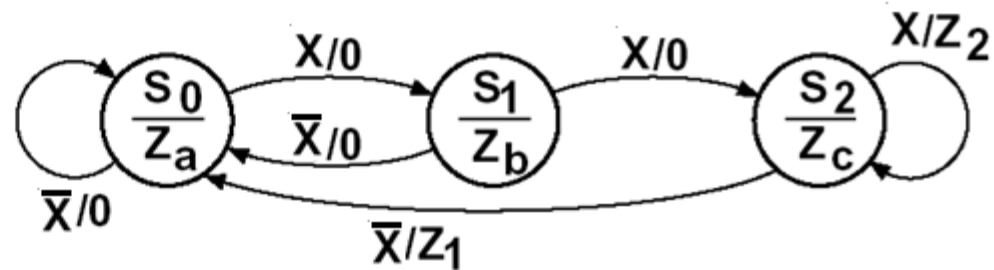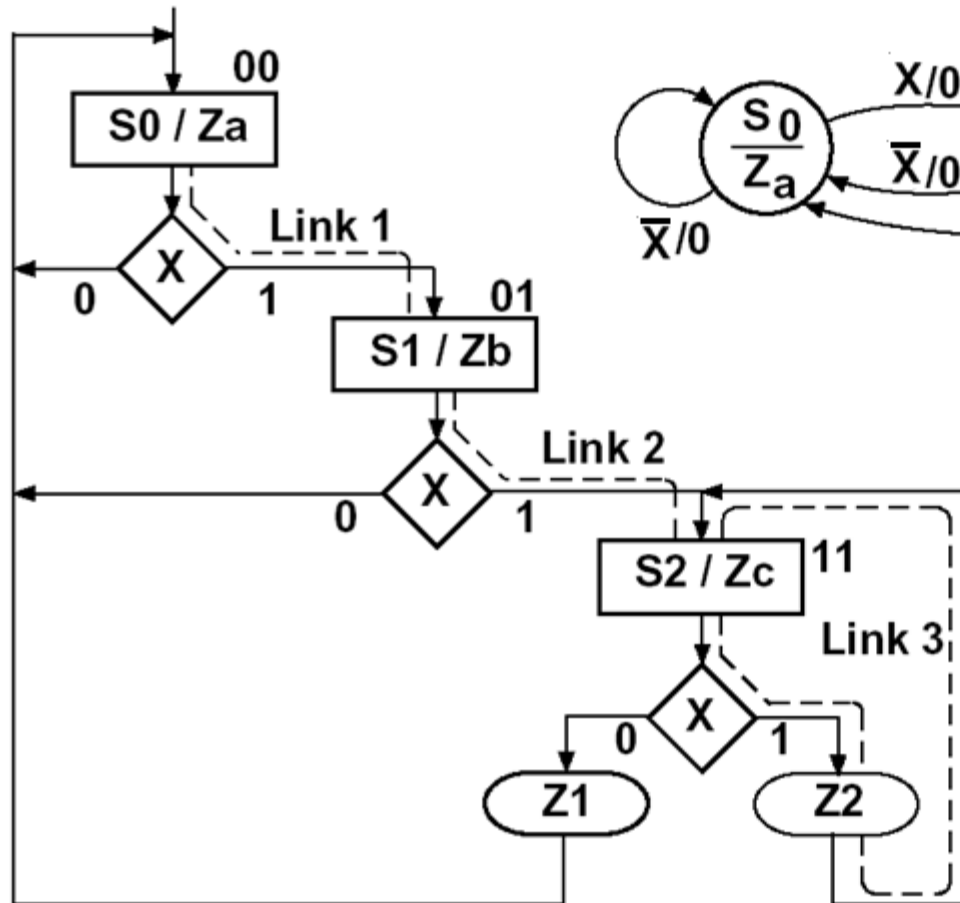
# Converting an Extended STG to an ASM Chart



Clock	
State	S <sub>0</sub> S <sub>1</sub> S <sub>2</sub> S <sub>2</sub> S <sub>0</sub> S <sub>0</sub>
X	
Z <sub>a</sub>	
Z <sub>b</sub>	
Z <sub>c</sub>	
Z <sub>1</sub>	
Z <sub>2</sub>	

# ASM Chart for Binary Multiplier

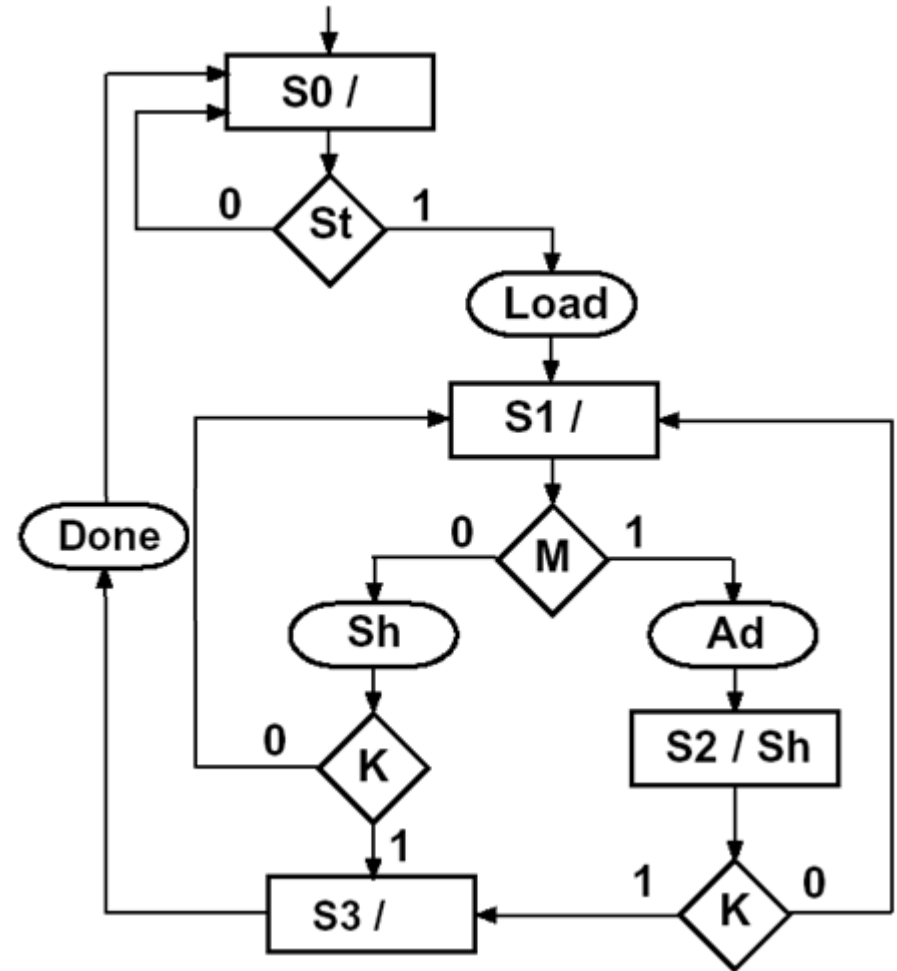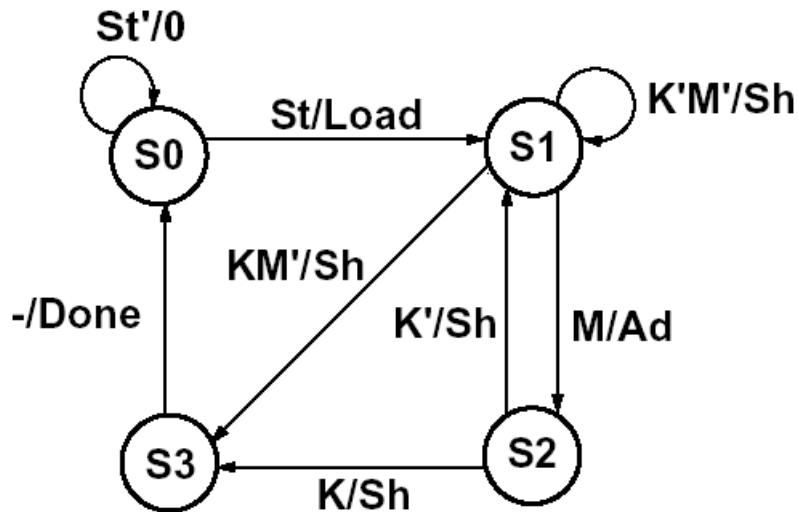

# ASM Chart for Binary Multiplier

