


### 3 MOS Amp Configurations.

Common Source - most popular. Good gain

Common Gate - gate grounded  $V_i$  @ Source

Common drain - voltage follower  $V_i$  @ gate

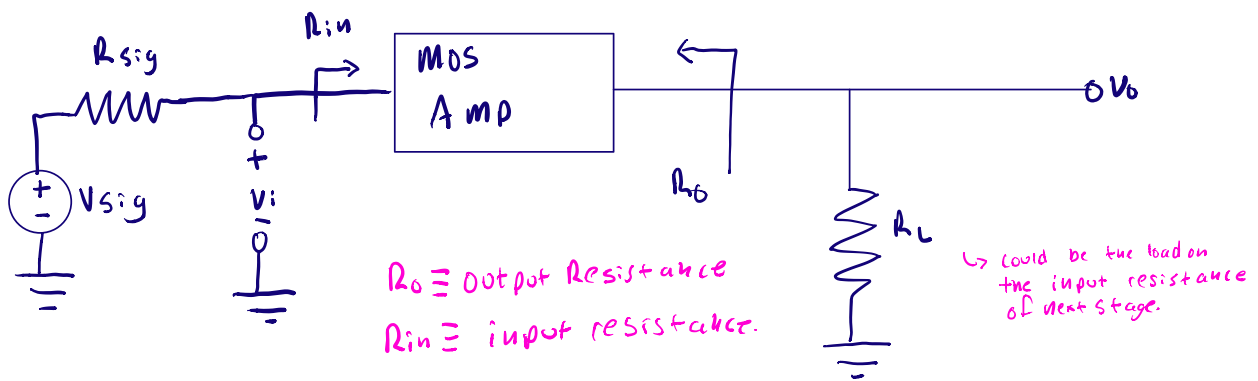Unilateral =  $R_L$  does not affect  $R_{in} \rightarrow$  no internal feedback



$$R_{in} = \frac{V_i}{I_i} \quad V_i = \frac{R_{in}}{R_{in} + R_{sig}} \cdot V_{sig}$$

$A_{vo} \equiv$  open circuit voltage gain ( $R_L \rightarrow \infty$ )


$$A_{vo} = \left. \frac{V_o}{V_i} \right|_{R_L \rightarrow \infty}$$

$R_o \equiv$  Look into the output of the transistor w/  $V_i = 0$

$A_v \equiv$  voltage gain of the amplifier proper.

$$A_v = \frac{V_o}{V_i} \text{ w/ } R_L \text{ included.}$$
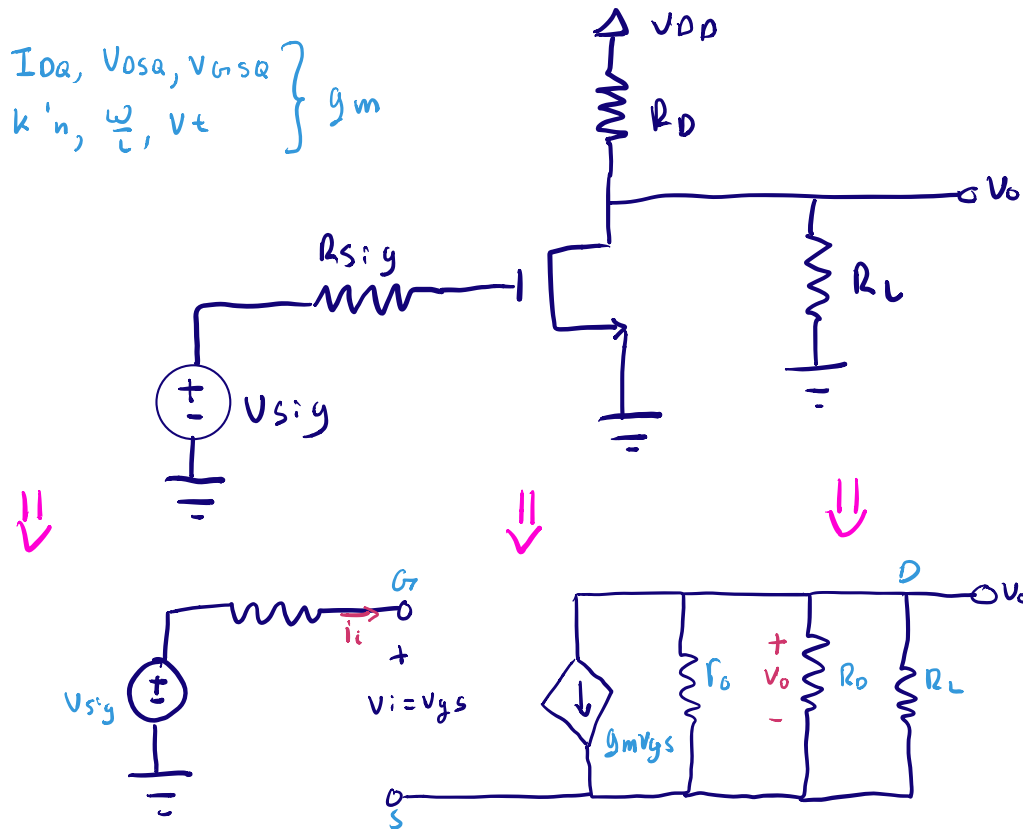
$$G_v \equiv \text{Closed (overall voltage gain)} = \frac{V_o}{V_{sig}}$$



$$R_{in} \Rightarrow i_L = 0 \quad R_{in} = \frac{V_i}{0} = \infty$$

$$R_o \Rightarrow V_i = 0 \quad R_o = R_D \parallel r_o \quad \text{usually } r_o \gg R_D \Rightarrow R_o \cong R_D$$

$$A_{vo} = \left. \frac{V_o}{V_i} \right|_{R_L \rightarrow \infty} \Rightarrow V_o = -g_m V_{gs} (r_o \parallel R_D)$$

$$V_o = -g_m (V_i) (r_o \parallel R_D)$$



$$g_m = k'n \frac{W}{L} (V_{GSQ} - V_t) \quad \frac{V_o}{V_i} = -g_m (r_o \parallel R_D)$$


$$A_v = \frac{V_o}{V_i} = -g_m (r_o \parallel R_D \parallel R_L)$$

$$G_{TV} = \frac{V_o}{V_{sig}} \Rightarrow V_i = V_{sig}$$

$$G_{TV} = \frac{V_o}{V_{sig}} = -g_m (r_o \parallel R_D \parallel R_L)$$

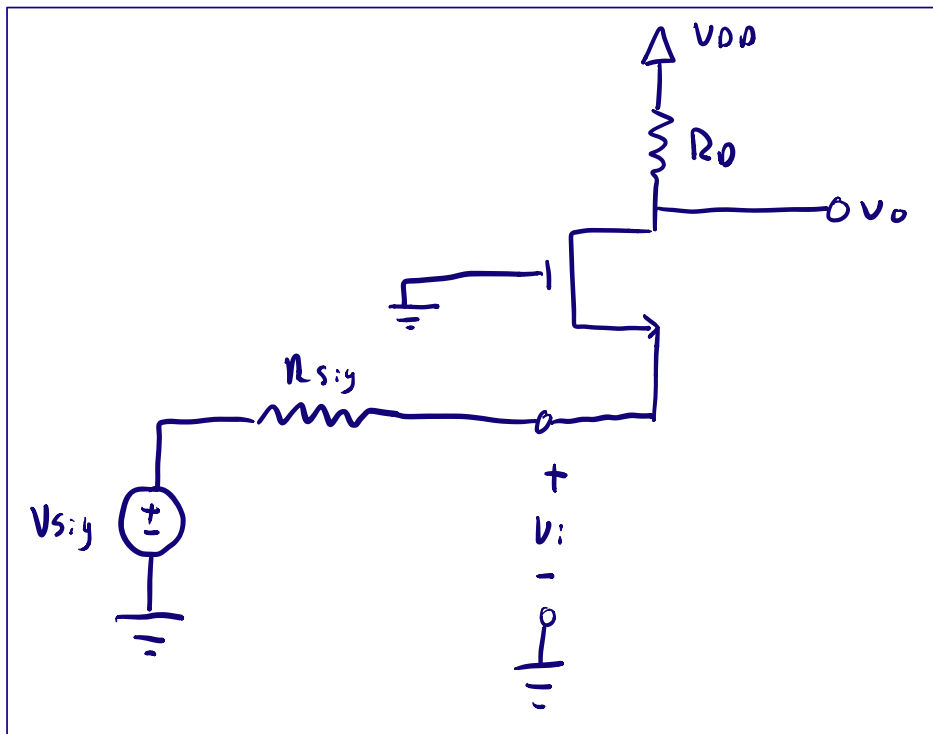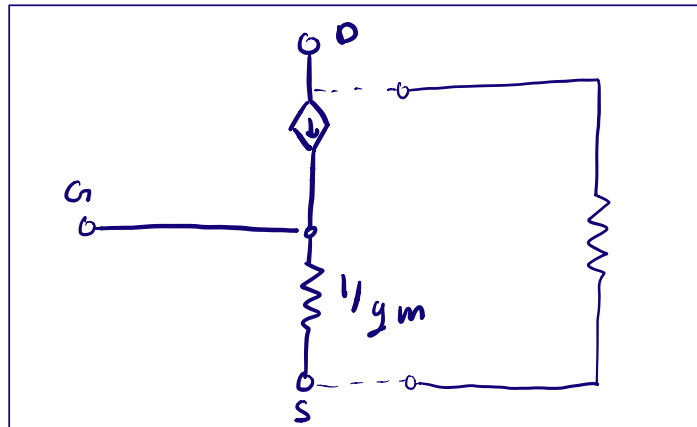
Common Gate Amplifier → Not common unless at high frequencies.  
 ↳ using the T model ⇒ small signal




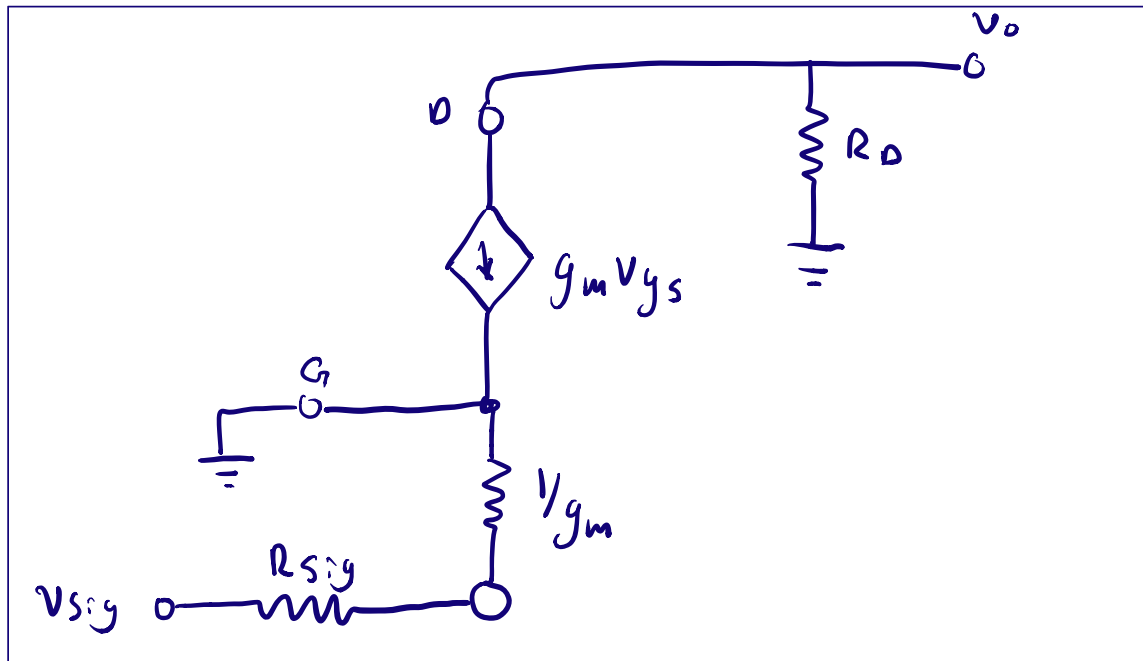

Note:  $V_{gs} = -V_i$

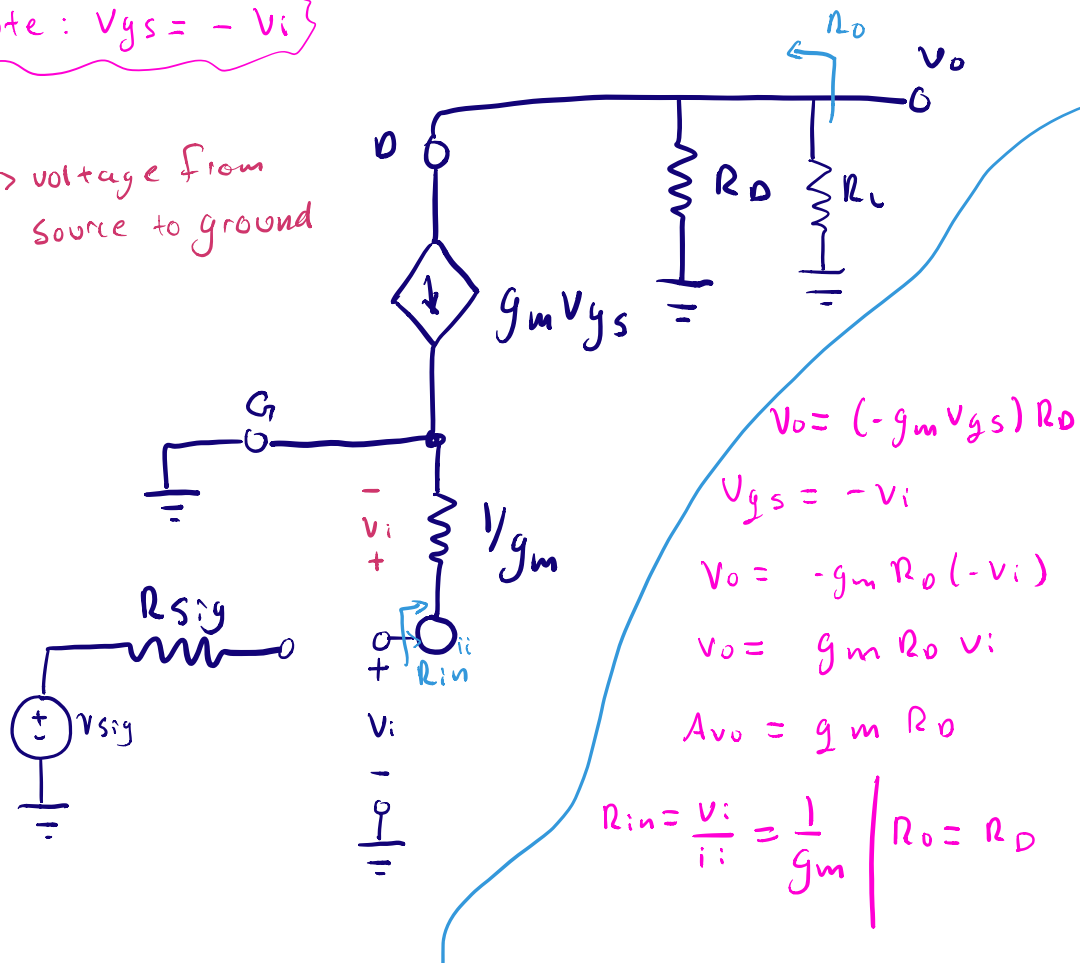$V_i \rightarrow$  voltage from source to ground



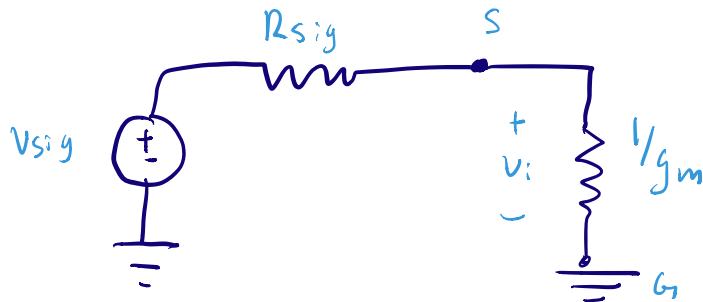

$$V_i = V_{sig} \left( \frac{1/g_m}{R_{sig} + 1/g_m} \right)$$

$$A_v = \frac{V_o}{V_i} = g_m (R_D \parallel R_L)$$

$$G_v = \frac{V_o}{V_i} \cdot \frac{V_i}{V_{sig}} = g_m (R_D \parallel R_L) \cdot \left( \frac{1/g_m}{R_{sig} + 1/g_m} \right)$$

$$G_v = \frac{R_D \parallel R_L}{R_{sig} + 1/g_m} \Rightarrow g_m = k'_n \frac{W}{L} (V_{GSQ} - V_t)$$



will result in }  $g_m \Rightarrow$  small  
smaller gain if  $R_D \Rightarrow$  small..

$R_{in} = 1/g_m \Rightarrow$  large  
 $R_D = R_D \Rightarrow$  small
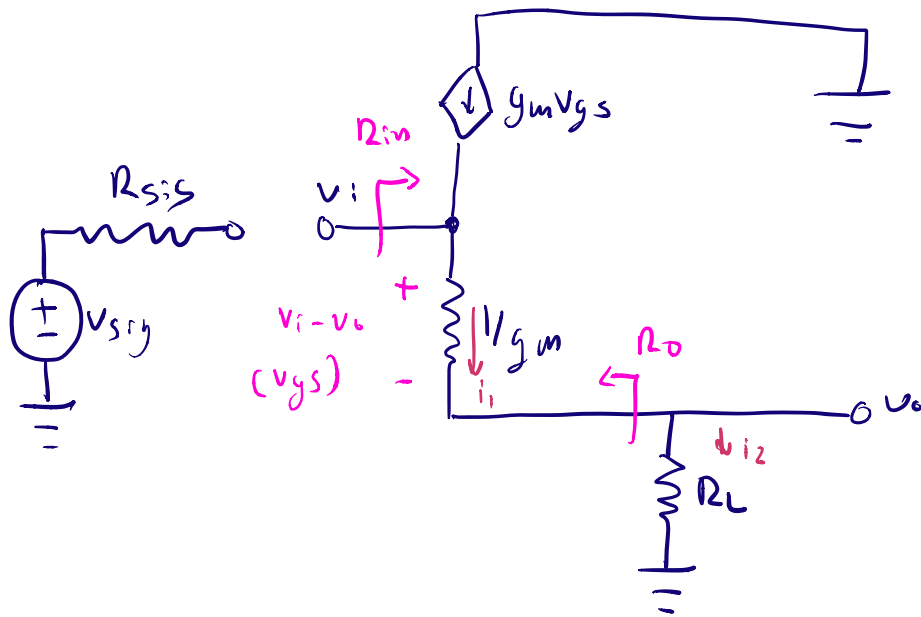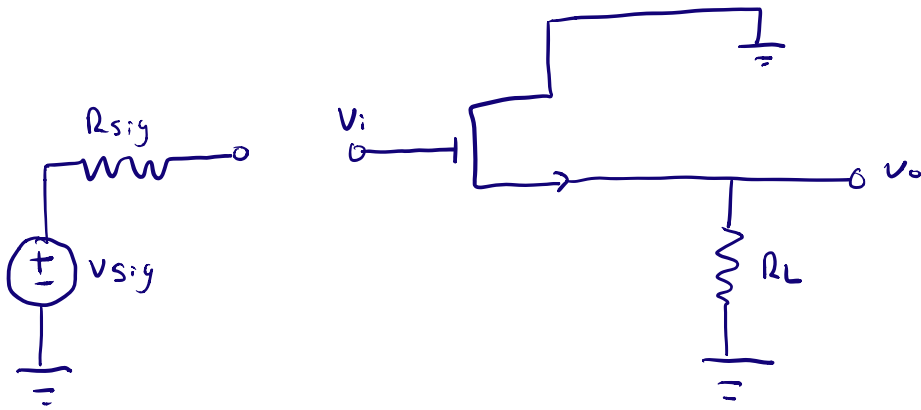
## Common Drain Amplifier

Source Follower.

Transistor eq. of voltage follower. Non inverting config to not lose any power.



$$R_{in} = \infty$$

$$R_o = 1/g_m$$

$$A_v = \frac{v_o}{v_i}$$

$$i_1 = \frac{v_i - v_o}{1/g_m}$$

$$i_2 = \frac{v_o}{R_L}$$

$$i_2 = i_1$$

$$\frac{v_i - v_o}{1/g_m} = \frac{v_o}{R_L} \quad v_o \left( \frac{1}{R_L} + \frac{1}{1/g_m} \right) = \frac{v_i}{1/g_m}$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + 1/g_m}$$

$$\text{for } R_L \rightarrow \infty \quad A_{v0} = \frac{v_o}{v_i} \Big|_{R_L \rightarrow \infty} = 1$$

$$A_v = \frac{v_o}{v_i} = \frac{R_L}{R_L + 1/g_m}$$

$$G_v = \frac{v_o}{v_{sig}} = \frac{R_L}{R_L + 1/g_m}$$

$$R_{in} = \infty$$

$$R_o = 1/g_m$$

high  $g_m$  for small  $R_o$

$$R_L \gg 1/g_m \Rightarrow G_v \approx 1$$