

Lab 1: Calculations

EE316-08 Spring 2021

Figure 1.3: Solve for I_1 , I_2 , and I_3

- Calculate...
 - Branch Voltages
 - Branch Currents
 - Node Voltages
 - Loop Currents


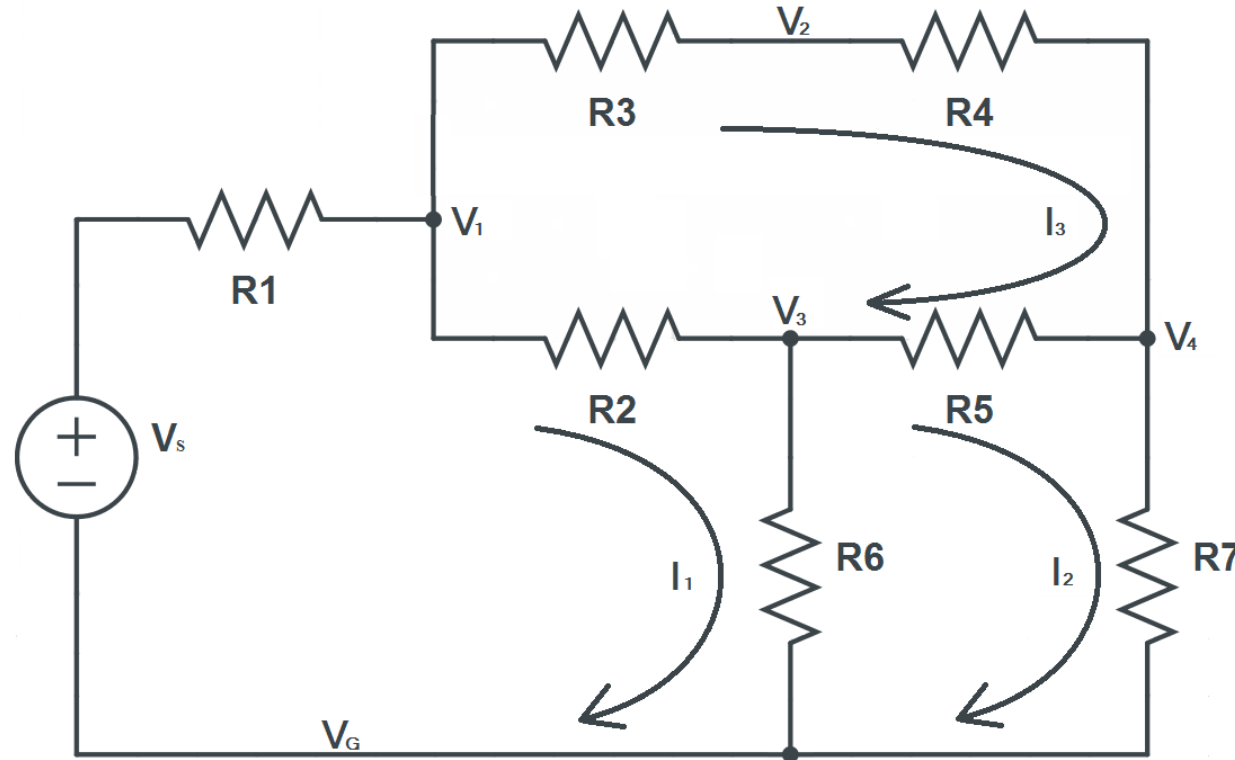


Figure 1.3: Solve for I_1 , I_2 , and I_3

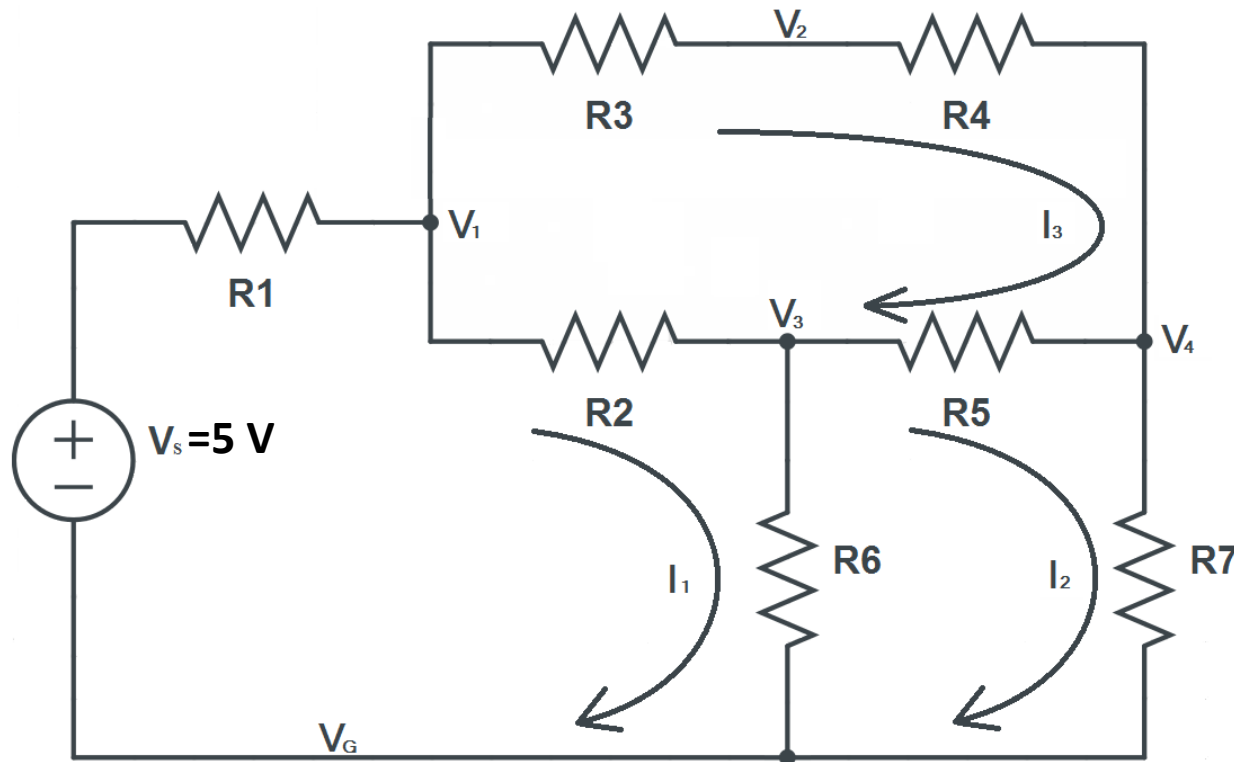

Use Mesh Analysis

Loop I_1 : $R_1 I_1 + R_2(I_1 - I_3) + R_6(I_1 - I_2) - 5 = 0$

$$R_1 I_1 + R_2 I_1 - R_2 I_3 + R_6 I_1 - R_6 I_2 = 5$$

$$(R_1 + R_2 + R_6)I_1 - R_6 I_2 - R_2 I_3 = 5 \quad (1)$$

Loop I_2 : $R_5(I_2 - I_3) + R_7 I_2 + R_6(I_2 - I_1) = 0$

$$R_5 I_2 - R_5 I_3 + R_7 I_2 + R_6 I_2 - R_6 I_1 = 0$$

$$-R_6 I_1 + (R_5 + R_6 + R_7)I_2 - R_5 I_3 = 0 \quad (2)$$

Loop I_3 : $R_3 I_3 + R_4 I_3 + R_5(I_3 - I_2) + R_2(I_3 - I_1) = 0$

$$R_3 I_3 + R_4 I_3 + R_5 I_3 - R_5 I_2 + R_2 I_3 - R_2 I_1 = 0$$

$$-R_2 I_1 - R_5 I_2 + (R_2 + R_3 + R_4 + R_5)I_3 = 0 \quad (3)$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

Recall,

$$(R_1 + R_2 + R_6)I_1 - R_6I_2 - R_2I_3 = 5 \quad (1)$$

$$-R_6I_1 + (R_5 + R_6 + R_7)I_2 - R_5I_3 = 0 \quad (2)$$

$$-R_2I_1 - R_5I_2 + (R_2 + R_3 + R_4 + R_5)I_3 = 0 \quad (3)$$

Now, we have 3 equations and 3 unknown variables (I_1 , I_2 , and I_3). We can solve for I_1 , I_2 , and I_3 by using Matrices.

$$\begin{bmatrix} (R_1 + R_2 + R_6) & -R_6 & -R_2 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

A **X** **B**

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\begin{bmatrix} (R_1 + R_2 + R_6) & -R_6 & -R_2 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$(R_1 + R_2 + R_6)I_1 - R_6I_2 - R_2I_3 = 5 \quad (1)$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\begin{bmatrix} (R_1 + R_2 + R_6) & -R_6 & -R_2 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$-R_6 I_1 + (R_5 + R_6 + R_7) I_2 - R_5 I_3 = 0 \quad (2)$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\begin{bmatrix} (R_1 + R_2 + R_6) & -R_6 & -R_2 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$-R_2 I_1 - R_5 I_2 + (R_2 + R_3 + R_4 + R_5) I_3 = 0 \quad (3)$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\begin{bmatrix} (R_1 + R_2 + R_6) & -R_6 & -R_2 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

* Reduced row echelon form *

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} \text{Answer for } I_1 \\ \text{Answer for } I_2 \\ \text{Answer for } I_3 \end{bmatrix}$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\begin{bmatrix} (R_1 + R_2 + R_6) & -R_6 & -R_2 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$



* augmented matrix form *

$$\left[\begin{array}{ccc|c} (R_1 + R_2 + R_6) & -R_6 & -R_2 & 5 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 & 0 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) & 0 \end{array} \right]$$

$$\left[\begin{array}{ccc|c} 1 & 0 & 0 & \text{Answer for } I_1 \\ 0 & 1 & 0 & \text{Answer for } I_2 \\ 0 & 0 & 1 & \text{Answer for } I_3 \end{array} \right]$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\left[\begin{array}{ccc|c} (R_1 + R_2 + R_6) & -R_6 & -R_2 & 5 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 & 0 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) & 0 \end{array} \right] \sim$$

Plug in R_1 - R_7 under the first assumption (the exact values)

$$\left[\begin{array}{ccc|c} (100 + 100 + 2,200) & -2,200 & -100 & 5 \\ -2,200 & (1,000 + 2,200 + 2,200) & -1,000 & 0 \\ -100 & -1,000 & (100 + 100 + 1,000 + 1,000) & 0 \end{array} \right] \sim$$

$$\left[\begin{array}{ccc|c} 2,400 & -2,200 & -100 & 5 \\ -2,200 & 5,400 & -1,000 & 0 \\ -100 & -1,000 & 2,200 & 0 \end{array} \right] \text{ Divided by 100 } \sim \left[\begin{array}{ccc|c} 24 & -22 & -1 & 0.05 \\ -22 & 54 & -10 & 0 \\ -1 & -10 & 22 & 0 \end{array} \right] \sim$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\left[\begin{array}{ccc|c} 24 & -22 & -1 & 0.05 \\ -22 & 54 & -10 & 0 \\ -1 & -10 & 22 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_2 \\ R_3 \end{array} \sim \left[\begin{array}{ccc|c} 24 & -22 & -1 & 0.05 \\ 2.2 & -5.4 & 1 & 0 \\ -1 & -10 & 22 & 0 \end{array} \right] \begin{array}{l} R_1 \\ \frac{-R_2}{10} \\ R_3 \end{array} \sim$$

$$\left[\begin{array}{ccc|c} 26.2 & -27.4 & 0 & 0.05 \\ 48.4 & -118.8 & 22 & 0 \\ -1 & -10 & 22 & 0 \end{array} \right] \begin{array}{l} R_1 + R_2 \\ 22R_2 \\ R_3 \end{array} \sim \left[\begin{array}{ccc|c} 26.2 & -27.4 & 0 & 0.05 \\ 49.4 & -108.8 & 0 & 0 \\ -1 & -10 & 22 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_2 - R_3 \\ R_3 \end{array} \sim$$

$$\left[\begin{array}{ccc|c} 1 & -\frac{137}{131} & 0 & \frac{1}{524} \\ 49.4 & -108.8 & 0 & 0 \\ -1 & -10 & 22 & 0 \end{array} \right] \begin{array}{l} \frac{R_1}{26.2} \\ R_2 \\ R_3 \end{array} \sim \left[\begin{array}{ccc|c} 1 & -\frac{137}{131} & 0 & 1/524 \\ 49.4 & -108.8 & 0 & 0 \\ -49.4 & -494 & 1086.8 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_2 \\ 49.4R_3 \end{array} \sim$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\left[\begin{array}{ccc|c} 1 & -\frac{137}{131} & 0 & 1/524 \\ 49.4 & -108.8 & 0 & 0 \\ 0 & -602.8 & 1086.8 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_2 \\ 49.4R_3 + R_2 \end{array} \sim$$

$$\left[\begin{array}{ccc|c} 1 & -\frac{137}{131} & 0 & 1/524 \\ 49.4 & -108.8 & 0 & 0 \\ 0 & -\frac{137}{247} & 1 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_2 \\ R_3 \end{array} \sim \left[\begin{array}{ccc|c} 49.4 & -\frac{(49.4)137}{131} & 0 & 49.4/524 \\ 49.4 & -108.8 & 0 & 0 \\ 0 & -\frac{137}{247} & 1 & 0 \end{array} \right] \begin{array}{l} 49.4R_1 \\ R_2 \\ R_3 \end{array}$$

$$\left[\begin{array}{ccc|c} 1 & -\frac{137}{131} & 0 & 1/524 \\ 0 & \frac{7485}{131} & 0 & 49.4/524 \\ 0 & -\frac{137}{247} & 1 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_1 - R_2 \\ R_3 \end{array} \sim \left[\begin{array}{ccc|c} 1 & -\frac{137}{131} & 0 & 1/524 \\ 0 & 1 & 0 & 0.00165 \\ 0 & -\frac{137}{247} & 1 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_2 \\ R_3 \end{array} \sim \left[\begin{array}{ccc|c} 1 & -\frac{137}{131} & 0 & 1/524 \\ 0 & 1 & 0 & 0.00165 \\ 0 & -\frac{137}{247} & 1 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_2 \\ R_3 \end{array} \sim$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\left[\begin{array}{ccc|c} 1 & -\frac{137}{131} & 0 & 0.00165 \left(\frac{137}{131} \right) \\ 0 & \frac{137}{131} & 0 & \\ 0 & -\frac{137}{247} & 1 & 0 \end{array} \right] \begin{array}{l} R_1 \\ R_2 \\ R_3 \end{array} \sim \left[\begin{array}{ccc|c} 1 & 0 & 0 & 0.003634 \\ 0 & 1 & 0 & 0.00165 \\ 0 & -\frac{137}{247} & 1 & 0 \end{array} \right] \begin{array}{l} R_1 + R_2 \\ R_2 \\ R_3 \end{array} \sim$$

$$\left[\begin{array}{ccc|c} 1 & 0 & 0 & 0.003634 \\ 0 & \frac{137}{247} & 0 & 0.00165 \left(\frac{137}{247} \right) \\ 0 & -\frac{137}{247} & 1 & 0 \end{array} \right] \begin{array}{l} R_1 \\ \left(\frac{137}{247} \right) R_2 \\ R_3 \end{array} \sim \left[\begin{array}{ccc|c} 1 & 0 & 0 & 0.003634 \\ 0 & 1 & 0 & 0.00165 \\ 0 & 0 & 1 & 0.0009152 \end{array} \right] \begin{array}{l} R_1 \\ R_2 \\ R_2 + R_3 \end{array}$$

Figure 1.3: Solve for I_1 , I_2 , and I_3 (cont.)

$$\left[\begin{array}{ccc|c} (R_1 + R_2 + R_6) & -R_6 & -R_2 & 5 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 & 0 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) & 0 \end{array} \right]$$



Assumption 1: All resistors are exact value.

$$\left[\begin{array}{ccc|c} 2,400 & -2,200 & -100 & 5 \\ -2,200 & 5,400 & -1,000 & 0 \\ -100 & -1,000 & 2,200 & 0 \end{array} \right]$$




$$\left[\begin{array}{ccc|c} 1 & 0 & 0 & \text{Answer for } I_1 \\ 0 & 1 & 0 & \text{Answer for } I_2 \\ 0 & 0 & 1 & \text{Answer for } I_3 \end{array} \right]$$



$$\left[\begin{array}{ccc|c} 1 & 0 & 0 & 0.003634 \\ 0 & 1 & 0 & 0.00165 \\ 0 & 0 & 1 & 0.0009152 \end{array} \right]$$

Therefore, $I_1 = 0.003634$ A, $I_2 = 0.00165$ A, and
 $I_3 = 0.0009152$ A.

Figure 1.3: Assume all resistors are the exact value

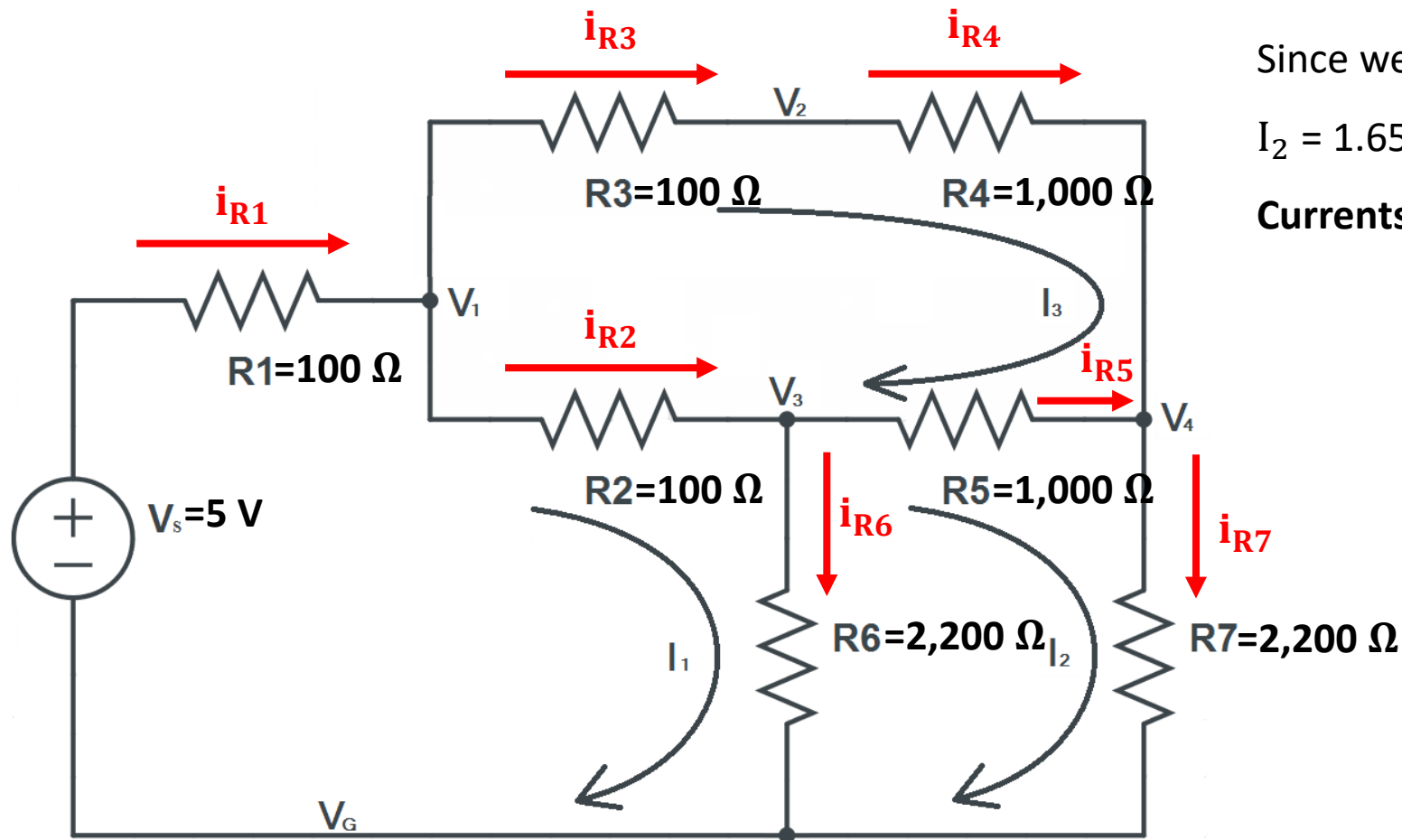

Since we know that '**Loop Currents**' are $I_1 = 3.634\text{ mA}$, $I_2 = 1.65\text{ mA}$, and $I_3 = 0.9152\text{ mA}$, we can find '**Branch Currents**'.

$$i_{R1} = I_1 = 3.634\text{ A}$$

$$i_{R2} = I_1 - I_3 = 3.634 - 0.9152 = 2.719\text{ mA}$$

$$i_{R3} = I_3 = 0.9152\text{ mA}$$

$$i_{R4} = I_3 = 0.9152\text{ mA}$$


$$i_{R5} = I_2 - I_3 = 1.65 - 0.9152 = 0.735\text{ mA}$$

$$i_{R6} = I_1 - I_2 = 3.634 - 1.65 = 1.984\text{ mA}$$

$$i_{R7} = I_2 = 1.65\text{ mA}$$

Note: I use **RED ARROW** as a reference direction of the current.

Figure 1.3: Assume all resistors are the exact value

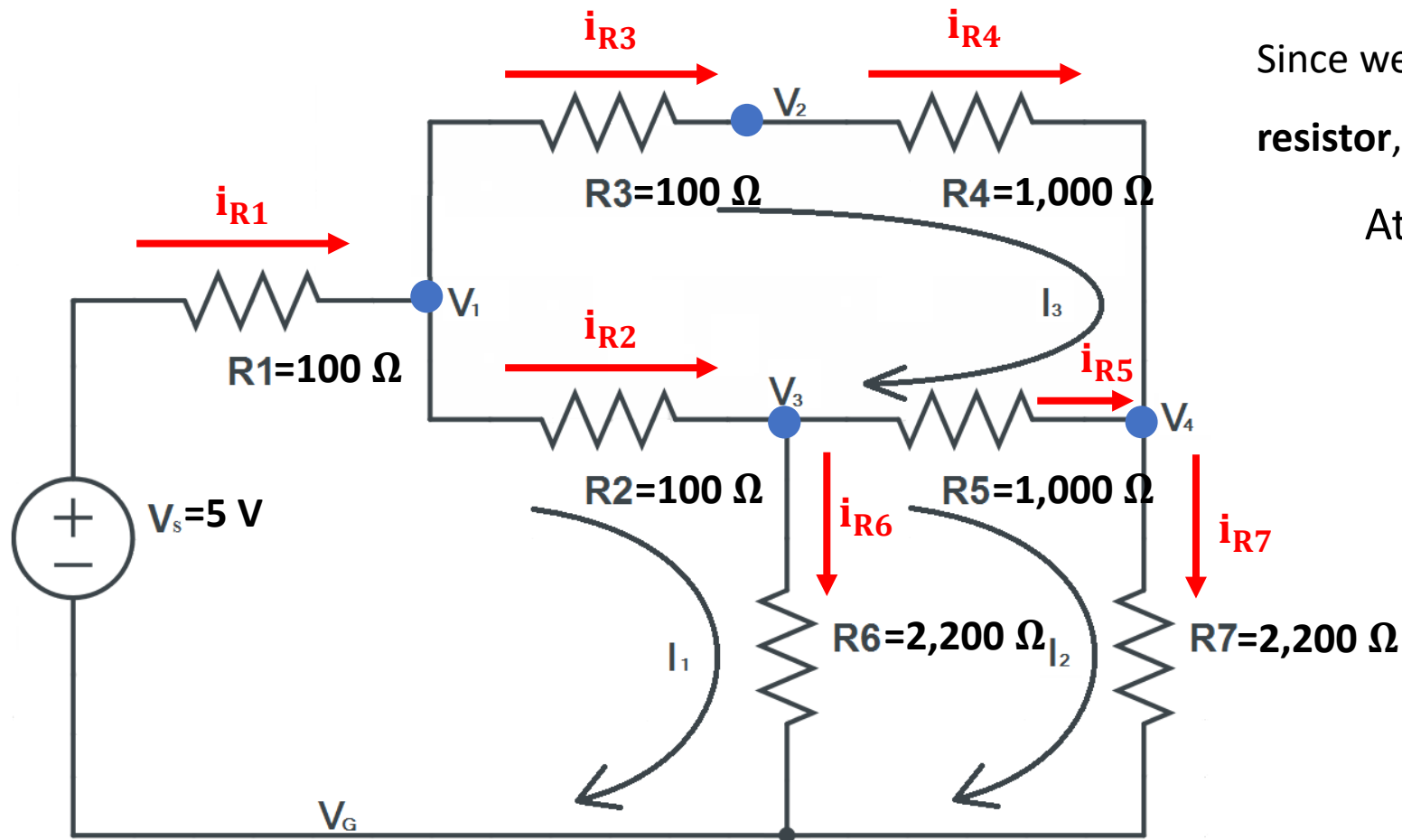

Since we know 'Branch Currents' and all values of resistor, we can find 'Node Voltage'.

$$\text{At } R_1: \quad 5 - V_1 = (i_{R1})(R_1)$$

$$V_1 = 5 - (i_{R1})(R_1)$$

$$V_1 = 5 - (0.003634)(100)$$

$$V_1 = 4.64\text{ V}$$

$$\text{At } R_3: \quad V_1 - V_2 = (i_{R3})(R_3)$$


$$V_2 = V_1 - (i_{R3})(R_3)$$

$$V_2 = 4.64 - (0.0009152)(100)$$

$$V_2 = 4.55\text{ V}$$

Note: I use **RED ARROW** as a reference direction of the current.

Figure 1.3: Assume all resistors are the exact value

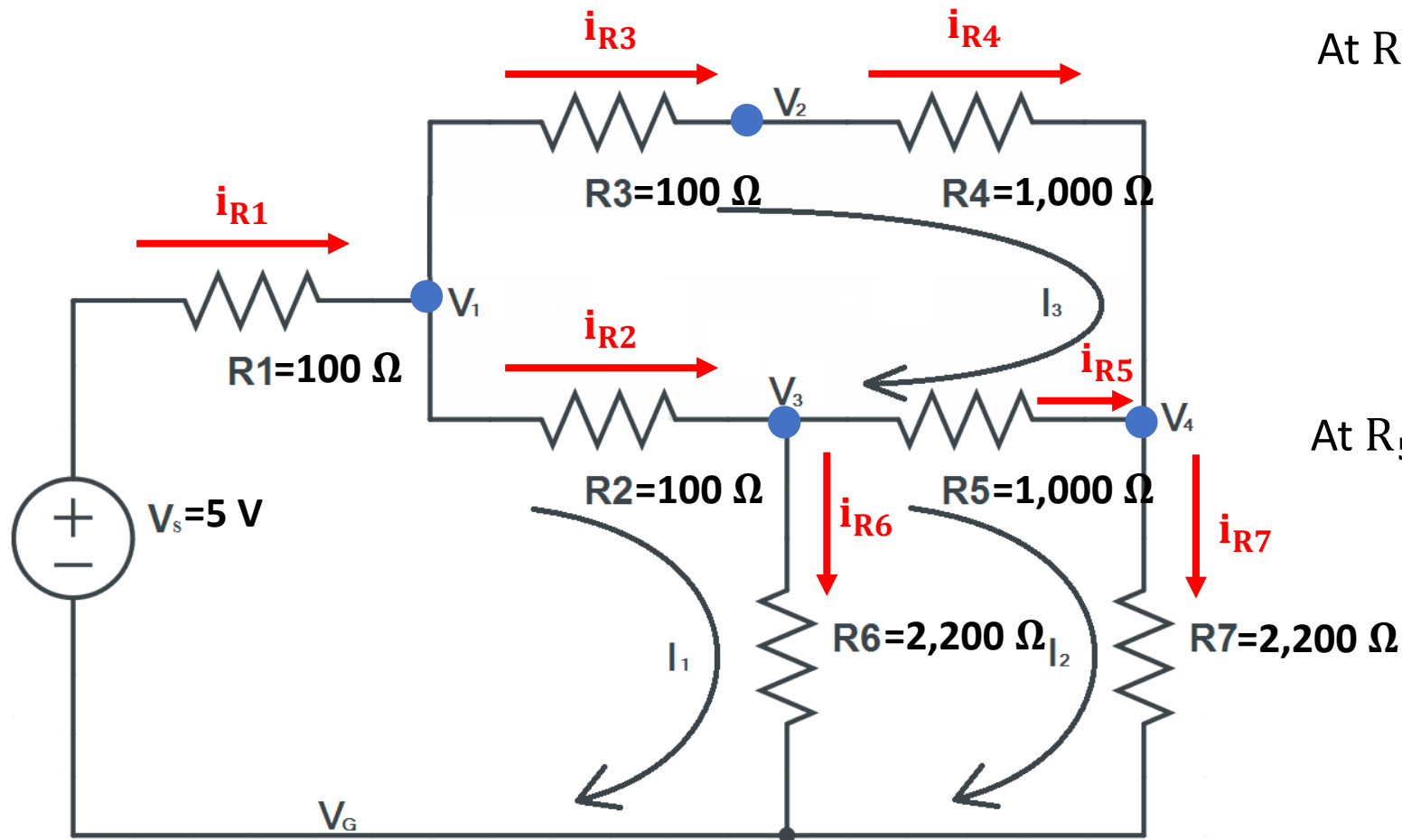

At R_2 : $V_1 - V_3 = (i_{R2})(R_2)$

$$V_3 = V_1 - (i_{R2})(R_2)$$

$$V_3 = 4.64 - (0.002719)(100)$$

$$V_3 = 4.37\text{ V}$$

At R_5 : $V_3 - V_4 = (i_{R5})(R_5)$

$$V_4 = V_3 - (i_{R5})(R_5)$$


$$V_4 = 4.37 - (0.000735)(1,000)$$

$$V_4 = 3.64\text{ V}$$

Note: I use **RED ARROW** as a reference direction of the current.

Figure 1.3: Assume all resistors are the exact value

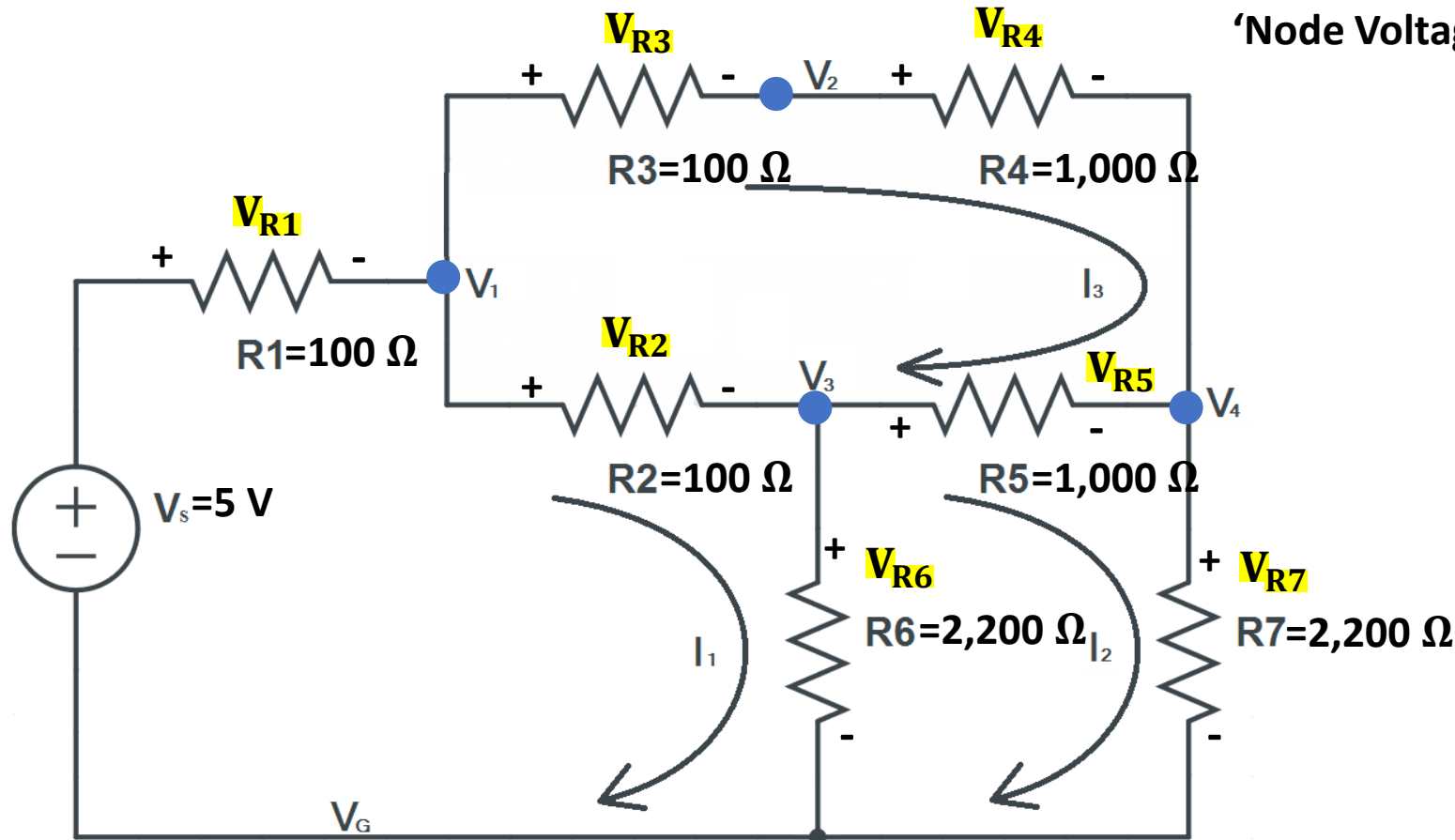Since we know 'Branch Currents', all values of resistor, and 'Node Voltage', we can find 'Branch Voltage'.



At R_1 : $V_{R1} = (\mathbf{i_{R1}})(R1)$ or $V_{R1} = 5 - V_1$

$\mathbf{V_{R1} = 0.36\ V}$

At R_2 : $V_{R2} = (\mathbf{i_{R2}})(R2)$ or $V_{R2} = V_1 - V_3$

$\mathbf{V_{R2} = 0.27\ V}$

At R_3 : $V_{R3} = (\mathbf{i_{R3}})(R3)$ or $V_{R3} = V_1 - V_2$

$\mathbf{V_{R3} = 0.09\ V}$

At R_4 : $V_{R4} = (\mathbf{i_{R4}})(R4)$ or $V_{R4} = V_2 - V_4$


$\mathbf{V_{R4} = 0.91\ V}$

At R_5 : $V_{R5} = (\mathbf{i_{R5}})(R5)$ or $V_{R5} = V_3 - V_4$

$\mathbf{V_{R5} = 0.73\ V}$

Figure 1.3: Assume all resistors are the exact value

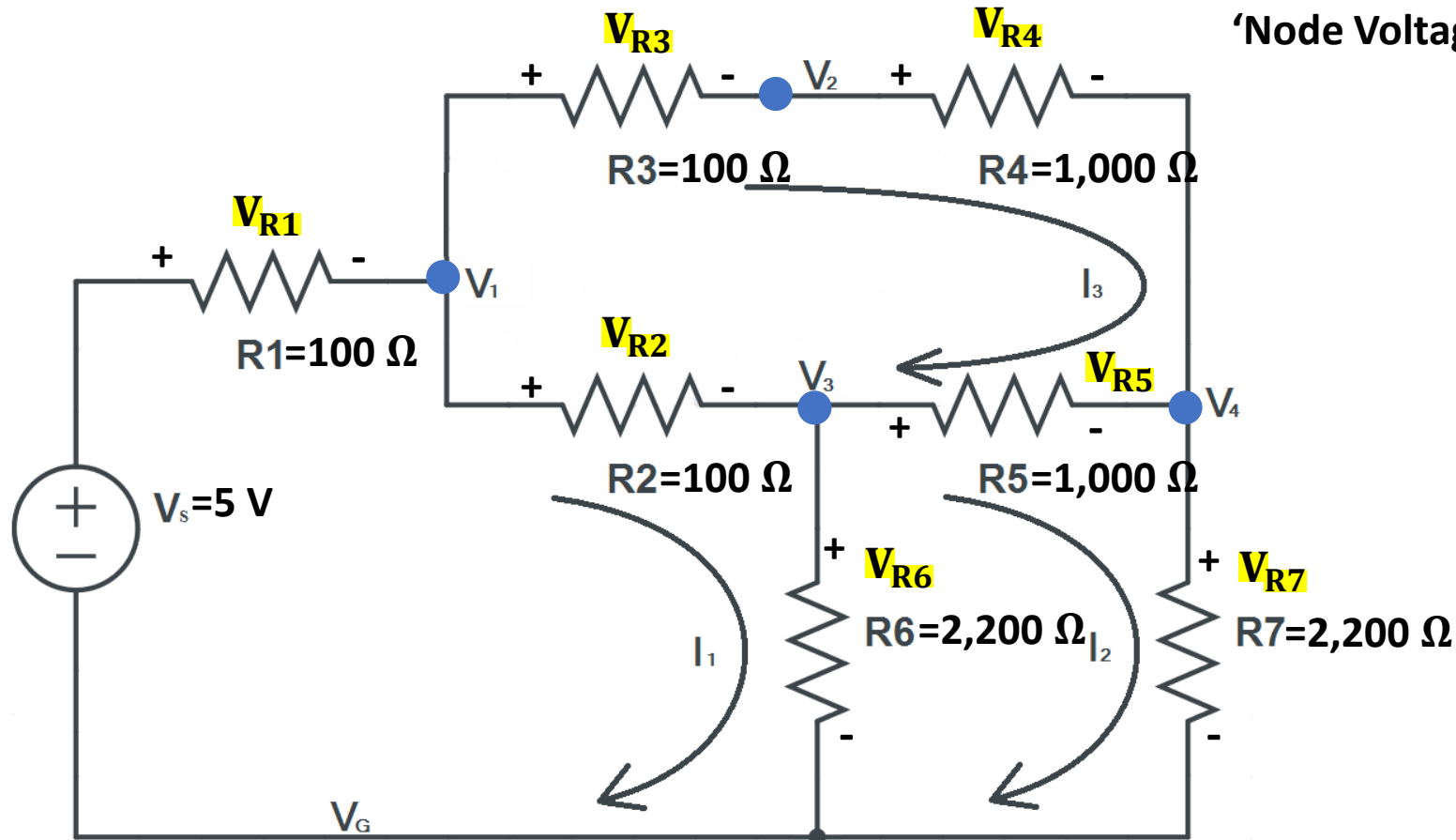Since we know 'Branch Currents', all values of resistor, and 'Node Voltage', we can find 'Branch Voltage'.



At R_6 : $V_{R6} = (i_{R6})(R6)$ or $V_{R6} = V_3 - V_G$

$$V_{R6} = V_3$$

$$V_{R1} = 4.37\text{ V}$$

At R_7 : $V_{R7} = (i_{R7})(R7)$ or $V_{R7} = V_4 - V_G$

$$V_{R7} = V_4$$

$$V_{R2} = 3.64\text{ V}$$


Next, let the fun part begin...

Re-calculate I_1 , I_2 , and I_3 again under two assumptions:

1. All resistors are 10% above the exact value.
2. All resistors are 10% below the exact value.

Recall,
$$\left[\begin{array}{ccc|c} (R_1 + R_2 + R_6) & -R_6 & -R_2 & 5 \\ -R_6 & (R_5 + R_6 + R_7) & -R_5 & 0 \\ -R_2 & -R_5 & (R_2 + R_3 + R_4 + R_5) & 0 \end{array} \right]$$

Figure 1.5: Norton and Thevenin Equivalent Circuits

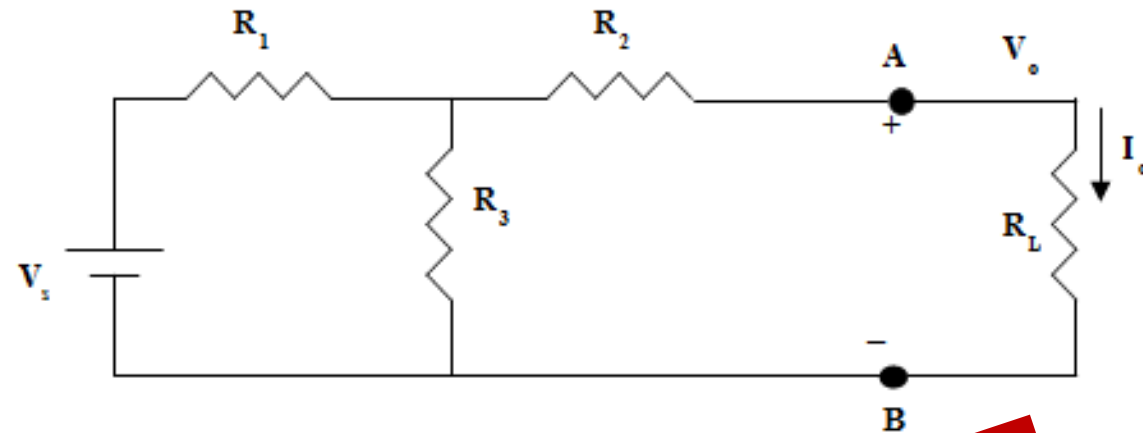

Calculate V_{oc} , I_{sc} , and R_{Th}


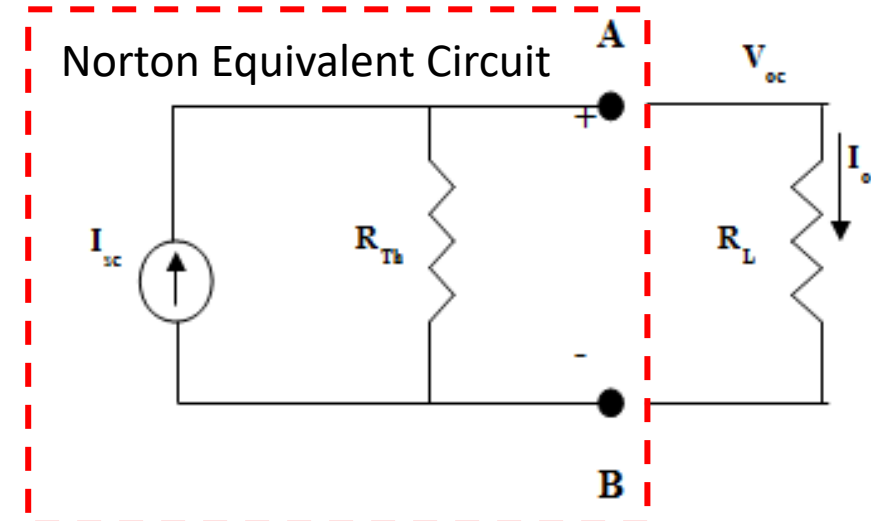
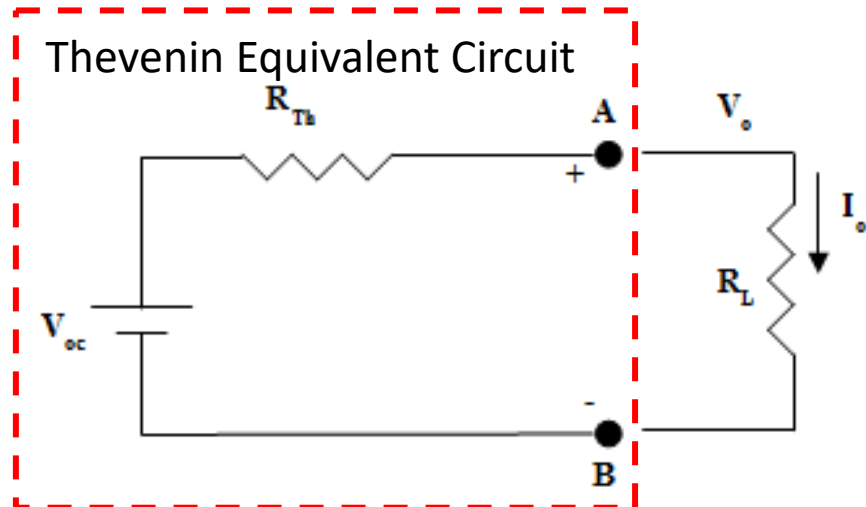


Figure 1.5: Norton and Thevenin Equivalent Circuits


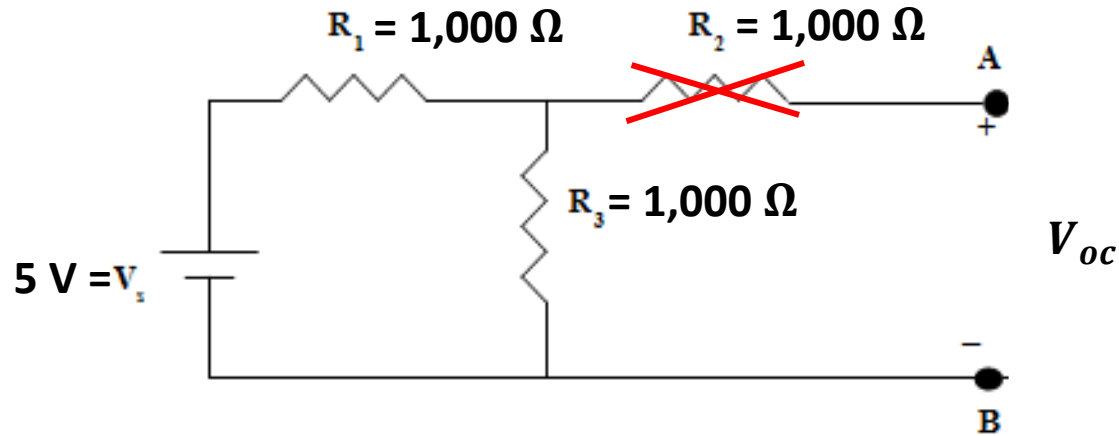


V_{oc} is a voltage drop across R_3 .

$$V_{oc} = \frac{V_s R_3}{R_1 + R_3}$$

$$V_{oc} = I_{sc} R_{Th}$$
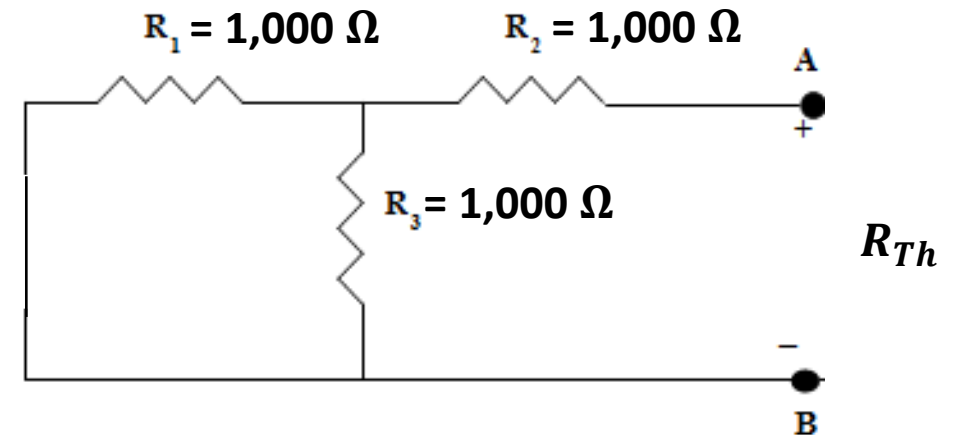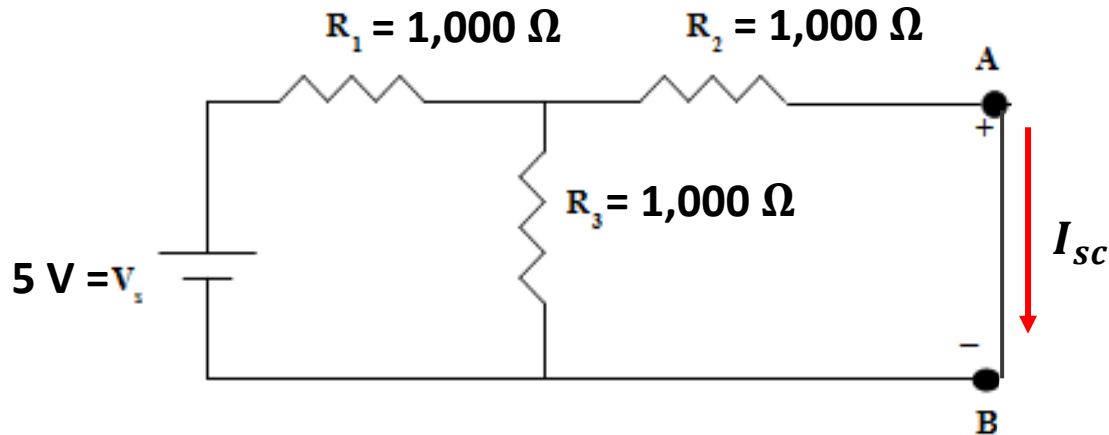
$$R_{Th} = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$



Note: The maximum power transfer to the load is when $R_L = R_{Th}$. Therefore, $P_{max} = \frac{V_{oc}^2}{4R_{Th}}$ (Watt)