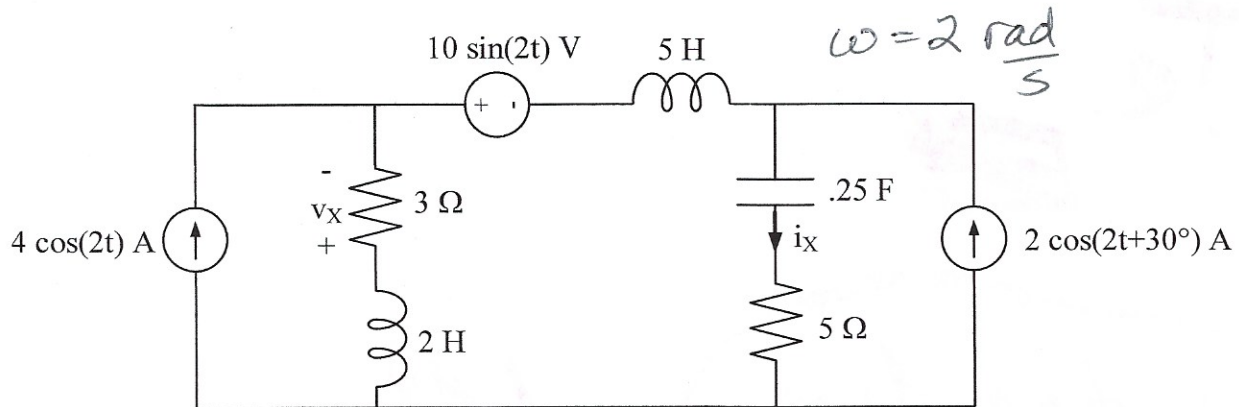


Quiz 4 - 20 points

- Convert the circuit from the time domain to the frequency domain.
- Using either nodal or mesh analysis, solve for the phasor current, I_x , and the phasor voltage V_x .
- What is the time domain current, $i_x(t)$ and the time domain voltage, $v_x(t)$? (Note: only the real parts of the time domain current/voltage are required.)
- Find the average power, P , delivered by each source and absorbed by each impedance.




$$\begin{aligned}
 4 \cos 2t \text{ A} &\rightarrow 4 \angle 0^\circ \text{ A} \\
 10 \sin 2t \text{ V} &\rightarrow 10 \angle -90^\circ \text{ V} \\
 2 \cos(2t + 30^\circ) \text{ A} &\rightarrow 2 \angle 30^\circ \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 3 \Omega &\rightarrow 3 \Omega \\
 5 \Omega &\rightarrow 5 \Omega \\
 2 \text{ H} &\rightarrow j4 \Omega \\
 5 \text{ H} &\rightarrow j10 \Omega \\
 0.25 \text{ F} &\rightarrow -j2 \Omega
 \end{aligned}$$

know
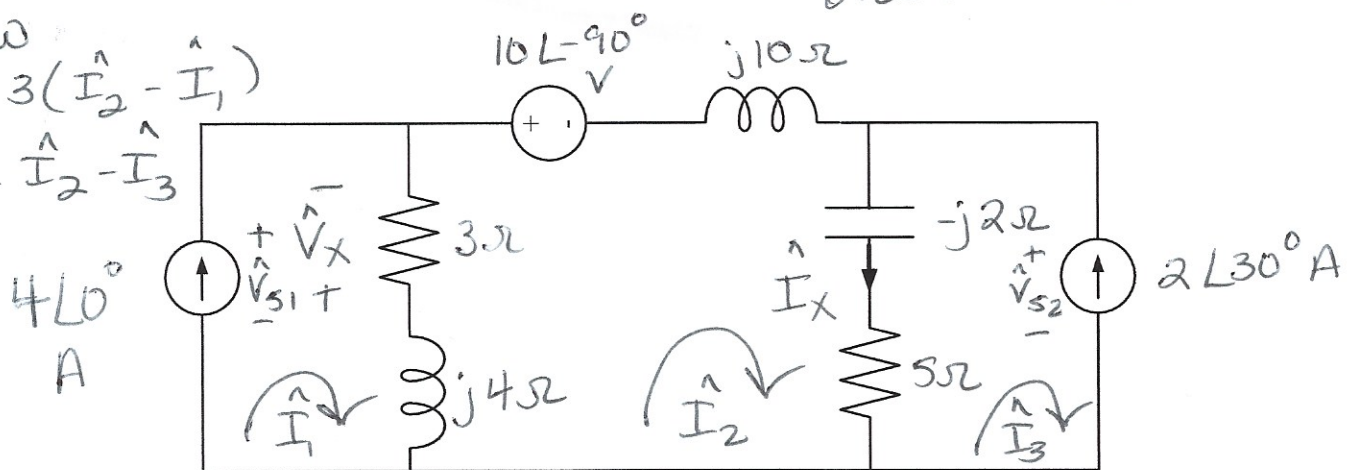
$$\begin{aligned}
 \hat{V}_x &= 3(\hat{I}_2 - \hat{I}_1) \\
 \hat{I}_x &= \hat{I}_2 - \hat{I}_3
 \end{aligned}$$



$$\hat{I}_1 = 4 \angle 0^\circ \text{ A} \quad \hat{I}_3 = -(2 \angle 30^\circ) \text{ A}$$

$$m2: -(3 + j4)(\hat{I}_2 - \hat{I}_1) - 10 \angle -90 - j10 \hat{I}_2 - (5 - j2)(\hat{I}_2 - \hat{I}_3) = 0$$

$$\hat{I}_2(-8 - j12) = (10 \angle -90) - (3 + j4)\hat{I}_1 - (5 - j2)\hat{I}_3$$

pg2

$$\hat{I}_2(-8-j12) = 10 \angle -90^\circ - (20 \angle 53.13^\circ) - (10.77 \angle -171.80^\circ)$$

$$\hat{I}_2(-8-j12) = 24.5 \angle -93.13^\circ$$

$$\hat{I}_2 = 1.70 \angle 30.55^\circ \text{ A}$$

$$(1.46 + j0.86) \text{ A}$$

$$\hat{V}_x = 3(\hat{I}_2 - \hat{I}_1)$$

$$\hat{V}_x = 8.04 \angle 161.20^\circ \text{ V}$$

$$\hat{V}_x = -7.61 + j2.59 \text{ V}$$

$$v_x(t) = 8.04 \cos(2t + 161.20^\circ) \text{ V}$$

$$\hat{I}_x = \hat{I}_2 - \hat{I}_3$$

$$\hat{I}_x = 3.70 \angle 30.26^\circ \text{ A}$$

$$(3.19 + j1.86) \text{ A}$$

$$i_x(t) = 3.70 \cos(2t + 30.26^\circ) \text{ A}$$

Find \hat{V}_{s1} and \hat{V}_{s2}

$$m1: \hat{V}_{s1} - (3+j4)(\hat{I}_1 - \hat{I}_2) = 0 \quad \hat{V}_{s1} = 13.40 \angle 34.31^\circ \text{ V}$$

$$(11.06 + j7.55) \text{ V}$$

$$m2: -(5-j2)(\hat{I}_3 - \hat{I}_2) - \hat{V}_{s2} = 0 \quad \hat{V}_{s2} = 19.92 \angle 8.45^\circ \text{ V}$$

$$(19.71 + j2.93) \text{ V}$$

Power (remember these are magnitude units)

$$\hat{V}_{s1} = 9.48 \angle 34.31^\circ \text{ Vrms}$$

$$\hat{V}_{s2} = 14.09 \angle 8.45^\circ \text{ Vrms}$$

$$\hat{I}_1 = 2.83 \angle 0^\circ \text{ Arms}$$

$$\hat{I}_2 = 1.20 \angle 30.55^\circ \text{ Arms}$$

$$\hat{I}_3 = 1.41 \angle -150^\circ \text{ Arms}$$

pg 3

$$\hat{V}_x = 5.69 \angle 161.20^\circ \text{ Vrms}$$

$$\hat{I}_x = 2.62 \angle 30.26^\circ \text{ Arms}$$

Power : Impedances

$$j4\Omega : P=0$$

$$j10\Omega : P=0$$

$$-j2\Omega : P=0$$

$$3\Omega : P = \frac{|\hat{V}_x|^2}{3} = 10.79 \text{ W, Abs}$$

$$5\Omega : P = |\hat{I}_x|^2(5) = 34.32 \text{ W, Abs}$$


Power Sources

~~10L-90°~~ $2.83 \angle 0^\circ$ Arms : $P = |\hat{V}_{s1}| \cdot (2.83) \cos(34.31^\circ - 0)$
 $P = 22.16 \text{ W, Del}$

$10L-90^\circ$ or $7.07 \angle -90^\circ \text{ Vrms}$
 $P = (7.07)(|\hat{I}_2|) \cos(-90 - 30.55)$
 $= -4.31 \text{ W, Abs}$
 $P = 4.31 \text{ W, Del}$

~~10L-90°~~ $1.41 \angle 30^\circ$ Arms
 $P = |\hat{V}_{s2}| \cdot (1.41) \cos(8.45 - 30^\circ)$
 $P = 18.48 \text{ W, Del}$

pg 4

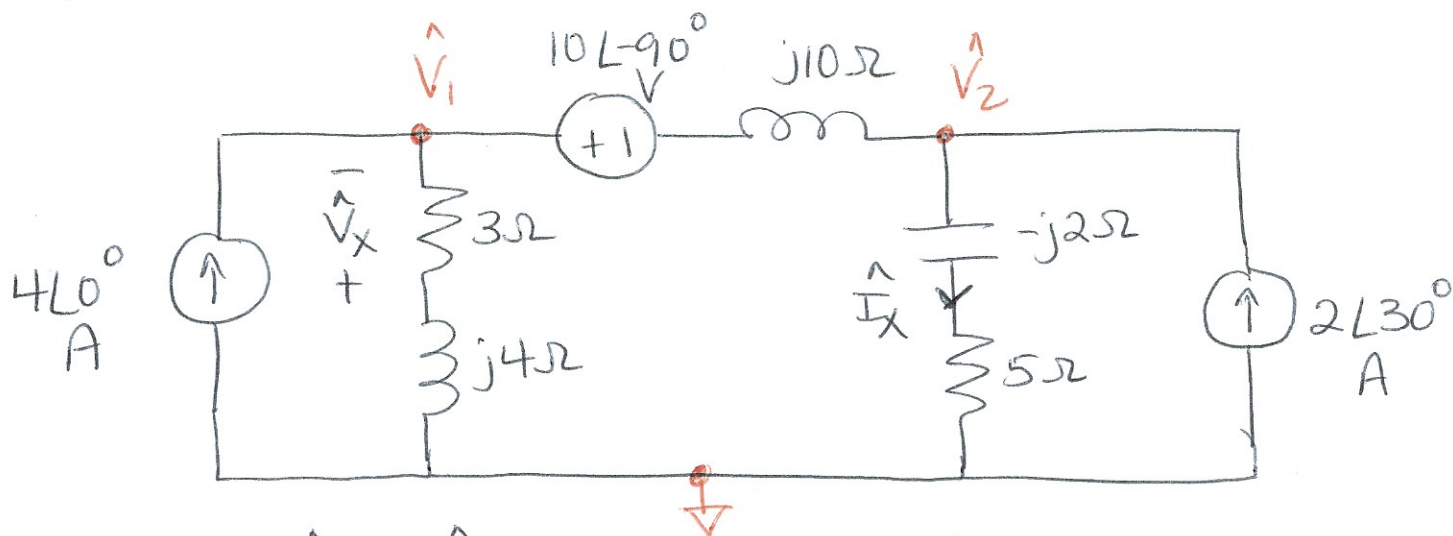

Know $\hat{I}_x = \frac{\hat{V}_2}{5-j2}$

$\hat{V}_x = \frac{-\hat{V}_1}{3+j4} \quad (3)$

(1) $\frac{\hat{V}_1 - 10\angle-90^\circ - \hat{V}_2}{j10} + \frac{\hat{V}_1}{3+j4} + (-4\angle0^\circ) = 0$

(2) $\frac{\hat{V}_2 + 10\angle-90^\circ - \hat{V}_1}{j10} + \frac{\hat{V}_2}{5-j2} + (-2\angle30^\circ) = 0$

$\hat{V}_1 (0.286\angle-65.22^\circ) + \hat{V}_2 (0.1\angle90^\circ) = 3\angle0^\circ$

$\hat{V}_1 (0.1\angle90^\circ) + \hat{V}_2 (0.175\angle-10.20^\circ) = 2.91\angle20.1^\circ$

$\hat{V}_1 = 13.42\angle34.28^\circ \text{ V}$

$\hat{I}_x = 3.70\angle30.22^\circ \text{ A}$

$i_x(t) = 3.70 \cos(2t + 30.22^\circ) \text{ A}$

$\hat{V}_2 = 19.94\angle8.42^\circ \text{ V}$

$\hat{V}_x = 8.05\angle161.15^\circ \text{ V}$

$v_x(t) = 8.05 \cos(2t + 161.15^\circ) \text{ V}$