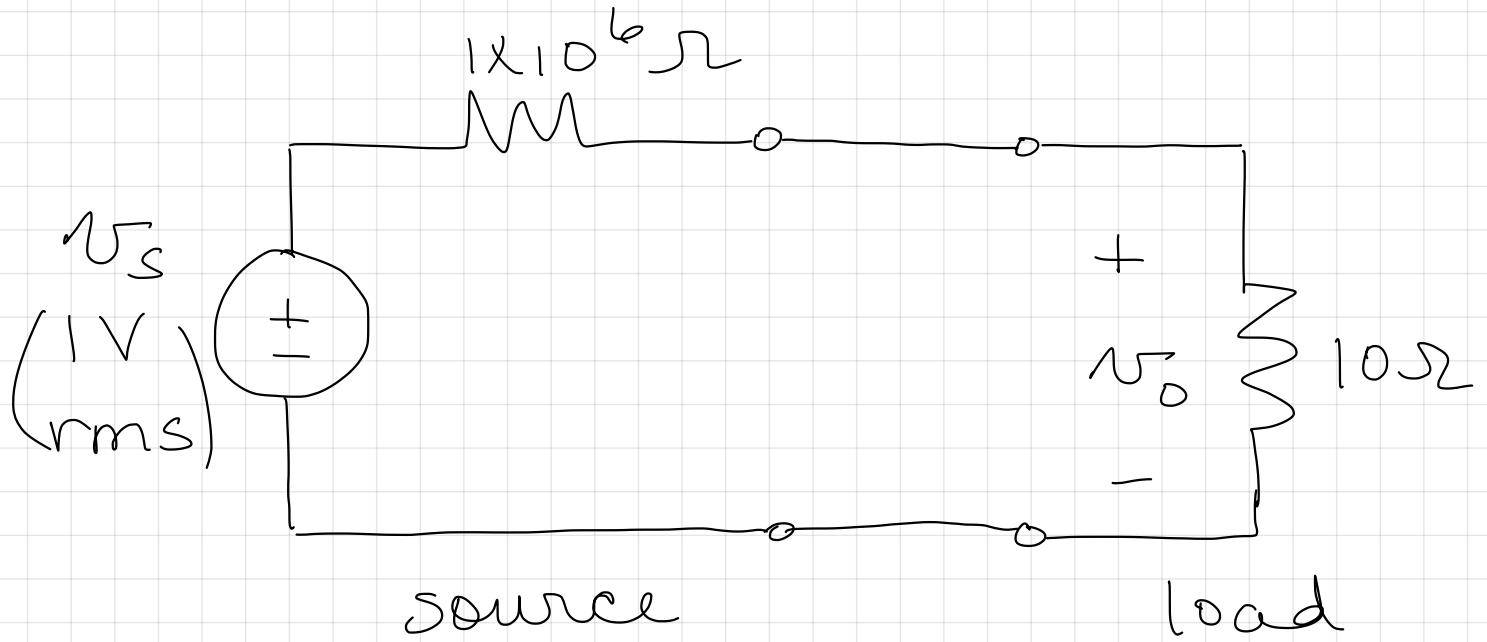


Ex

$$V_s = I \sqrt{r_m s} \quad , \quad R_s = I m s \Omega$$

$$R_L = 10\Omega$$



$$v_o = v_s \left( \frac{10}{10 + 1 \times 10^6} \right)$$

$$v_0 = v_s ( .999 \times 10^{-5} )$$

$$\approx V_s (10 \times 10^{-6})$$

$$N_D \approx 10 \mu V_{rms}$$

$$P_L = \frac{V_0^2}{10} = \frac{(10 \times 10^{-6})^2}{10} = 10^{-11} \text{ W}$$

Remember max power transfer?


$$R_{TH} = R_L$$

$$1 \times 10^6 \ggg 10$$

¶

Severe mismatch

add amplifier in between source & load.

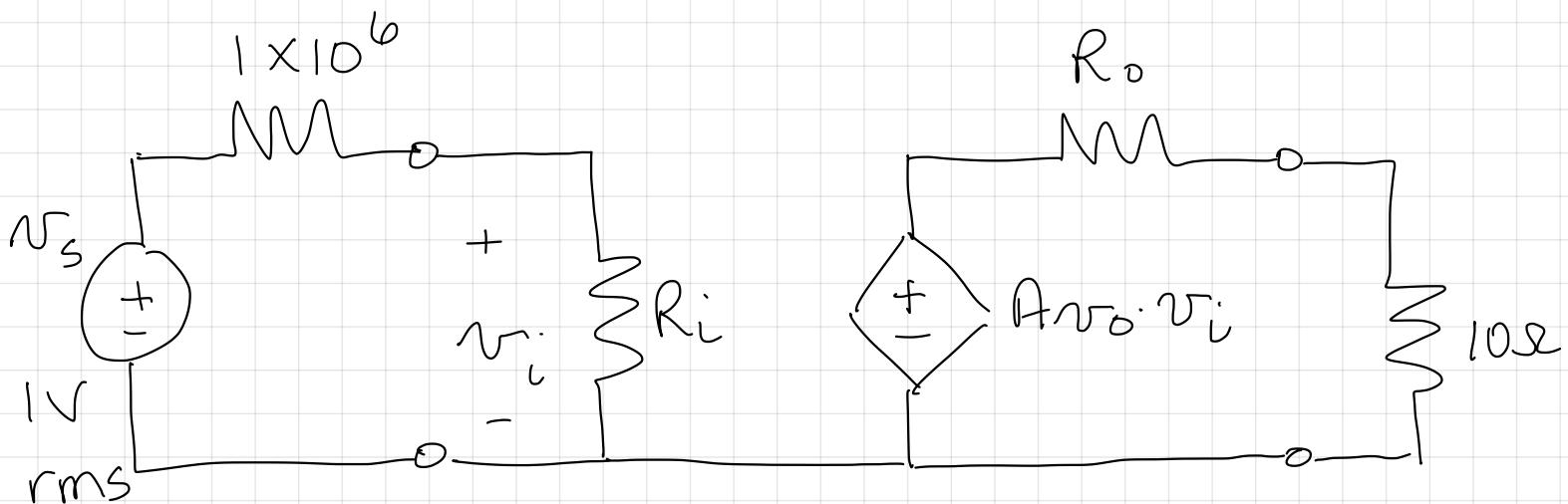

$$A_{vo} = 1 \text{ V/V}$$

$$R_i = 1 \text{ M}\Omega$$

$$R_o = 10 \Omega$$

$$\frac{V_o}{V_s} = A_{vo} \left( \frac{\frac{R_L}{10}}{\frac{R_L + R_o}{10}} \right) \left( \frac{\frac{R_L}{10}}{\frac{R_s + R_i}{1 \text{ M}\Omega}} \right)$$

$$\frac{V_o}{V_s} = (1) \left( \frac{1}{2} \right) \left( \frac{1}{2} \right)$$

$$\frac{V_o}{V_s} = 0.25 \frac{V}{V}$$

$$V_o = 0.25 \text{ V rms}$$

$$P_L = \frac{V_o^2}{10} = \frac{(0.25)^2}{10} = 6.25 \text{ mW}$$

$$Av = \frac{V_o}{V_s} = \frac{0.25}{1} = 0.25 \frac{V}{V}$$

$$= -12.04 \text{ dB}$$

$$A_P = \frac{P_o}{P_i} = \frac{(6.25 \times 10)^{-3}}{(0.5)^2 / 1 \times 10^{-6}}$$

$$A_P = \frac{6.25 \times 10^{-3}}{0.25 \times 10^{-6}} = 25 \times 10^3 \frac{W}{W}$$

$$\alpha = 43.98 \text{ dB}$$

$$V_S \Rightarrow R_S = 100k\Omega \quad R_L = 100\Omega$$

$$\text{Stage 1 : } R_{i1} = 1M\Omega$$

$$R_{o1} = 1k\Omega$$

$$A_{v01} = 10 \text{ V/V}$$

high  
input resistance

$$\text{Stage 2 : } R_{i2} = 100k$$

$$R_{o2} = 1k\Omega$$

$$A_{v02} = 100 \text{ V/V}$$


high  
gain

$$\text{Stage 3 : } R_{i3} = 10k\Omega$$

$$R_{o3} = 10\Omega$$

$$A_{v03} = 1 \text{ V/V}$$

low output  
resistance.

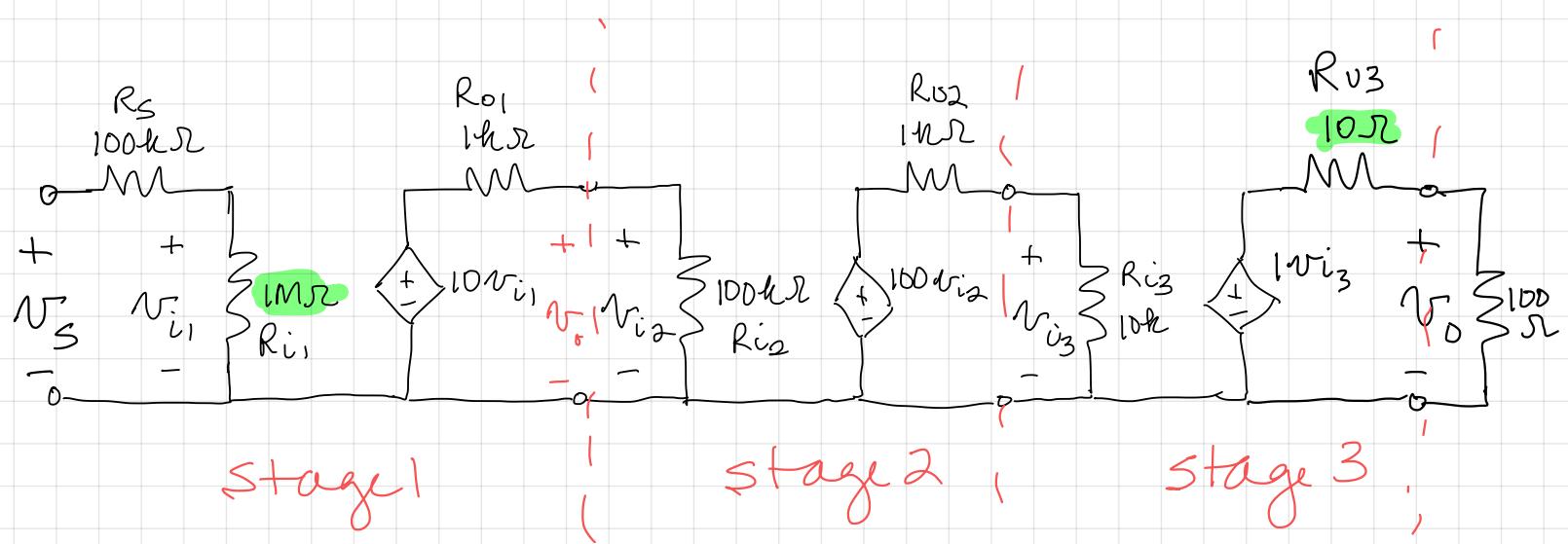

$$V_O = V_{i3} \left( \frac{100}{100+10} \right) = 0.91 V_{i3}$$

$$V_{i3} = 100 V_{i2} \left( \frac{10 \times 10^3}{10 \times 10^3 + 1 \times 10^3} \right) = 90.91 V_{i2}$$


$$V_{i2} = 10 V_{i1} \left( \frac{100 \times 10^3}{100 \times 10^3 + 1 \times 10^3} \right) = 9.90 V_{i1}$$

$$V_{i1} = V_S \left( \frac{1 \times 10^6}{1 \times 10^6 + 100 \times 10^3} \right) = 0.91 V_S$$

$$\frac{V_O}{V_S} = \left( \frac{V_O}{V_{i3}} \right) \left( \frac{V_{i3}}{V_{i2}} \right) \left( \frac{V_{i2}}{V_{i1}} \right) \left( \frac{V_{i1}}{V_S} \right)$$

$$= (0.91) (90.91) (9.90) (.91)$$



$$\frac{U_0}{U_S} = 745.29 \frac{V}{V}$$

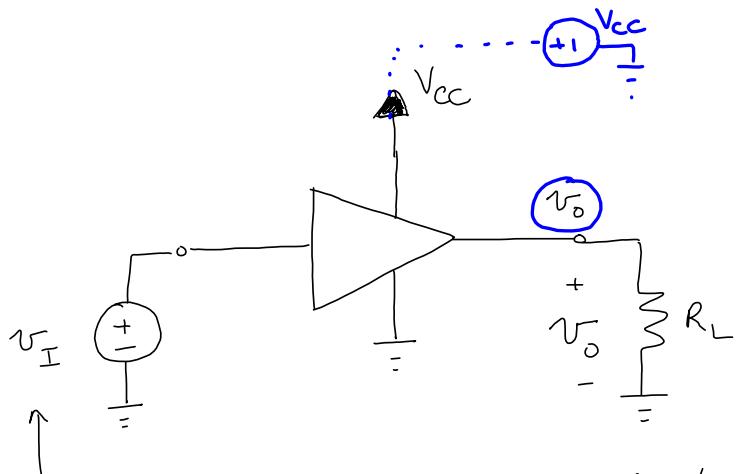



$v_I$  is a weak or small signal (mV to  $\mu$ V)

$v_O$  is the amplified version of  $v_I$  (.1V to 1V)

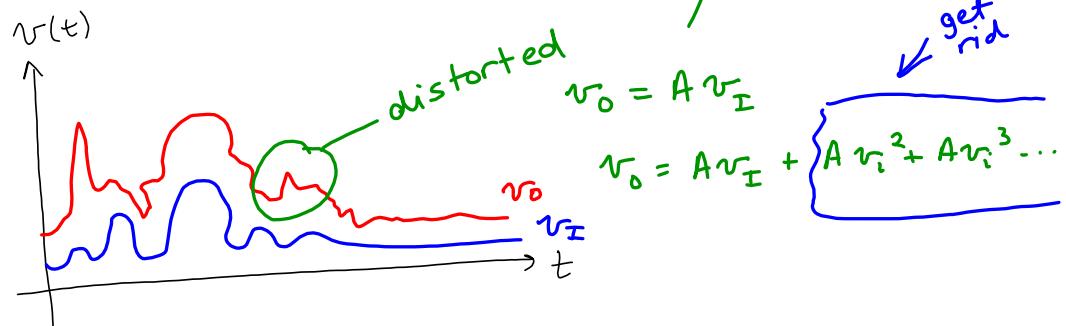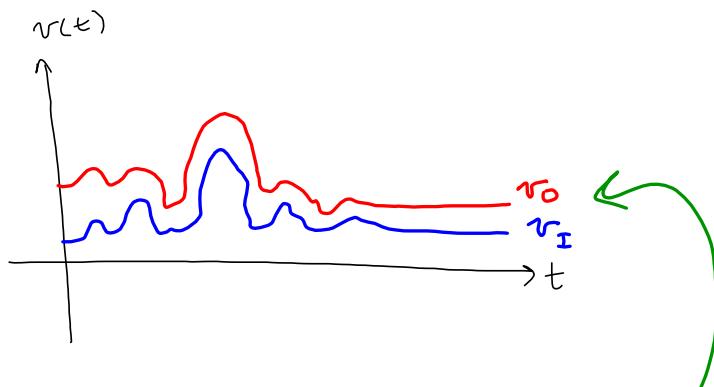Good amplification  $\Rightarrow$  Linear  $v_O = A v_I$   
 $\uparrow$   
 constant



voltage transfer characteristic: (VTC)

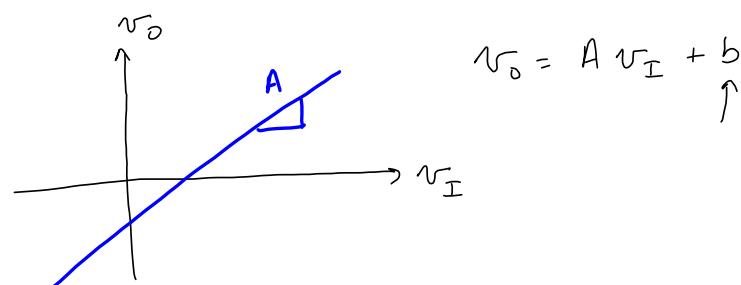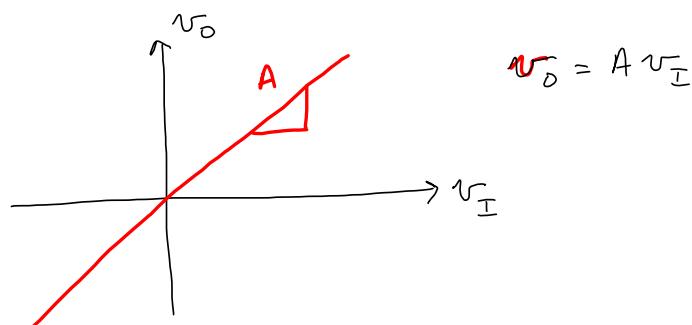

Amplifier design goals  $\Rightarrow$  linear amplification  
no distortion

## Amplifier Types

$$\text{voltage amps} \Rightarrow V_o = A_v \cdot V_I \quad A_v \equiv \text{voltage gain}$$

$$\text{current amps} \Rightarrow i_o = A_i \cdot i_I \quad A_i \equiv \text{current gain}$$

$$\text{power amps} \Rightarrow P_o = A_p \cdot P_I \quad A_p \equiv \text{power gain}$$

$$A_v = \frac{V_o}{V_I} \left( \frac{V}{V} \right) \quad A_i = \frac{i_o}{i_I} \left( \frac{A}{A} \right) \quad A_p = \frac{P_o}{P_I} \left( \frac{W}{W} \right)$$


$$\text{if using log scale} \Rightarrow \text{express gain in dB.}$$

$$= \frac{V_o i_o}{V_I i_I} = \left( \frac{VA}{VA} \right)$$

$$\frac{dB}{A_v} = 20 \log |A_v| \quad A_v = -10 V/V$$

$$A_i = 20 \log |A_i|$$

$$A_p = 10 \log |A_p|$$

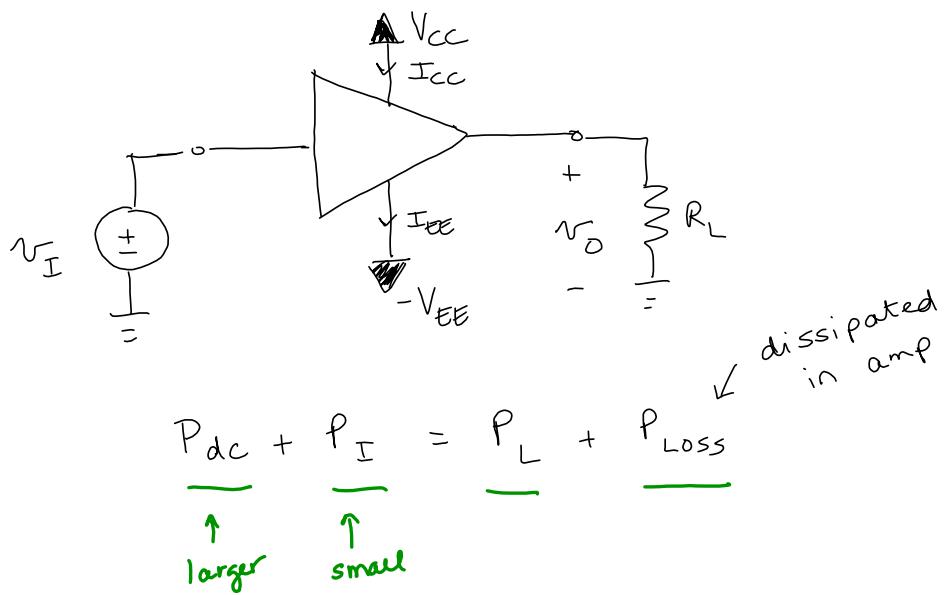


$$\text{amplifier efficiency: } \eta = \frac{P_L}{P_{dc}} \times 100 \Rightarrow \text{percent efficiency}$$



Amplifier saturation

$$v_o = A v_i$$
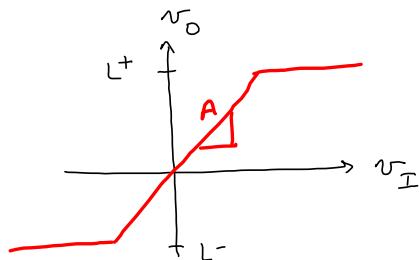
$$\frac{L^-}{A} \leq v_i \leq \frac{L^+}{A}$$



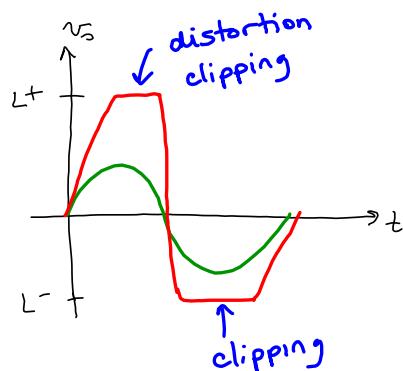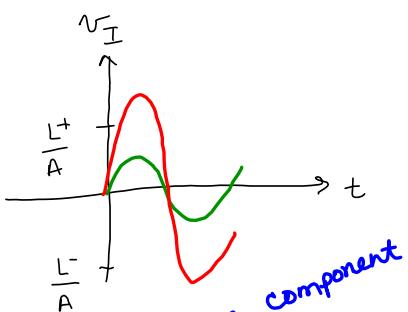$L^+$ ,  $L^-$  are typically 90-99% of the dc supply



total signal  $v_o$  =  $v_o$  (DC component) +  $v_o(t)$  (AC component)

$i_A$  =  $i_A$  (DC bias) +  $i_a(t)$  (small-signal component)


large signal resistance  $R_i$ ,  $R_o$ ,  $R_I$ ,  $R_o$

small signal resistance  $r_{\pi}$ ,  $r_o$ ,  $r_i$

Ex 1

Design an inverting op-amp with a closed loop gain of  $-50 \text{ V/V}$ . Maximum resistor size is  $5 \text{ M}\Omega$ .

Design for the largest input resistance.

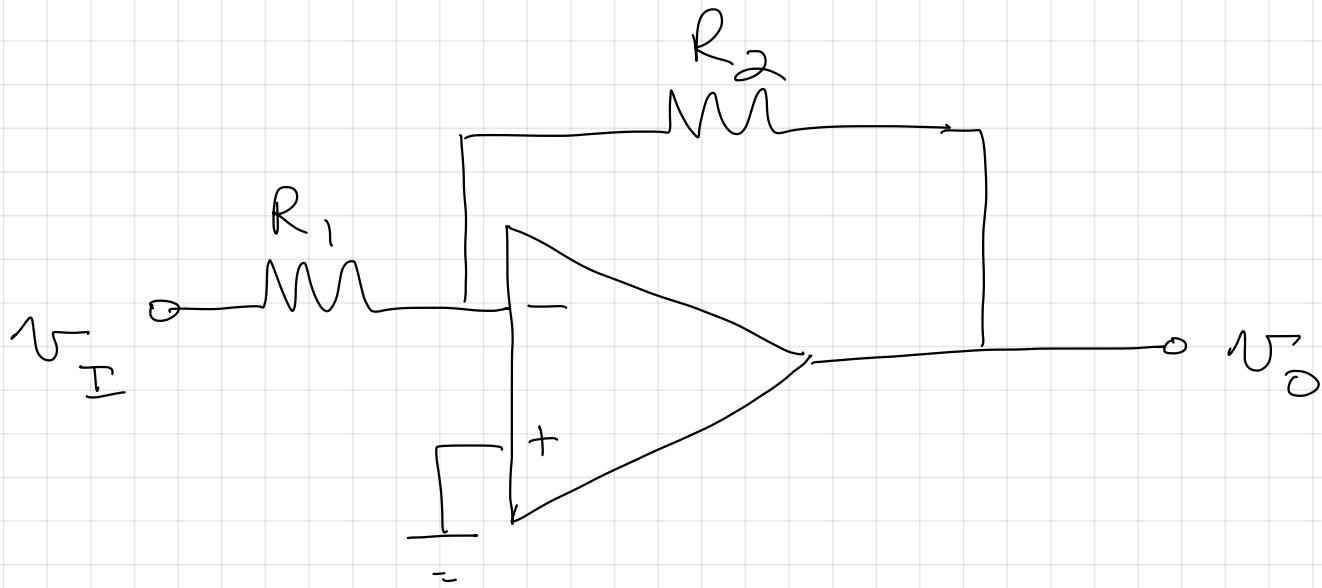

$$\frac{V_O}{V_S} = G = -50 \frac{V}{V} = -\frac{R_2}{R_1}$$

$$R_i = R_1$$

$$\frac{R_2}{R_1} = 50$$

$$R_1 = 5 \text{ M}\Omega \Rightarrow R_2 = 250 \text{ M}\Omega$$

$$\text{let } R_2 = 5\text{M}\Omega$$

$$R_1 = \frac{R_2}{50} = 100\text{k}\Omega$$

$$R_1 = 100\text{k}\Omega$$


$$R_2 = 5\text{M}\Omega$$

Example 2: Design an inverting amp.

$$V_{\text{I}} : \pm 3\text{V}$$

$$V_o : \pm 60\text{V}$$

$$i_{\text{max}} = 20\text{mA}$$

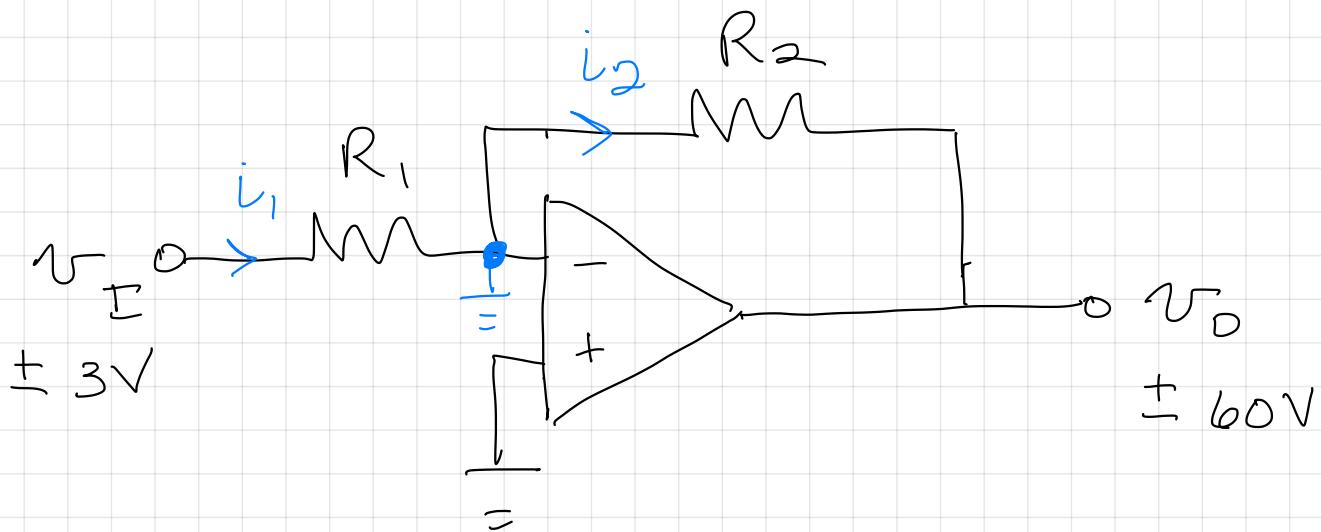

$$\frac{V_o}{V_s} = \frac{\pm 60}{\pm 3} = -20 \frac{V}{V} = G = -\frac{R_2}{R_1}$$

$$\frac{R_2}{R_1} = 60$$

$$i_2 = \frac{0 - V_o}{R_2} \leq 20 \mu A$$

$$i_1 = \frac{V_I - 0}{R_1} \leq 20 \mu A$$

$$i_2 = -\frac{V_o}{R_2} \text{ for } V_o \text{ at } 60V$$

$$i_2 = \left[ \frac{60}{R_2} \leq 20 \mu A \right]$$

$$R_2 \geq \frac{60}{20 \times 10^{-6}}$$

$$R_2 \geq 3M\Omega$$

$$\text{let } R_2 = 3M\Omega$$

$$R_1 = \frac{R_2}{20} = 150 k\Omega$$

$$\frac{V_I}{R_1} \leq 20 \mu A$$

$$V_I \leq R_1 (20 \times 10^{-6})$$

$$V_I \leq 3V$$

A possible design

$$R_2 = 3M\Omega$$


$$R_1 = 150 k\Omega$$

### Example 3

inverting op-amp that drives a  $1\text{ k}\Omega$  load. The input voltage varies from  $\pm 2\text{ V}$ .

The load must be able to absorb  $1\text{ mW}$  at peak output

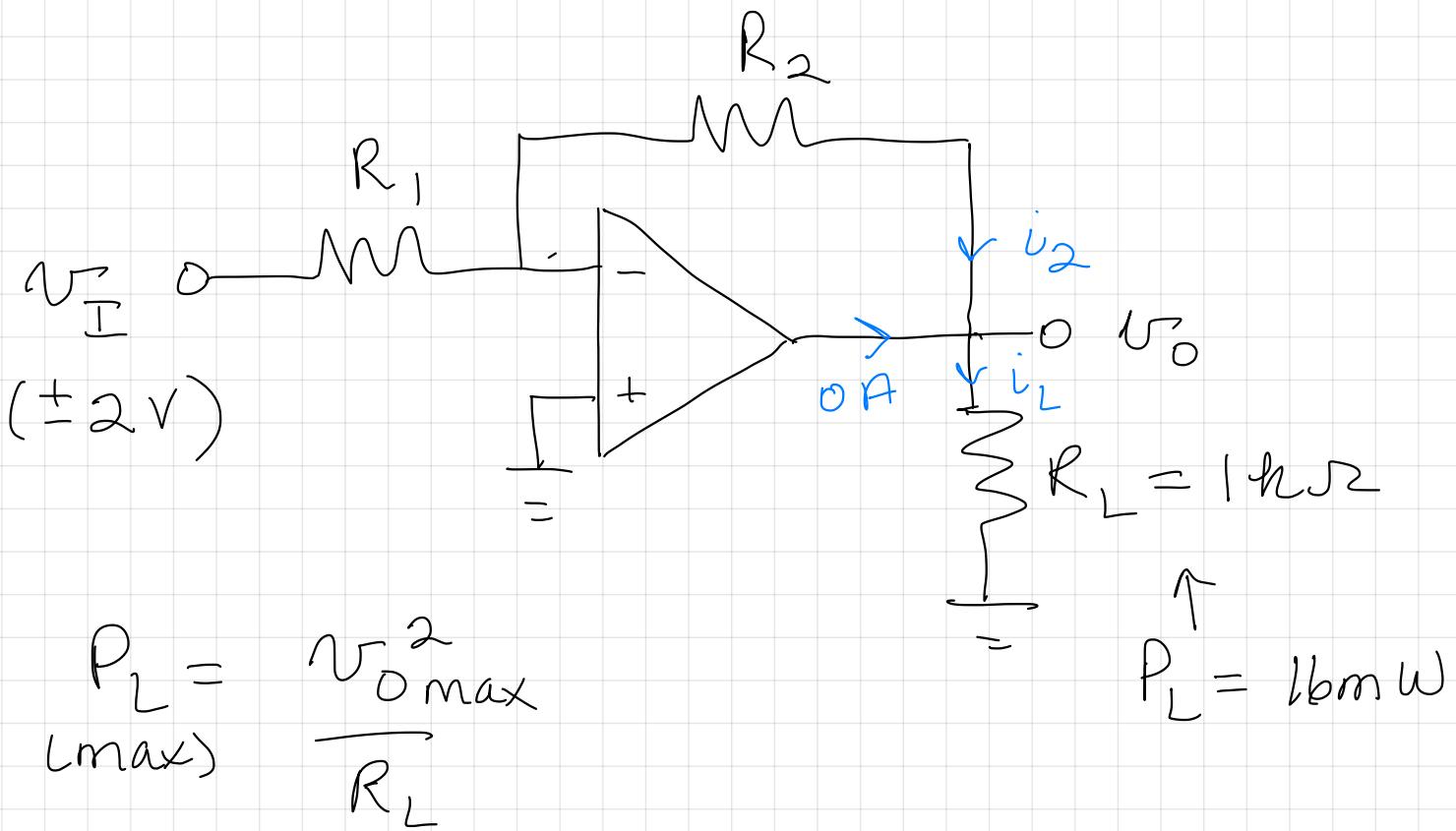$G$ ,  $R_1$ ,  $R_2$  and the  $V_o$  range.



$$1\text{ mW} \times 10^{-3} = \frac{V_{o\max}^2}{1000}$$

$$V_{o\max} = \pm 4\text{ V}$$

$$G = \frac{V_o}{V_s} = -\frac{4}{2} = -2 \frac{V}{V}$$

$$-\frac{R_2}{R_1} = -2$$

$$V_o = \pm 4V$$

$$V_I = \pm 2V$$


$$G = -2 \frac{V}{V}$$

$$P_L = 16mW$$

$$R_2 = 2R_1$$

$$R_2 = 2\Omega$$

$$R_1 = 1\Omega$$

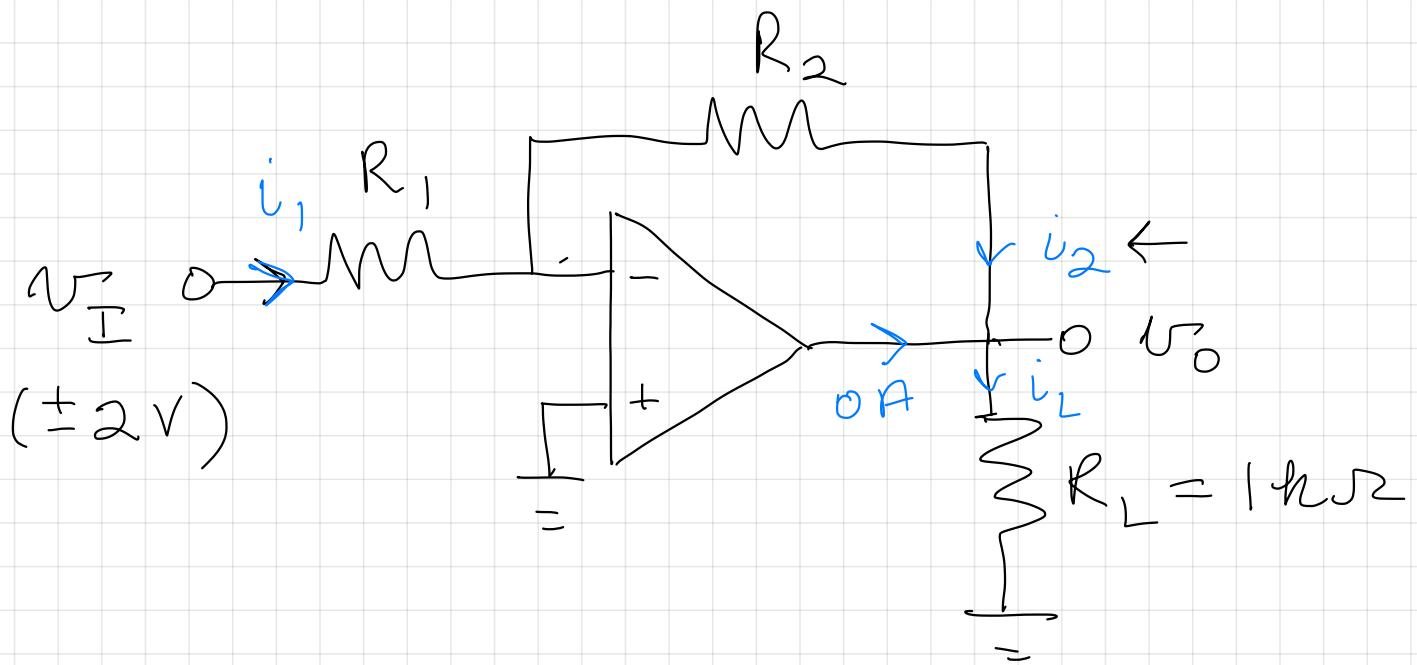

$$i_L = \frac{V_o}{R_L} = \frac{4}{1000} = 4 \text{ mA}$$

$$i_2 = \frac{0 - V_o}{R_2} = 4 \text{ mA}$$

$$R_2 = \frac{V_o}{4 \text{ mA}} = 1 \text{ k}\Omega$$


$$R_2 = 1 \text{ k}\Omega$$

$$R_1 = 500 \Omega$$

$$i_1 = \frac{V_I}{R_1} = \frac{2}{500}$$

$$i_1 = 4 \text{ mA}$$

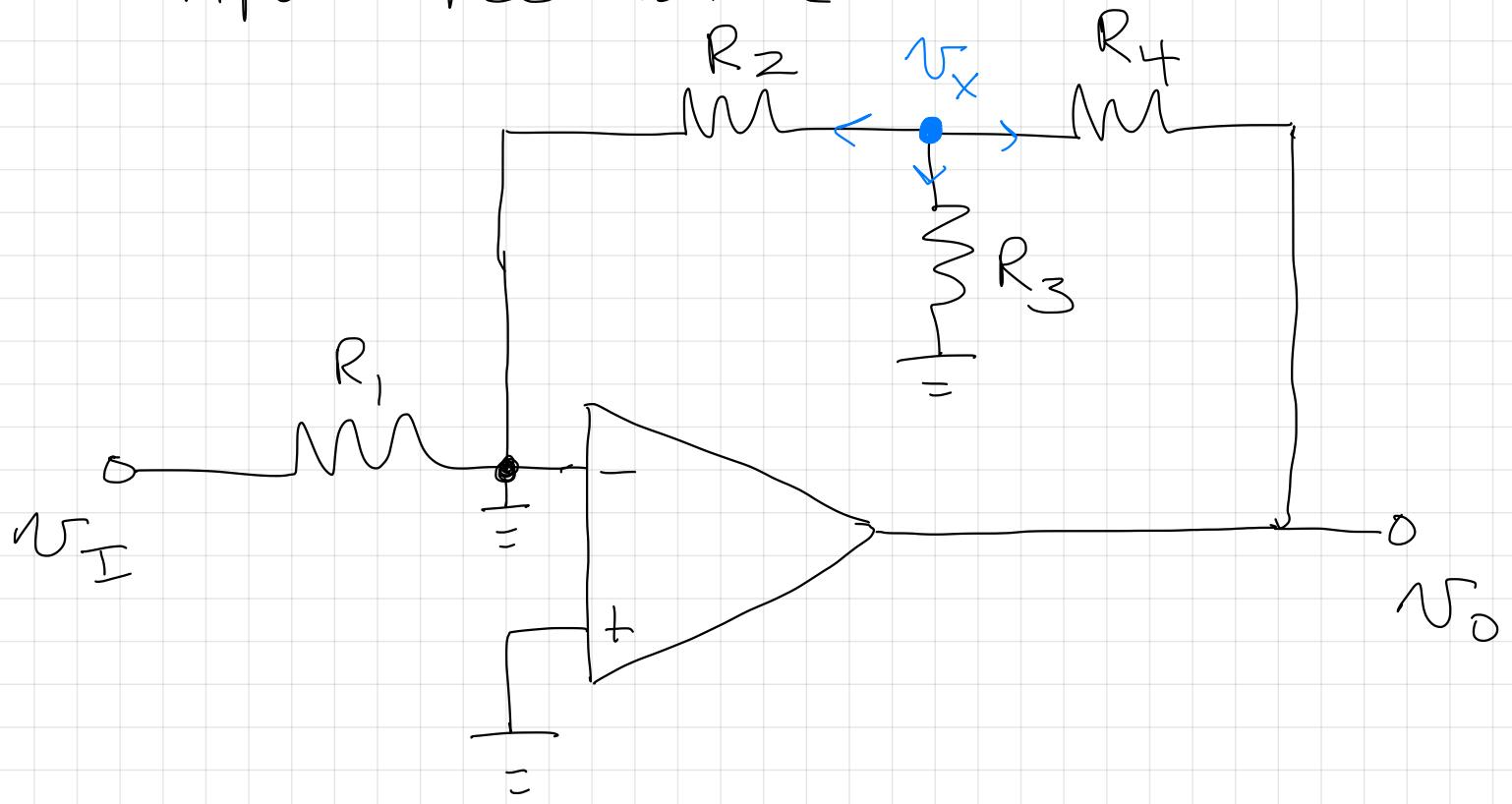add a "T"-resistor network in feedback loop to boost input resistance.



by nodal analysis at  $\times$  node

$$\frac{V_X - 0}{R_2} + \frac{V_X - 0}{R_3} + \frac{V_X - V_O}{R_4} = 0$$

$$\frac{V_O}{R_4} = \frac{V_X}{R_2} + \frac{V_X}{R_3} + \frac{V_X}{R_4}$$

$$\boxed{\frac{V_O}{V_X} = \frac{R_4}{R_2} + \frac{R_4}{R_3} + 1}$$

$$\boxed{\frac{V_X}{V_I} = -\frac{R_2}{R_1}}$$

$$\frac{V_0}{V_I} = \left( -\frac{R_2}{R_1} \right) \left( \frac{R_4}{R_2} + \frac{R_4}{R_3} + 1 \right) = -100$$

Ex  
Want  $R_i = 1\text{M}\Omega$

$$G = -100 \text{ V/V}$$

$$R_{\max} = 1\text{M}\Omega$$

let  $R_1 = 1\text{M}\Omega$

$$R_2 = 1\text{M}\Omega$$

$$R_4 = 1\text{M}\Omega$$

$$\left( -\frac{1\text{M}}{1\text{M}} \right) \left( \frac{1\text{M}}{1\text{M}} + \frac{1\text{M}\Omega}{R_3} + 1 \right) = -100$$


$$\left( 2 + \frac{1 \times 10^6}{R_3} \right) = 100$$

$$\frac{1 \times 10^6}{R_3} = 98$$


$$R_3 = \frac{1 \times 10^6}{98}$$

$$R_3 = 10.2 \text{ k}\Omega$$




—

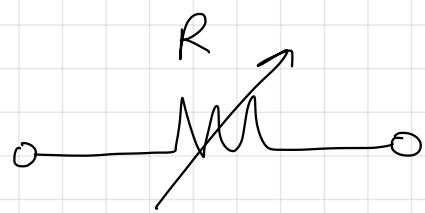


$R$  = range of value

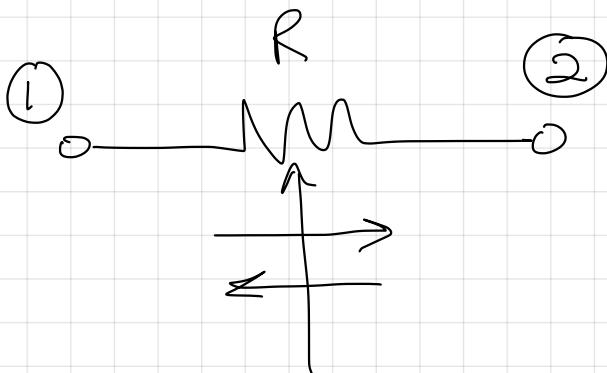

③ Knob

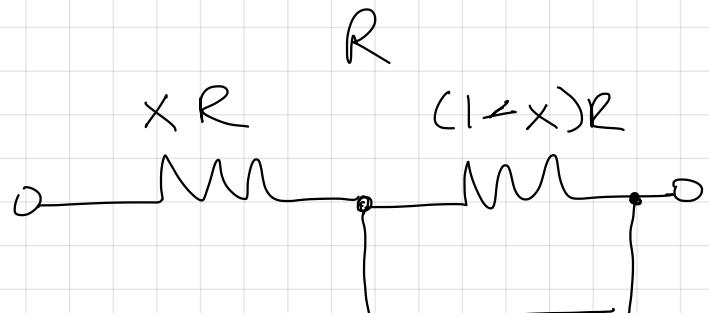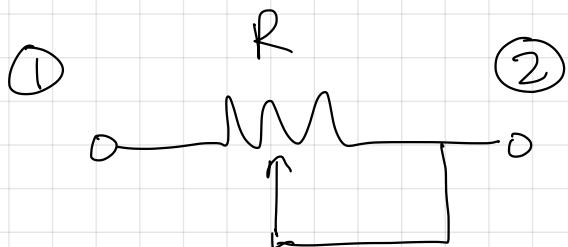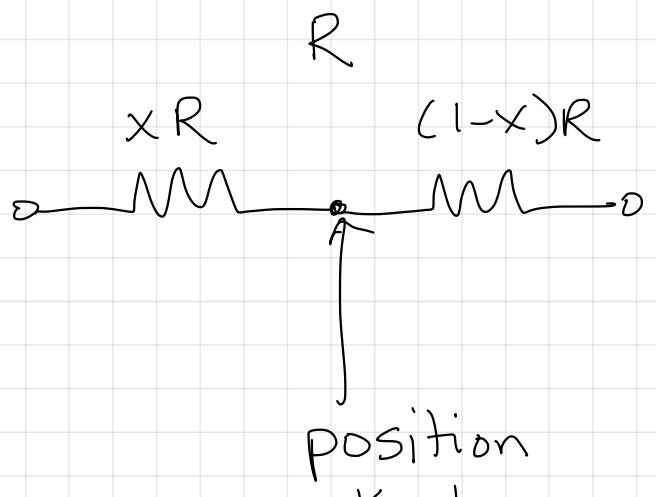

Ex of using a pot in the T network.

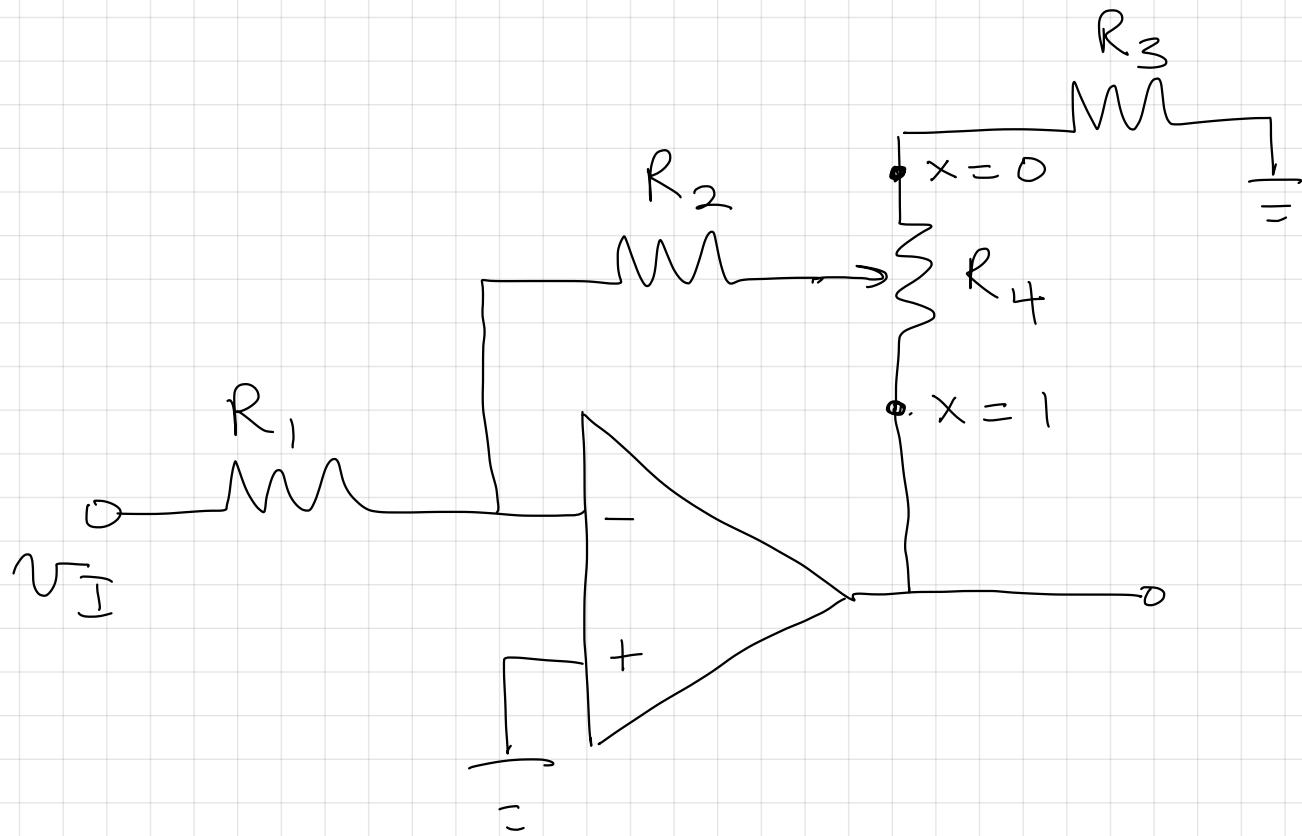

$$R_4 = 100k\Omega \text{ pot}$$

$$R_i = 100k\Omega$$

$x=0$   $R_4$  connects  $R_2$  and  $R_3$  to  $V_o$   
 $R_4 = 100k\Omega$

$$x=1 \quad R_4 \rightarrow 0$$

$R_2$  &  $R_3$  are shorted to output

$$R_4 = 0$$

$$R_3' = R_3 + 100k\Omega$$

Design  $R_1, R_2, R_3$  such that

$$G \Rightarrow -1 \text{ to } -100 \text{ V}$$

$$\frac{V_o}{V_I} = -\frac{R_2}{R_1} \left( \frac{R_4}{R_2} + \frac{R_4}{R_3} + 1 \right)$$

①

$$G = -1 \frac{V}{V} \quad R_4 = 0 \Omega$$

$$R_3' = R_3 + 100k\Omega$$

②

$$G = -100 \frac{V}{V} \quad R_4 = 100k\Omega$$

$$R_3' = R_3$$

①

$$-\frac{R_2}{R_1} \left( \frac{0}{R_2} + \frac{0}{R_3} + 1 \right) = -1$$

$$\frac{-R_2}{R_1} = -1$$

$$R_2 = R_1$$

$$R_1 = R_i = 100k\Omega$$

$$R_2 = 100k\Omega$$

②

$$\frac{V_o}{V_I} = -\frac{R_2}{R_1} \left( \frac{R_4}{R_2} + \frac{R_4}{R_3} + 1 \right) = -100$$




$$-\frac{100k}{100k} \left( \frac{100k}{100k} + \frac{100k}{R_3} + 1 \right) = -100$$

$$\left( 1 + \frac{100 \times 10^3}{R_3} + 1 \right) = 100$$



$$\frac{100 \times 10^3}{R_3} = 98$$

$$R_3 = 1.02 \text{ k}\Omega$$


# Weighted Summer

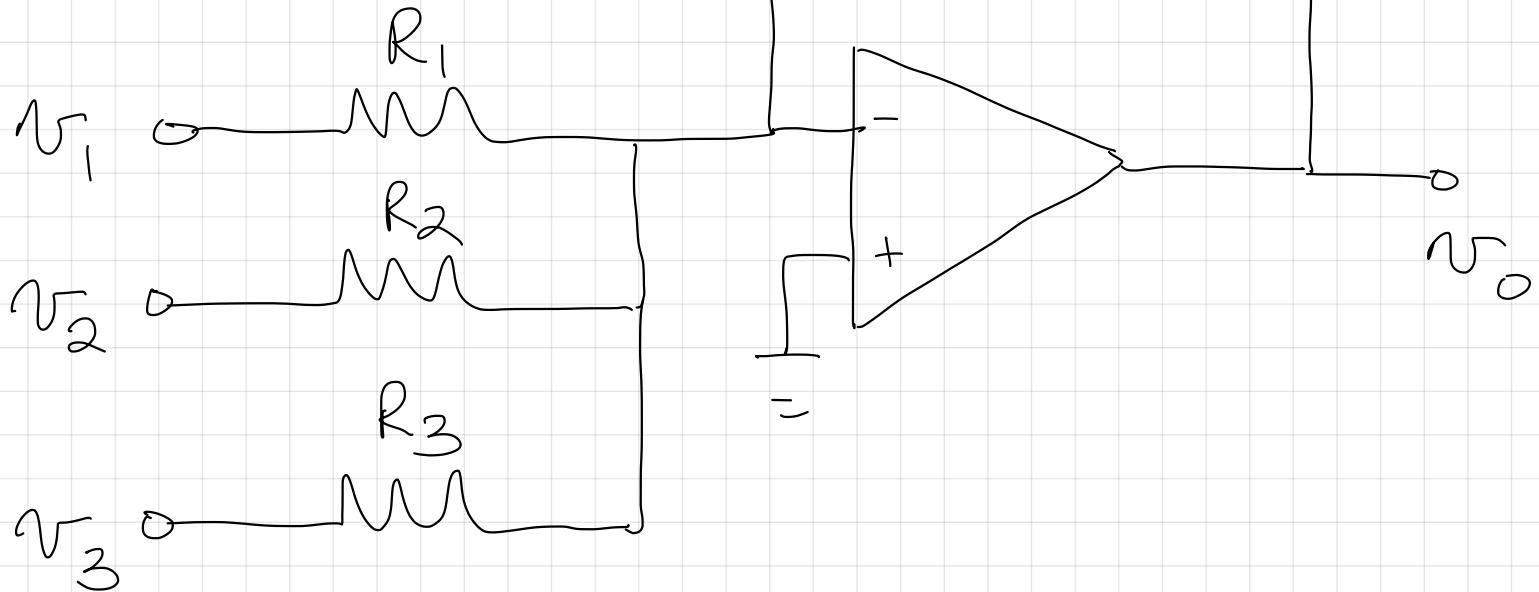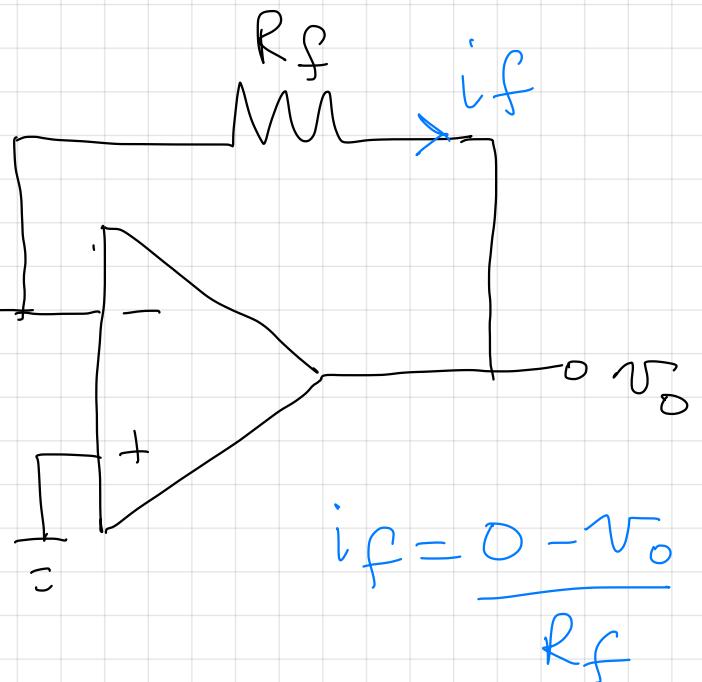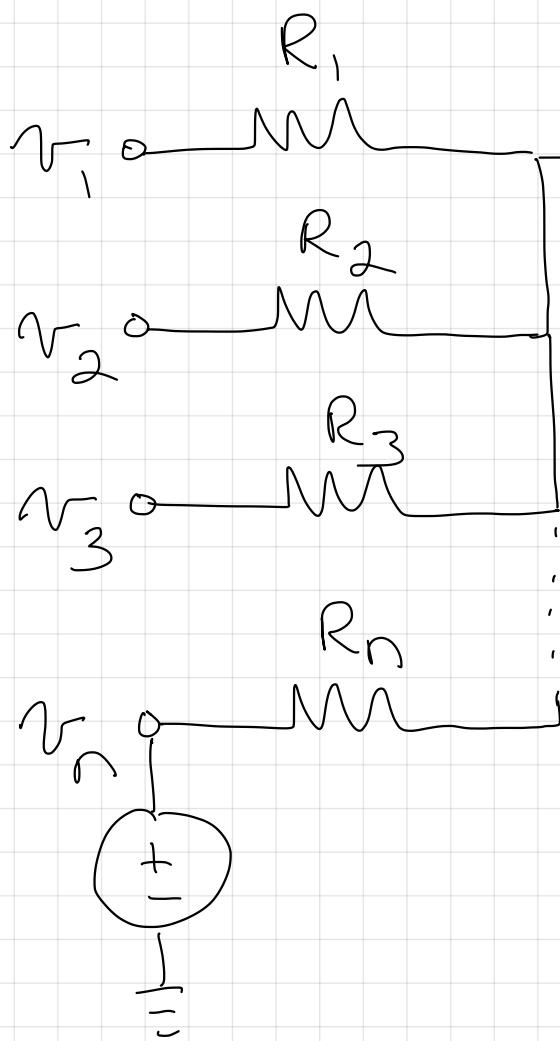

$V_i$  on

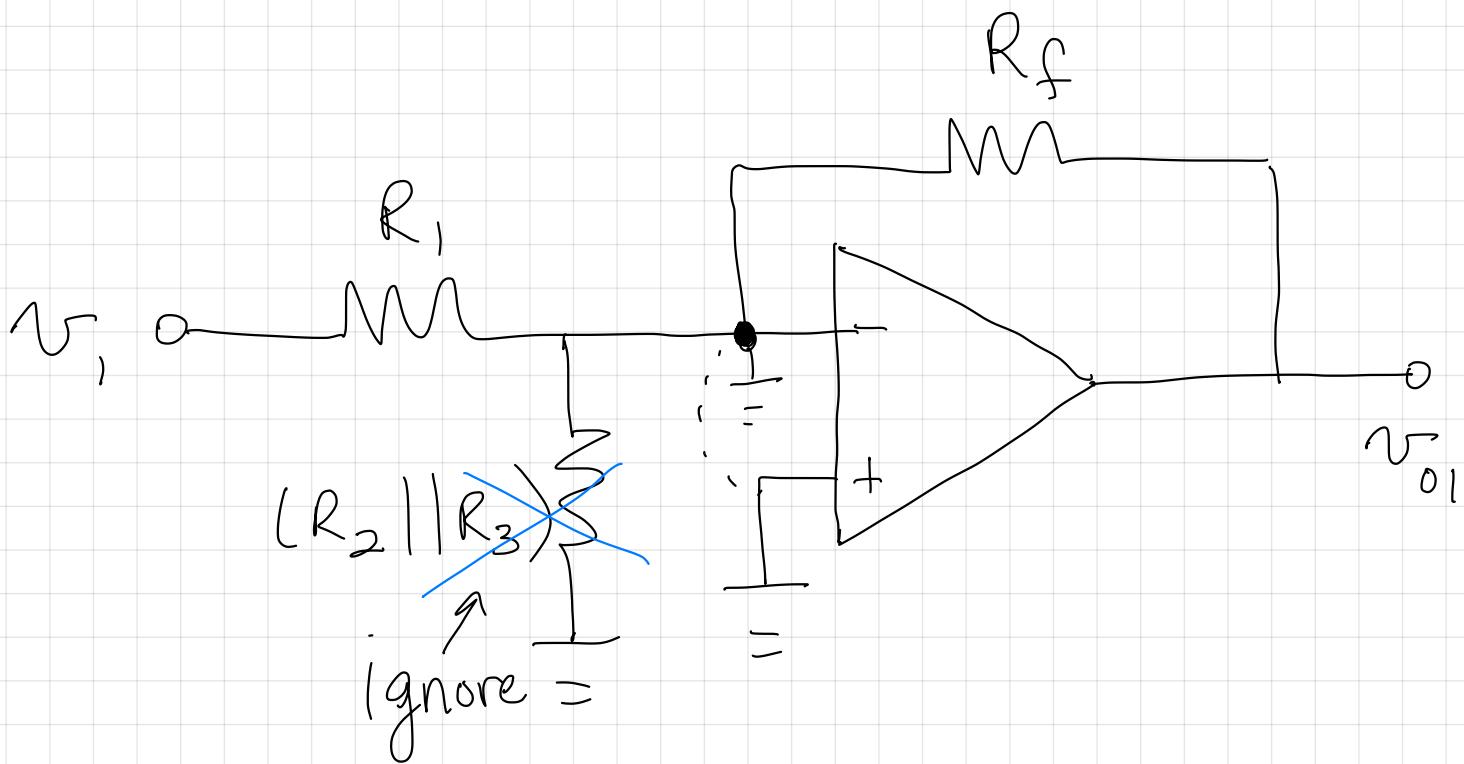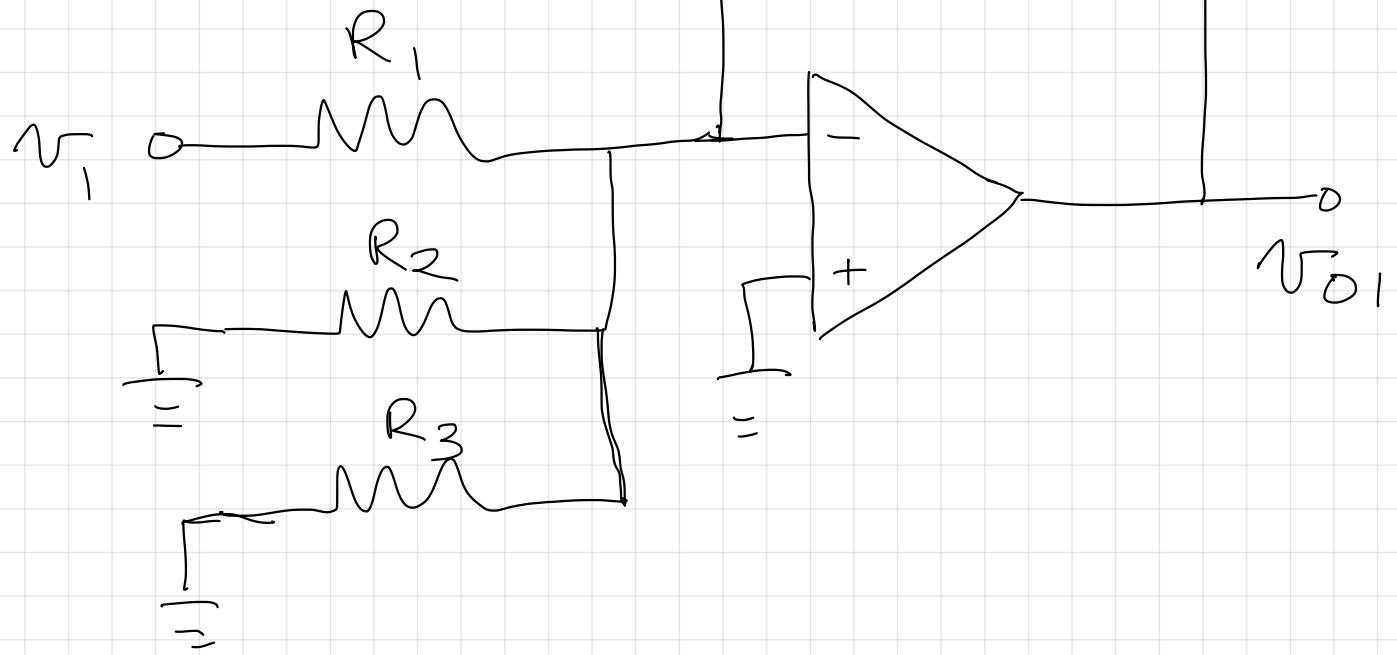

$$V_{o1} = -\frac{R_f}{R_1} V_i$$

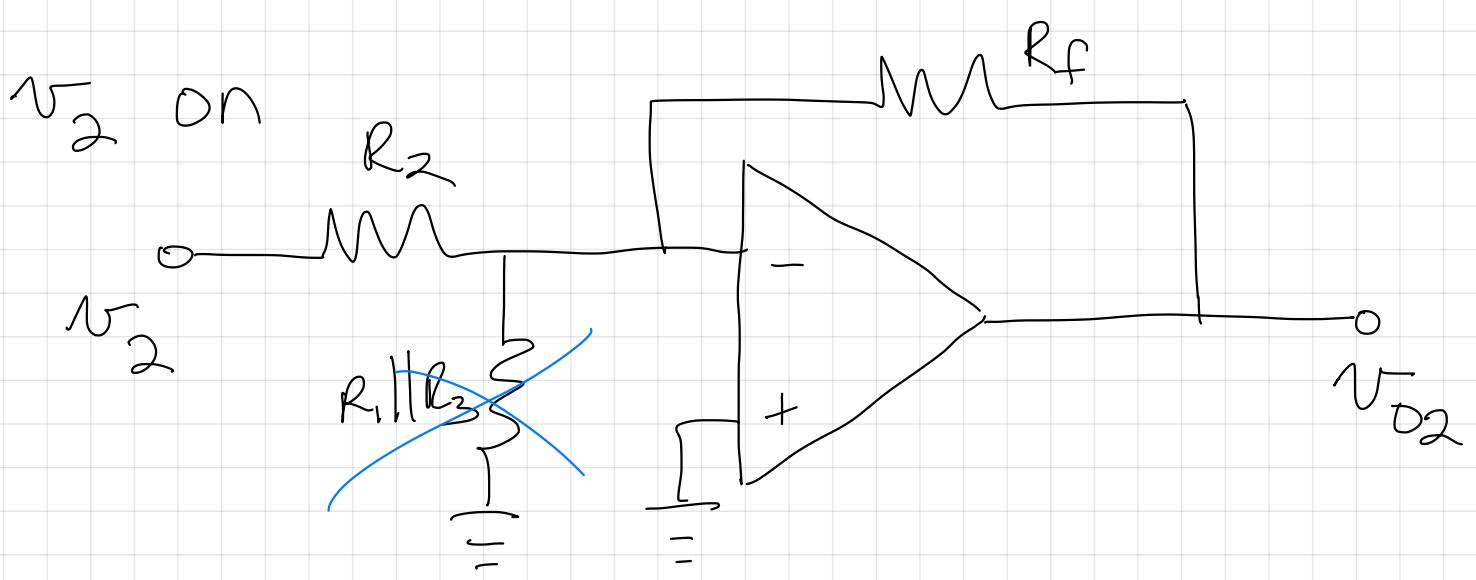

$$V_{02} = -\frac{R_f}{R_2} V_2$$

$$V_{03} = -\frac{R_f}{R_3} V_3$$

$$V_0 = V_{01} + V_{02} + V_{03}$$

$$V_0 = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

$$\underline{\text{Ex}} : V_0 = -5V_1 - 2V_2 - 7V_3$$

$$\text{Design} \rightarrow -5 = -\frac{R_f}{R_1} \quad \left. \right\} \quad R_f = 1 \text{ M}\Omega$$

$$R_1 = 200 \text{ k}\Omega$$

$$-2 = -\frac{R_f}{R_2} \quad \left. \right\} \quad R_2 = 500 \text{ k}\Omega$$

$$-7 = -\frac{R_f}{R_3} \quad \left. \right\} \quad R_3 = 142.86 \text{ k}\Omega$$

Design 2

$$V_0 = -5V_1 - 2V_2 - 7V_3 \leftarrow$$

$$\boxed{i_{\max} \text{ in } R_f = 10 \text{ mA} \\ V_{0\max} = 5V}$$

$$\frac{R_f}{R_1} = 5$$

$$i_f = \frac{V_{0\max}}{R_f}$$

$$\frac{R_f}{R_2} = 2$$

$$10 \times 10^{-6} \geq \frac{5}{R_f}$$

$$\frac{R_f}{R_3} = 7$$

$$R_f \geq \frac{5}{10 \times 10^{-6}}$$

$$R_f \geq \frac{5}{10 \times 10^{-6}}$$

$$R_1 = \frac{R_f}{5}$$

$$R_f \geq 0.5 \text{ M}\Omega$$

$$R_2 = \frac{R_f}{2}$$


$$R_f = 100 \text{ k}\Omega$$

$$R_3 = \frac{R_f}{7}$$

$$R_1 = 20 \text{ k}\Omega$$

$$R_2 = 50 \text{ k}\Omega$$

$$R_3 = 14.29 \text{ k}\Omega$$

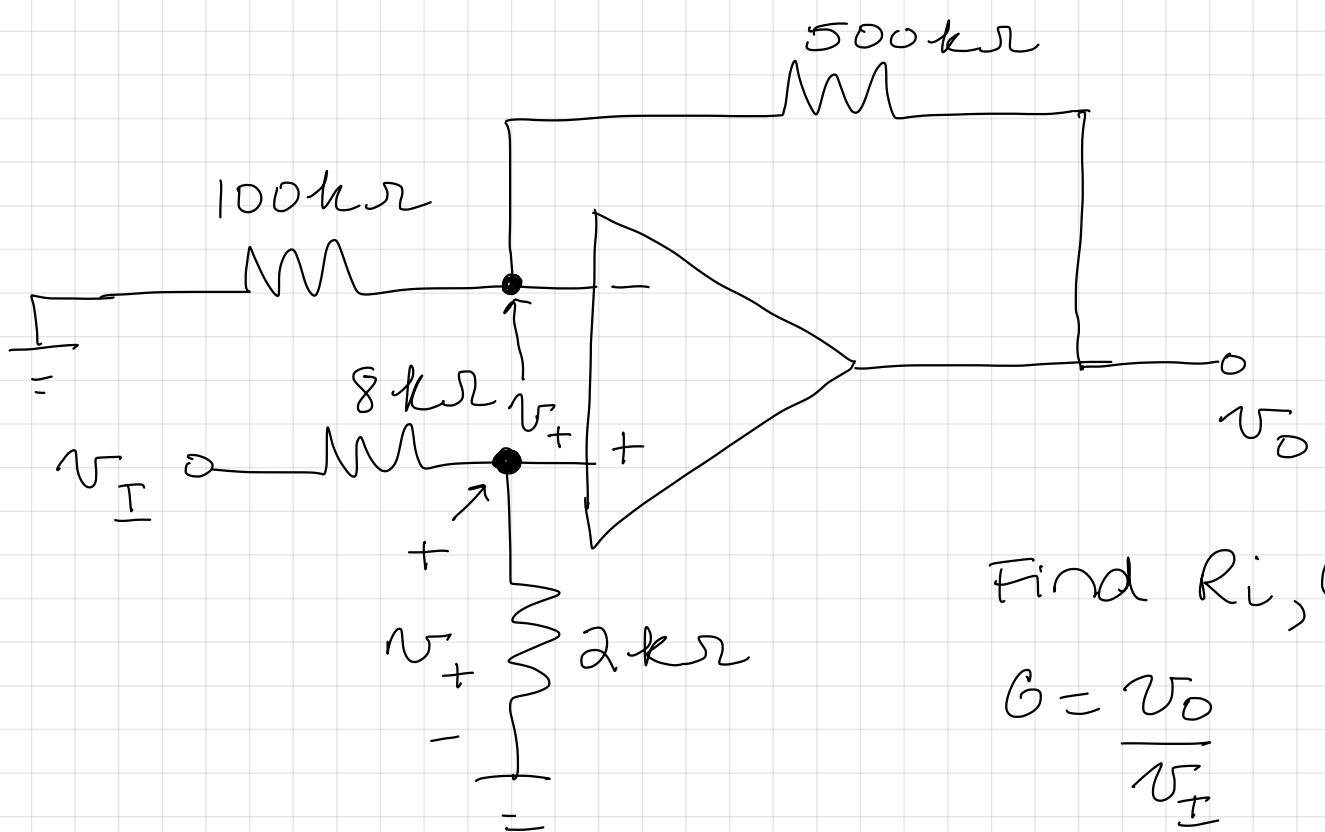

Find  $R_i, G$

$$G = \frac{v_O}{v_I}$$

$$R_i = \infty$$

$$v_+ = v_I \left( \frac{2k}{8k + 2k} \right)$$


$$\frac{v_O}{v_+} = \left( 1 + \frac{500k}{100k} \right)$$

$$\frac{v_O}{v_I} = \left( 1 + \frac{500k}{100k} \right) \left( \frac{2k}{8k + 2k} \right)$$

$$= (6)(0.2)$$

$$\frac{v_O}{v_I} = 1.2 \frac{V}{V}$$
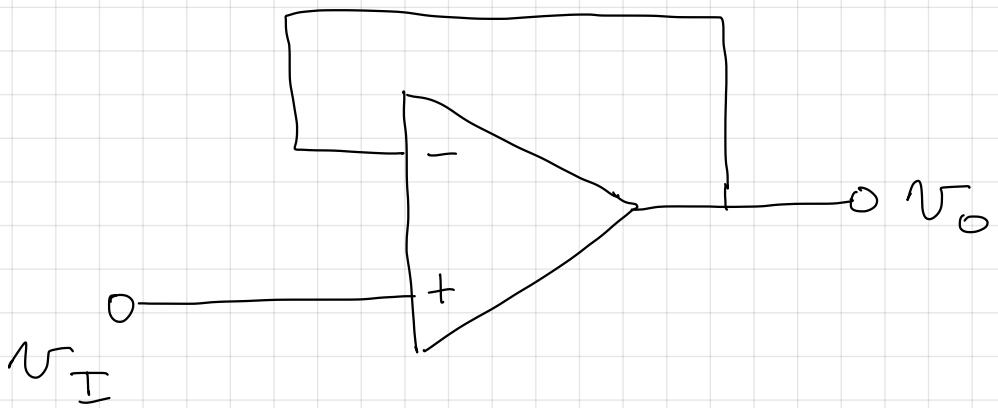
# Voltage Follower (version of non-inverting configuration)



$$R_1 = \infty$$

$$R_2 = 0$$


$$G = \frac{V_O}{V_I} = \left( 1 + \frac{R_2}{R_1} \right) = 1$$

$V_O = V_I \Rightarrow$  voltage follower


Ex

2V source that drives 1kΩ load.


The source resistance is 1MΩ

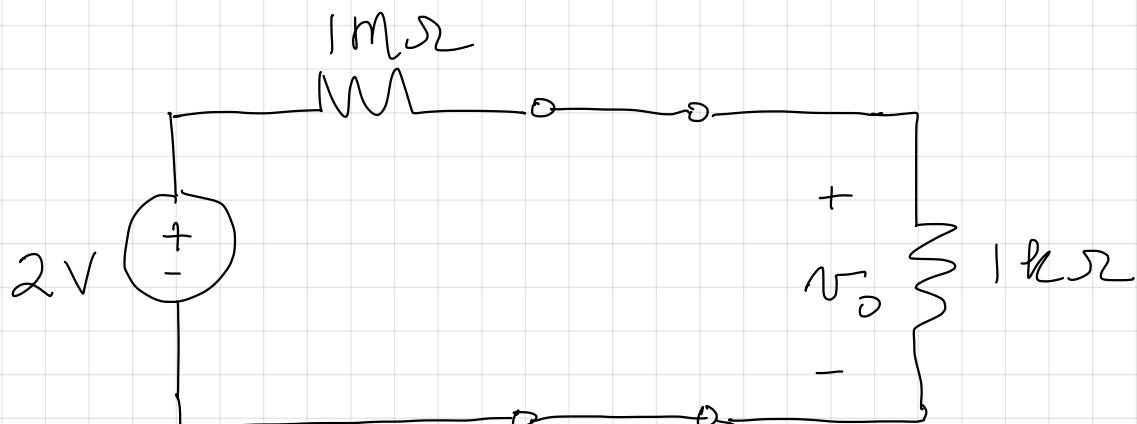

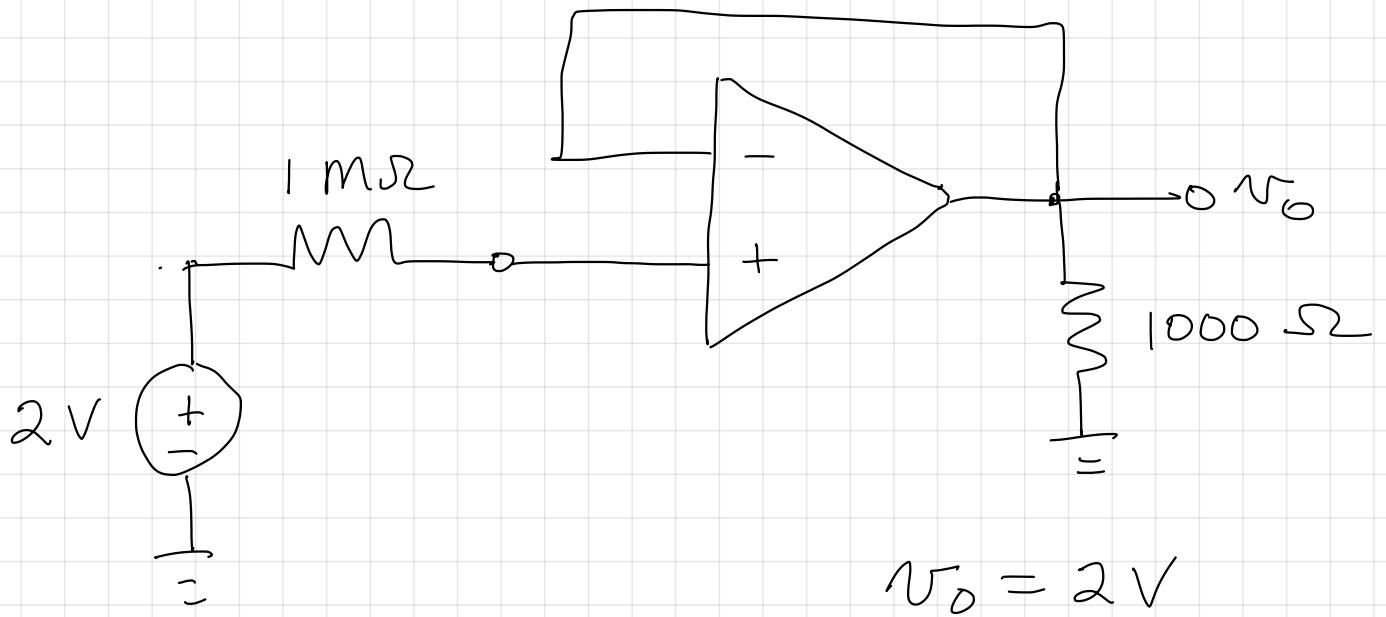
$$v_o = 2 \left( \frac{1000}{1000 + 1 \times 10^6} \right) = 0.2 \text{ mV}$$



$$v_o = 2V$$

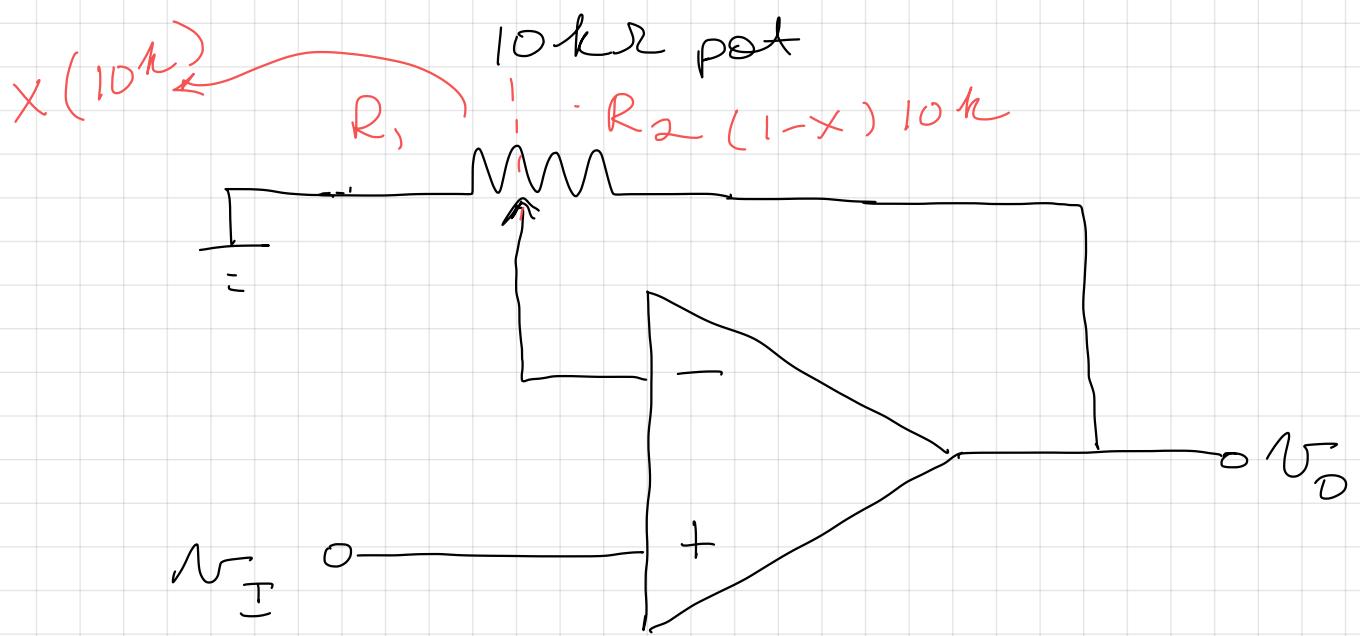

Find the range of gain

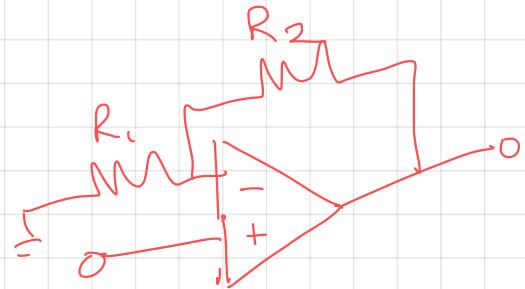

$$x = 0$$

$$R_1 = 0$$

$$R_2 = 10k\Omega$$

$$G = \left( 1 + \frac{R_2}{R_1} \right)^\infty$$

$$x = 1$$

$$R_2 = 0$$


$$R_1 = 10k\Omega$$

$$G = \left( 1 + \frac{R_2}{R_1} \right)^0$$

$$G = \infty$$

$$G = 1$$

# Difference Amplifiers

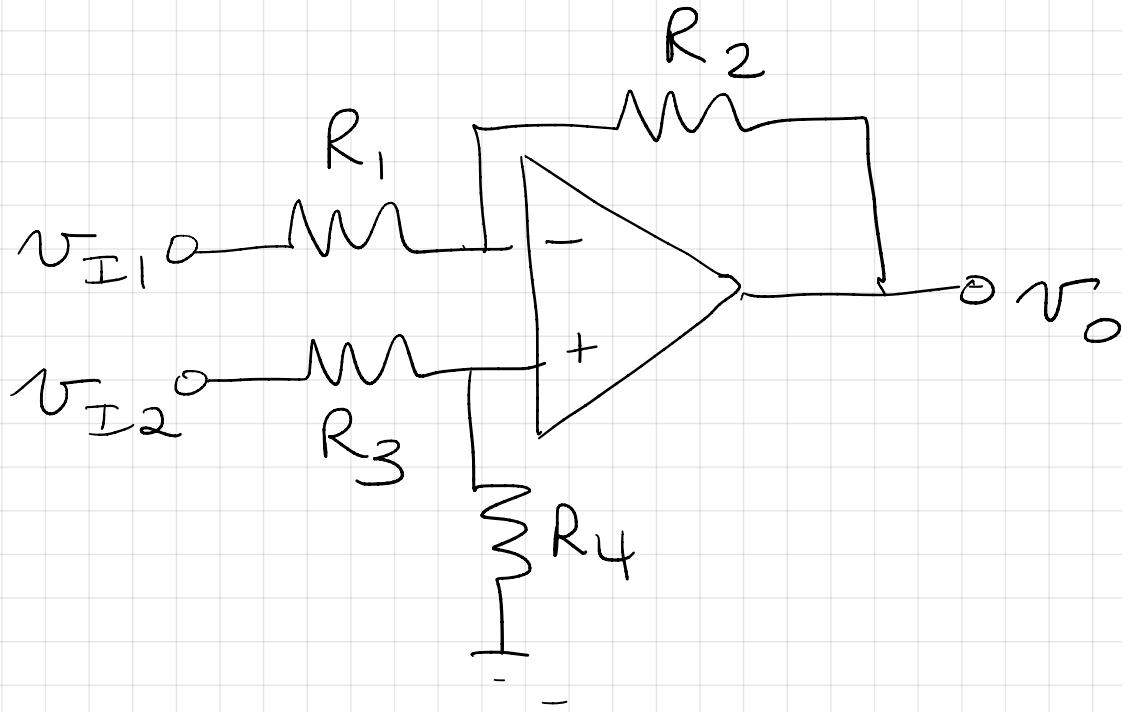

$$A_{cm} = -\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) \left( \frac{R_4}{R_3 + R_4} \right)$$

$$R_1 = R_3 = 2\text{k}\Omega$$

$$R_2 = R_4 = 200\text{k}\Omega$$

$A_{cm} = 0$   
 $\uparrow$   
 perfectly  
 match  
 resistors

$$A_d = \frac{R_2}{R_1} = \frac{200}{2} = 100 \frac{\text{V}}{\text{V}} \text{ or } 40 \text{dB}$$

$$R_{id} = 2R_1 = 4\text{k}\Omega \quad R_o = 0$$

$$CMRR \rightarrow \infty$$

$R_1 - R_4$  have 1% tolerance.

-

$$A_{cm} = -\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right)$$

$$= \left(\frac{R_4}{R_3 + R_4}\right) \left[ -\frac{R_2}{R_1} \left(\frac{R_3 + R_4}{R_4}\right) + \left(1 + \frac{R_2}{R_1}\right) \right]$$

$$= \left(\frac{R_4}{R_3 + R_4}\right) \left[ -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4}\right) + \left(1 + \frac{R_2}{R_1}\right) \right]$$

$$= \left(\frac{R_4}{R_3 + R_4}\right) \left[ \left(-\frac{R_2}{R_1} - \frac{R_3}{R_4} \frac{R_2}{R_1}\right) + \left(1 + \frac{R_2}{R_1}\right) \right]$$

$$= \left(\frac{R_4}{R_3 + R_4}\right) \left[ 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right]$$

$$= \frac{1}{\frac{R_3}{R_4} + 1} \left[ 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right]$$

$$\begin{aligned}
 &= \left( \frac{1}{\frac{R_3}{R_4} + 1} \right) \left( 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right) \left( \frac{\frac{R_4}{R_3}}{R_4/R_3} \right) \\
 &= \frac{\left[ \frac{R_4}{R_3} - \frac{R_2}{R_1} \right]}{1 + \frac{R_4}{R_3}}
 \end{aligned}$$

$$R_1 = R_3 = 2 \text{ k}\Omega$$

$$R_2 = R_4 = 200 \text{ k}\Omega$$

$$200 \text{ k}\Omega \pm 1\% (200 \text{ k}\Omega)$$

$$200 \text{ k}\Omega (1 \pm .01)$$

$$2 \text{ k}\Omega (1 \pm .01)$$

$$\frac{200(1-.01)}{2(1+.01)} \leq \frac{R_4}{R_3} \leq \frac{200(1+.01)}{2(1-.01)}$$

$$\frac{198}{2.02} \leq \frac{R_4}{R_3} \leq \frac{202}{1.98}$$

$$98.02 \leq \frac{R_4}{R_3} \leq 102.02$$

$$98.02 \leq \frac{R_2}{R_1} \leq 102.02$$

$$A_{cm} = \frac{\left[ \frac{R_4}{R_3} - \frac{R_2}{R_1} \right]}{1 + \frac{R_4}{R_3}}$$

← large      ← small

want to know the worst case

$A_{cm}$

$$\text{let } \frac{R_4}{R_3} = 98.02 \quad \frac{R_2}{R_1} = 102.02$$

$$A_{cm} = \frac{(98.02 - 102.02)}{1 + 98.02} = -0.04$$

$V/V$

$$|A_{cm}| = 0.04 \frac{V}{V}$$

$$A_d = \frac{R_2}{R_1} = \frac{102.02}{0.04} \frac{V}{V}$$



$$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right|$$

$$= 20 \log \left| \frac{102.02}{0.04} \right|$$

$$= 68.04 \text{ dB}$$

Using a pot to vary gain:

$xR$  |  $(1-x)R \Rightarrow$  shorted

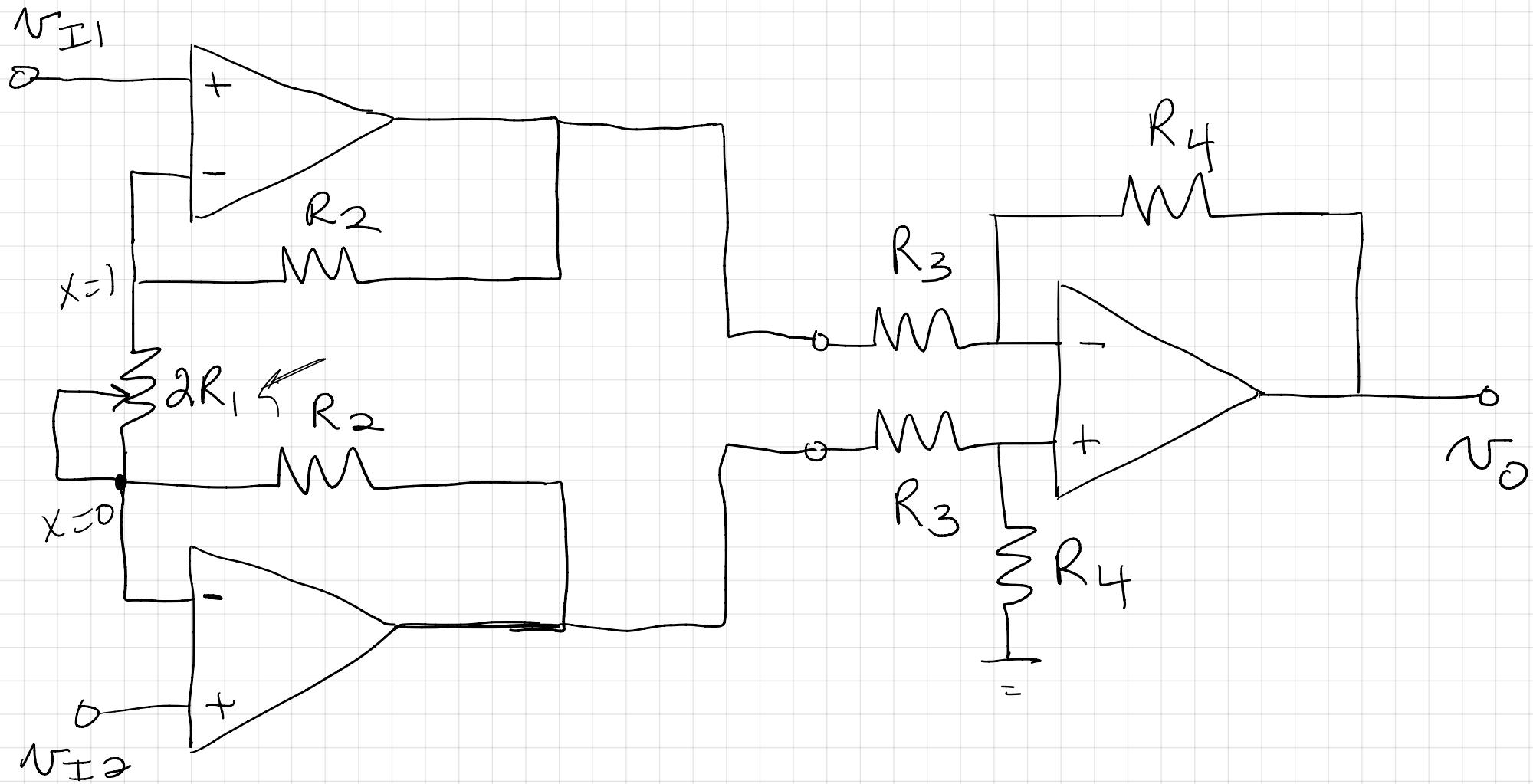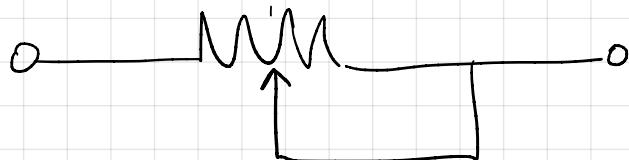

$$2R_1 = 100 \text{ k}\Omega \text{ pot.}$$

$$Ad = \left( 1 + \frac{2R_2}{2R_1} \right) \left( \frac{R_4}{R_3} \right)$$

$$x=0 \quad 2R_1 = 100 \text{ k}\Omega$$


$$Ad = \left( 1 + \frac{2R_2}{100\text{k}} \right) \left( \frac{R_4}{R_3} \right)$$

$$x=1 \quad 2R_1 = 0$$

$$Ad = \left( 1 + \frac{2R_2}{0} \right) \left( \frac{R_4}{R_3} \right)$$

$$x=0 \quad Ad = \text{minimum}$$

$$x=1 \quad Ad \rightarrow \infty$$

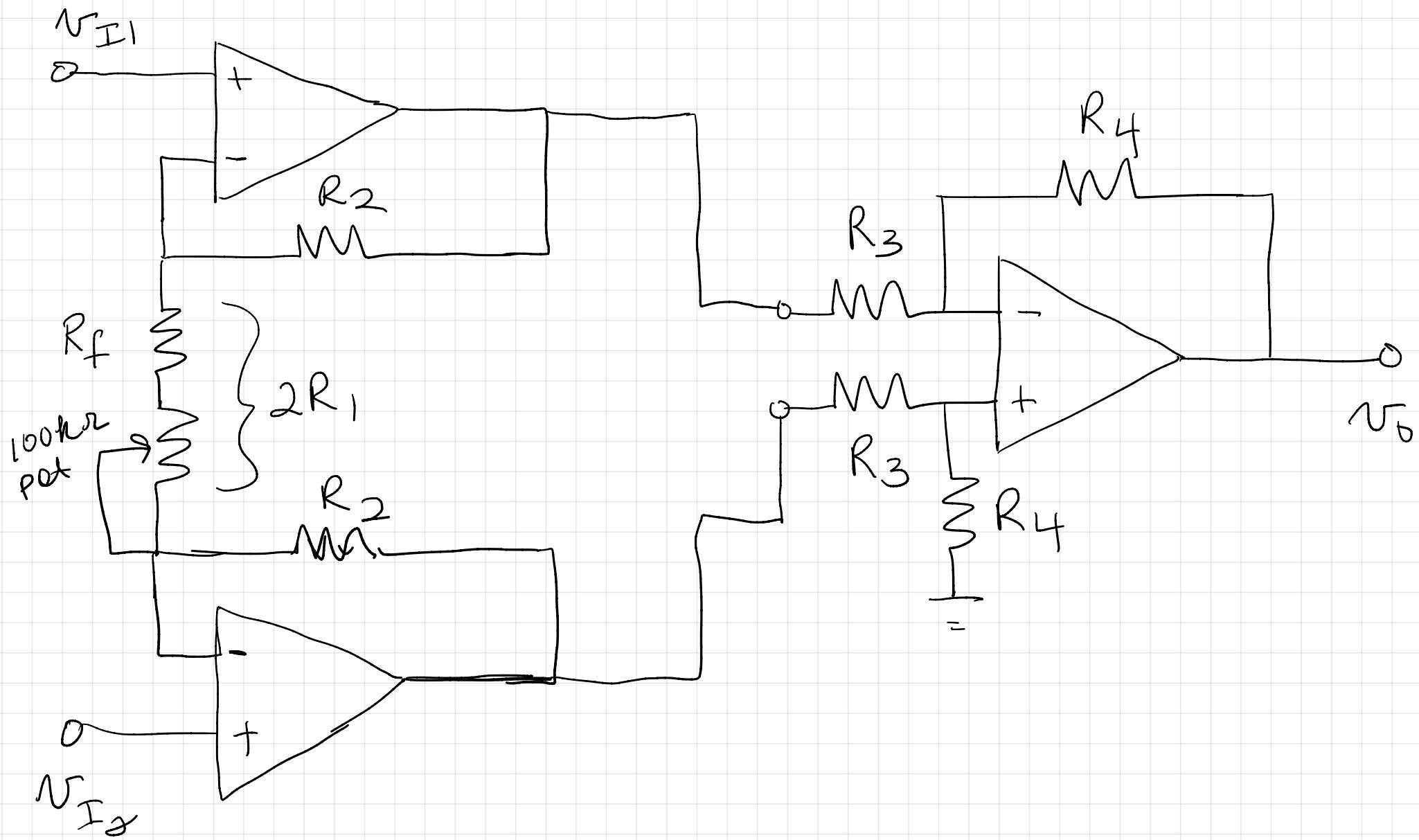

# Design instrumentation

amp

$$A_d \rightarrow \frac{2V}{V} \text{ to } 1000 \text{ V/V}$$

$$A_d = \left( 1 + \frac{2R_2}{2R_1} \right) \left( \frac{R_4}{R_3} \right)$$

$$2R_1 = R_f + 100k\Omega$$

$$x=0 \quad 2R_1 = R_f + 100k\Omega$$

$$\left( 1 + \frac{2R_2}{2R_1} \right) \left( \frac{R_4}{R_3} \right) = 2$$

$$\left( 1 + \frac{2R_2}{R_f + 100 \times 10^3} \right) \left( \frac{R_4}{R_3} \right) = 2$$

$$\text{let } R_4 = R_3 = 100k\Omega$$

$$\left( 1 + \frac{2R_2}{R_f + 100k} \right) = 2$$

$$x=1 \quad 2R_1 = R_f$$

$$\left(1 + \frac{2R_2}{2R_1}\right) \left(\frac{R_4}{R_3}\right) = 1000$$

$$\boxed{\left(1 + \frac{2R_2}{R_f}\right) = 1000}$$

$$\frac{2R_2}{R_f + 100k} = 1$$

$$\frac{2R_2}{R_f} = 999$$

$$\boxed{2R_2 = R_f + 100k}$$


$$\boxed{2R_2 = 999R_f}$$

$$R_f + 100k\Omega = 999R_f$$


$$998R_f = 100k\Omega$$

$$R_f = 100.2\Omega$$

$$R_2 = 50.05 \text{ k}\Omega$$

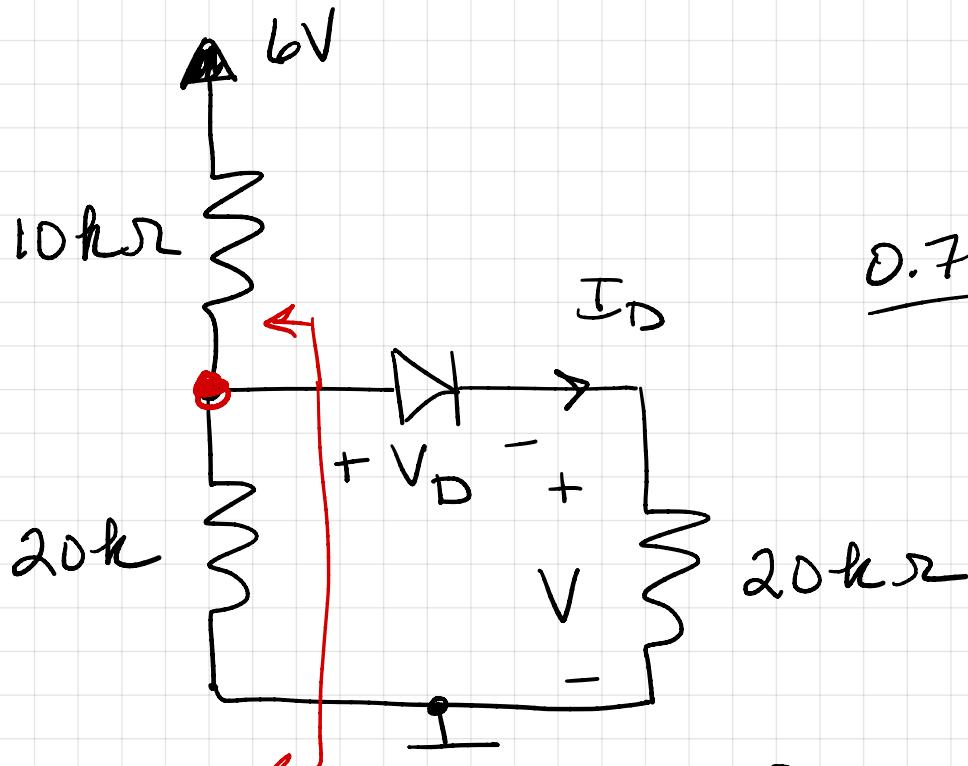

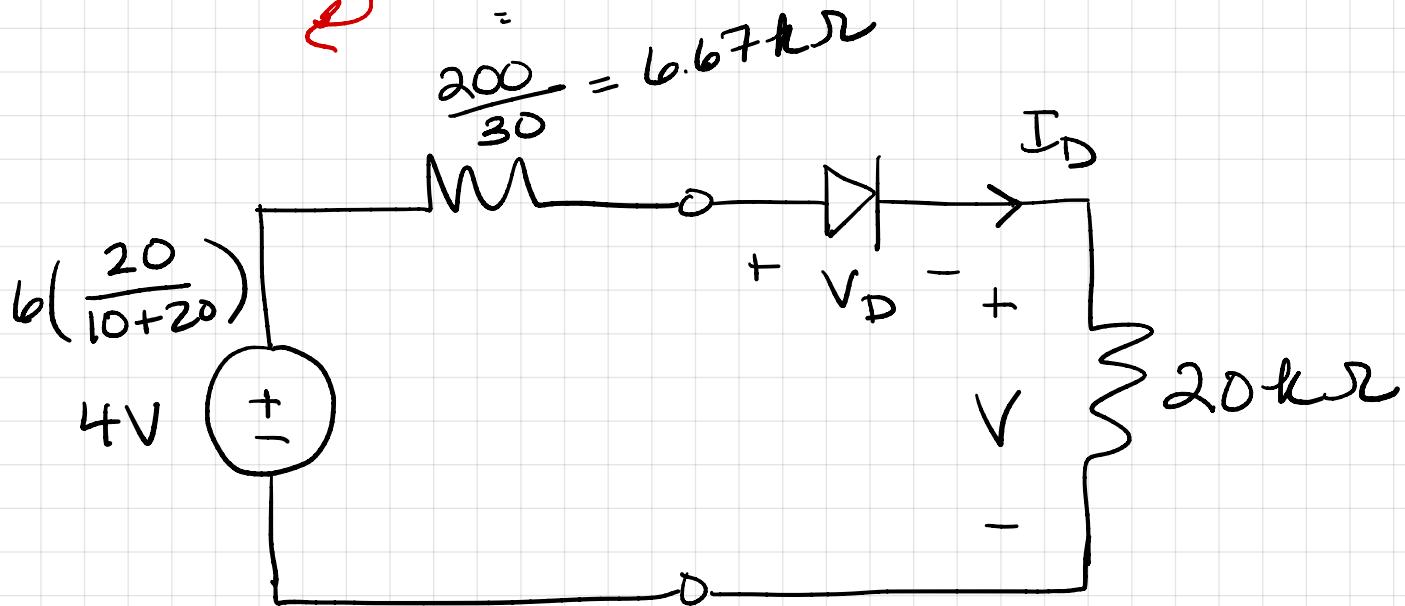Apply ideal  
constant drop  
 $0.7V$  ← exponential model



ideal  $V_D = 0$

$$V = 4 \left( \frac{20}{20 + 6.67} \right)$$

$$V = 3V$$

$$I_D = \frac{4}{26.67} = 0.15mA$$

constant drop

$$V_D = 0.7V$$

$$I_D = \frac{4 - 0.7}{26.67k\Omega}$$

$$I_D = 0.124mA$$

$$V = (I_D 20) = 2.48V$$

```
clc
```

```
Vdd=4;  
Rs=6.6667;  
Rl=20;
```

```
Vd=0.7;  
Id=1; %units of mA  
x=1;  
count=0;
```

```
while x > 0.000000001  
    Idtest=(Vdd-Vd) / (Rs+Rl);  
    Vdtest=Vd+0.025*log(Idtest/Id);  
    x=abs(Vd-Vdtest);  
    Vd=Vdtest;  
    Id=Idtest;  
    count=count+1;
```

```
end
```

```
Id  
Vd  
count  
Vl=Id*20
```


for exp  
mA, 0.7V

$$I_D = 0.1257 \text{ mA}$$

$$V_D = 0.6482 \text{ V}$$

$$V = 2.5139 \text{ V}$$

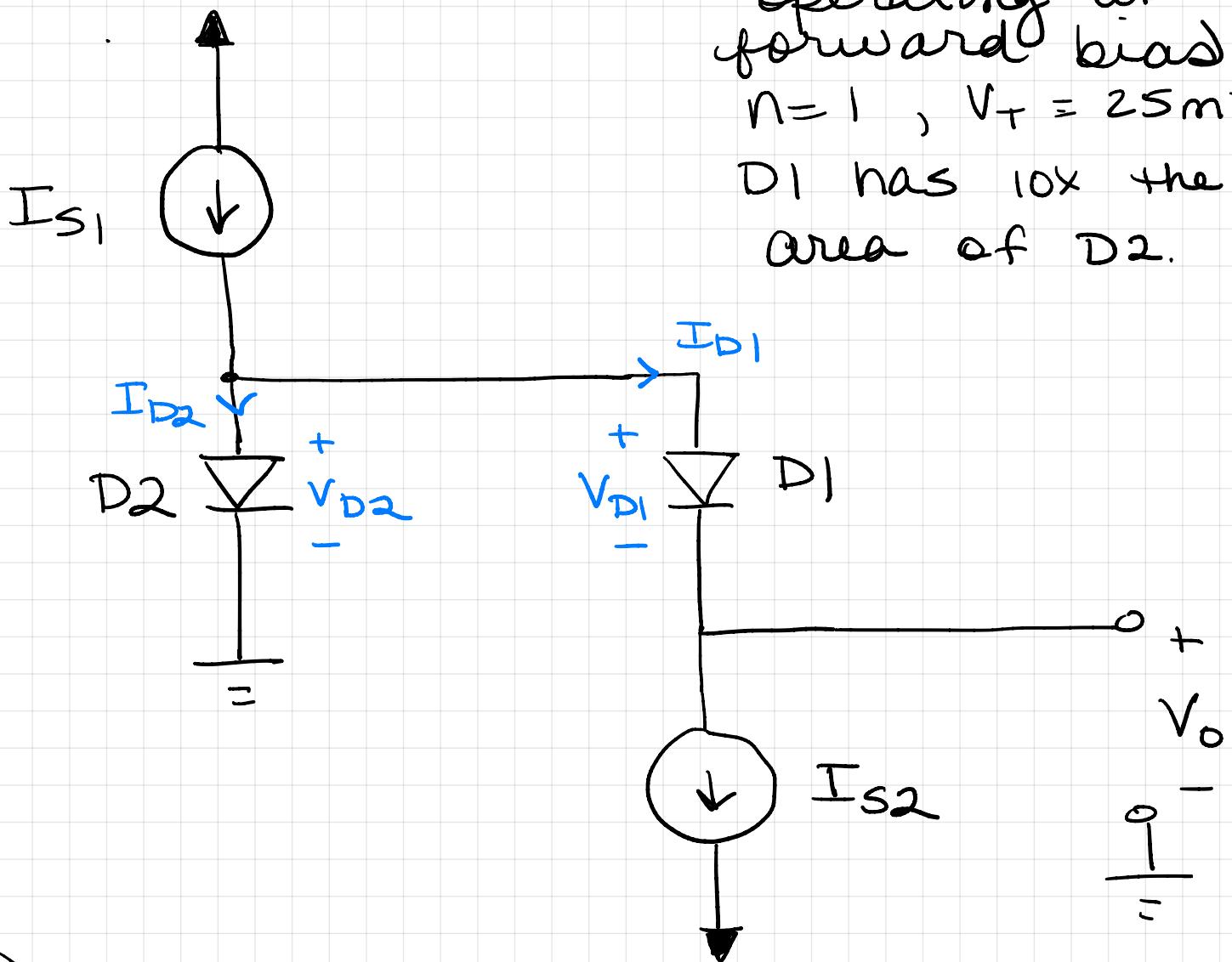D1 & D2 are operating in forward bias  
 $n = 1$ ,  $V_T = 25mV$   
D1 has 10x the area of D2.



a)  $I_{S1} = 10mA$   
 $I_{S2} = 2mA$   
What is  $V_0$ ?

$$I = I_S \exp\left(\frac{V}{V_T}\right)$$

$\uparrow$   
saturation or scale

$$I_{D1} = 2mA$$

$$\text{by KCL } I_{D2} = 10 - I_{D1}$$

$$I_{D2} = 8mA$$

$$D_2 \rightarrow I_S$$

$$D_1 \rightarrow 10I_S$$

$$\text{by KVL: } V_{D2} - V_{D1} - V_o = 0$$

$$V_o = V_{D2} - V_{D1}$$

$$I_{D2} = I_S \exp\left(\frac{V_{D2}}{V_T}\right)$$

$$I_{D1} = 10I_S \exp\left(\frac{V_{D1}}{V_T}\right)$$

$$\frac{I_{D1}}{I_{D2}} = \frac{10 I_S \exp(V_{D1}/V_T)}{I_S \exp(V_{D2}/V_T)}$$

$\xrightarrow{2mA}$   
 $\xrightarrow{8mA}$

$$\frac{2}{8} = 10 \exp\left(\frac{V_{D1} - V_{D2}}{V_T}\right)$$

$$\frac{2}{8} = 10 \exp(-V_o/V_T)$$

$$\exp\left(-\frac{V_o}{V_T}\right) = 0.025$$

$$V_D = - ( .025 ) \ln ( .025 )$$

$$V_D = 92.22 \text{ mV}$$

b)  $V_D = 50 \text{ mV}$ , what must  $I_{S2}$  be changed to?

$$I_{D2} = I_{S1} - I_{S2}$$

$$I_{D1} = I_{S2}$$

$$\frac{I_{D2}}{I_{D1}} = \frac{I_{S1} - I_{S2}}{I_{S2}} = \frac{I_S \exp(V_{D2}/V_T)}{10 I_S \exp(V_{D1}/V_T)}$$

$$\frac{10 - I_{S2}}{I_{S2}} = \frac{1}{10} \exp \left( \frac{V_{D2} - V_{D1}}{V_T} \right)$$

$$V_D = V_{D2} - V_{D1} = 50 \text{ mV}$$


$$\frac{10 - I_{S2}}{I_{S2}} = \frac{1}{10} \exp\left(\frac{50}{25}\right)$$

$$\frac{10 - I_{S2}}{I_{S2}} = 0.739$$



$$10 - I_{S2} = 0.739 I_{S2}$$

$$I_{S2} = 5.75 \text{ mA}$$

EX 1

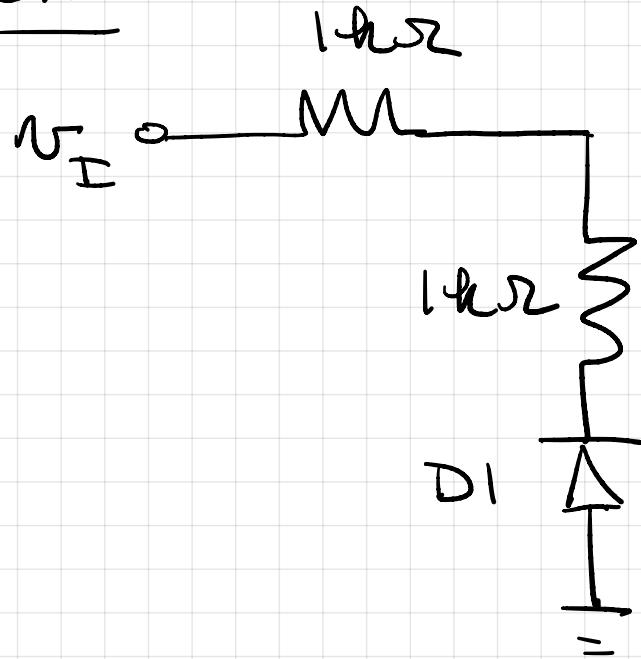


Find & plot  $V_O$

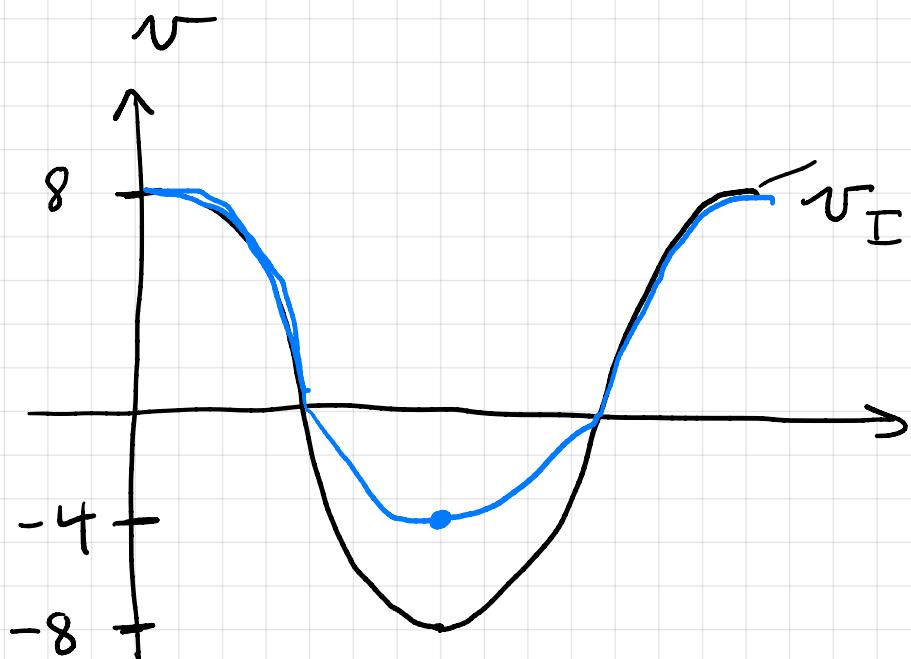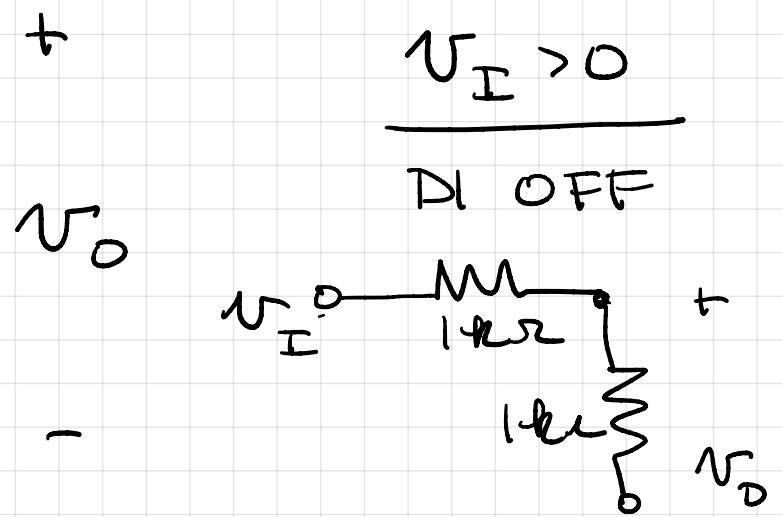

$$\frac{V_O}{V_I} = \frac{1}{1} = 1$$


$$V_O = V_I$$

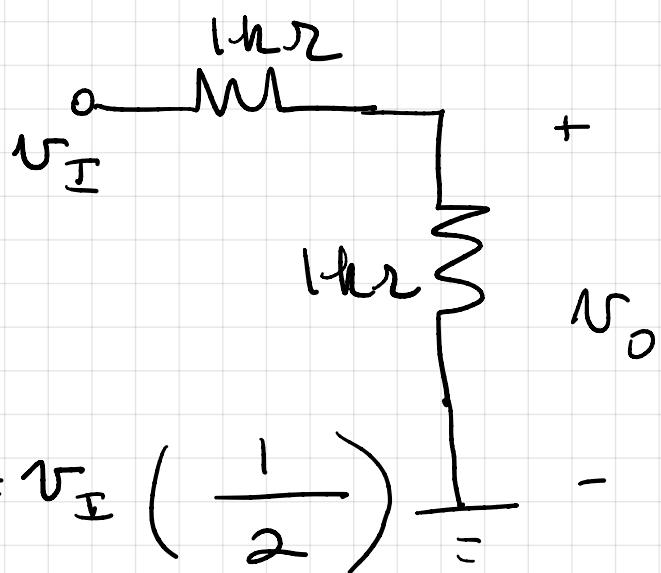

$$V_O = V_I \left( -\frac{1}{2} \right) \frac{1}{1} = -\frac{1}{2} V_I$$

$$V_O = \frac{1}{2} V_I$$

Ex 2

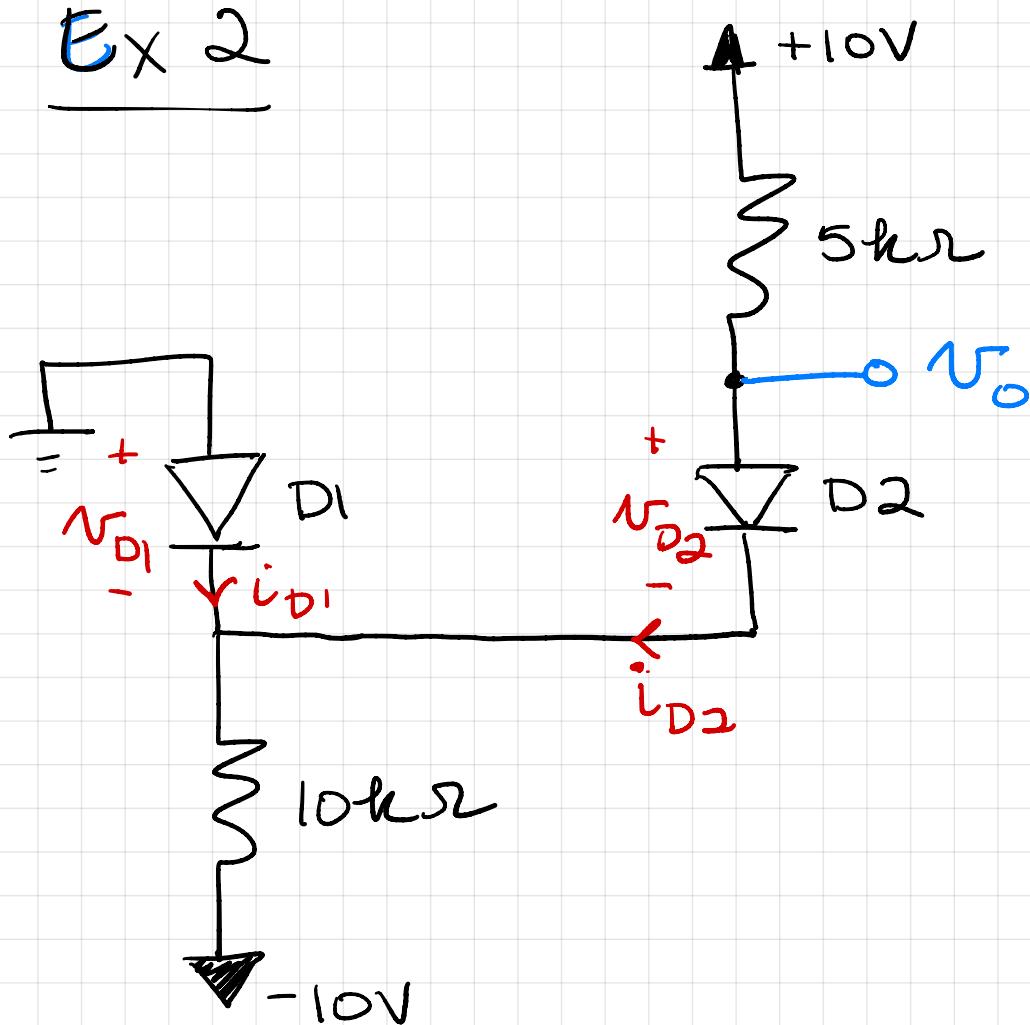


Start  $D_1$  &  $D_2$  ON

$$i_{D1} > 0, i_{D2} > 0$$



$$i_{D2} = \frac{10 - 0}{5k\Omega}$$

$$i_{D2} = 2mA$$

$$i_X = \frac{0 - (-10)}{10k}$$

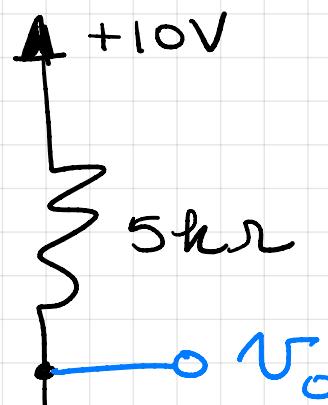

Solve  $U_O$ .

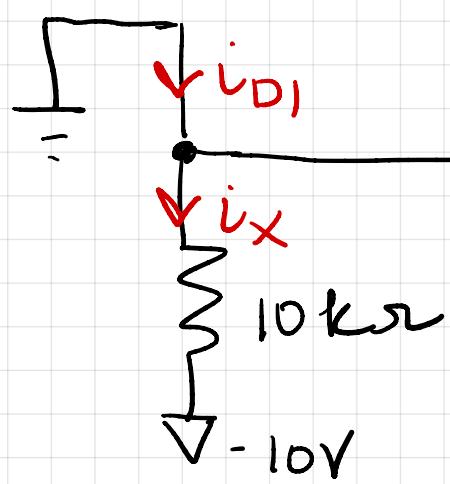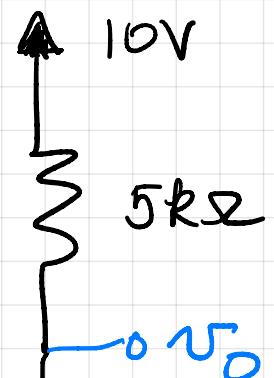

$$i_x = 1 \text{ mA}$$

by KCL

$$i_{D1} + i_{D2} = i_x$$

$$i_{D1} = i_x - i_{D2}$$


$$i_{D1} = -1 \text{ mA}$$

D1 & D2 are not both on.

D1 OFF & D2 ON

$$V_{D1} < 0$$

$$i_{D2} > 0$$

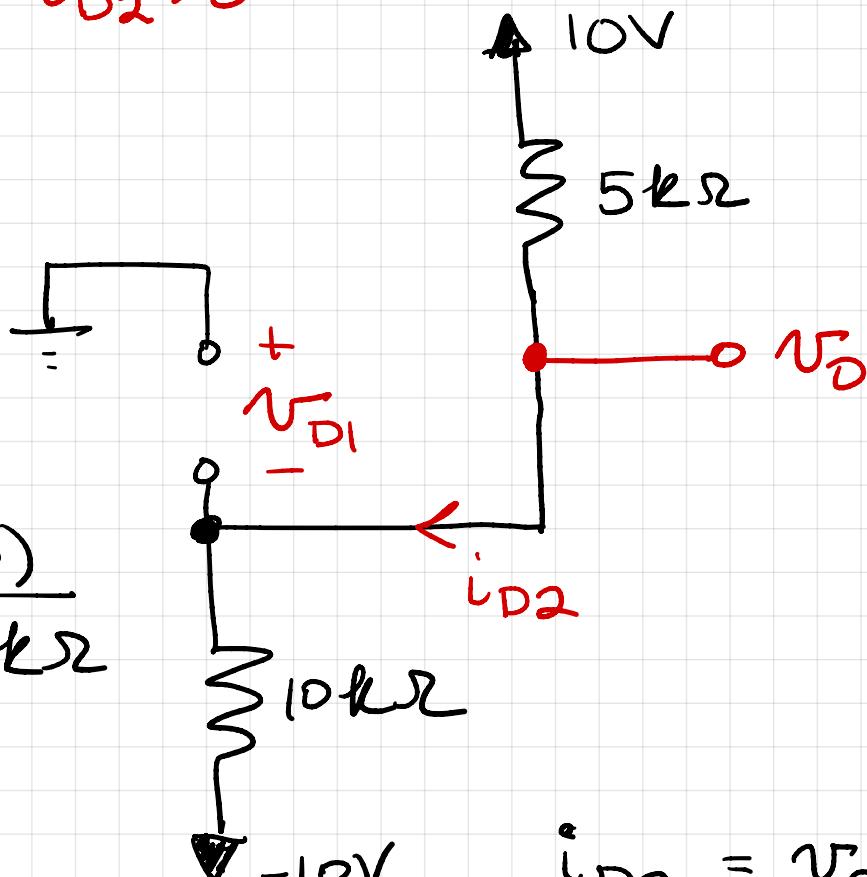

$$i_{D2} = \frac{10 - (-10)}{(5 + 10) \text{ k}\Omega}$$

$$= \frac{20}{15 \times 10^3}$$

$$i_{D2} = 1.33 \text{ mA}$$



$$i_{D2} = \frac{V_o - (-10)}{10 \times 10^3}$$


$$= 1.33 \text{ mA}$$

$$V_o = 3.33 \text{ V}$$

$$V_{D1} = 0 - V_0$$


$$V_{D1} = -3.33V$$

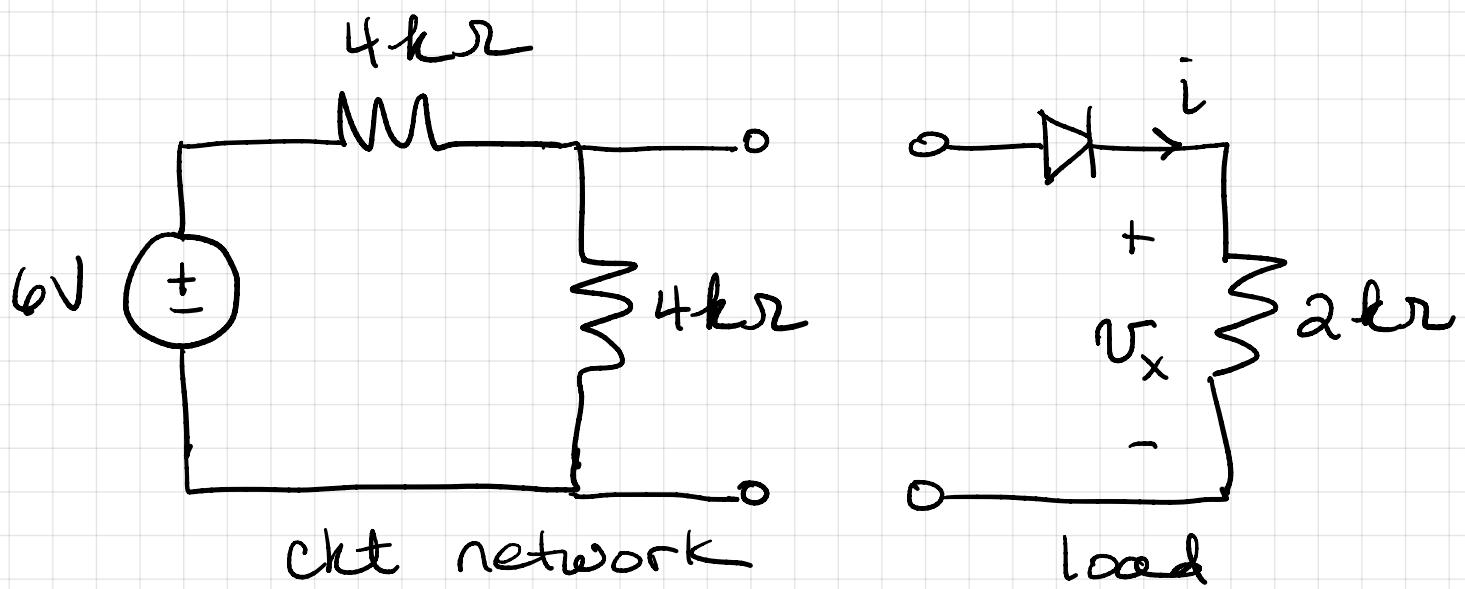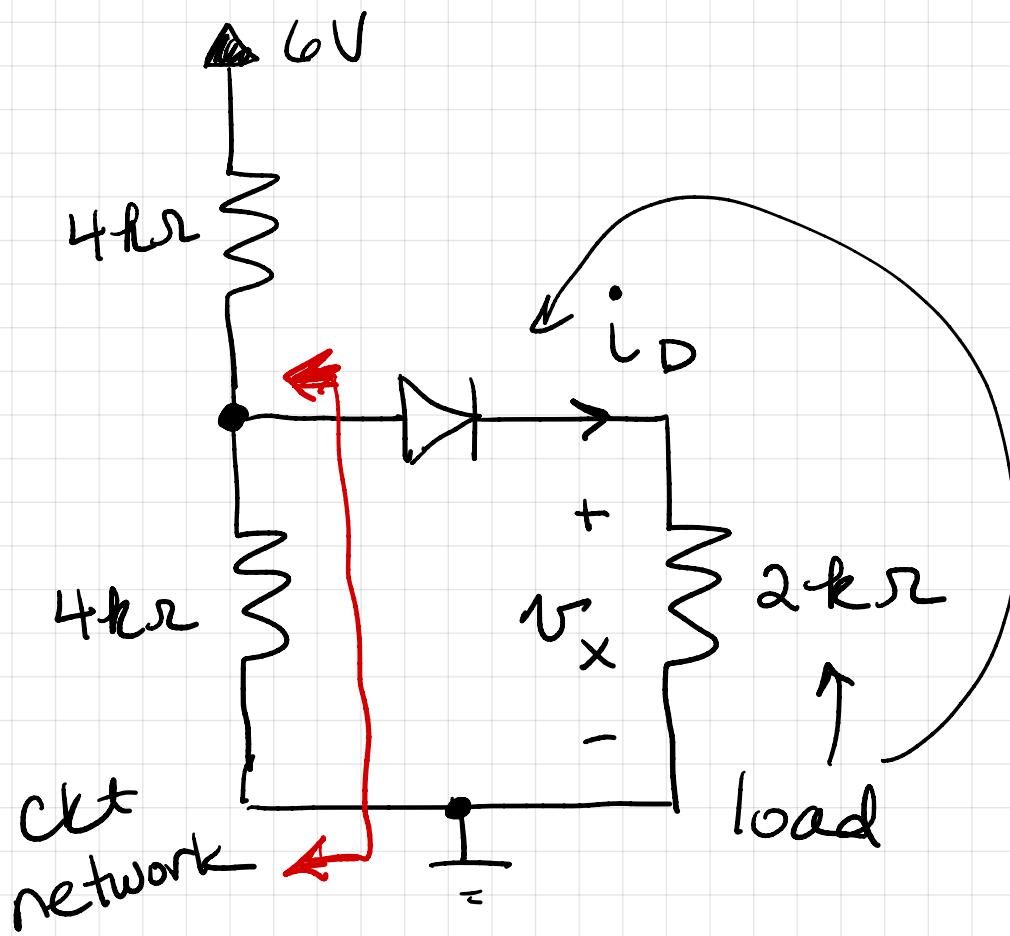

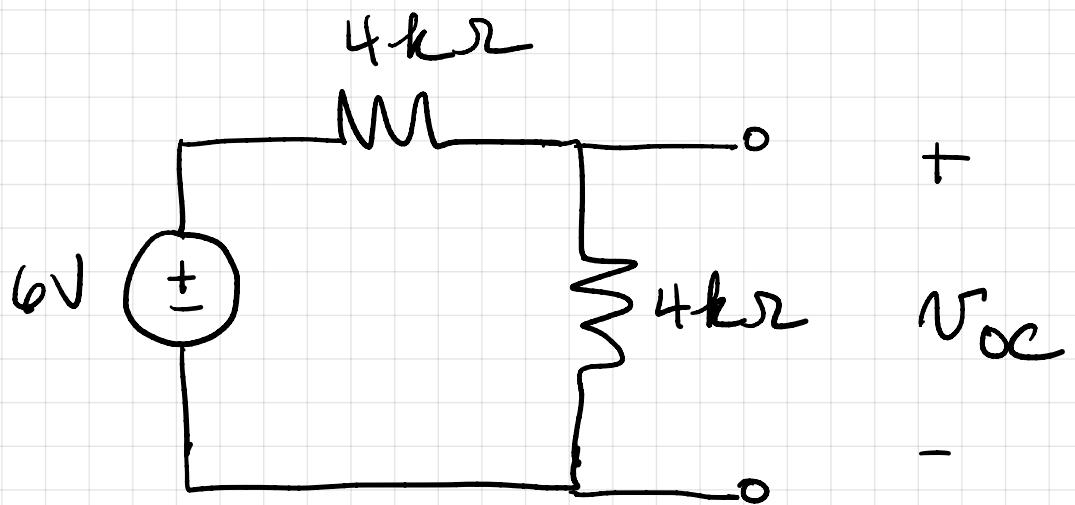


$$V_{oc} = 6 \left( \frac{4}{8} \right) = 3V$$

$$V_{Th} = 3V$$

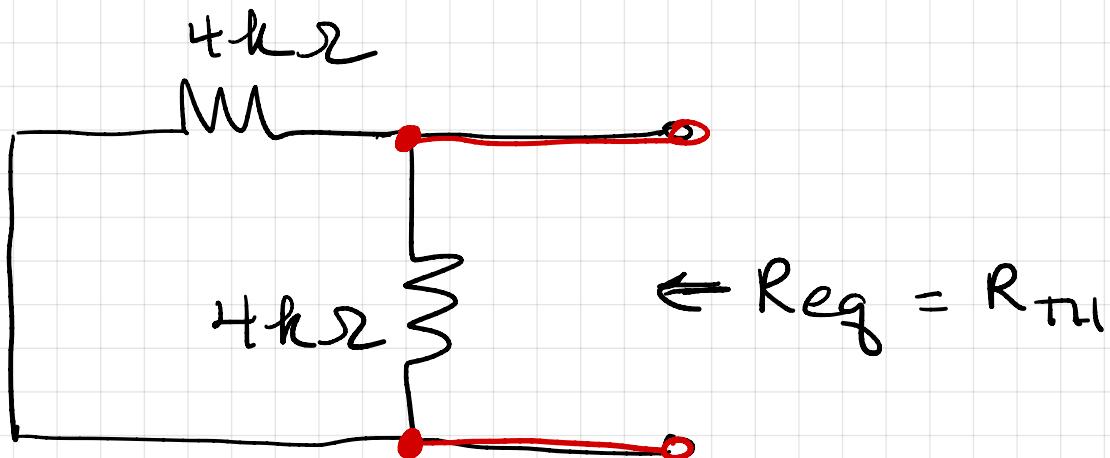
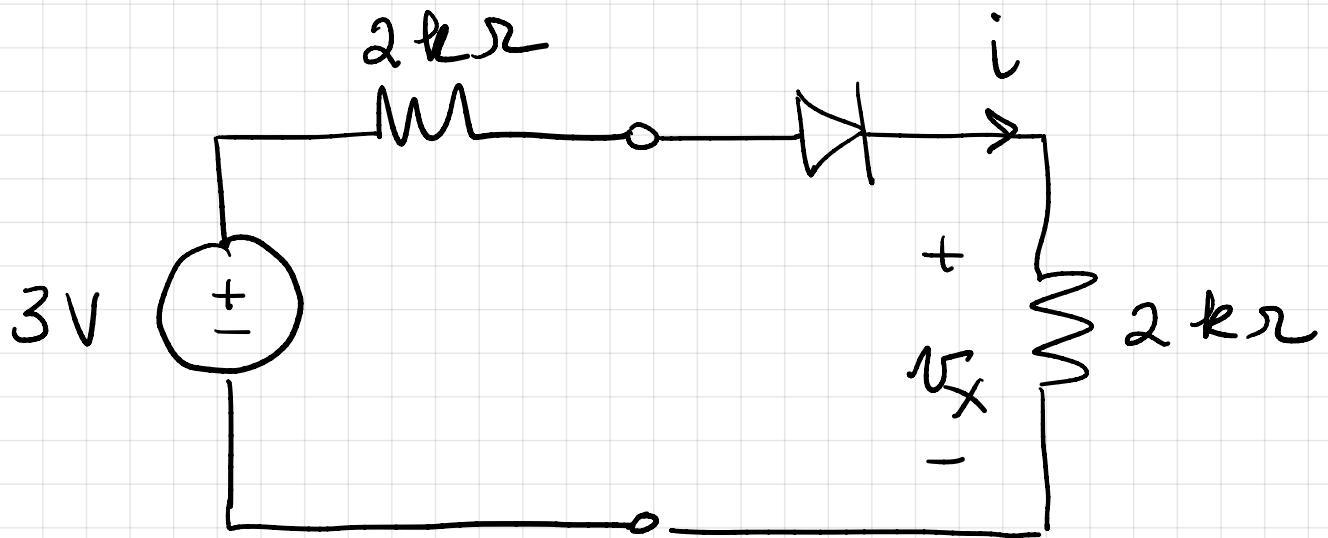
$$R_{th} = (4 \parallel 4) k\Omega = 2 k\Omega$$



Assume diode is on.

$$V_x = 3 \left( \frac{2 \times 10^3}{4 \times 10^3} \right)$$


$$V_x = 1.5 \text{ V}$$

$$i_x = \frac{V_x}{2 \times 10^3}$$

$$i_x = \frac{1.5}{2 \times 10^3}$$

$$i_x = 0.75 \text{ mA}$$

6.8 V Zener diode  
Voltage Regulator

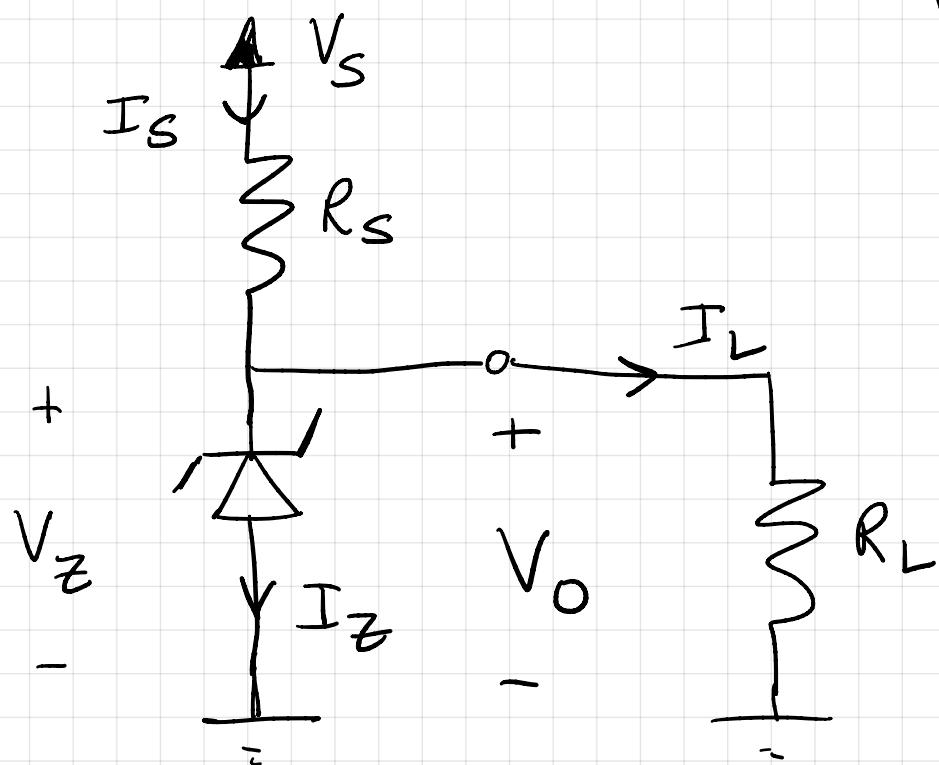

$$V_S = 10 \pm 1 \text{ V}$$


$$R_S = 500 \Omega$$

$$V_Z = 6.8 \text{ V}$$

$$I_Z = 5 \text{ mA}$$

$$r_Z = 20 \Omega$$

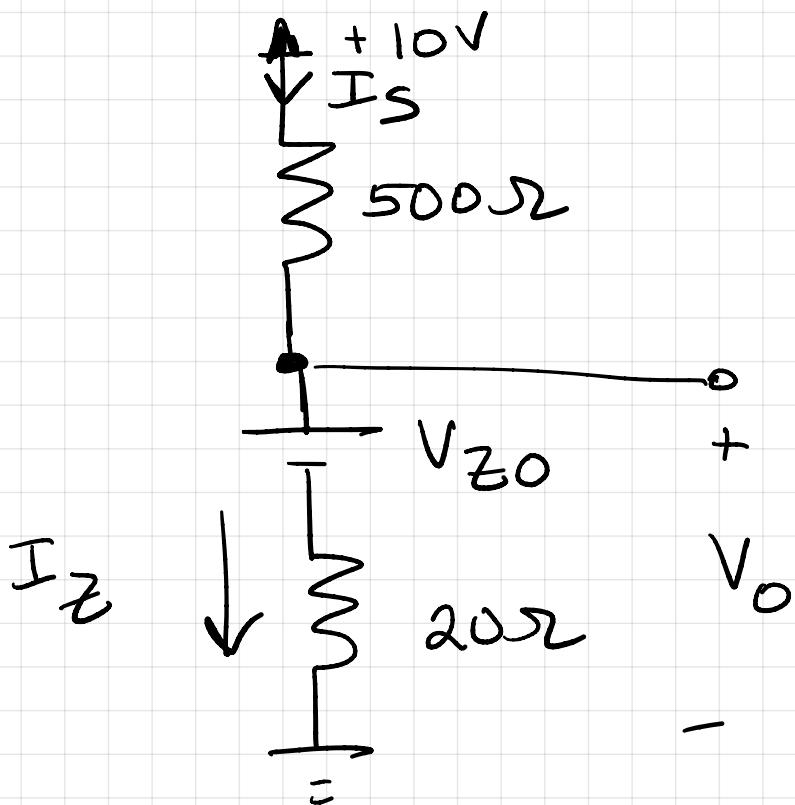- a) Find  $V_o$  assume no load  $R_L \rightarrow \infty$   
and  $V_S$  is nominal 10V



$$V_Z = 6.8 \text{ V}$$

$$I_Z = 5 \text{ mA}$$

$$V_{Z0} = V_Z - I_Z r_Z$$

$$= 6.8 - (5 \times 10^{-3})(20)$$

$$V_{Z0} = 6.7 \text{ V}$$

$$I_Z = \frac{10 - V_{Z0}}{500 + 20}$$

$$I_Z = \frac{10 - 6.7}{520} = 6.35 \text{ mA}$$

$$V_O = V_{Z0} + 20 I_Z \\ = 6.7 + 20(6.35 \times 10^{-3})$$

$V_O = 6.83 \text{ V}$

b)  $\Delta V_O$  w/ respect to  $V_S$

$\pm 1 \text{ V}$  change in  $V_S \Rightarrow \Delta V_O$

$$\frac{\Delta V_O}{\Delta V_S} = \text{line regulation} \frac{mV}{V}$$

$$I_Z = \frac{V_S - V_{Z0}}{R_S + r_Z}$$

$$V_O = V_{Z0} + I_Z r_Z$$

$$V_O = V_{Z0} + (V_S - V_{Z0}) \left( \frac{r_Z}{R + r_Z} \right)$$

$\Delta V_o$  as function of  $\Delta V_s$

$$\Delta V_o = \frac{r_z}{R+r_z} (\Delta V_s)$$

$$\frac{\Delta V_o}{\Delta V_s} = \frac{r_z}{R+r_z} = \frac{20}{520} = 38.5 \times 10^{-3}$$

$$= 38.5 \frac{mV}{V} \rightarrow \text{line regulation}$$

$$\Delta V_o = \left( 38.5 \frac{mV}{V} \right) (\pm 1)$$

$$\Delta V_o = \underline{38.5 mV} \rightarrow \text{output voltage change for a given } \pm 1V$$

c) Find  $\Delta V_o$  if we connect a load resistor that draws 1mA away from the zener diode

$$I_L = 1mA$$

$$\frac{\Delta V_o}{\Delta I_L} = \text{load regulation}$$

$$\frac{\Delta V_o}{\Delta I_L} \Rightarrow \frac{mV}{mA}$$

$$V_o = V_{Z0} + I_Z r_Z$$

$$\Delta V_o = \Delta I_Z (r_Z)$$

$$\boxed{\frac{\Delta V_o}{\Delta I_Z} = r_Z = 20 \frac{mV}{mA}}$$

$$\Delta I_Z = -1mA$$

$$\frac{\Delta V_o}{\Delta I_L} = -20 \frac{mV}{mA}$$

$$I_L = 1mA$$

$$\Delta V_o = -20mV$$

$$d) \Delta V_o \text{ for } R_L = 2k\Omega$$

$$I_L \approx \frac{6.8}{2000} = 3.4mA$$


$$\Delta V_o = r_Z \Delta I_Z = -(20)(3.4 \times 10^{-3})$$

$$\Delta V_0 = -68 \text{ mV}$$

e)  $R_L = 500 \Omega$

$$I_L \approx \frac{6.8}{500} = 13.6 \text{ mA}$$


Zener diode is no longer in breakdown

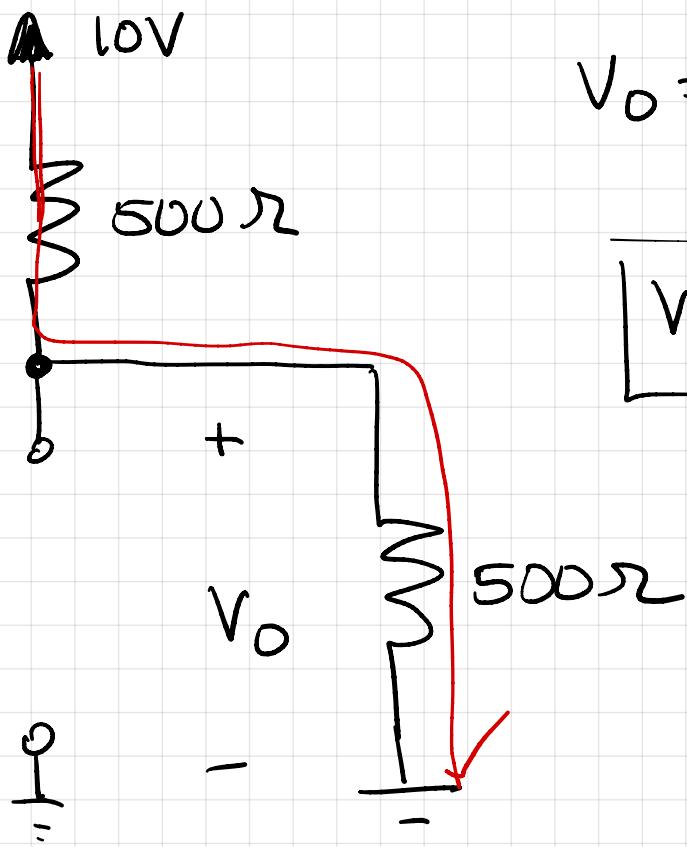

$$V_0 = 10 \left( \frac{500}{1000} \right)$$

$$V_0 = 5 \text{ V}$$

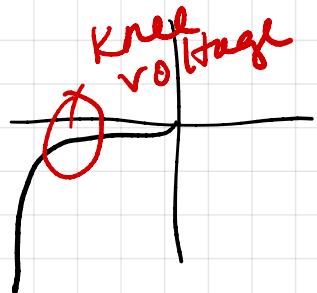f) What is the minimum  $R_L$  value such that we are on the edge of breakdown.




$$I_{ZK} = 0.2 \text{ mA}$$

$$I_Z \approx I_{ZK} = 0.2 \text{ mA}$$

$$V_Z \approx V_{Z0} = 6.7 \text{ V}$$
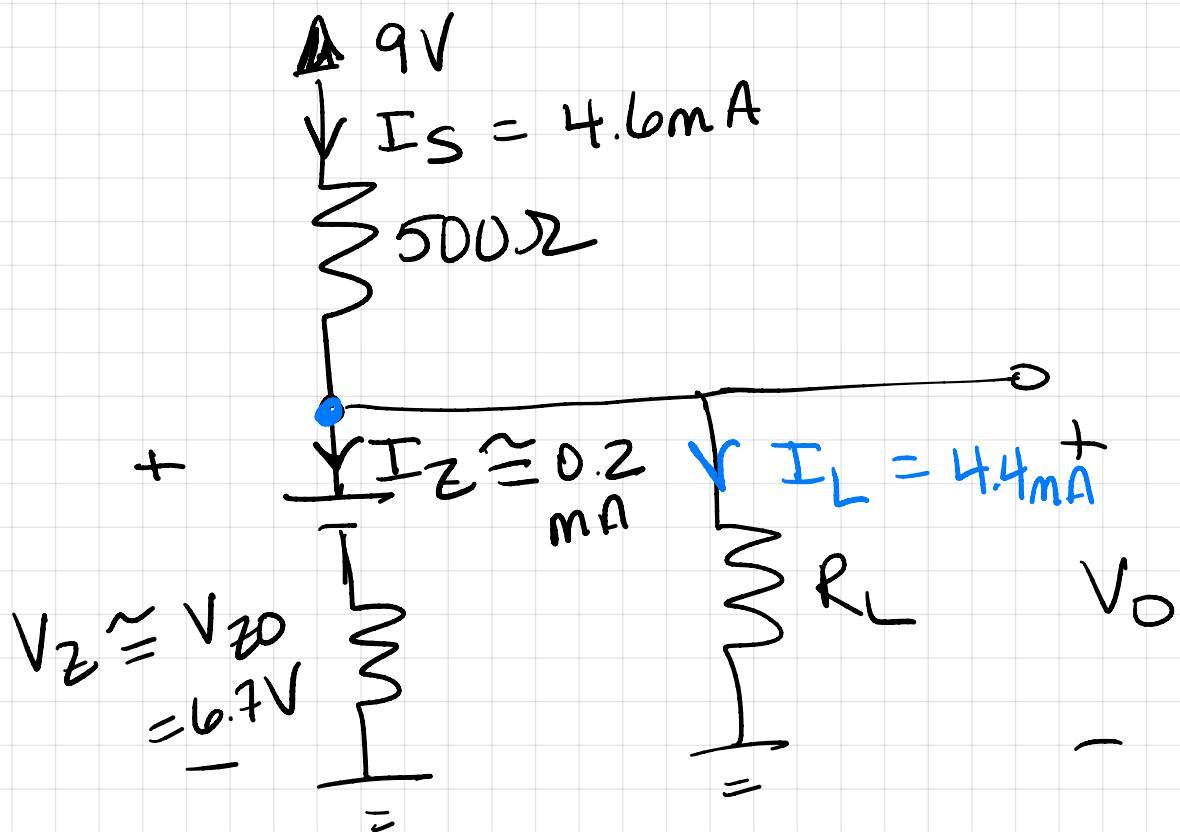
$$I_S = \frac{9 - 6.7}{500} = 4.6 \text{ mA}$$



$$R_L = \frac{V_Z}{I_L} = \frac{6.7}{4.4 \times 10^{-3}}$$

$$R_L \approx 1.5 \text{ k}\Omega$$