
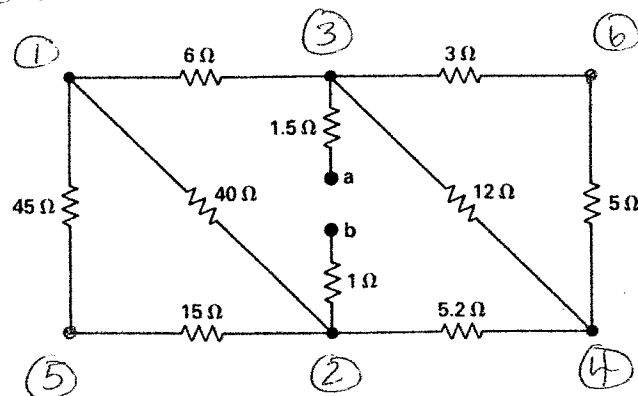


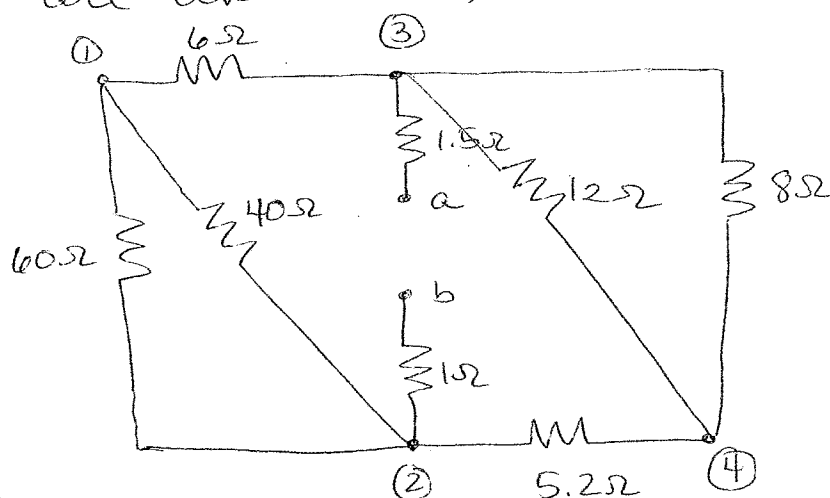Find the equivalent resistance, R_{ab}
at nodes a & b.




3 & 5 are in series, lose ⑥ $R_{eq} = 8\Omega$

45 & 15 are in series, lose ⑤ $R_{eq} = 60\Omega$



$\sqrt{24}$
 $60 \parallel 40$ at ① & ②


$8 \parallel 12$ at ③ & ④
 (4.8Ω)

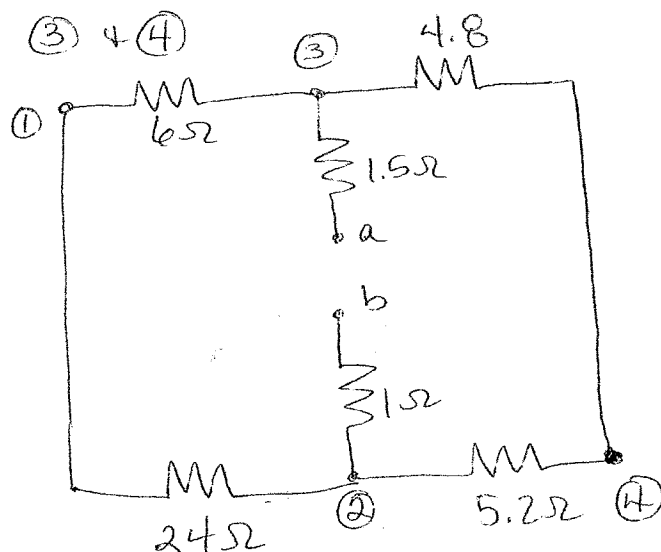


4.8 & 5.2 in series = 10Ω (lose ④)

EE213 pg 2


6 & 24 in series = 30Ω (lose ①)

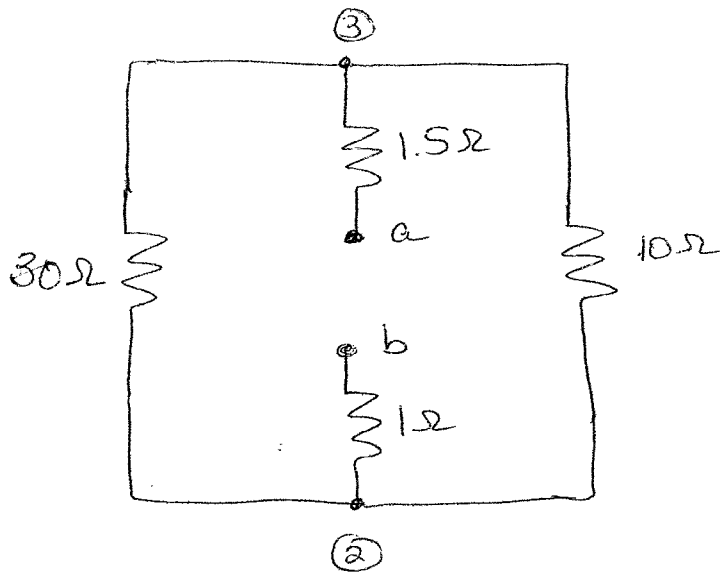

$30 \parallel 10$ @ ③ & ②

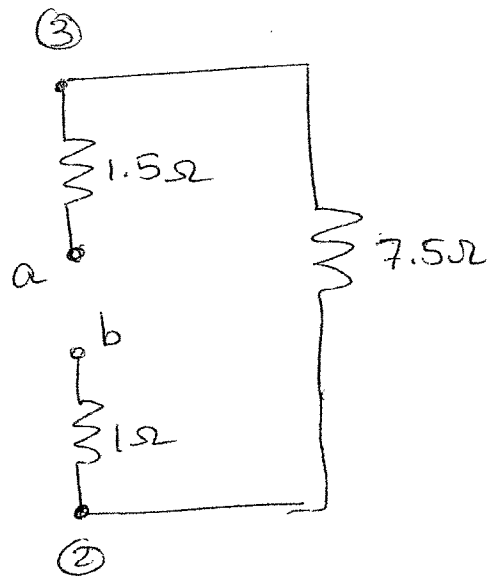


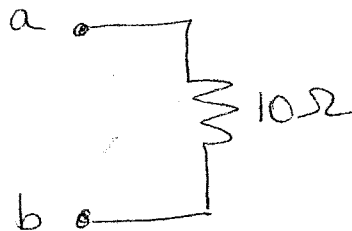7.5, 1.5, & 1 in
series = 10Ω
(lose ③ & ②)




Extra Problem

Simplification & Expansion

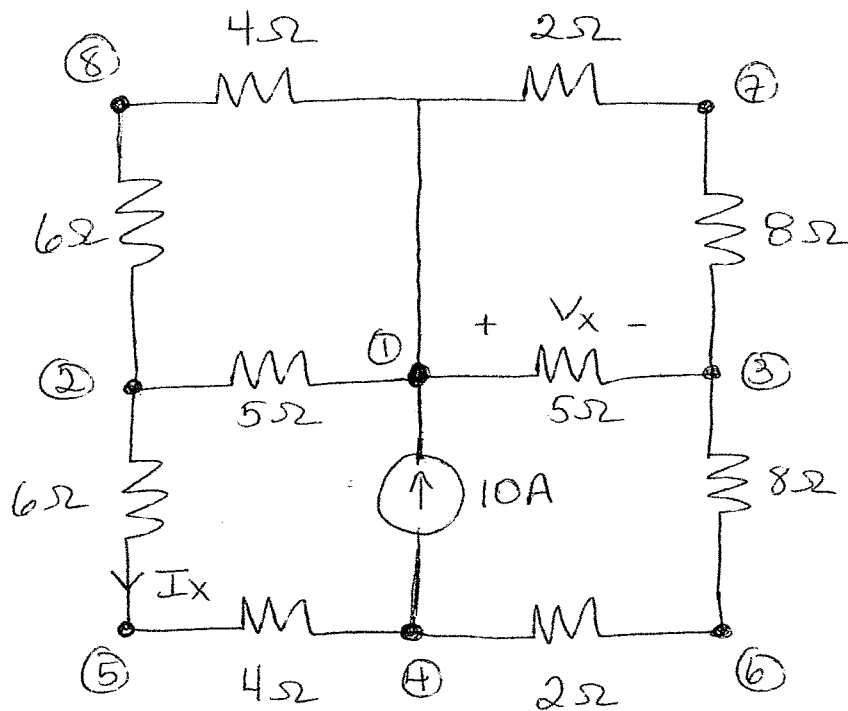Find V_x & I_x (note how much
is connected
@ ①)

Step 1 4Ω & 6Ω ^{10Ω} on the top & bottom
are in series (lose ⑧ & ④)

2Ω & 8Ω on the top & bottom
are in series (lose ⑤ & ⑥)
 _{10Ω}

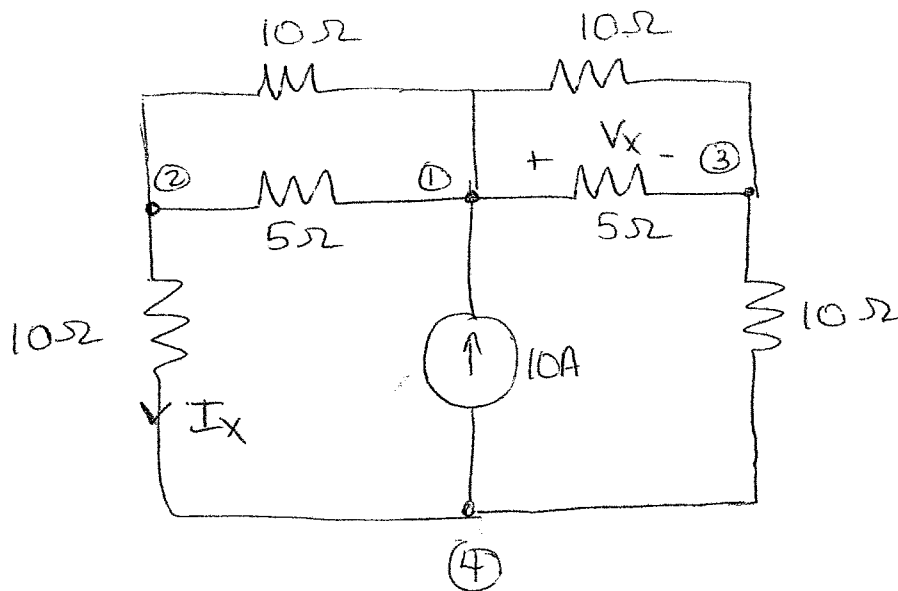 I_x still on
ckt V_x still on
ckt.

Simp. & Expansion example - cont

Step 2


on both right & left

$$5 \parallel 10 = 3.33 \Omega$$

① & ②

and


① & ③

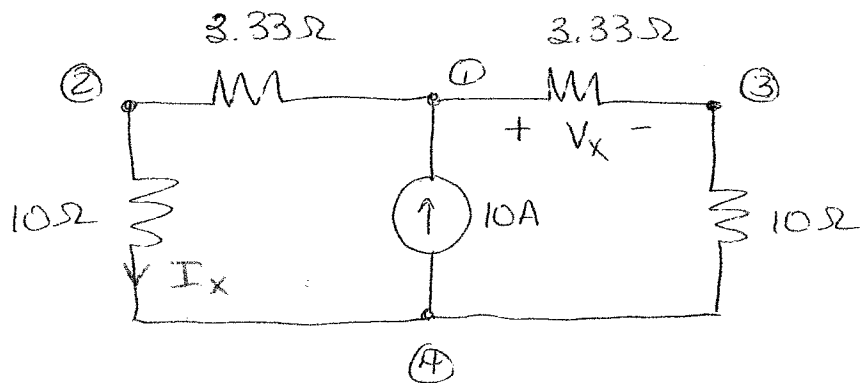

I_x still on
ckt
 V_x still on
ckt.

Step 3

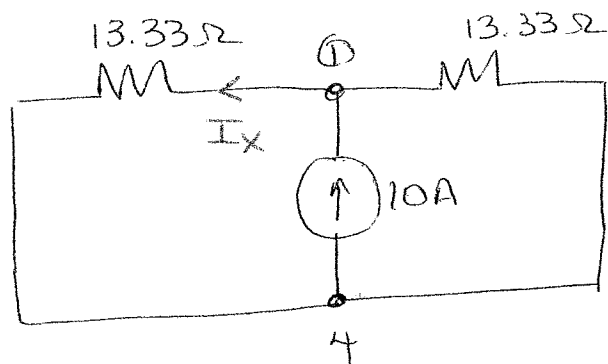
on each side 3.33 & 10 are in series
lose ② & ③



I_x still on ckt.
 V_x not on
ckt

Step 4

$13.33 \parallel 13.33$ at ① & ④

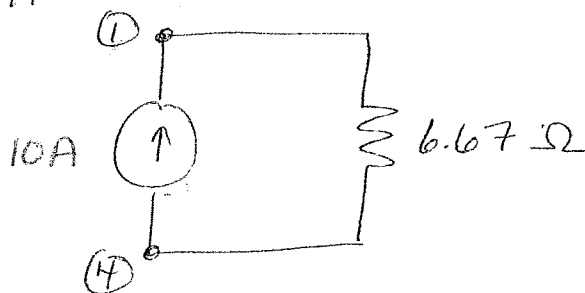


I_x not
on the
ckt.

Simplification & Expansion

EE 213 ~~Q2~~


Step 5

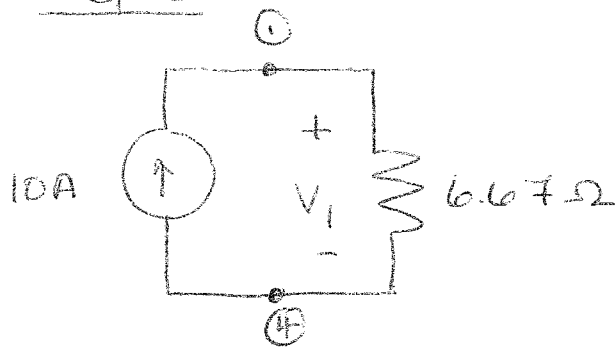

$$V_1 = 10(6.67)$$

$$V_1 = 66.67V$$

Step 6 (using ckt from ^{step} 3)

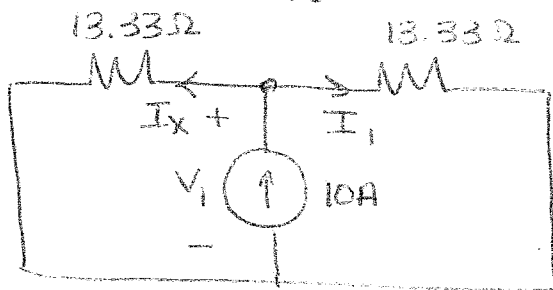


V_1 is the voltage from ① to ④


$$\text{So } I_x = \frac{V_1}{13.33} = 5A$$

$$\text{and } I_1 = \frac{V_1}{13.33} = 5A$$

Step 7 (using ckt from step 2)

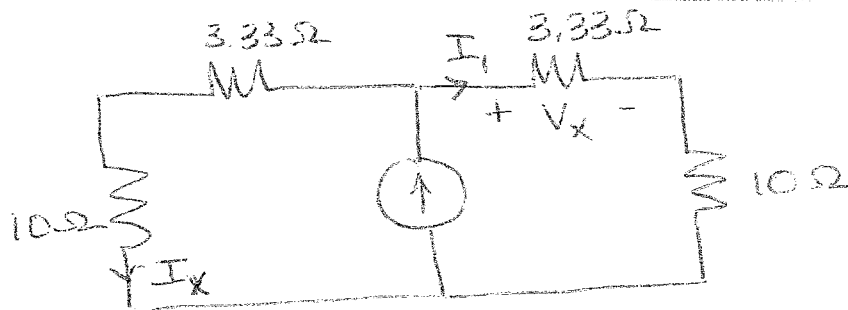


$$V_x = I_1(3.33) = 16.65V$$

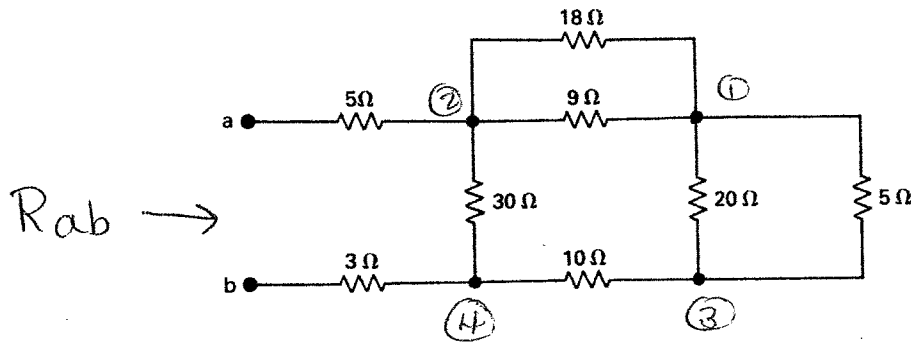Find equivalent resistor, R_{ab} 


at ① & ② $18 \parallel 9 = 6\Omega$

at ① & ③ $20 \parallel 5 = 4\Omega$

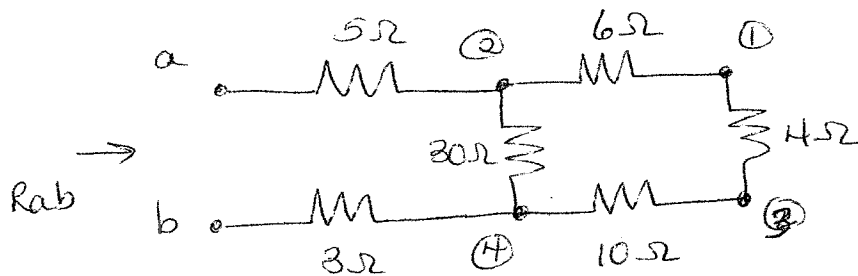


$6\Omega, 4\Omega, \text{ and } 10\Omega$ are now in series

$6 + 4 + 10 = 20\Omega$
(lose ① & ③)

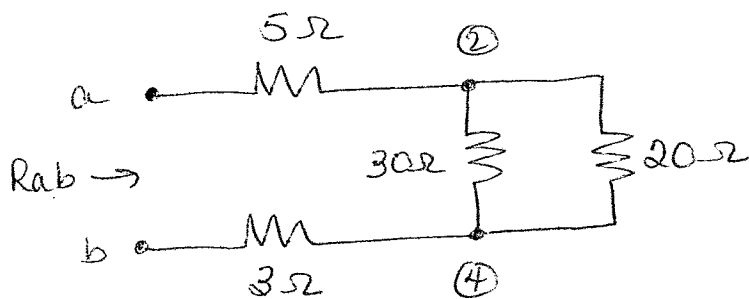


$20 \parallel 30$ @ ② & ④

$20 \parallel 30 = 12\Omega$

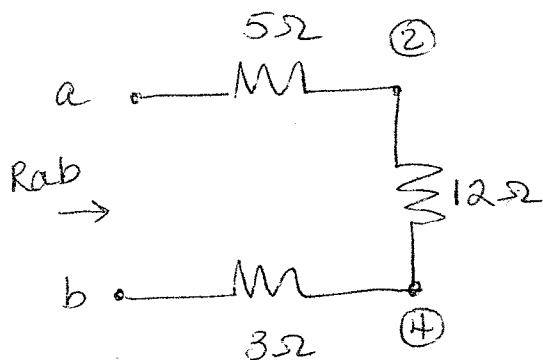

$5, 12 \text{ and } 3$ are in series
(lose ② & ④)

$5 + 12 + 3 = 20\Omega$

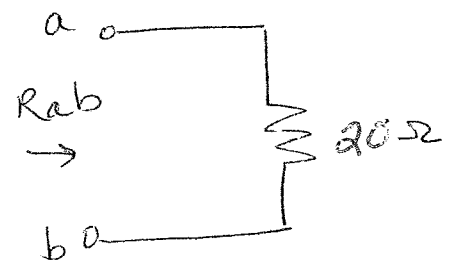

Find equivalent resistor, R_{ab}

$$R_{ab} = 15\Omega$$

$R_{ab} \rightarrow$

