

# CPE 322

## Digital Hardware Design Fundamentals

---

Electrical and Computer Engineering  
UAH

Extended State Graph Finite State Machine  
Representations




# Extended State Graph

---

- Similarities to basic State (Transition) Graph
  - Nodes represent states
  - Arcs (or edges) represent transition between states
  - Labelling on arcs represent Inputs/Outputs on Mealy Machines
  - Labelling on arcs represent Inputs and labelling on nodes represent Outputs on Moore Machines
- Differences with basic State (Transition) Graph
  - To reduce Clutter
    - Only Inputs that impact a transition from one state to another are present on the graph – others are ignored.
    - Only Outputs that are TRUE (logic high) for a given transition are listed.


# BCD to Excess 3 Mealy FSM Example

**X/Z**

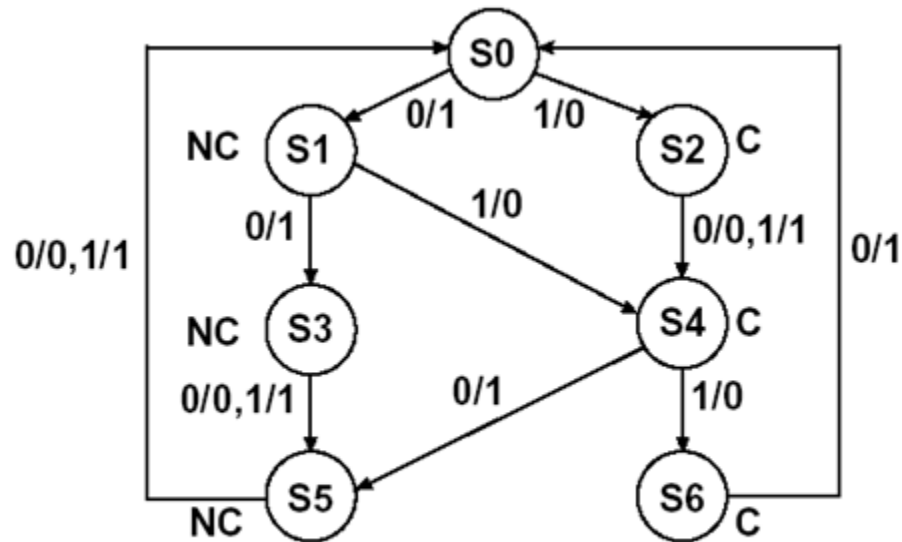

**Standard State Graph Notation**



# BCD to Excess 3 Mealy FSM Example

 


## Extended State Graph Notation

- Only Inputs that impact a transition from one state to another are present on the graph – others are ignored.
- Only Outputs that are TRUE (logic high) for a given transition are listed.

# BCD to Excess 3 Mealy FSM Example

 
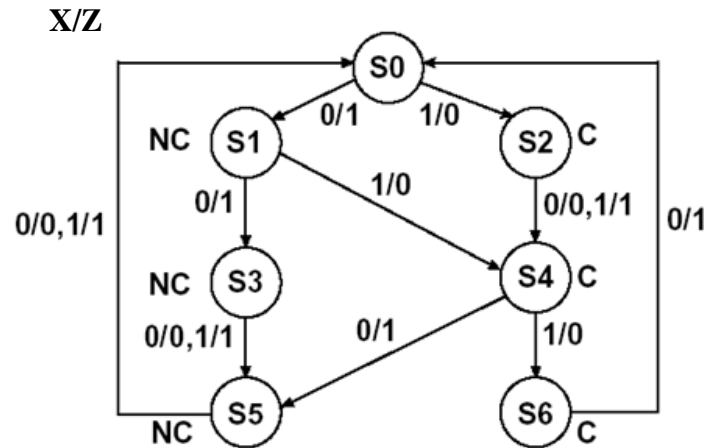


# Example: Faster Multiplier

 

- Move wires from the adder outputs one position to the right => add and shift can occur at the same clock cycle
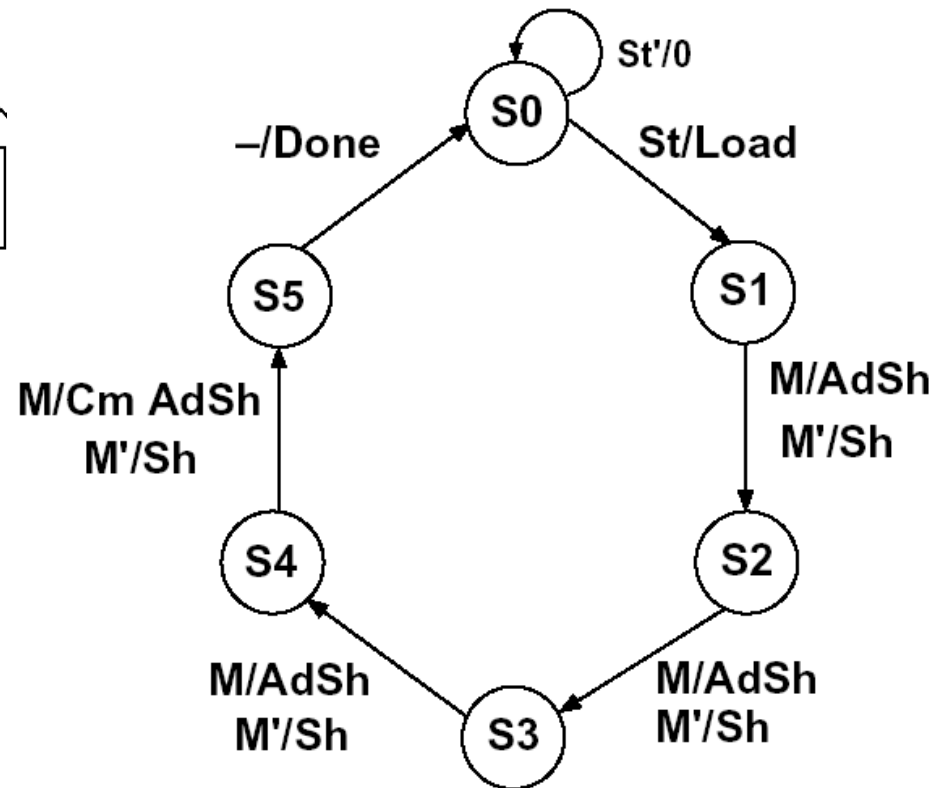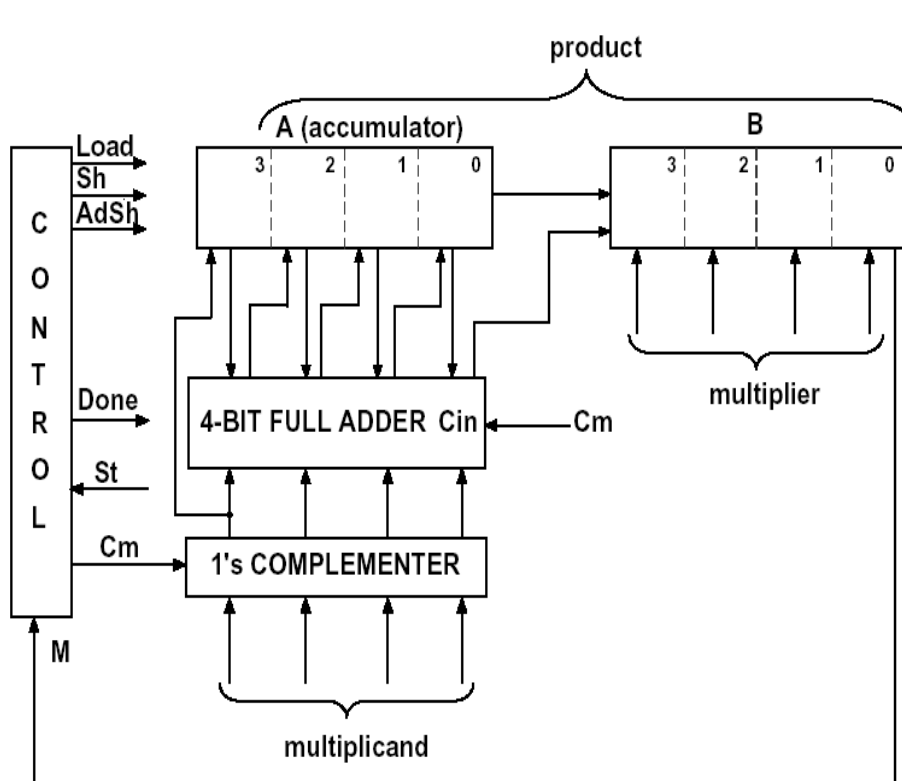
# Extended State Graph for Fast Multiplier




- Note: '-' on the input means no inputs are monitored and transition occurs to the next state no matter what the inputs are







# BCD to Excess 3 Moore FSM Example

## (Extended State Graph Representation)

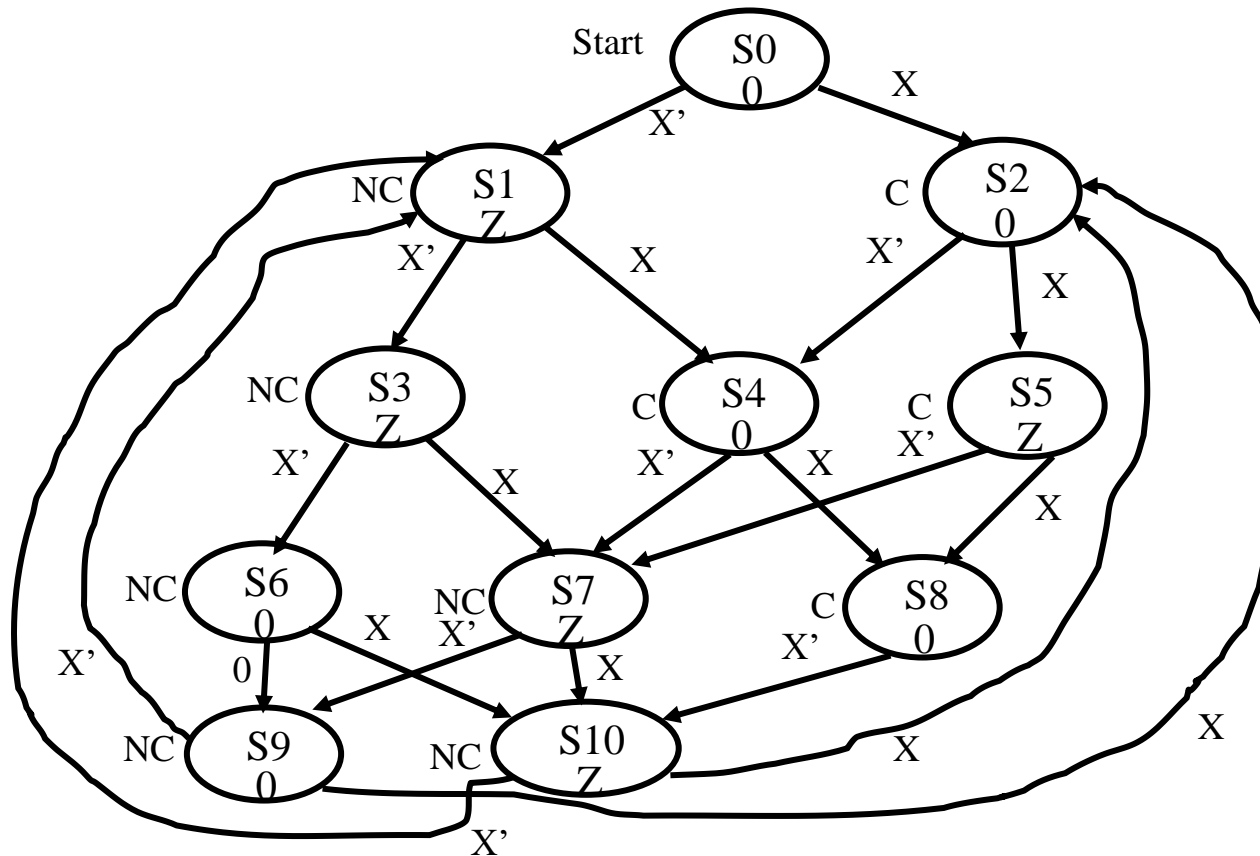

# Combined Mealy/Moore FSM

## (Extended State Graph Representation)

  

**Input:**

$X$

**Outputs:**

$Z_a, Z_b, Z_c$  { Moore Outputs

$Z_1, Z_2$  { Mealy Outputs

