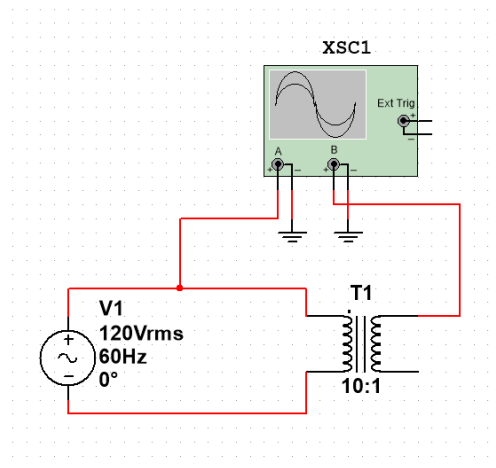


Prelab 6 AC Signals, Transformers and Bridge Rectifiers

Nolan Anderson

February 24, 2021



Circuit 1: Figure 6.1 In Multisim

Part 1 – Transformer Figure 6.3

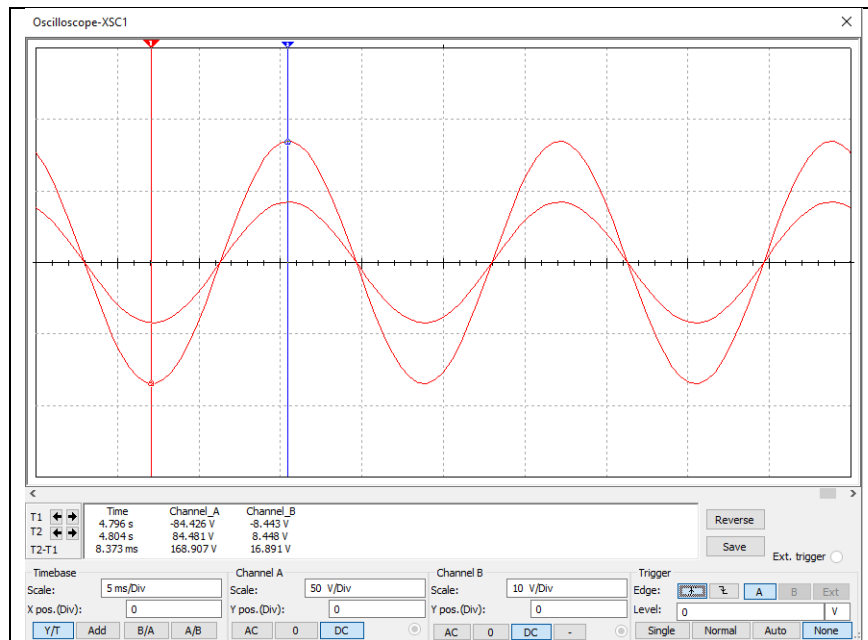


Figure 1: Peak Voltage graph Figure 6.3

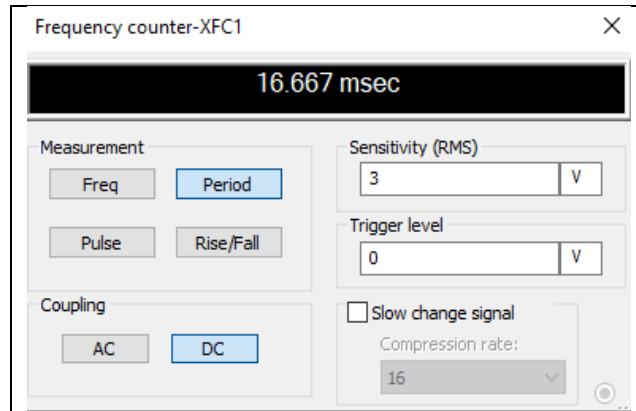


Figure 2: Period from Frequency Counter

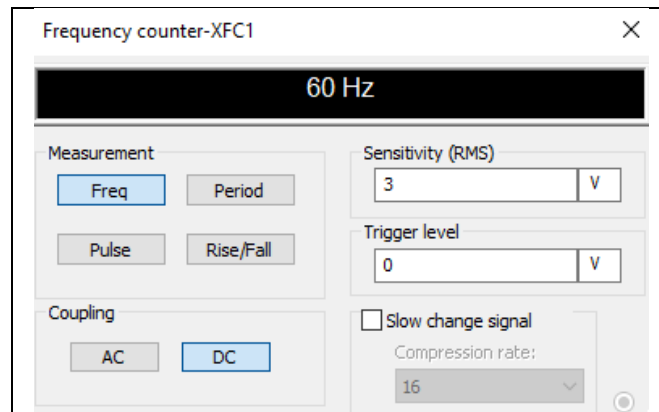


Figure 3: Frequency from Frequency Counter


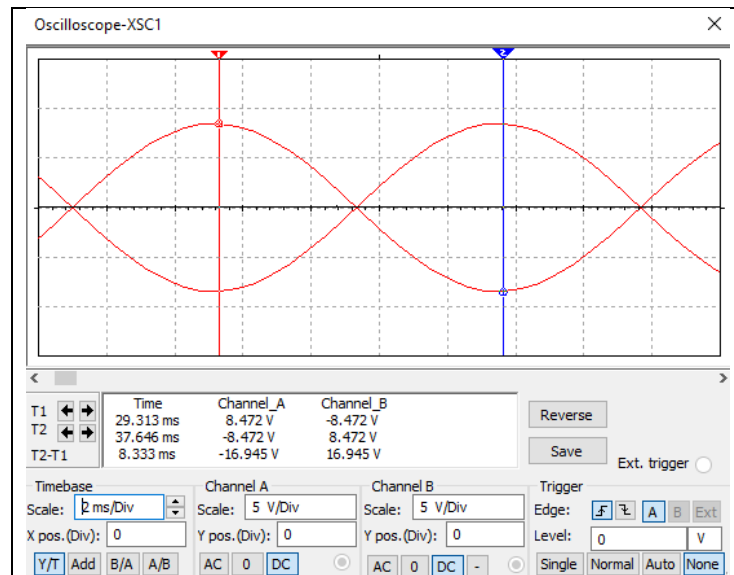


Figure 4: Node C vs. Node D

Figure 4 shows that Node C and D are off by 180 degrees and perfectly out of phase. The difference between the out terminals of the transformer is just sign.

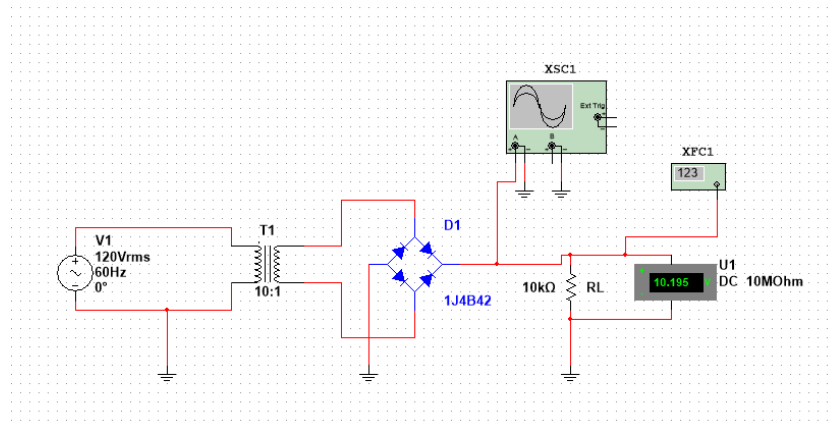

Circuit 2: Figure 6.4

Part 2 – Transformer Figure 6.4

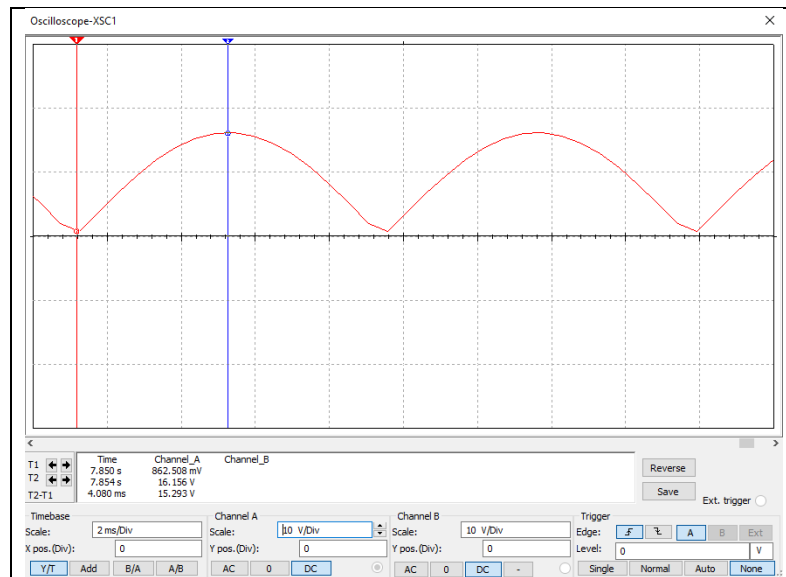


Figure 5: Peak Voltage graph Figure 6.4

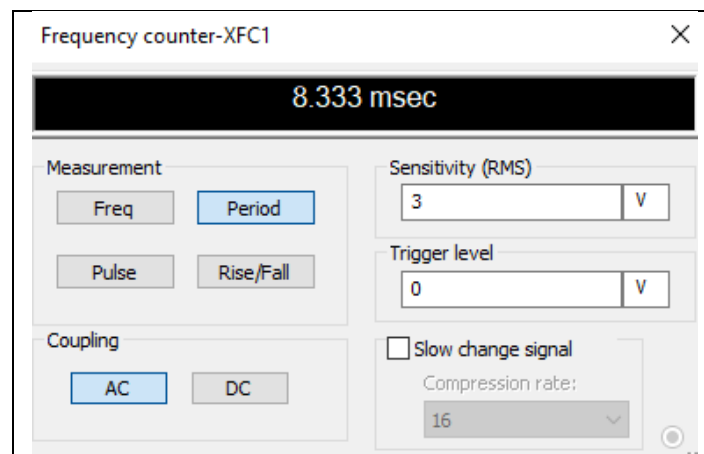


Figure 6: Period from Frequency Counter

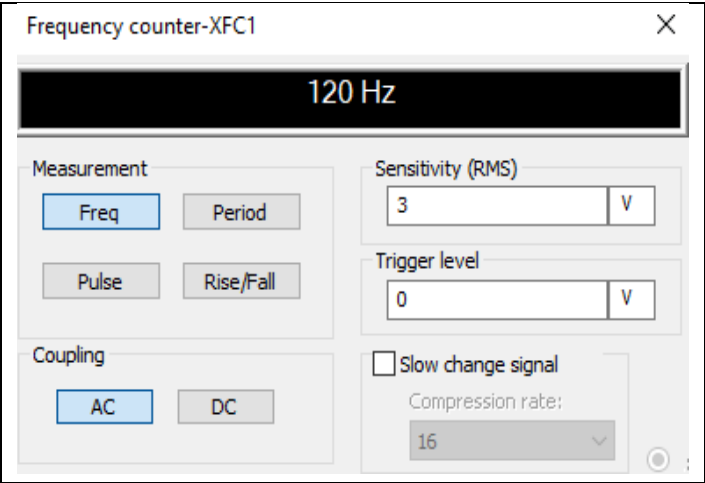


Figure 7: Frequency from Frequency Counter