

Basics

Charge: $Q \equiv$ constant charge
 $q(t) \equiv$ instantaneous charge

Units = Coulombs [C]

Current: Charge in motion
 $I \equiv$ constant current
 $i(t) \equiv$ instantaneous current

Units = Amperes [A]
 "Amps"

$$i(t) = \frac{dq(t)}{dt} = \frac{\Delta q}{\Delta t} = \frac{C}{s}$$

To describe a current:

- (1) Value (+ or -)
- (2) Direction

Jan 6-2:40 PM

Voltage: work done to move charge

$V \equiv$ constant voltage
 $v(t) \equiv$ instantaneous voltage

Units = Volts [V]

$$v(t) = \frac{dw}{dq}$$

To describe a voltage:

- (1) value (+ or -)
- (2) polarity \pm pair

$$V = 5V$$

$$V = -5V$$

$$V_x = + (5) - (2) = 3V$$

$$V_y = + (-6) - (4) = -10V$$

$$V_A = + (-10) - (-2) = -8V$$

Jan 6-3:08 PM

Power: rate at which energy is used or created

$P \equiv$ constant power
 $p(t) \equiv$ instantaneous power

Units = Watts [W]
 W - 1c

$$p(t) = \frac{dw}{dt} \quad v(t) = \frac{dw}{dq} \quad i(t) = \frac{dq}{dt}$$

$$p(t) = v(t) \cdot i(t) \Rightarrow \frac{dw}{dq} \cdot \frac{dq}{dt} = \frac{dw}{dt}$$

$$P = VI$$

To describe to power:

- (1) value (+ or -)
- (2) Reference \Rightarrow delivered (D) or absorbed (A)

Jan 6-3:17 PM

To solve for power:

- (1) Find the $v \cdot i$ product
- (2) Look at current direction relative to voltage polarity

* when current flows from (+) to (-) \Rightarrow Absorbed

* when current flows from (-) to (+) \Rightarrow Delivered


$$P = VI = (6)(3) = 18W, D$$

$$P = VI = (-3)(-1) = 3W, Del$$

$$P = VI = (-10)(-2) = 20W, Del$$

$\Rightarrow 18W, A$
 $\Rightarrow 3W, Del$
 $\Rightarrow 20W, Abs$

Jan 6-3:22 PM

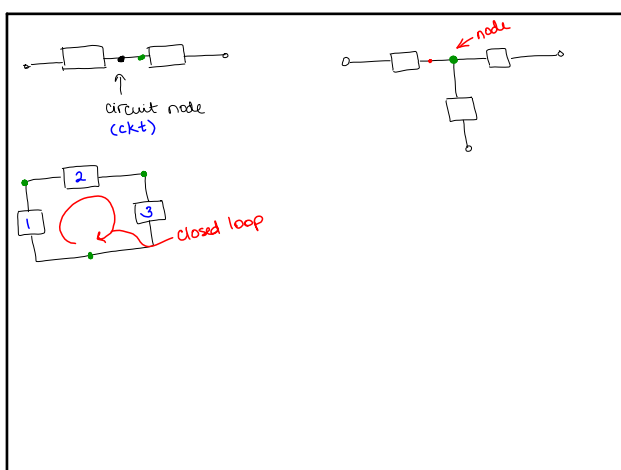

Jan 6-3:32 PM

Kirchoff's Laws

Kirchoff's Current Law (KCL)
 Kirchoff's Voltage Law (KVL)

KCL

- (1) All currents entering a node must sum to zero.
 $-I_1 - I_2 + I_3 + I_4 = 0$
- (2) All currents leaving a node must sum to zero.
 $I_1 + I_2 - I_3 - I_4 = 0$
- (3) Currents in = Currents out
 $I_3 + I_4 = I_1 + I_2$

Find I_x using KCL

$$3 + (-7) = I_x + 4$$


$$I_x = -8A$$

$$I_x + 4 + (-3) + (7) = 0$$

$$I_x = -8A$$

Jan 6-3:36 PM

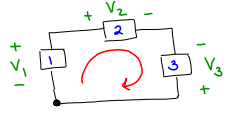KVL : sum the voltages around a loop
Sum must equal = 0



KVL process

- ① Pick a loop direction
CW or CCW
- ② Sign Convention
relative to the polarities

Active sign convention
Passive sign convention.

Jan 6-3:45 PM